

\$1.50


# ham radio

magazine



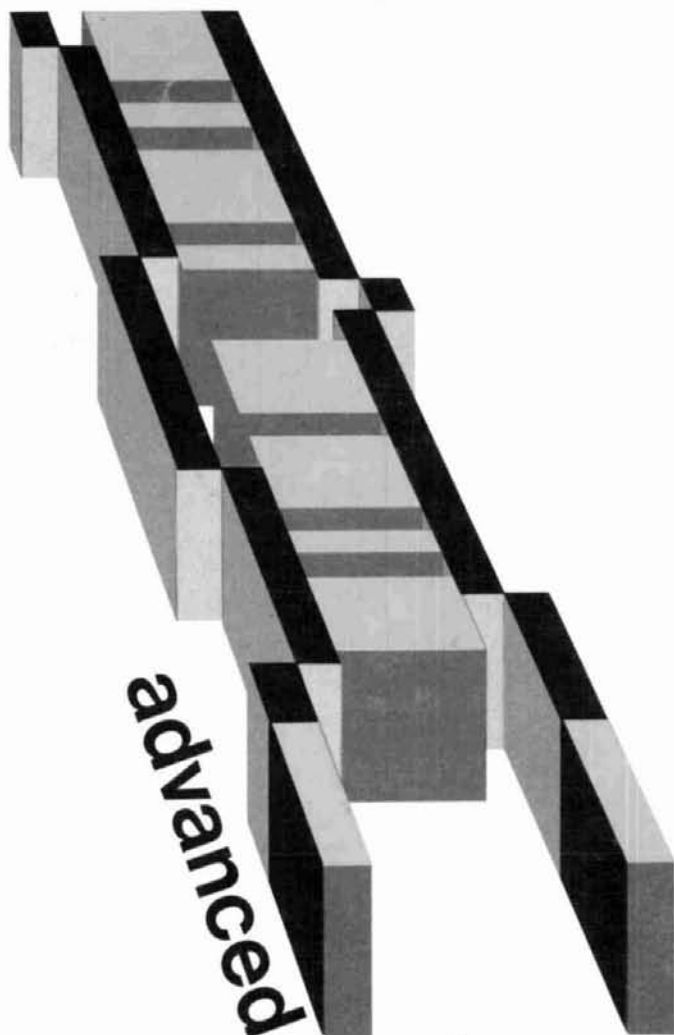**APRIL 1978**

- OSCAR 8 16
- 432-MHz GaAs fet preamp 22
- spectrum analyzer tracking generator 30
- matching network design 44
- testing power tubes 60
- and much, much more . . .



**electronic  
keyer**

This is the amplifier  
you have been waiting for



## The new 2KD-5 linear amplifier... a one piece desk model with the power and reliability of a console

At Henry Radio, we know how to build only one kind of amplifier ... the best. We want you to compare the 2KD-5 with any other desk model at any price.

Remember, the 2KD-5 is only one model in the world's broadest line of amplifiers ... both vacuum tube and solid state ... for HF, VHF and UHF ... fixed station and mobile ... low power and high power.

Never before has any one company offered such a cornucopia of high power RF amplifiers.

Remember also that Henry Radio offers a broad line of commercial and FCC type accepted amplifiers covering the range of 3 MHz to 500 MHz. Henry amplifiers are

in use all around the world. Commercial and export inquiries are invited.

- The 2KD-5 is a 2000 watt PEP input (1200 watt PEP nominal output) RF linear amplifier, covering the 80, 40, 20, 15 and 10 meter amateur bands.
- Two Eimac 3-500Z glass envelope triodes operating in a grounded grid circuit.
- Pi-L plate circuit with a rotary silver plated tank coil for greatest efficiency and maximum attenuation of unwanted harmonics.
- Full legal input in all modes. 2000 watts PEP input for SSB, 1000 watts DC input for CW, RTTY and AM.
- Jumper for 115 or 230 VAC, 3 wire single phase.
- 10.5" high x 15" wide x 17.5" deep
- Price ... \$895.00

**2K-4...LINEAR AMPLIFIER.** Offers engineering, construction and features second to none. Provides a long life of reliable service, while its heavy duty components allow it to loaf along even at full legal power. Operates on all amateur bands, 80 thru 10 meters. If you want to put that strong clear signal on the air that you've probably heard from other 2K users, now is the time. Move up to the 2K-4. Floor console...\$995.00

**TEMPO 6N2** brings the same high standards to the 6 and 2 meter bands. A pair of advanced design Eimac 8874 tubes provide 2,000 watts PEP input on SSB or 1,000 watts on FM or CW. Complete with self-contained solid state power supply, blower and RF relative power indicator. ...\$895.00

**TEMPO 2002.** The same fine specs and features as the 6N2, but for 2 meter operation only. ...\$745.00

**TEMPO 2006.** Like the 2002, but for 6 meter operation. ...\$795.00

**TEMPO VHF/UHF AMPLIFIERS.** Solid state power amplifiers for use in most land mobile applications. Increases the range, clarity, reliability and speed of two-way communications. FCC type accepted also.

Model	Drive Power	Output Power	Price
-------	-------------	--------------	-------

**LOW BAND VHF AMPLIFIERS (35 to 75 MHz)**

Tempo 100C30	30W	100W	\$159.
Tempo 100C02	2W	100W	\$179.
Tempo 100C10	10W	100W	\$149.

**HIGH BAND VHF AMPLIFIERS (135 to 175 MHz)**

Tempo 130A30	30W	130W	\$189.
Tempo 130A10	10W	130W	\$179.
Tempo 130A02	2W	130W	\$199.
Tempo 80A30	30W	80W	\$149.
Tempo 80A10	10W	80W	\$139.
Tempo 80A02	2W	80W	\$159.
Tempo 50A10	10W	50W	\$ 99.
Tempo 50A02	2W	50W	\$119.
Tempo 30A10	10W	30W	\$ 69.
Tempo 30A02	2W	30W	\$ 89.

**UHF AMPLIFIERS (400 to 512 MHz)**

Tempo 70D30	30W	70W	\$210.
Tempo 70D10	10W	70W	\$240.
Tempo 70D02	2W	70W	\$270.

Tempo 40D10	10W	40W	\$145.
Tempo 40D02	2W	40W	\$165.
Tempo 40D01	1W	40W	\$185.
Tempo 25D02	2W	25W	\$125.
Tempo 10D02	2W	10W	\$ 85.
Tempo 10D01	1W	10W	\$125.

**TEMPO 100AL10 VHF LINEAR AMPLIFIER.** Completely solid state, 144-148 MHz. Power output of 100 watts (nom.) with only 10 watts (nom.) in. Reliable and compact ...\$199.00

**TEMPO 100AL10/B BASE AMPLIFIER ...\$349.00**

Tempo solid state amplifiers are available at Tempo dealers throughout the U.S.

please call or write for complete information.

**Henry Radio**

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701  
931 N. Euclid, Anaheim, Calif. 92801 714/772-9200  
Butler, Missouri 64730 816/679-3127

We also carry the complete line of BIRD products.

Prices subject to change without notice.

# Which model should you choose now that you've chosen Rockwell-Collins?

If you work mainly voice, and just dabble in CW, RTTY, or SSTV, build your station around our KWM-2A Transceiver. The unit is compact and lightweight, designed for portable as well as fixed operations.



You're not limited to SSB voice communication, though. The KWM-2A's CW features include break-in and sidetone monitoring circuits. And with the optional 516F-2 Power Supply and external cooling air, you can operate RTTY communications as well.

But if your communications interest is varied and you want maximum voice, CW, RTTY or SSTV capability, we recommend the Rockwell-Collins 75S-3C Receiver and 32S-3A Transmitter.

Optional filters, rejection tuning and variable BFO on the receiver, plus features like carrier reinsertion on our transmitter, give you as much control of your equipment as possible.



And our S/Line is famous as the cleanest sound around.

Give your local Rockwell-Collins dealer a call. Or contact Amateur Radio Marketing, Collins Telecommunications Products Division, Rockwell International, Cedar Rapids, Iowa 52406. Phone: 319/395-4493.



**Rockwell International**

...where science gets down to business

# This NEW MFJ Versa Tuner II . . .

has SWR and dual range wattmeter, antenna switch, efficient airwound inductor, built in balun. Up to 300 watts RF output. Matches everything from 160 thru 10 Meters: dipoles, inverted vees, random wires, verticals, mobile whips, beams, balance lines, coax lines.



**BRAND NEW**

**\$79<sup>95</sup>**

Antenna matching capacitor. 208 pf. 1000 volt spacing.

Sets power range, 300 and 30 watts. Pull for SWR.

Meter reads SWR and RF watts in 2 ranges.

Efficient airwound inductor gives more watts out and less losses.

Transmitter matching capacitor. 208 pf. 1000 volt spacing.

Only MFJ gives you this MFJ-941 Versa Tuner II with all these features at this price:


**A SWR and dual range wattmeter** (300 and 30 watts full scale) lets you measure RF power output for simplified tuning.

**An antenna switch** lets you select 2 coax fed antennas, random wire or balance line, and tuner bypass.

**A new efficient airwound inductor** (12 positions) gives you less losses than a tapped toroid for more watts out.

**A 1:4 balun** for balance lines. 1000 volt capacitor spacing. Mounting brackets for mobile installations (not shown).

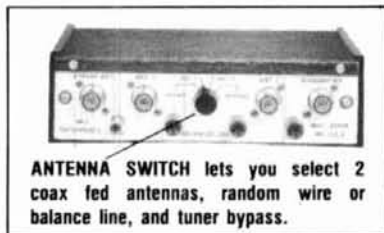**With the NEW MFJ Versa Tuner II** you can run your full transceiver power output — up to 300 watts RF power output — and match your



**ANTENNA SWITCH** lets you select 2 coax fed antennas, random wire or balance line, and tuner bypass.

transmitter to **any** feedline from 160 thru 10 Meters whether you have coax cable, balance line, or random wire.

**You can tune out the SWR on your dipole**, inverted vee, random wire, vertical, mobile whip, beam, quad, or whatever you have.

**You can even operate all bands** with just


one existing antenna. No need to put up separate antennas for each band.

**Increase the usable bandwidth** of your mobile whip by tuning out the SWR **from inside your car**. Works great with all solid state rigs (like the Atlas) and with all tube type rigs.

**It travels well, too.** Its ultra compact size 5x2x6 inches fits easily in a small corner of your suitcase.

**This beautiful little tuner** is housed in a deluxe eggshell white Ten-Tec enclosure with walnut grain sides.

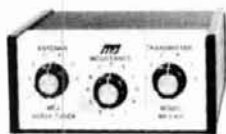**S0-239 coax connectors** are provided for transmitter input and coax fed antennas. Quality five way binding posts are used for the balance line inputs (2), random wire input (1), and ground (1).



**\$59<sup>95</sup>**

**BRAND NEW**

## MFJ-901 VERSA TUNER

New efficient air wound coil for more watts out.

Only MFJ uses an efficient air wound inductor (12 positions) in this class of tuners to give you more watts out and less losses than a tapped toroid. Matches everything from 160 thru 10 Meters: dipoles, inverted vees, random wires, verticals, mobile whips, beams, balance lines, coax lines. Up to 200 watts RF output. 1:4 balun for balance lines. Tune out the SWR of your mobile whip **from inside your car**. Works with all rigs. Ultra compact 5x2x6 inches. S0-239 connectors. 5 way binding posts. Ten Tec enclosure.



**\$49<sup>95</sup>**

**BRAND NEW**

## MFJ-900 ECONO TUNER

Same as MFJ-901 Versa Tuner, but does not have built-in balun for balance lines. Tunes coax lines and random lines.



**\$39<sup>95</sup>**

## MFJ-16010 RANDOM WIRE TUNER

Operate 160 thru 10 Meters. Up to 200 watts RF output. Matches high and low impedances. 12 position inductor. S0-239 connectors. 2x3x4 inches. Matches 25 to 200 ohms at 1.8 MHz.



**\$49<sup>95</sup>**

**BRAND NEW**

## MFJ-202 RF NOISE BRIDGE

This MFJ RF Noise Bridge lets you adjust your antenna quickly for maximum performance. Measure resonant frequency, radiation resistance and reactance. **Exclusive** range extender and expanded capacitance range ( $\pm 150$  pf) gives you much extended measuring range.

Tells resonant frequency and whether to shorten or lengthen your antenna for minimum SWR. Adjust your single or multi-band dipole, inverted vee, beam, vertical, mobile whip or random system for maximum performance. 1 to 100 MHz. S0-239 connectors. 2x3x4 inches. 9 volt battery.

For Orders

**Call toll-free 800-647-8660**

For technical information, order and repair status, and in Mississippi, please call 601-323-5869.

Order any product from MFJ and try it. If not delighted, return within 30 days for a prompt refund (less shipping).

Order today. Money back if not delighted. One year unconditional guarantee. Add \$2.00 shipping/handling.

Order By Mail or Call TOLL FREE 800-647-8660 and Charge It On



**MFJ ENTERPRISES**

P. O. BOX 494

MISSISSIPPI STATE, MISSISSIPPI 39762



# ham radio

magazine

**APRIL 1978**

volume 11, number 4

**T. H. Tenney, Jr., W1NLB**  
publisher

**James R. Fisk, W1HR**  
editor-in-chief

**editorial staff**

Charles J. Carroll, K1XX  
Patricia A. Hawes, WA1WPM  
Alfred Wilson, W6NIF  
assistant editors

Thomas F. McMullen, Jr., W1SL  
Joseph J. Schroeder, W9JUV  
associate editors

Wayne T. Pierce, K3SUK  
cover

**publishing staff**

C. Edward Buffington, WB1AMU  
assistant publisher

Fred D. Moller, Jr., WA1USO  
advertising manager

James H. Gray, W1XU  
assistant advertising manager

Therese R. Bourgault  
circulation manager

ham radio magazine  
is published monthly by  
Communications Technology, Inc  
Greenville, New Hampshire 03048  
Telephone: 603-878-1441

**subscription rates**

U.S. and Canada: one year, \$12.00  
two years, \$22.00  
three years, \$30.00

Europe, Japan, Africa:  
(via Air Forwarding Service)  
one year, \$25.00

North America, South America, Australia  
and Asia (except Japan):  
(via Surface Mail)  
one year, \$18.00

**foreign subscription agents**

Foreign subscription agents are  
listed on page 101

Microfilm copies  
are available from  
University Microfilms, International  
Ann Arbor, Michigan 48106  
Order publication number 3076

Cassette tapes of selected articles  
from ham radio are available to the  
blind and physically handicapped  
from Recorded Periodicals  
919 Walnut Street, 8th Floor  
Philadelphia, Pennsylvania 19107


Copyright 1978 by  
Communications Technology, Inc  
Title registered at U.S. Patent Office

Second-class postage  
paid at Greenville, N.H. 03048  
and at additional mailing offices  
Publication number 233340


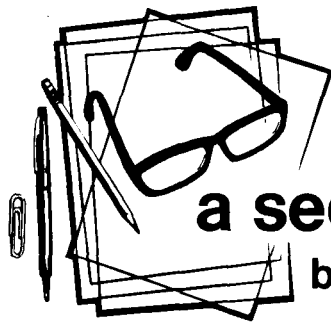
## contents

- 10 advanced electronic keyer**  
Pavel Horvath, OK3IA
- 16 AMSAT-OSCAR-D**  
Perry I. Klein, W3PK
- 22 432-MHz GaAs fet preamplifier**  
Shigeru Sando, JH1BRY
- 28 simple paddle for electronic keyers**  
Vidi la Grange, ZS6AL
- 30 spectrum analyzer tracking generator**  
Wayne C. Ryder, W6URH
- 34 battery charger for portable operation**  
Francis E. Hinkle, Jr., K5PA
- 38 modifying linear amplifiers  
for full break-in operation**  
Richard B. Frey, K4XU
- 44 designing matching networks**  
Leonard H. Anderson
- 50 overtone crystal oscillators**  
Courtney Hall, WA5SNZ
- 54 correcting repeater interference**  
Robert P. Haviland, W4MB
- 60 testing power tubes**  
Joseph J. Carr, K4IPV
- 66 microprocessors:  
microcomputer interfacing**  
Peter R. Rony  
Jonathan A. Titus  
David G. Larsen, WB4HYJ
- 72 improve audio quality  
for vhf-fm**  
Budd M. Meyer, K2PMA
  
- 4 a second look**
- 126 advertisers index**
- 101 flea market**
- 116 ham mart**
- 66 microprocessors**
- 82 new products**
- 126 reader service**
- 60 repair bench**
- 6 stop press**



## a second look

by Jim Fisk

If you look at technological advances with the eye of a historian, you'll see periodic peaks in new technology, followed by nulls where everything seems to come to a standstill. This phenomenon is most noticeable in the semiconductor industry during the past few years, but if you look back to the 19th century, you'll see the same thing happened then, with George Stephenson's steam-powered locomotives and Eli Whitney's cotton gin early in the century, and later with the development of mass production techniques, the electric telegraph, and Marconi's wireless. Every few years, it seems, a major breakthrough in technology occurs which produces an avalanche of new products on the market place. If you analyze it carefully, in most cases you'll find that the "major breakthrough" didn't happen all at once as it first appears, but was the culmination of years of research by many different workers in many diverse fields.

In many ways the cyclic rise and fall of technological achievement is an extension of the well-known domino theory — the apparent lulls in activity occur when the dominoes are being lined up; the breakthrough comes when the last domino is set in place and the whole line is knocked down, one domino after the other. It takes but one missing or misplaced domino to prevent the whole line from going down.

In the field of gallium-arsenide field-effect transistors (GaAs fets or "gas" fets, for short), the last of the dominoes has been set in place, and in the near future there will be devices on the market which will provide noise figures of less than 1 dB at 4000 MHz, and power outputs of 6 watts or more at 10 GHz. At a conference last summer at Cornell University, researchers from Bell Labs reported on a GaAs fet amplifier which yielded 10 dB gain at 4 GHz with a noise figure of 0.7 dB; at 6 GHz the noise figure increased to 1.25 dB and gain dropped to 9 dB. At the same conference, scientists from Rockwell International were talking about a device which gave a 2.2 dB noise figure at 10 GHz with 8.5 dB gain. These devices and similar ones from other manufacturers will be available on the commercial market this year, but be prepared to pay a pretty healthy price for the privilege of building a circuit around them. As manufacturing processes are improved and yields go up, however, I expect device cost will drop within the amateur price range. If you can't wait, in this issue JH1BRY describes a high-performance GaAs fet preamp for 432 MHz that has a noise figure below 1 dB.

At Texas Instruments the accent is on power GaAs fets with claimed power output of 4.2 watts at 10 GHz; and RCA has announced 140 mW output at 22 GHz. The most impressive of the power GaAs fets, however, is a device from Fujitsu which provides 10 watts output at 4000 MHz. In theory 14 or 15 watts should be possible at 4 GHz with GaAs fet devices, and 6-7 watts at 10 GHz, but there are still a number of problems to be solved, so this capability may be five years in the future.

Some of the same technology that has produced high-performance microwave GaAs fets is also being used in other areas. At the International Solid State Conference in February, an engineer from Hewlett-Packard described a monolithic 4-GHz integrated amplifier which provides 28 dB gain from dc to 2000 MHz (gain is 7 dB from dc to 4 GHz). The three-stage amplifier is built on a single GaAs chip and uses reverse biased Schottky diodes as capacitors and MESFETs as resistors. At the same conference, Bell Labs reported on a uhf operational amplifier which has a unity gain frequency in excess of 1000 MHz. Silicon NPN transistors are used in the design, which provides 20 dB gain at 300 MHz; the operational frequency range is 10-500 MHz.

While GaAs fets threaten to displace bipolars above 3000 MHz, silicon MOSFETs are quietly moving in on microwave bipolars from the lower end of the frequency spectrum. Attention has been focused recently on advances in VMOS devices for vhf and uhf applications. Since the first commercial VMOS device was announced by Siliconix two years ago (*ham radio*, September, 1976), a number of semiconductor manufacturers have gotten on the VMOS bandwagon including Intersil, Motorola, and Westinghouse. One firm has reportedly obtained 10 watts at 1000 MHz and more than 5 watts at 1500 MHz with a VMOS transistor. One of the big advantages of VMOS is its negative temperature coefficient which eliminates thermal runaway and secondary breakdown. This means that emitter resistors, temperature sensing diodes, and other protection circuitry required for bipolars can be eliminated, resulting in a substantial cost savings. VMOS also offers better linearity with third-order IMD typically 3 to 5 dB better than bipolar power amplifiers.

As I said earlier, technological breakthroughs seem to come in spurts. During the past year or so there have been some remarkable achievements in the world of digital electronics, but it has been pretty quiet on the analog front. With the latest rf devices just now emerging from the laboratory, how long will we have to wait before all the dominoes are gathered for the next breakthrough?

Jim Fisk, W1HR  
editor-in-chief



# IC-22S, Small wonder

ICOM's matchless mobile **IC-22S** has, since its introduction, been the standard against which all other VHF mobile transceivers have been measured. It is a prime example of ICOM's quality engineering, peak performance and phenomenal flexibility blended into one splendidly simple and affordable radio. Small wonder that the **IC-22S** has been the most popular radio that ICOM has ever offered.

Built to be viable operating hardware for years to come, with a magnificent high sensitivity receiver and instant programming and reprogramming of any 22 of 256 possible frequencies, the **IC-22S** is priced for the mobile beginner and the multi-vehicle serious VHF enthusiast. Small wonder that many hams own and operate more than one **IC-22S**.

With Touch Tone adaptability, quick change mobile mount, external speaker provisions, optional AC base power supply and other great flexible growth characteristics, the **IC-22S** is the perfectly affordable radio for those to whom present performance and future possibilities are important. Small wonder.

All ICOM radios significantly exceed FCC Specifications limiting spurious emissions.

**Specifications:**  Frequency Range: 146-148 MHz  Voltage: 13.8 VDC negative ground  Current Required: TX, 2 amps at 10 W, 0.9 amp at 1 W; RX, 700 ma at max audio  Size: 58mm(h) x 156mm(w) x 218mm(d)  Weight: 1.9 Kg  Number of Channels: 22 selected from 256 possible  Power Output: 10 W or 1 W, selected  Modulation Width: 5 KHz  Microphone Impedance: 500 ohms  Spurious Level: -60 dB below carrier  Modulation Acceptance: 16F3  Receiver Sensitivity: 4 mv for 20 dB quieting  Spurious Response: 60 dB or more attenuation  Bandpass:  $\pm 7.5$  KHz/-6 dB;  $\pm 15$  KHz/-60 dB  Squelch Sensitivity: -8 dB below 1 mv

HF/VHF/UHF AMATEUR AND MARINE COMMUNICATION EQUIPMENT

DISTRIBUTED BY:



# ICOM

ICOM WEST, INC.  
Suite 3  
13256 Northrup Way  
Bellevue, Wash. 98005  
(206) 747-9020

ICOM EAST, INC.  
Suite 307  
3331 Towerwood Drive  
Dallas, Texas 75234  
(214) 620-2780

ICOM CANADA  
7087 Victoria Drive  
Vancouver B.C. V5P 3Y9  
Canada  
(604) 321-1833



TEN-METER AMATEUR LINEARS WERE BANNED by the FCC Commissioners in an early February meeting, and it seemed evident that most had already decided on the ban before the meeting began. The ban covers the commercial manufacture, distribution and sale of any RF power amplifier covering the 24-35 MHz range. It appears that linears in the marketing "pipeline" — in manufacturers' stock or on dealers' shelves — will receive some sort of "blanket" waiver to be sold providing that they meet all the Type Acceptance criteria other than frequency coverage. Any that don't will have to be considered individually. Amplifier sales between individual Amateurs are still permitted, and individual Amateurs are still permitted to build their own 10-meter linears.

LIMITED TYPE ACCEPTANCE of Amateur amplifiers below 144 MHz was also adopted with technical standards similar to those already in Part 97; actual implementation of Type Acceptance won't take place until detailed specifications and procedures are ready in several months.

To Meet The New Type Acceptance requirements an amplifier will have to be capable of accepting 50 watts (mean power) of drive, have less than 15 dB power gain, require external transmit-receive switching (no RF sensing) — and, of course, not operate in the 24-35 MHz spectrum. How difficult a manufacturer is supposed to make it for an individual Amateur to modify his product to cover 10 meters is still unclear.

It's Expected that the ban and Type Acceptance will go into effect at the same time, but just when won't be known until a Report and Order on the two dockets is released. Further clouding the issue is what action industry plans, with several manufacturers, ARMA, and the ARRL all likely candidates for filing petitions for reconsideration. In both industry, and among individual Amateurs, the feeling is that the Type Acceptance requirements in themselves would have been sufficient to drive the illegitimate amplifiers off the market, so the ban on top of Type Acceptance serves only to unnecessarily penalize Amateurs.

AMATEUR SECONDARY STATION licenses for individuals will be phased out as their present terms expire as a result of the first Report and Order on Docket 21135, effective March 24. Special events stations and callsigns were also eliminated as the Commissioners attempted to reduce the Amateur Radio workload at Gettysburg to within budgetary limitations. For Amateurs who presently hold more than one station license, the effect will be a decision on their part as to which callsign to keep when it is time to renew; the freeze on issuance of new secondary licenses, in effect for almost a year, is now permanent.

Extra Class Requests for specific 1x2 or 2x2 callsigns will no longer be honored under the newly adopted rules, though they will still be able to request an unspecified 2-letter-suffixed callsign. Eventually, but well in the future, it's planned to offer 1x3 callsigns to all the holders of Advanced or Extra Class licenses who wish them. Also, the present process by which a 1x3 callsign holder receives a 1x2 "preferred" callsign when changing call areas is to be eliminated. However, as the rules now permit an Amateur to retain his former callsign even after moving permanently to a new call area, it's likely many present 1x3 and 1x2 callsign holders will elect that option. Along that line, future initial callsign assignments are now going to be based on the applicant's mailing address rather than station location.

Club, RACES, and Military Amateur station licenses are to be further considered under a new Notice of Proposed Rule Making on Docket 21135. Distinctive prefixes for club stations (WK) and military stations (WM) are also proposed in that NPRM, while RACES stations would continue with WC callsigns as at present. It's also proposed that the criteria for a club station license be tightened considerably, requiring that the organization demonstrate a "compelling need" (distinctive use, past and present) for a club license before one would be issued or renewed. RACES licenses would also be reduced to only one per Civil Defense organization, and licenses for all three classes of organizations would be issued to the organization, not an individual trustee. Due date for Comments on this NPRM is June 2, with Reply Comments June 30.

REPEATER LICENSES AREN'T REQUIRED to put a repeater on the air under terms of a recent waiver. No prior FCC approval or additional license is now required to operate a repeater, auxiliary link, control, or remotely controlled Amateur station — all may be operated with the individual's primary station license, callsign, and appropriate ID. The waiver is effective until the Commission releases an Order on Docket 21033.

KH1 THROUGH KH0 are the new prefixes for U.S. Pacific islands, while KP1-KP0 will identify Caribbean areas; the change was effective March 24. As some spots such as KX6 and KC6 are not FCC administered and would apparently continue with present prefixes, there seems to be enough in each block to handle the needs.

THE 2-METER DX RECORD has been stretched again, this time to 6300 km (3940 miles), as KP4EOR worked LU8DIN. YV52Z has heard LU3AAT on 432.1 MHz, and they plus KP4EOR are attempting schedules on that band as well as on 2 meters.

# This one's for you.

Because you asked for it . . . we built it. The all-new JR. MONITOR™ Antenna Tuner.


Call it what you will — antenna tuner, matchbox, or matching network, the JR. MONITOR™ has it all wrapped up in one neat 5¼"Wx2¼"Hx6"D all metal cabinet.

Here are the features you said you wanted:

Continuous tuning from 1.8-30 MHz. 300 watt power capability. Forward reading relative output power meter — simply tune JR. MONITOR™ controls for maximum RF output on the meter. Built-in balun. Mobile mounting bracket. Ceramic rotary 12-position switch. Capacitor spacing 1000 volts. Tapped toroid inductor. Antenna inputs: coax unbalanced SO 239, random wire, balanced feed line 75-660 ohm. Weight: 2½ pounds.

With so many special features — think of the unlimited possibilities you'll have for experimenting with dozens of antennas! For instance, the DenTron All Band Doublet fed with balanced feed line hooked to the JR. MONITOR™ covers 1.8-30 MHz in one antenna. . . or try this mobile suggestion: 108" mobile whip fed with coax to the JR. MONITOR™ located under the dash will give you 10-40 meter mobile coverage and no coils to change!

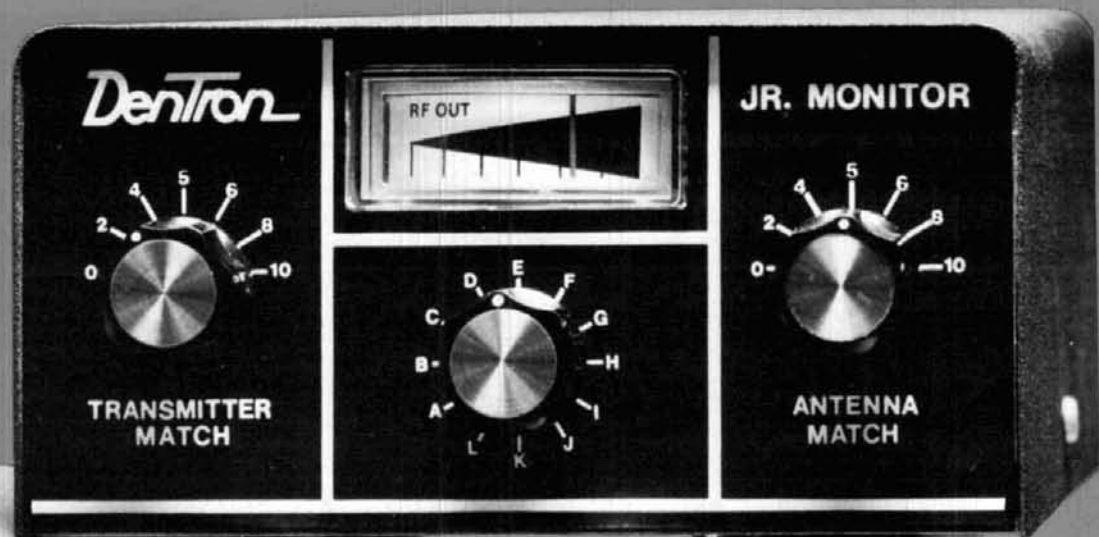It's easy to understand the excitement the JR. MONITOR™ has created. Wherever you are — home, boat, car, plane, or campsite you'll always be in contact. It's a fun little tuner that easily fits in a briefcase or coat pocket — but why would anyone want to smuggle it into their radio room?



JR. MONITOR™ \$79.50  
ALL BAND DOUBLET \$24.50

**DenTron**  
Radio Co., Inc.

2100 Enterprise Pkwy.,  
Twinsburg, Ohio 44087

(216) 425-3173



**KENWOOD**  
...pacesetter in amateur radio


**Kenwood's exciting 2-meter transceiver... still the most powerful. 800 channels, repeater offset over all 4 MHz (144-148 MHz), dual frequency readout, easy to read 6 digit display, Kenwood's unique continuous tone coded squelch system and outstanding receiver performance. All in a rugged, compact package.**

The TR-7400A lets you go anyplace on the 2-meter band... covers the entire band without compromise. It exceeds all FCC emission requirements for amateur transceivers. Its RF output is factory spec'd at 25 watts... but is typically over 30! It offers a dual frequency readout with large easy to read 6 digit LED display plus a functional dial readout system, fully synthesized 800 channel operation and repeater offset over all 4 MHz (144-148 MHz). The unique Continuous Tone Coded Squelch system is a Kenwood exclusive.

Outstanding sensitivity, large-sized helical resonators with High Q to minimize undesirable out-of-band interference, and give a 2-pole 10.7 MHz monolithic crystal filter combine to give your TR-7400A outstanding receiver performance. Intermodulation characteristics (Better than 66dB), spurious (Better than -60dB), image rejection (Better than -70dB), and a versatile squelch system make the TR-7400A tops in its class.

(Active filters and Tone Burst Modules optional)

# TR-7400A

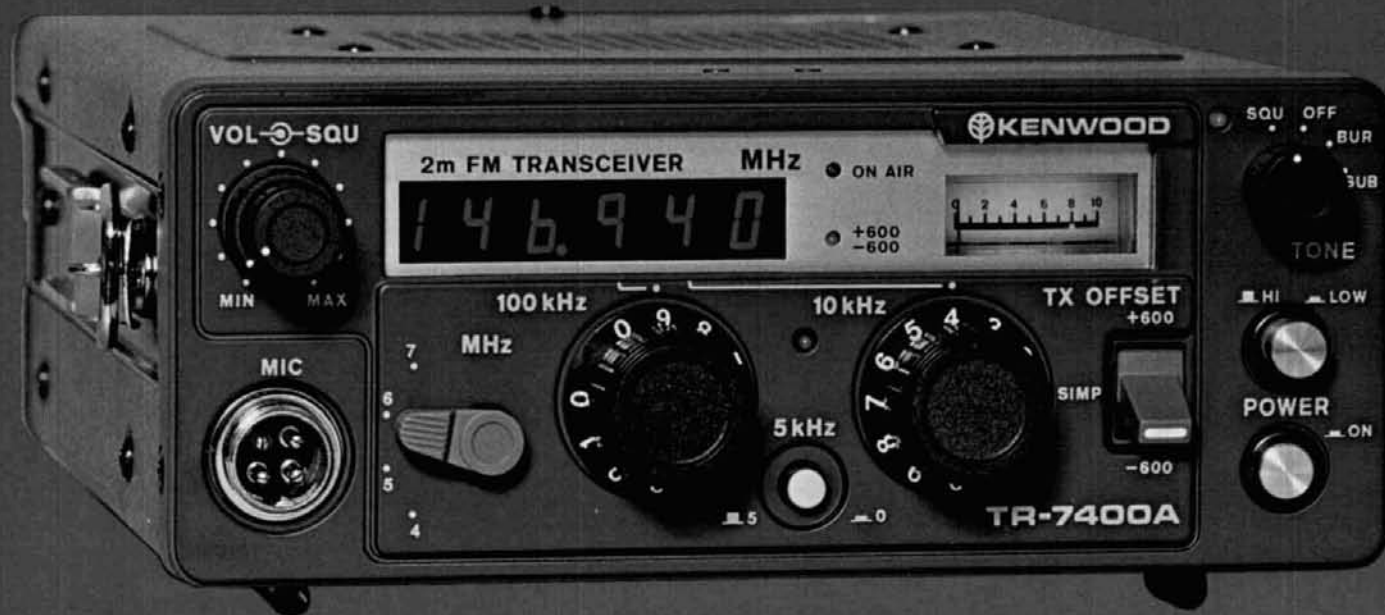

The TR-7400A is shown with its furnished hand mike and the PS-8 DC power supply (optional). Take your TR-7400A out of the car and you can use it as a powerful base station. The PS-8 is rated at 8 Amps and is among the most rugged, well-regulated supplies available for VHF transceivers requiring 12V DC.



## Specifications

**TR-7400A**

Range: 144.00 MHz to 147.995 MHz	Mode: FM	800 Channels: 5 KHz spaced	Sensitivity: Better than 0.4 $\mu$ V for 20 dB quieting Better than 1 $\mu$ V for 30 dB S/N	Squelch Sensitivity: Better than 0.25 $\mu$ V	Selectivity: 12 KHz at -6 dB down 40 KHz at -70 dB down	Image Rejection: Better than -70 dB	Spurious Interference: Better than -60 dB	Intermodulation: Better than 66 dB	Receive System: Double conversion	First IF: 10.7 MHz	Second IF: 455 KHz	Audio Output: More than 1.5 Watts (8 ohm load)	RF Output Power: 25 Watts (High) 5-15 Watts (Low-adjustable)	Antenna Impedance: 50 ohms	Frequency Deviation: $\pm$ 5 KHz	Spurious Response: Better than -60 dB	Microphone: Dynamic, with PTT switch, 500 ohms	Current Drain: Less than 1A in receive (no input signal)	Current Drain: Less than 8A in transmit
----------------------------------	----------	----------------------------	--	---	--	-------------------------------------	---	------------------------------------	-----------------------------------	--------------------	--------------------	--	--	----------------------------	----------------------------------	---------------------------------------	--	--	---

The TR-7500 is a 100 channel PLL synthesized 146-148 MHz mobile transceiver offering the dependability you've come to expect from Kenwood products.

ALL THE FREQUENCIES YOU NEED FOR MOST REPEATER OPERATIONS AND RECOMMENDED SIMPLEX CHANNELS ARE PRE-PROGRAMMED. 88 channels are pre-programmed for use on all standard repeater frequencies (as per ARRL Band Plan) and most simplex channels. For added flexibility, there are 6 diode-programmable switch positions. The 15 KHz shift function makes these 6 positions into 12 channels.

THE 7500 FEATURES AN EASY TO READ, LED DIGITAL FREQUENCY DISPLAY... unlike the difficult to read mechanical displays on many mobile units.

ALSO, A SINGLE KNOB CHANNEL SELECTOR makes the TR-7500 one of the most convenient units to operate while driving.

Its output is a full 10 watts and it offers  $\pm 600$  KHz offset, along with other worthwhile features.

The man to see... your local Authorized Kenwood Dealer. He can give you all the information you need and the best deal.

THE TR-7500 IS AN ADVANCED 2 METER FM TRANSCEIVER OFFERING EXCITING FEATURES AND EXTREME RELIABILITY AT A REASONABLE PRICE

# TR-7500



## AND PS-6

... matching power supply for the TR-7500. Regulated 13.8 VDC @ 3.5 amps... built in speaker. A perfect companion for home use of the TR-7500.



# TR-8300

The luxury of 450 MHz at an economical price. The TR-8300 is capable of  $F_3$  emission on 23 crystal controlled channels (3 supplied). The transmitter output is 10 watts. It incorporates a 5 section helical resonator and a two-pole crystal filter in the IF section of the receiver for improved inter-modulation characteristics. Receiver sensitivity, spurious response and temperature characteristics are excellent.

TRIO-KENWOOD COMMUNICATIONS INC.  
1111 WEST WALNUT/COMPTON, CA 90220



## advanced electronic keyer

By defining  
keying intervals  
the author has developed  
a practical keyer  
that permits  
maximum time for  
character keying —  
enabling you to send  
letter-perfect code.

**About thirty years ago**, the bug was the most popular keying device, being widely used by hams all over the world. Only a small minority were using a new device, the electronic keyer, which had just begun to appear on CW bands, to produce fast and perfect machine keying. In the late 1940s, W6OWP described in *QST*<sup>1</sup> a new and simple principle for the electronic keyer. In Europe, this keyer was modified and popularized on the amateur bands by OZ7BO.

The W6OWP electronic keyer was simple, yet reliable. It did not use any clock-pulse generator, with the timing of dots, dashes and spaces performed by RC circuits, two triode vacuum tubes, and two relays. The dot, dash, and space time ratio was practically constant over the whole speed range. The most important features, though, were the self completing dots and dashes (including the following space), instant response when the paddle was closed, and sufficient time to release the paddle when the character generation was to be stopped.

### electronic keyer requirements

Are there new requirements for the electronic keyer today? The optimum timing of characters, (dots, dashes, and spaces) over the entire speed

**By Pavel Horvath, OK3IA**, Institute of Physics, Slovak Academy of Sciences, 899 30 Bratislava, Czechoslovakia

range, and simple but reliable control of the keyer with the paddles are, of course, still expected. This can be easily understood by examining the timing of characters as shown in **fig. 1**. The time durations of the dash, dot, space within a character, space between characters, and space between words are defined as 3, 1, 1, 3, and 7 elementary time intervals. This timing of characters seems to be optimal for fast speeds. A different timing could be required at very low speeds; this problem, however, is not discussed here. Even though the keyer must accept imperfect keying, the output characters should be generated without errors.

Control of the keyer with the paddles is very important. Two types of paddles are generally used; the single paddle for standard keying and the dual paddle

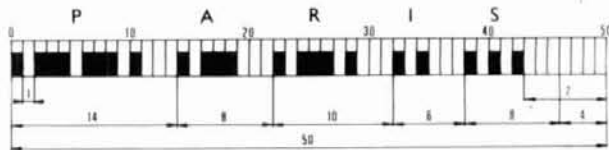


fig. 1. Timing of characters and spaces.

for squeeze or iambic keying. The single paddle, when released, slips into the neutral position and can be closed for a dot or for a dash. The dual paddle can be closed simultaneously for a dot and for a dash. Keying with a dual paddle is somewhat different than that with a single one.

Using the single paddle, there are two distinct groups of characters. First, those characters having an alternate sequence of dots and dashes (C for example) are generated by alternatively closing the


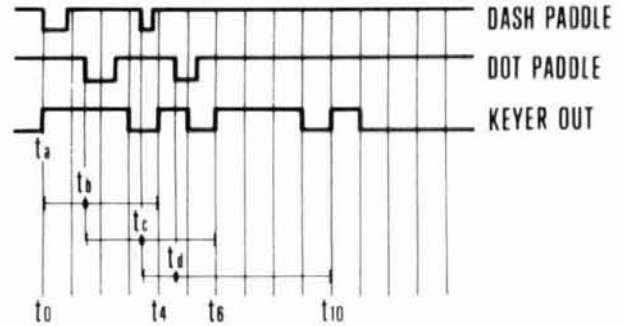


fig. 2. Permitted time intervals for closing the paddles to generate the character C.

paddle for a dash and then a dot. The first dash starts at the instant  $t_a = t_0$ , when the paddle is closed. No delay time should occur. By using dot and dash memories, the paddle can be moved to the dot side after the first dash begins. **Fig. 2** shows the permitted time intervals for closing the paddle to generate the character C without errors.

The second group of characters are those which have a series of dots or dashes. **Fig. 3** shows the keying required for the character = (BT). The paddle is first closed to generate a dash at the instant  $t_a = t_0$ , but yet, must be released and moved to the dot side before  $t_4$ . During the interval  $t_c$  to  $t_{10}$ , the paddle must be repositioned to form the last dash. For example, the paddle could be closed during  $t_c$  to  $t_{14}$  and released during  $t_d$  to  $t_{14}$ .

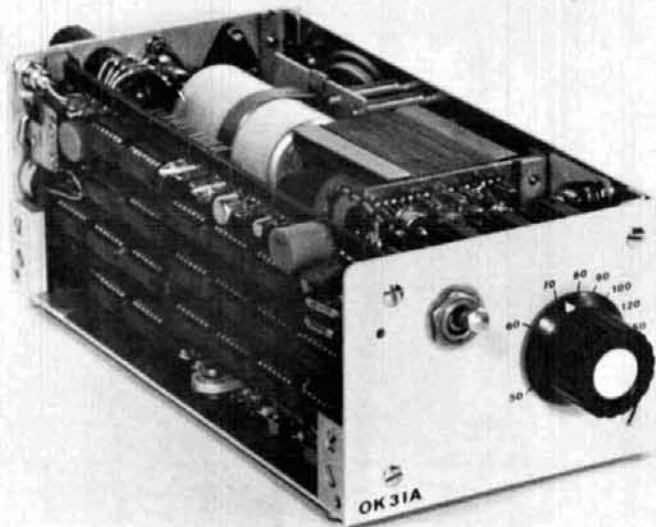A somewhat different situation arises if you use dual paddles for iambic keying. The output with both paddles closed is called an iambic sequence. **Fig. 4** shows the keying for CQ. You start by closing the dash paddle, followed by closing the dot paddle. The



Front view showing the construction and placement of the printed circuit boards, power supply, speaker, and other components.



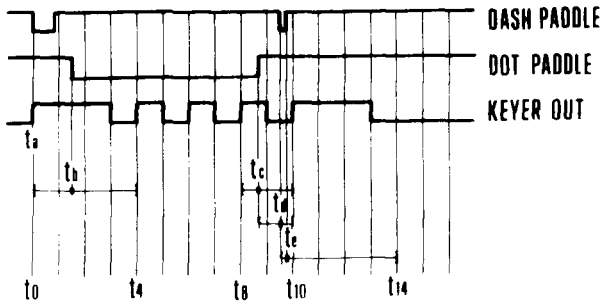


fig. 3. Permitted time intervals for closing and releasing paddles to generate the character = (BT).

dot paddle can be closed any time during the  $t_0$  to  $t_4$  interval. Both paddles are held until you recognize the last dot in the character C. Then you release both paddles. The sequence for releasing the paddles is not important, but both must be released during  $t_{10}$  to  $t_{12}$ . If the keyer also completes the spaces between characters, you can re-close the dash paddle anytime during the  $t_{12}$  to  $t_{14}$  interval. After the second dash in the Q has started ( $t_{18}$ ), you must close the paddle for a dot during  $t_{18}$  to  $t_{22}$ , keeping both paddles closed to produce the character in the iambic mode. If both paddles are released anytime during  $t_{24}$  to  $t_{28}$ , the Q will be completed. When both paddles are released, the iambic sequence must stop after one bit (dash or dot) is completed. No second bit should be generated.

The permitted time intervals previously discussed are the maximum intervals in which the paddles can be closed or released, allowing the characters to be

generated without errors. Any shorter time intervals make the keying worse. A summation of the previous points produces a list of features which an electronic keyer should incorporate:

1. Keying by both single and dual paddles.
2. Maximum possible permitted time intervals to make the keying easy.
3. At the beginning of the message, the character should start the instant the paddle is closed.
4. Optimum timing of dots, dashes, and spaces, throughout the entire speed range.
5. Stable clock generator, without clock pulse variations after triggering.

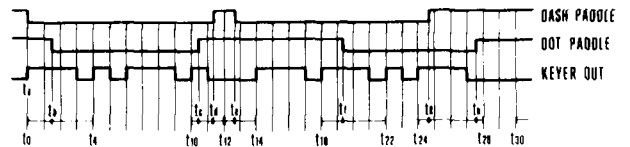


fig. 4. Keying of the word CQ in the iambic mode.

I began my design with the circuit described by WB2DFA.<sup>2</sup> In my version, I use very similar timing circuits, modified for a triggered clock and complete timing of spaces. My efforts were concentrated on improving the control of the keyer with paddles, making keying easy and convenient.

A block diagram of this keyer, with the significant signal names, is shown in fig. 5.

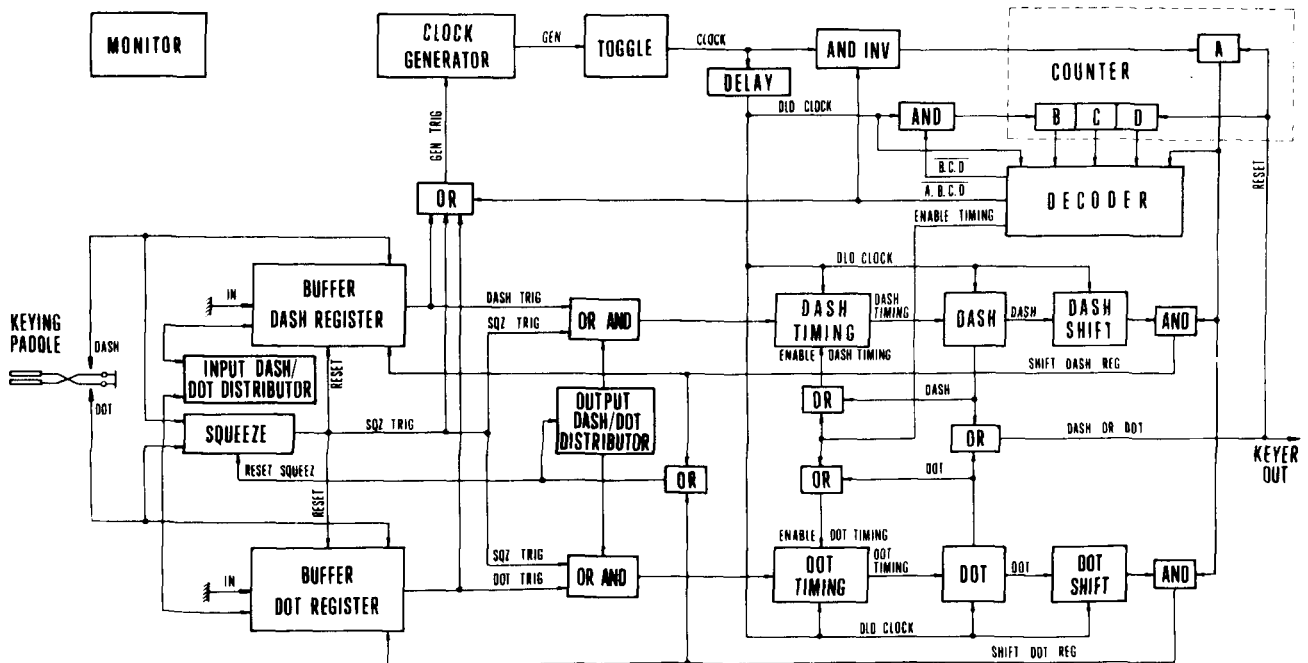



fig. 5. Block diagram of the advanced electronic keyer showing the most significant signals.



**Clock generator.** As shown in **fig. 6**, the schematic diagram, the clock pulses are generated by transistors  $T_4$ ,  $T_5$ , and the associated logic. In the initial state, the clock generator is off since GEN TRIG is low (0). The signal GEN TRIG is the logical sum of DASH TRIG, DOT TRIG, SQZ TRIG, MESSAGE START, and  $A \cdot B \cdot C \cdot D$ . Because of the low from GEN TRIG,  $T_4$  is turned on by the current flowing through D3 and subsequently  $T_5$  is also turned on. At the instant the paddle is closed, GEN TRIG goes high, enabling the clock generator. Simultaneously, a short, negative pulse is formed by the gates connected to D4. This negative pulse turns off  $T_4$  and starts the generation of clock pulses. This circuit philosophy allows the generator to start in synchronization with the paddle. The clock pulses (GEN) are perfectly formed, the first pulse being the same as the following ones. The clock frequency is continuously variable and corresponds to speeds of 10 to 50 words per minute.

either paddle. Now, if a dash is to be sent, for example, the paddle is pressed, causing the clock generator to be activated, and the DASH signal to be generated. This signal, DASH, is the actual eventual output from the keyer. And, in addition to being the output, it is used to reset the binary counter for the duration of the signal. When DASH resets the counter, through the RO(1) and RO(2) inputs, the  $B \cdot C \cdot D$  and  $A \cdot B \cdot C \cdot D$  are high, thus feeding the clock pulses to the binary counter. But, the pulses will not be counted until the completion of the dash since the resets override the normal clock input.

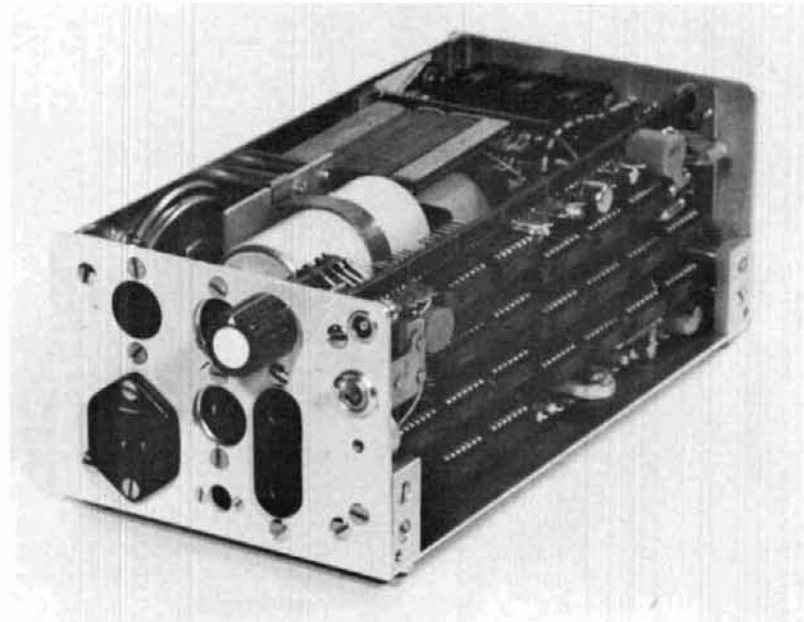When the dash is completed, the CLOCK and DLD CLOCK pulses will then be counted. The gates connected to the B and D outputs of the binary counter will give an ENABLE TIMING pulse at the completion of the first or third timing interval; if there is a dot or dash waiting in the buffers, it will be generated after the first interval and the process will start again. If a



Rear panel view showing connectors for the ac line, 12-volt battery, paddles, manual key, external speaker, message memory, keyer output, S1 and S2, and speaker volume control.

The toggle and delay circuits divide the GEN signal by two, producing CLOCK and DLD CLOCK signals, with a delay of about 200 nS.

**Space generation timing circuits.** The circuitry in this portion of the keyer is used to provide a constant-width space following each element of a character, whether a dot or a dash. This self-completing space corresponds to the length of one dot. In addition, the timing of the space between characters and words can also be made self-completing, corresponding to 3 and 7 elementary-time intervals.

In the initial state (completion of a space), the four outputs of the binary counter are all high, causing the ENABLE TIMING line to also be high. When this line is high, the circuits for generating a dot or dash are not inhibited, and can be activated by pressing

dot or dash is not waiting, another ENABLE TIMING pulse will occur after the third timing interval (character space). If a character is still not in the input buffers, the word space will be generated (seven time intervals) by the gates connected to the B, C, and D outputs of the counter. At the completion of the word space, the  $A \cdot B \cdot C \cdot D$  line will go low, stopping the pulse generator. If a character had been keyed in as the beginning of a new word, however, the pulse generator will not stop. Thus, if you are keying properly, the clock generator runs without interruption through the whole message.

**Buffers and registers.** The input buffers (or dot and dash memories) are used to store the code elements as they are put into the keyer. The dash and dot memories are actually 2-bit shift registers set up

as FIFO registers, composed of D-type flip-flops. During keying, the dots and dashes are not only stored, but are also simultaneously shifted into the timing circuits. Therefore, it is possible to buffer characters in which the sum of the dots and dashes is greater than four.

**Dash and dot distributors.** The input and output dash/dot distributors remember which kind of a bit, dash or dot, was stored first. The input distributor stores the dots and dashes in a sequence depending on the first bit keyed in; the output distributor correctly loads the content of the buffers into the timing circuits.

The character C, if stored in the buffers, is processed to the keyer output in the following manner. The output dash/dot distributor, being enabled for a dash, allows the DASH TRIG signal to pass through the gates into the dash timing circuit, triggering the first dash. When the dash and the following single width space are completed, the signal SHIFT DASH REG shifts the dash register and clocks the output distributor to the dot memory, thus enabling the DOT TRIG signal through the gates into the dot timing circuit, triggering the dot. When the dot and the single width space are completed, the signal SHIFT DOT

REG shifts the dot register, turning the output distributor back to the dash buffers. The same procedure is followed until the character C is shifted out of the buffers.

**Dash and dot timing.** The timing of a dash will start if the DASH TRIG or SQZ TRIG signal is low, the output dash/dot distributor enabled for a dash, and the signal ENABLE DASH TIMING high. The pulses, DLD CLOCK, transfer the high level on the D input to the output of the flip-flop, causing DASH TIMING to go high. With this signal high, a four-state binary counter receives the DLD CLOCK pulses. The counter states are then decoded into the signal DASH, which is three elementary-time intervals long. While the DASH is executed, the DOT circuit is disabled.

**Dash shift and dot shift.** The signals SHIFT DASH REG and SHIFT DOT REG, shown in fig. 7, are short pulses positioned at the end of the single width space following the dash or the dot. By having these pulses at the end of the space, you have the maximum amount of time in which to key in another dot or dash.

The block diagram in fig. 5 illustrates how these signals are formed. The signal CLOCK is delayed 200

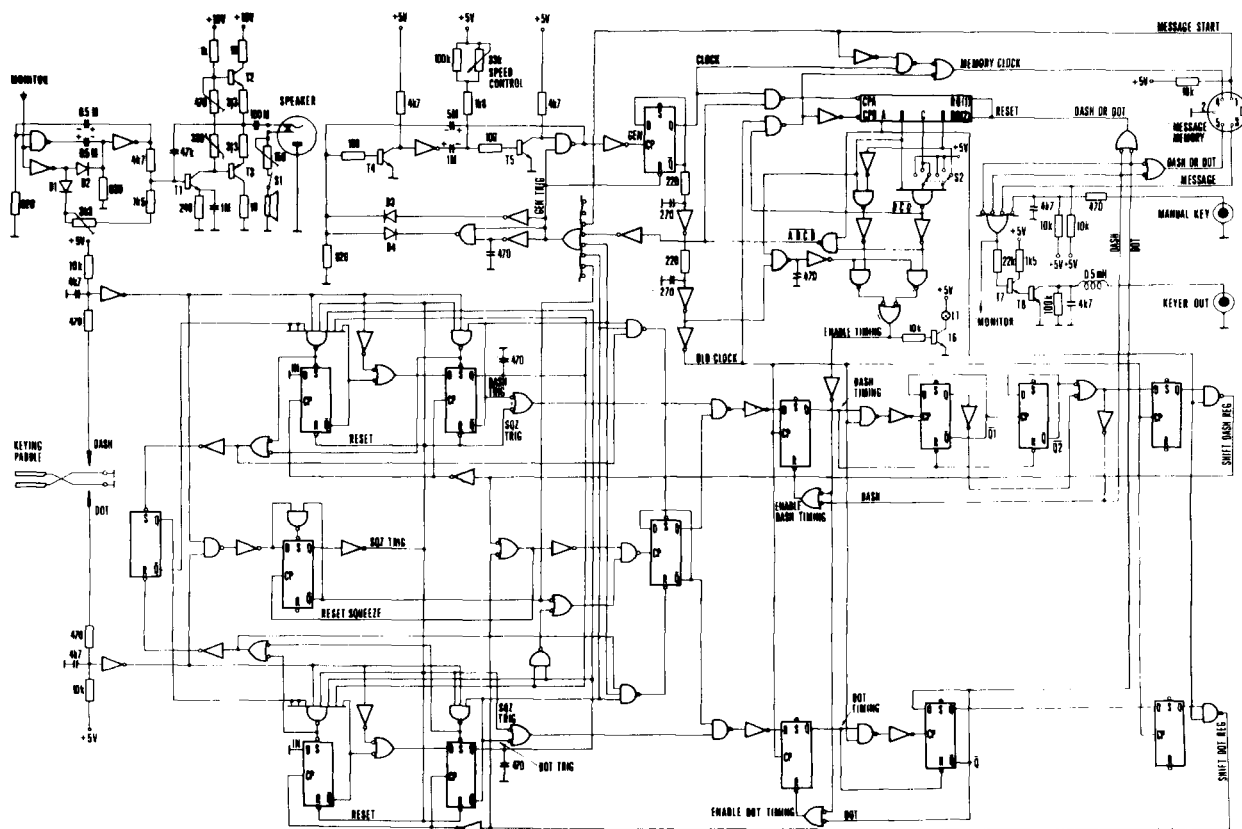


fig. 6. Schematic diagram of the advanced electronic keyer.

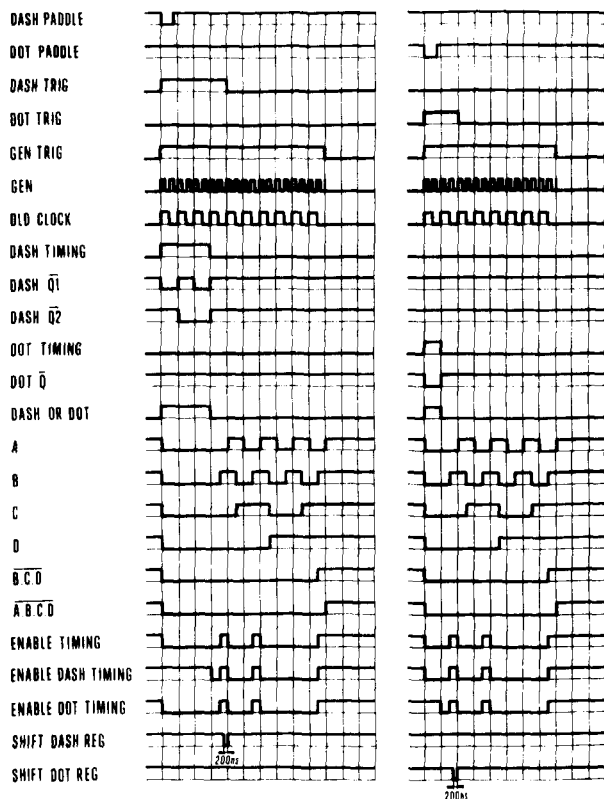


fig. 7. Timing diagrams for the signals shown in figs. 5 and 6.

nS, producing DLD CLOCK. Also, CLOCK is used to drive the A section of the binary counter. After the DASH and DOT signals are formed, they're shifted into another D-type flip-flop, which is clocked by DLD CLOCK. The dash or dot therefore initiates the shift register signal, while the DLD CLOCK stops it, 200 nS later.

**Squeeze.** During the initial phase of keying, the buffers, dash and dot registers, and input and output dash-dot distributors are involved. When both paddles are squeezed, SQZ TRIG goes low, clearing both buffer registers, enabling the clock generator, and executing the iambic sequence. When both paddles are released, RESET SQZ resets the squeeze circuit forcing SQZ TRIG to go high at the end of the first completed single-width space.

**Monitor.** The keyer contains an internal side-tone oscillator, which consists of a multivibrator, an integrating amplifier, and internal speaker. The multivibrator generates a 1-kHz rectangular waveform, which is integrated in the amplifier. The triangularly shaped sidetone drives an internal 8-ohm permanent magnet speaker.

**Message memory.** Provisions have been made to connect the keyer to an external random-access

memory. Four signals are available on a rear panel connector for operation of the memory. During the "message write operation" the MEMORY CLOCK and DASH or DOT are used for synchronous storing of the message. The MEMORY CLOCK automatically starts when the paddle is activated and continues to run during the manual keying. When the manual keying stops, the MEMORY CLOCK runs for seven clock pulses after message generation ceases. MEMORY CLOCK can be enabled to run through the remaining addresses by taking MESSAGE START low. During the "message read operation" MESSAGE represents the memory content previously stored and is transmitted through the OR gate to the keyer output.

### construction

The electronic keyer is built in a 7 x 10 x 21 cm (2 3/4 x 4 x 8 1/4 inch) steel cabinet. The overall view is shown in the photographs. The ICs are mounted on a universal printed-circuit board with wire wrap used for the circuit connections. The parts list is shown in table 1.

### concluding thoughts

This advanced electronic keyer could seem to some readers to be rather complicated. However, even an inexperienced homebrewer can expect perfect performance by exercising reasonable care during construction. Additionally, there are no special circuit adjustments necessary.

table 1. Semiconductors used in the electronic keyer

integrated circuits	transistors
7400 9 each	KC507 Silicon, 0.3 W T1, T4 - T7
7404 6 each	KF508 Silicon, 0.8 W T2, T8
7410 2 each	KF517 Silicon, 0.8 W T3
7420 1 each	
7430 3 each	
7474 8 each	Diodes
7493 1 each	KA221 Silicon, Switching D1 - D4

Only inexpensive TTL ICs were used in this project. The more experienced builder could change some circuit components or integrated circuits to ones more available in the United States. Or he could use NOR gates, monostable multivibrators, or MSI shift registers to minimize the number of parts and energy consumption. This should not be in contradiction with the aim of this article, however, which is to provide optimum keyer control and timing.

### references

1. F. A. Bartlett, W6OWP, "Further Advances in Electronic Keyer Design," *QST*, October, 1948, page 27.
2. J. W. Pollock, WB2DFA, "Cosmos IC Electronic Keyer," *ham radio*, June, 1974, page 6.

ham radio



## AMSAT-OSCAR D

The AMSAT-OSCAR D spacecraft is scheduled for launch sometime this month — here are the complete operating parameters for this new amateur satellite

AMSAT-OSCAR D, the next spacecraft in the OSCAR series, is a Phase II spacecraft which was built over the past two years by radio amateurs in the United States, Canada, Japan, and West Germany and is the first spacecraft in which AMSAT, Project OSCAR, and the ARRL have joined together to build flight hardware. The spacecraft makes extensive use of parts left over from the OSCAR 7 and Phase III programs, and was built primarily because the Phase III spacecraft will not be available until 1979. By stretching its resources almost to the limit, AMSAT has been able to work on both the Phase III spacecraft (with lots of publicity) and OSCAR D (with little publicity).

The new spacecraft carries transponders for two modes of operation. There is a conventional 145.9 MHz to 29.4 MHz Mode A transponder, and a new 145.9 MHz input, 435.1 MHz output, Mode J transponder — a similar frequency combination was used on the short-lived OSCAR IV spacecraft in 1966. In addition, six channels of telemetry are provided to monitor the onboard status of the satellite.

### mission objectives

The principal objective of AMSAT-OSCAR D is its use as an educational tool in schools. Other objec-

**By Perry Klein, W3PK, and Joe Kasser, G3ZCZ, AMSAT, Post Office Box 27, Washington, D.C. 20044.**

tives include the continuation of communications demonstrations by means of stations in the amateur-satellite service, of the feasibility of using satellites with small amateur terminals for emergency communications, communications between medical centers and isolated areas, aeronautical, maritime, and land-mobile communications, direct satellite-to-home voice "broadcasting" to simple amateur receivers, and other similar applications. Further objectives are to demonstrate special operating techniques that enhance the usefulness of low orbits for these satellite applications, and to test the suitability of a new communications transponder frequency combination (Mode J) for small terminal users.

AMSAT-OSCAR D will permit the continuation of the education program, which began with OSCARs 5, 6, and 7, over the next several years, the anticipated lifetime of the satellite. OSCAR satellites have begun to play an important role in a new approach to science education. Used as remote laboratory tools, these satellites represent a pioneering utilization of an active space system in the classroom. Using inexpensive ground terminals for OSCAR satellites in schools, students can gain firsthand experience in space science. This type of direct, active involvement has relevance to the study of communications, astronomy, engineering, physics, mathematics, and meteorology. The low-cost OSCAR ground terminal puts an active satellite system at the disposal of the instructor and student.

### spacecraft description

OSCAR D is a communications satellite in the Phase II (low-orbit) series which is designed to operate with small stations in the amateur-satellite service on a non-commercial basis. The spacecraft contains two communications transponders and command and telemetry systems; it is solar powered, weighs 27 kg (60 pounds), and is a 38 cm (15-inch) rectangular solid 33 cm (13 inches) high. Its anticipated useful operating lifetime is three years.

Two types of communications transponders are aboard the spacecraft. Normally, only one transponder will be operated at a time because of spacecraft battery constraints.

**Two-to-ten meter transponder.** The *Mode A* transponder is a two-to-ten meter unit similar to the one used on OSCAR 7 (input frequency passband 145.85-145.95 MHz, and output frequency passband between 29.40 and 29.50 MHz). A 250 mW telemetry beacon provides telemetry data in Morse code at a frequency of 29.402 MHz. Approximately -95 dBm

is required at the transponder input terminals for an output of one watt. This corresponds to an effective radiated power from the ground of 80 watts for a distance to the satellite of 1930 km (1200 miles) and a polarization mismatch of 3 dB. The transponder translation frequency (input frequency minus output frequency) is 116.458 MHz. Thus, the relationship between the uplink ( $f_u$ ) and downlink ( $f_d$ ) is

$$f_d = f_u - 116.458 \pm \text{Doppler}$$


where both  $f_d$  and  $f_u$  are in MHz.

An uplink signal at 145.900 MHz, for example, will produce a down-link signal from the transponder on 29.442 MHz  $\pm$  Doppler. As in the two-to-ten meter transponders in OSCAR 6 and 7, the passband is *not* inverted, and upper-sideband uplink signals become upper-sideband downlink signals. Output power is 1 to 2 watts.

Note that the downlink frequency will be slightly different (8 kHz) from that of the equivalent OSCAR 7 Mode A transponder which has an equivalent frequency relationship of

$$f_d = f_u - 116.450 \pm \text{Doppler}$$

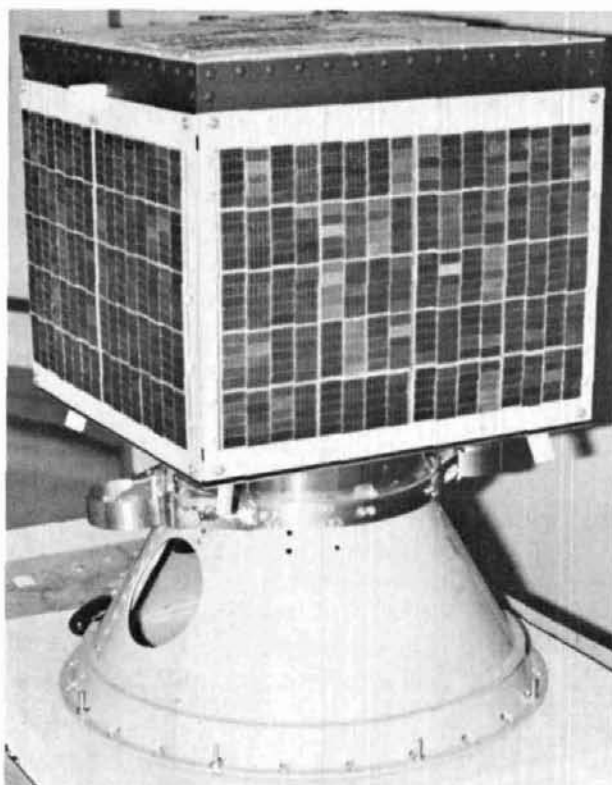AMSAT OSCAR D spacecraft to be launched in March, 1978, by NASA. When it is in orbit it will be designated AMSAT OSCAR 8.





**Two meter-to-70cm transponder.** The Mode J transponder, constructed by members of the Japan AMSAT Association in Tokyo, uses a two-meter input, 70 centimeter output combination which has not yet been flown in the AMSAT Phase II series. This transponder operates with an input frequency passband of 145.90-146.00 MHz, and an output frequency passband of 435.10-435.20 MHz. Power output is



JA1CBL of Japan AMSAT Association (JAMSAT) building parts of the Mode J transponder.

about 1-2 watts PEP, and the output passband is *inverted*, *i.e.*, upper-sideband uplink signals become lower-sideband downlink signals. The transponder translation frequency (input frequency plus output frequency) is  $581.1 \text{ MHz} \pm \text{Doppler}$ . Uplink sensitivity for one-watt output is  $-105 \text{ dBm}$ , corresponding to an effective radiated power from the ground of 8 watts for a distance to the satellite of 1930 km (1200 miles).\* Note the greatly improved sensitivity of this mode, and keep your power down. A 100-milliwatt beacon carries telemetry at a frequency of 435.095 MHz. The relationship between the uplink ( $f_u$ ) and downlink ( $f_d$ ) is

$$f_d = 581.1 - f_u \pm \text{Doppler}$$

where both  $f_d$  and  $f_u$  are in MHz.

### antenna system

Both the Mode A and Mode J transponders use the same receiving antenna, a canted turnstile comprised of four 48 cm (19-inch) lengths of 12.5 mm (1/2-inch) carpenter's rule fed by a hybrid and matching network so as to develop circular polarization.

\*Sensitivity may decrease by a factor of ten (10 dB) under different conditions of battery voltage and satellite operating temperature, so that as much as 80 watts may be required at certain times.

One port of the hybrid feeds the Mode A receiver; left-hand circular polarization is required by users in the Northern Hemisphere and right-hand circular polarization is required in the Southern Hemisphere. A second port of the hybrid is connected to the Mode J receiver; right-hand circular polarization is required in the Northern Hemisphere, and left-hand circular polarization in the Southern Hemisphere. The antenna gain should approach 5 dB in the  $-Z$  direction (*i.e.*, toward the bottom of the satellite).

The Mode A ten-meter downlink antenna is a linearly-polarized dipole which is oriented perpendicular to the stabilization magnets in the spacecraft as in OSCAR 6 (but unlike OSCAR 7, which has the ten-meter antenna parallel to the axis of the magnets).

The 435-MHz Mode J downlink antenna is a simple monopole, linearly polarized, and located on the top of the spacecraft. Note that its location may result in some radiation shielding at high Southern Hemisphere latitudes.

### telecommand system

A five-function telecommand system of a new design is carried on OSCAR D. The system is based on the best features of the OSCAR 6 and 7 telecommand systems, and is designed to be virtually immune to noise and interference. The command functions are:

- Mode A Select** (Two-to-ten meter transponder ON)
- Mode J Select** (2 meter to 70 cm transponder ON)
- Mode D Select** (recharge mode; both transponders OFF)
- Ten-meter Antenna Deployment**
- Ten-meter Antenna Reset**

### telemetry system

OSCAR D contains a six-channel Morse code telemetry system similar to the units flown in OSCARs 6 and 7. Telemetry is sent at 20 words per minute as three-digit numbers; *A1* emission is used in keying the Mode A or Mode J telemetry beacons, depending upon which transponder is in use. The six telemetry parameters are:

- Channel 1.** Total Solar Array Current —  
 $I_T = 7.15 (101 - N) \text{ ma.}$
- Channel 2.** Battery Charge-Discharge Current —  
 $I_{Bat} = 57 (N - 50) \text{ ma.}$
- Channel 3.** Battery Voltage —  
 $V_B = 0.1 N + 8.25 \text{ Volts}$

**Channel 4.** Baseplate Temperature —

$$T_{bp} = 95.8 - 1.48 N (^{\circ}C)$$

**Channel 5.** Battery Temperature —

$$T_{Bat} = 95.8 - 1.48 N (^{\circ}C)$$

**Channel 6.** RF Power Output, Mode J —

$$P_{JT} = 23N \text{ milliwatts}$$

Note that, unlike OSCAR 6 and 7 telemetry, OSCAR D has only one parameter per line (OSCARs 6 and 7 had 4). As a result, a complete telemetry frame is sent in approximately 20 seconds.

### power supply

The spacecraft contains solar panels on its four sides (along the +X, -X, +Y, and -Y axes), and on the top (the +Z axis). No panels are contained on the bottom (-Z axis) since this is where the spacecraft is attached to the launch vehicle. The solar cells, combined with a 12-cell, six-ampere-hour rechargeable nickel-cadmium battery should be adequate to power the spacecraft with a positive power budget in Mode A for several years, even considering solar cell degradation in the radiation environment. The power drain in Mode J, however, is somewhat larger, so the Mode J transponder probably cannot be operated continuously.

A battery charge regulator is also contained which

converts from the 28-30 volt solar array voltage to the 14-16 volts required by the battery. It also tapers the charge rate so the battery trickle-charges as the battery approaches full charge (as indicated by the battery voltage).


### stabilization system

Four permanent magnets located inside the spacecraft and aligned along the Z axis provide stabilization, as in OSCARs 6 and 7. The polarity of the magnets is such that the top (+Z axis) of the spacecraft always points toward the magnetic north pole of the earth. Hysteresis permalloy damping rods mounted behind the +X, -X, +Y, and -Y solar panels are designed to reduce the spin of the spacecraft about the Z axis; they function in a manner similar to a shorted transformer turn as it cuts the lines of flux of the earth's magnetic field. The permalloy rods are left over from OSCAR 7, which successfully used the same type of stabilization system.
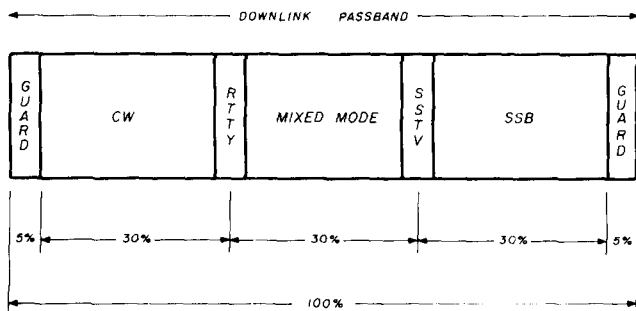
### launch interface and orbit

The OSCAR D spacecraft is being launched from the NASA Western Test Range as a secondary payload with the NASA Landsat-C earth resources technology satellite and the NASA PIX (Plasma Interaction Experiment). The spacecraft will be ejected from the second stage of the two-stage Thor-Delta 2910 launch vehicle 5120.6 seconds after lift-off, at an approximate position of 78 degrees N. latitude and 15 degrees W. longitude. Programmed orbital parameters are:

- Apogee** 928 km (577 statute miles)
- Perigee** 884 km (549 statute miles)
- Period** 103 minutes
- Inclination** 99.0 degrees
- Time of Descending Node** 9:30 AM  
(launch window from 1754-1824 UTC)



1. Guard bands to avoid interference to beacons. These frequencies are available for emergency and bulletin stations.
2. RTTY and slow-scan television are placed at the edge of the CW and ssb passbands. This conforms to their high-frequency use where RTTY is present within the CW space, and SSTV is transmitted in the ssb sub-band.
3. Mixed-mode area is recommended for crystal-controlled stations, DXpedition stations, or anyone wishing to work both CW and ssb stations.

fig. 1. Basic satellite band plan proposed by G3ZCZ and adopted by the AMSAT Board of Directors in October, 1977. This band plan allocates a percentage of the available radio frequency spectrum as seen on the downlink to different modes of communication. The relative amount of spectrum for each mode is thus the same for any transponder in any satellite. Band plan frequencies for AMSAT OSCARs 7 and 8 are shown in fig. 2.

The orbit is planned to be sun-synchronous with passes repeating at the same time each day on a one-day cycle (as opposed to the two-day cycle of OSCARs 6 and 7).

### spacecraft initialization

AMSAT-OSCAR D will automatically be powered up upon ejection from the Thor-Delta launch vehicle over northern Greenland at which time it will assume the next available number in the OSCAR series. It is designed to initialize itself in Mode J (two-meter-to-70-cm transponder ON). The two-to-ten meter (Mode A) transponder will be initialized OFF and should be kept off until the spacecraft is nearly completely stabilized, which may require as much as a

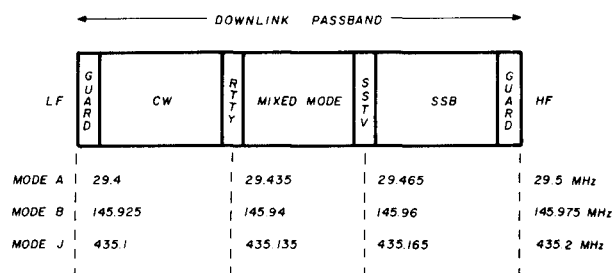


fig. 2. Satellite band plan for AMSAT OSCAR 7 and 8. As shown in fig. 1, this plan is based on percentages of the downlink passband, and applies to both inverting and non-inverting transponders. In Modes A and J the guard channels are 5 kHz wide; the guard channels in Mode B are 2.5 kHz wide.

week. Because of the non-rigidity of the deployable ten-meter dipole antenna, this antenna must *not* be deployed until the spacecraft spin rate is less than 1 rpm; otherwise, the antenna may be severely damaged or may not deploy properly. OSCAR D's ten-meter antenna is comprised of tubular extendable members which are slowly unreeled from the spacecraft by small motors. The deployment process takes approximately 15 seconds and is non-reversible (*i.e.*, the antenna elements cannot be retracted once they are deployed). During the time when the antenna is being deployed, the telemetry beacon switches from its normal Morse code format to a series of keying pulses, the rate of which is a function of the tip-to-tip length of the ten-meter dipole; the rate-of-change of the telemetry pulses will be carefully tape-recorded during deployment of the antenna to permit analysis later to verify success.

### telecommand verification

OSCAR D's telecommand and telemetry systems have been designed to provide two means to verify whether the spacecraft is accepting commands. First, when the telecommand system has been enabled and is ready to accept a command, the Morse code telemetry will be interrupted and an unmodulated carrier will be heard on the beacon frequency. The beacon will revert back to Morse code telemetry when the telecommand system is no longer enabled.

The second method of telecommand verification is to use the "Ten-meter Antenna Deployment" command. This will cause a series of keying pulses to be heard on the telemetry beacon in place of the Morse code telemetry if the command has been accepted. The "Ten-meter Antenna Reset" command should be sent soon afterward to restore the beacon to the Morse code telemetry mode.

### telemetry interpretation

The most important telemetry channel that will af-

fect operations decisions is *channel 3* (battery voltage). In Mode A the spacecraft should maintain a positive power budget so there should not be a net discharge of the battery over an orbit average. Mode J operation, however, requires somewhat more power, which may result in a net discharge of the battery, especially under conditions of high transponder loading; therefore it will be necessary for telemetry and telecommand stations to keep a close watch on the battery voltage so that action can be taken as necessary to command the spacecraft into Mode D (the recharge mode) before the battery discharges too far. Three cutoff levels are specified below:

- Red Level A** (1.2 volts/cell) Channel 3 = 61 counts
- Red Level B** (1.1 volts/cell) Channel 3 = 50 counts
- Red Level C** (1.0 volts/cell) Channel 3 = 38 counts

Red Level **A** should be used during the first year or so of the spacecraft's life as the cutoff point below which telecommand stations should command the satellite into Mode D for recharging. Later in the spacecraft's life, as the battery discharge characteristic curve changes, Red Level **B** should be used; Red Level **C** should be used if there is evidence of battery deterioration or if it is desired to recondition the battery.

**Channel 1** (solar array current) provides an indication of whether the spacecraft is in the sun or eclipse (it should read in the nineties in counts when in eclipse). Fluctuation in channel 1 telemetry is the best indicator of the rate of spin of the spacecraft, along with observations of fading, particularly of the 435-MHz Mode J downlink signal from the quarter-wave 435-MHz monopole antenna.

**Channel 2** (battery charge-discharge current) gives information on whether the battery is charging or discharging. A reading larger than 50 counts indicates that the battery is charging, while a reading of less than 50 counts means the battery is discharging. There is a two-second integration time associated with the current telemetered on this channel. The total power drain of the spacecraft can be determined by observing channel 2 while the spacecraft is in darkness (as indicated by channel 1, which should read in the 90s in darkness).

**Channels 4 and 5** (baseplate temperature and battery temperature) should generally track within a few degrees (except perhaps in the first day or so after launch when the spacecraft has not yet stabilized at thermal equilibrium). Experience from OSCARs 6 and 7 indicate that the battery can overcharge and overheat during periods of the year when the spacecraft

sees the most sunlight. If this is the case, channel 5 may exceed channel 4 in temperature by 10 degrees celsius or more, and action should be taken to reduce this overheating. This can be accomplished by keeping the spacecraft in Mode J to consume any extra charge current from the battery.

**Channel 6** is a measure of the Mode J transponder 435-MHz rf power output. Associated with the telemetered readings is an integration time of 2.5 seconds, so that it is average power rather than peak power that is telemetered. There is no telemetry of the Mode A transponder. The Mode A transponder power consumption (largely determined by power amplifier current) can be measured by observing channel 2 telemetry as noted above.

### operating schedule

Since the prime mission of the AMSAT-OSCAR D spacecraft is to use the Mode A transponder for the ARRL OSCAR educational program in schools, the spacecraft may be left in Mode A during weekdays (Monday through Fridays, United States time), and put in Mode J on weekends. Note that all communications should conform to the G3ZCZ band plan shown in **figs. 1** and **2**. Additionally, if not an excessive burden on the telecommand stations, evening orbits in the Western Hemisphere (morning orbits in the Eastern Hemisphere) can be switched to Mode J, battery permitting. In any case, all operation in Mode J will require careful monitoring of the battery charge level (as indicated from channel 3 telemetry). The power budget may not support the Mode J transponder for continuous fulltime operation in this mode over an entire weekend. In any event, details of the operational modes of the spacecraft will be announced by AMSAT in the *Newsletter*, with late updates on the AMSAT Nets.

OSCAR D will operate in a 900 km (560 statute mile) orbit, *i.e.*, at just over half the altitude of the orbit of OSCAR 7. Thus, communication ranges will be different. The usable time on an overhead pass will be about 18 minutes instead of the 22 minutes provided by OSCAR 7, and the horizon range will be 3220 km (2000 miles) instead of the 3940 km (2450 miles) of OSCAR 7. This means that transatlantic communications will still be possible, but not as often as with OSCAR 7.

Keeping track of this satellite is going to be much simpler than for OSCAR 7. It will come into range at approximately the same time each day; the overhead descending node pass is planned for 9:30 AM local time.

### credits

It is impossible to single out all those who contrib-

uted to the construction of the spacecraft, but a few calls can be listed.

JAMSAT — Mode J Transponder: JA1ANG, JA1CBL, JG1CDM, JA1VDV, JA1JHF, JR1SWB

AMSAT — Mode A Transponder: WA4DGU, W3PK

Morse Code Telemetry System: W5CAY, WA4DGU

Telecommand System: W3GEY, WA3LND, WA3ZCE, W3HUC, W3ITO, K1RT/WA1JZC

Antenna and Antenna Deployment Module: W3GEY, W3HUC, W3ITO, K1RT, WA3LND

Power System: DJ4ZC, JA1TUR, JF1DMQ, K1RT, W3HQ


Structure and Module Containers: K6GSJ and Project OSCAR, K1JX/WA1JLD, K1RT, WA4DGU, VE3DPB, W3HSO, WB0GIM, Henry Smith, David Vanderbeke, W3ZKI

Cables and Wiring: Marie Marr, W3TMZ


Engineering Drafting: WB4GIB

To others who contributed or assisted, our thanks and the thanks of thousands of radio amateurs, school children, and educators. Let's use the satellite wisely so that it will further help the educational program until the Phase III satellites are flying high.

**ham radio**

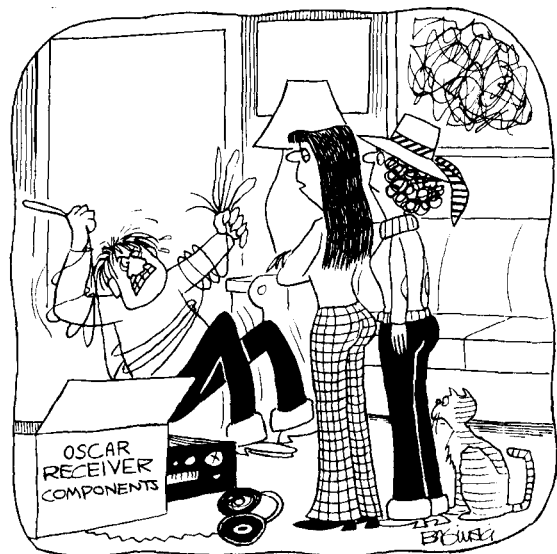

"Alfred was never any good in a crisis!"

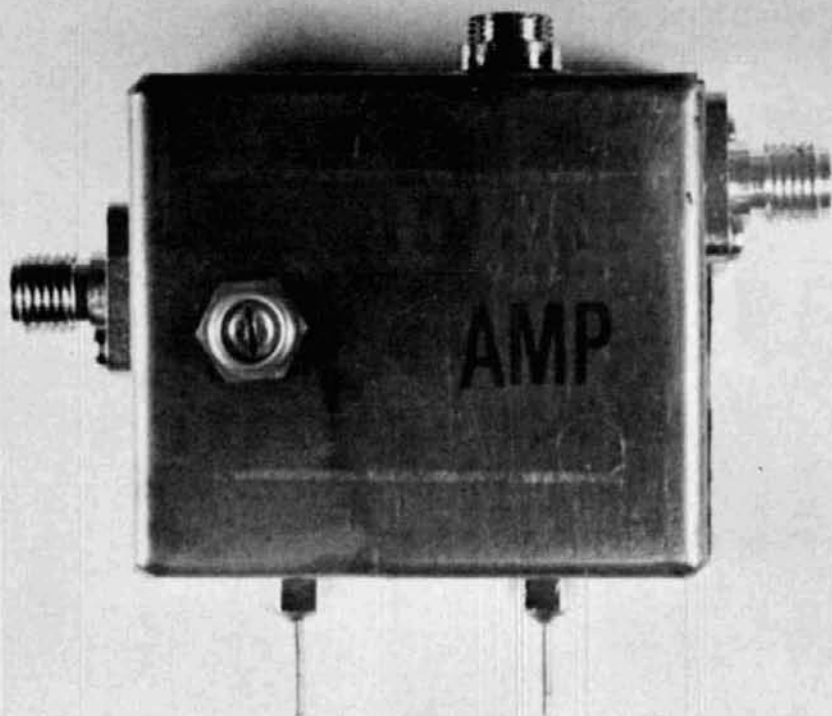

## very low-noise GaAs FET Preamp for 432 MHz

Construction details  
for a uhf GaAs fet preamp  
that will provide  
a 0.7 dB noise figure  
with 18 dB gain  
at 432 MHz

Every amateur who is active on the uhf bands is looking for ways to improve his system performance. One of these ways is to use a receiver preamplifier with lower noise figure and higher gain; some excellent preamplifier circuits have been published in *ham radio*. The low-noise uhf preamplifier described by W1JR in the March, 1975, issue is perhaps the best known of these circuits,<sup>1</sup> and is widely used by EME operators and others who are interested in long distance, weak-signal uhf communications.

This article describes a low-noise, state-of-the-art preamplifier for 432 MHz which uses an NEC NE24406 (2SK85) GaAs fet. This preamp is capable of a 50°K (0.7 dB) noise figure at 423 MHz, so it can improve the performance of your uhf receiving system by about 100°K, as compared with a conventional bipolar transistor.

**By Shigeru Sando, JH1BRY, 8-17-204 Sakonyama Asahi-ku, Yokohama 241, Japan.** Mr. Sando is a microwave semiconductor development engineer at the Semiconductor Division of the Nippon Electric Company.



## field-effect transistors

The history of the fet is older than most people realize. In fact, it's one of the oldest three-terminal solid-state devices. Dr. Shockley first proposed the fet in 1952, but because of a variety of technological and fabrication difficulties, fets did not become practical until the early 1960s.

Basically, there are three different types of fets. The junction fet or *jfet* is the simplest of the three types and became commercially available about the same time as the first bipolar microwave transistors.

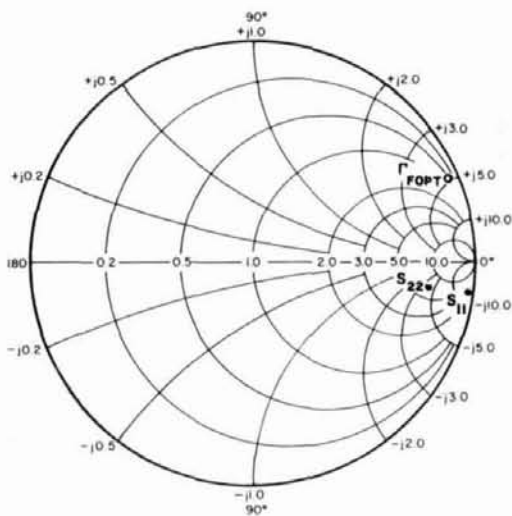


fig. 1. Smith chart plot of the NE24406 impedance characteristics at 432 MHz.  $\Gamma_{FOPT}$  is the optimum source impedance for noise figure at 423 MHz.

Advances in fabrication techniques and requirements for lower power fostered the development of the metal-oxide-semiconductor fet or *mosfet*. Both the *jfet* and *mosfet* are widely used in applications which require high input impedances, such as in the input stages of test instruments. The same fabrication processes developed for *mosfets* are also useful in the manufacture of integrated circuits.

In the microwave region the bipolar transistor has reigned supreme for a number of years — it wasn't threatened by either the *jfet* or the *mosfet*. However, a third type of fet has changed that. This new fet, which uses a Schottky barrier at the gate electrode, is called the metal-semiconductor fet or *mesfet*. Mesfets use Gallium Arsenide (GaAs) as the semiconductor material and are usually referred to as GaAs fets (pronounced *gas* fets).

Gallium arsenide has high electron mobility (5 to 7 times as high as silicon), and offers significant advan-

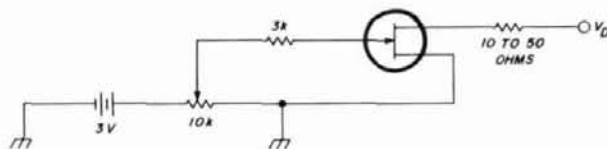



fig. 2. Recommended GaAs fet bias circuit uses a series resistor in the gate circuit to protect the device from transients.

tages over silicon at microwave frequencies. The intrinsic characteristics of GaAs result in shorter transit times and lower resistance, thereby providing higher gain, lower noise figures, and extremely high cut-off frequencies — all important characteristics for microwave transistors.

Gallium arsenide has been under development for several years, and practical microwave GaAs fets are now available off the shelf. Recently I had an opportunity to experiment with the NEC NE24406 (2SK85) GaAs fet. Although there have been many published reports which describe the performance of the NE24406 in amplifiers up to X band (about 12 GHz), there have been no published data on their use below 500 MHz. This article describes the first experimental results of the NE24406 GaAs fet on the amateur 70 cm band.
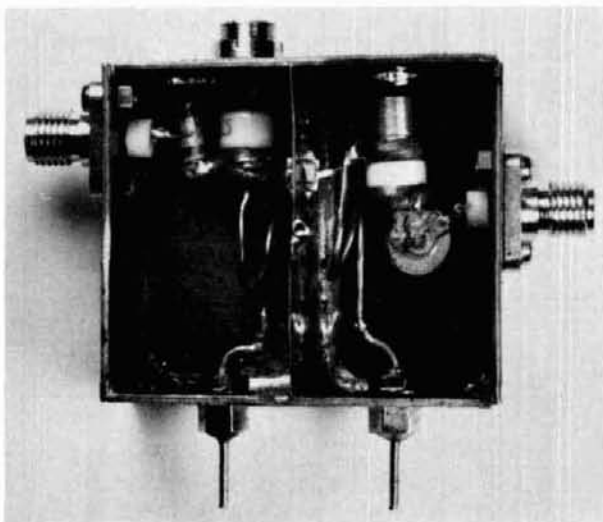
## noise figure

Obviously a transistor with a low noise figure is required in a low noise preamplifier, but that's not the



Layout of the low-noise 432-MHz preamplifier. The input is to the left, output to the right. The GaAs fet is installed in the center shield partition. Capacitors C1 and C3 are supported by their own leads; C2 (left compartment) and C4 (right compartment) are mounted in the side walls of the chassis.

only requirement. Also to be considered are the effects of the next stage's noise figure and the requirements for a low-loss matching circuit, low feedback, and good stability.

The overall noise figure of a receiving system is given by the following formula

$$NF_T = NF_1 + \frac{NF_2 - 1}{G_1} \quad (1)$$

Where

$NF_T$  = Total overall noise factor

$NF_1$  = Noise factor of the first stage


$NF_2$  = Noise factor of the second stage

$G_1$  = Available power gain of the first stage

Note that the noise factors and power gains must be in ratios, *not* in dB. For example, consider that you have a preamplifier with a 1.0 dB noise figure ( $NF_1 = 1.259$ ) and 10 dB power gain ( $G_1 = 10$ ); the noise figure of the second stage is 5 dB ( $NF_2 = 3.162$ ). The calculated overall noise factor  $NF_T$  is 1.475 (or a noise figure of 1.688 dB).

Note that the system noise figure has increased about 17 per cent as compared to the preamplifier's noise figure. For best results, it's recommended that you use a lower noise second stage with a higher gain preamp.

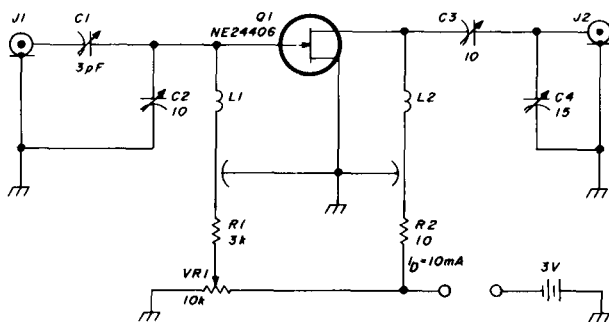One question that often arises is, "Can the noise figure of the preamplifier be as low as the noise figure of the transistor itself?" No, it cannot, even on the



- C1 3 pF piston trimmer (Johanson 7274 or 7284)
- C2, C3 10 pF piston trimmer (Johanson 5202)
- C4 15 pF piston trimmer (Johanson 5402)
- L1, L2 1 turn no. 20 (0.8mm), 1/4" (6mm) ID (see fig. 5)
- J1, J2 SMA type coaxial connectors
- Q1 NEC NE24406 GaAs fet

fig. 4. Schematic diagram of the low-noise preamp for 432 MHz which provides a 0.7 dB noise figure and 18 dB gain. Lowest noise figure occurs at drain current flow of 10 mA (see fig. 7).

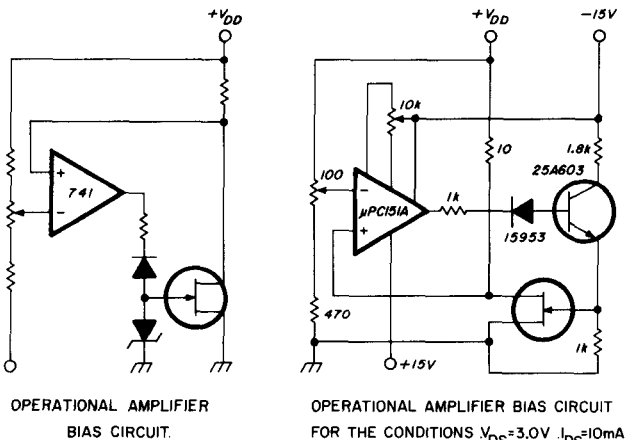
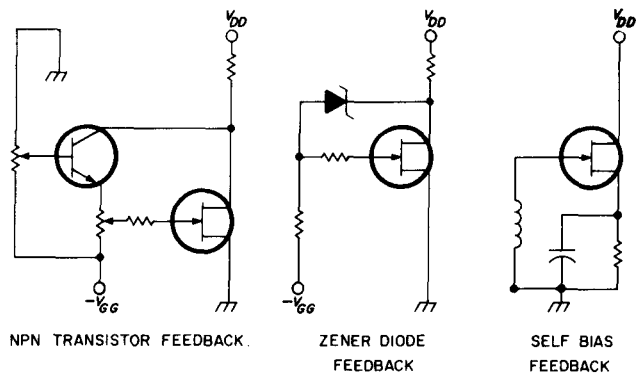


fig. 3. Several circuits that may be used to provide bias in fet circuits. Note that all circuits must be bypassed at rf.

assumption that there are no matching or circuit losses. One way to describe the optimum noise figure of a transistor is *noise measure* which is expressed as

$$M + 1 = \frac{NF - 1}{1 - \frac{1}{G}} \quad (2)$$

where

$NF$  = Noise figure of the transistor

$G$  = Associated gain of the transistor

The value of  $M + 1$  shows the ideal total system noise figure, and indicates the same result where an infinite number of transistors with the same characteristics are used in cascade.

Assume you have a transistor which has a specified noise figure of 1.2 dB ( $NF = 1.318$ ) and 14 dB gain ( $G = 25.12$ ). From eq. 2

$$M + 1 = \frac{1.318}{1 - \frac{1}{25.12}} = 1.351 \text{ or } 1.243 \text{ dB}$$

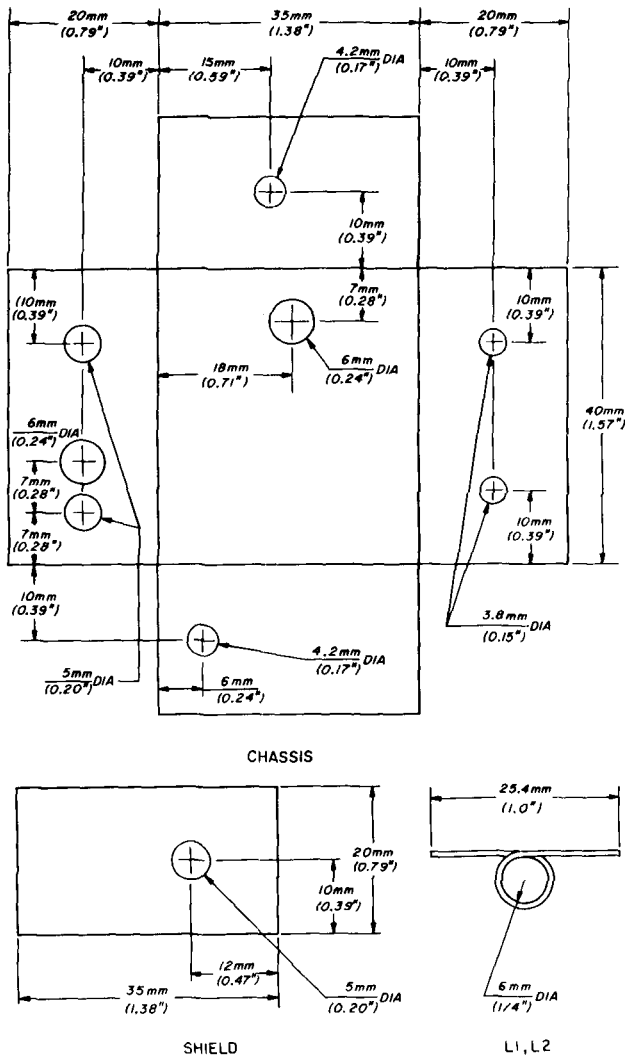


fig. 5. Layout of the low-noise GaAs fet preamp for 432 MHz. The enclosure is made from brass sheet, 0.028"–0.048" (0.7–1.2mm) thick.

This shows the minimum value of amplifier noise available from a transistor with a 1.2 dB noise figure and 14 dB gain (assuming no matching or connector losses).

### circuit description

The GaAs fet has several disadvantages which make it somewhat more difficult to use than the bipolar transistor. For one thing, as shown in the Smith chart plot of fig. 1, the impedances are very high. This also indicates that the GaAs fet is a high  $Q$  device and not easy to match to low impedances such as 50 ohms. Also to be considered is the bias circuit. Once an operating point has been established for the GaAs fet, a bias circuit must be chosen which will provide stable operation over the required temperature and frequency range.

The importance of affording adequate protection against transients and change in  $I_{DSS}$  cannot be over emphasized. As every designer who uses GaAs fet will eventually discover, transients are the leading "fet killer." The most likely burn-out mode is a short from gate to drain or from gate to source which is caused by high field or high current transients. The highest field in common-source operation is between the drain and gate, and should never exceed 10 volts.

The best way of applying bias is to use a battery through a series resistor to the gate, as shown in fig. 2. Although two power supplies are normally required, a source resistor may be used to develop the necessary reverse bias, but it may reduce both gain and noise figure. Several bias circuits are shown in fig. 3. It should be mentioned that all bias circuits must be bypassed to rf; a series gate resistor from 1000 ohms to 10k will protect the gate from high-frequency transients.

For best performance a low-loss input matching circuit is very important; low-loss components should be used in the simplest possible low  $Q$  circuit. As can be seen in the Smith chart plot of the NE24406's S-parameters,  $|S_{11}|$  and  $|S_{22}|$  are very large; the optimum source impedance for noise figure,  $\Gamma_{FOPT}$ , is also very high. Fortunately, the optimum source impedances for gain and noise figure are not greatly different. Therefore, the input matching circuit can consist of a series capacitance or inductance. Since the series reactance must be carefully selected, the capacitor has the advantage of being easily tuned.

Theoretically the preamplifier will work fine with only a series capacitance in the input circuit, but the NE24406 can provide 12 dB gain in the 4-GHz band, so there's a possibility of oscillation outside the 430-MHz band. The parallel resonant circuit, L1-C2, in fig. 4 suppresses these oscillations. L1 is also used to supply bias to the gate of the GaAs fet. The resonant impedance of L1-C2 is very high, and input matching is actually provided only by C1.

As was shown in eq. 2, the noise figure of a transistor amplifier depends greatly on the available gain of the device being used. Since a gain increment of 4.0 to 4.5 dB ( $|S_{22}| \cong 0.8$ ) can be anticipated at 432 MHz for the NE24406 when the output is matched,

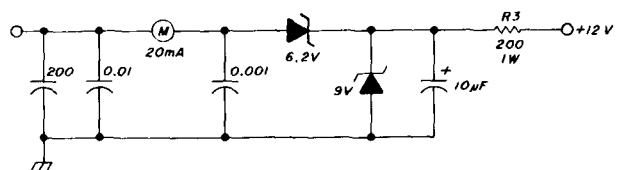


fig. 6. Recommended drain voltage supply circuit for the NE24406 GaAs fet preamplifier.

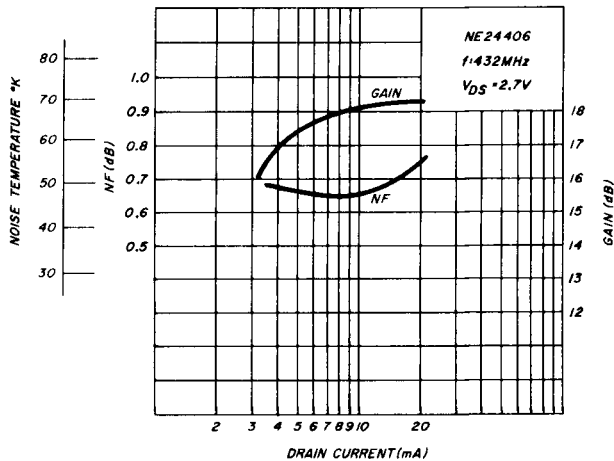


fig. 7. Preamp noise figure and power gain as a function of drain current. Note that lowest noise figure occurs at  $I_D = 10$  mA.

improper output matching will degrade noise figure. Since the output impedance of the GaAs fet is extremely high, I installed a simple parallel resonant circuit at the output (L2, C2, C3), and matched to the 50-ohm output with the capacitive portion of the network. Both the input and output circuits have relatively high  $Q$ , so stable operatin is obtained over a narrow bandwidth.

**construction**

Basic construction of the low-noise 432-MHz preamplifier is shown in fig. 5. The enclosure is made from no. 18 to no. 22 (0.028-0.048 inch or 0.7-1.2mm thick) brass sheet. Do not omit the center shield — it's absolutely necessary to obtain stable operation.

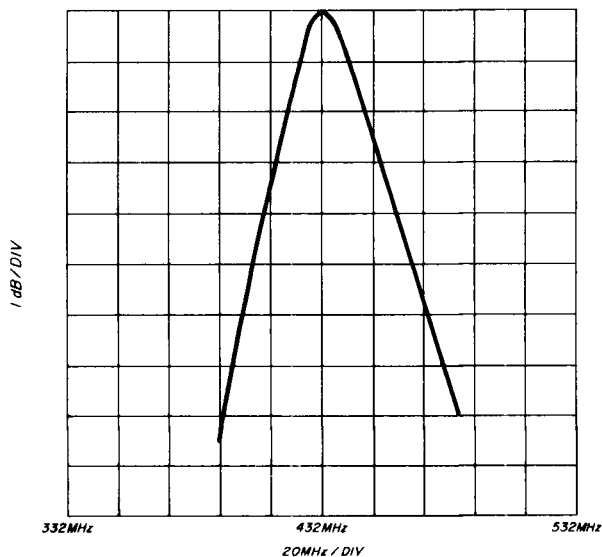


fig. 8. Passband response of the low-noise 432-MHz preamp; gain is 3 dB down at approximately 414 and 456 MHz.

Although no particular care is required when mounting the GaAs fet, the source leads should be separated and soldered directly to the holes in the shield plate. Also, when soldering the drain and gate leads to the input and output coils, take care not to pull on them too strongly.

Any type of coaxial connector may be used at the input and output, but for best noise performance it's important that the connector have good uhf characteristics. The losses of BNC connectors will degrade the noise figure. I used type SMA connectors. Type N or TNC connectors could also be used, but SMA types are much smaller and therefore more suitable

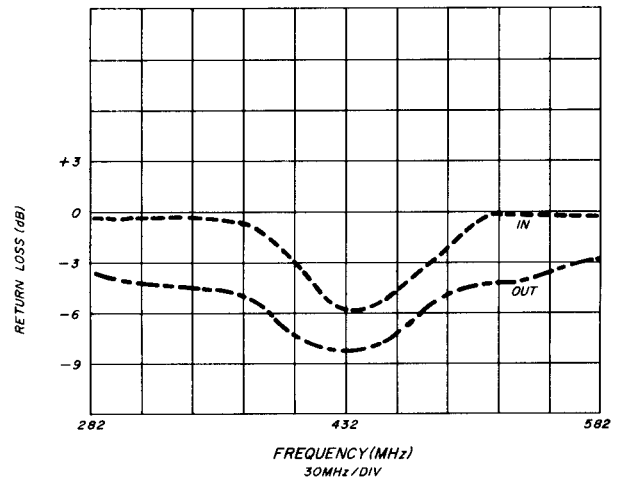


fig. 9. Return loss (vswr) of the GaAs fet preamp.

for a miniature low-noise preamplifier such as this one.

**operation and test**

After construction is completed, inspect each part to make sure you haven't made any wiring errors. The components in the bias circuit should be checked and double checked. When you are satisfied that the circuit is correctly built, the bias and drain supply voltages should be applied to the GaAs fet in the following manner:

1. Voltage is initially applied to the gate circuit with a 3-volt battery (see fig. 4). This reverse biases the gate and prevents current flow in the drain circuit, which may reach the magnitude of  $I_{DSS}$ . There is no problem in allowing current flow up to  $I_{DSS}$ , but the intention here is to suppress any transient phenomenon due to this current (there are examples where  $I_{DSS}$  reaches 100 mA).
2. Next apply the drain voltage, but make sure that the voltage between drain and source,  $V_{DS}$ ,



does not exceed 3 volts. When the drain voltage approaches 2.7 volts, the drain current should be set to 10 mA by adjusting the 10k pot in the bias circuit.

With the completion of these two steps, amplifier bias is established. A recommended drain bias circuit is shown in **fig. 6**.


Note that when a reverse bias is applied to the gate and drain, and current flows with only a slight application of drain voltage, either the gate circuit is open or a breakdown has occurred in the GaAs fet.

After completing the bias adjustments, adjust the input tuned circuit to resonance with a grid dipper. Apply a *weak* signal in the 430-MHz band and tune C1, C3, and C4 for maximum gain. When the preamp is adjusted for maximum gain, the noise figure will deteriorate slightly, but not seriously.


## performance

The performance of the GaAs fet preamplifier is shown in the graphs of **figs. 7, 8, and 9**. The plot of noise figure vs drain current (**fig. 7**) shows that lowest noise figure occurs at  $I_D = 10 \text{ mA}$ . The band-pass characteristic of the preamp is shown in **fig. 8**; when the preamplifier is peaked up to 432 MHz, gain is 3 dB down at approximately 414 and 456 MHz. In most applications no external bandpass filter should be required. **Fig. 9** shows the vswr at the input and output of the preamplifier. The *third-order IMD* products are shown in **fig. 10**; 1 dB compression occurs at about 0 dBm — the third-order intercept point is at a very respectable +20 dBm (100 mW).

When this preamplifier is adjusted for maximum

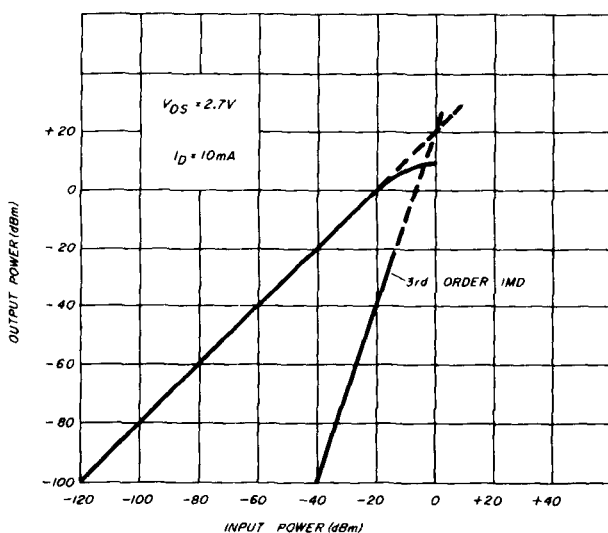

**fig. 10. Input-output characteristics of the GaAs fet preamp. Third-order intercept point is at +20 dBm (100 mW); 1 dB compression is at approximately 0 dBm (1 mW).**

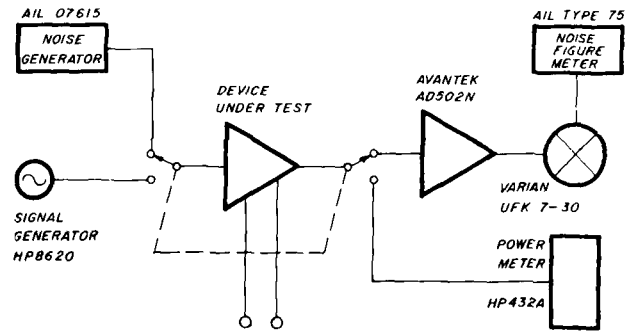

**fig. 11. Block diagram of the noise-figure measurement set-up used by JH1BRY when evaluating preamplifier performance.**

gain, the measured noise figure is about 0.75 dB. If an automatic noise figure meter is available, the input and output circuits can be adjusted for best noise figure — my measurements indicate that a noise figure improvement of about 0.1 dB is possible.

When making noise-figure measurements, I use an AIL noise-figure meter with a *solid-state* noise source (**fig. 11**). Gaseous-discharge noise sources are also available for this frequency range, but they should *never* be used with fragile GaAs fet circuits which are susceptible to damage from surge transients.

## summary

This GaAs fet preamplifier should bring you right up to the state-of-the-art in noise figure at 432 MHz. The NE24406 GaAs fets are available in the United States from California Eastern Laboratories\* or one of their sales representatives.


I would like to express my deep appreciation to Aki Munezuka, JA1VDV, for providing me with detail information on 432-MHz EME and kindling the fire of uhf ssb, and to Carl Peterson, K6VJN, who gave me an opportunity to publish this article. I also wish to thank the Nippon Electric Company for the use of test equipment and devices necessary to design this preamplifier. Special thanks go to Haruo Yoneda, JA1ANG, for all his helpful suggestions.

\*California Eastern Laboratories, Inc., One Edwards Court, Post Office Box 915, Burlingame, California 94010; telephone (415) 342-7744. The NE24406 is priced at \$190.00 in small quantities. After this article was written, NEC announced the basic GaAs fet in a smaller package at a lower price; this device is designated the NE24483 and is priced at \$120.00.

## references

1. Joseph Reisert, W1JR, "Ultra Low-Noise UHF Preamplifier," *ham radio*, March, 1975, page 8.
2. Jerry Arden, "The Design, Performance, and Application of the NEC V244 and V388 GaAs FET," California Eastern Labs, Burlingame, California, June, 1976.

ham radio

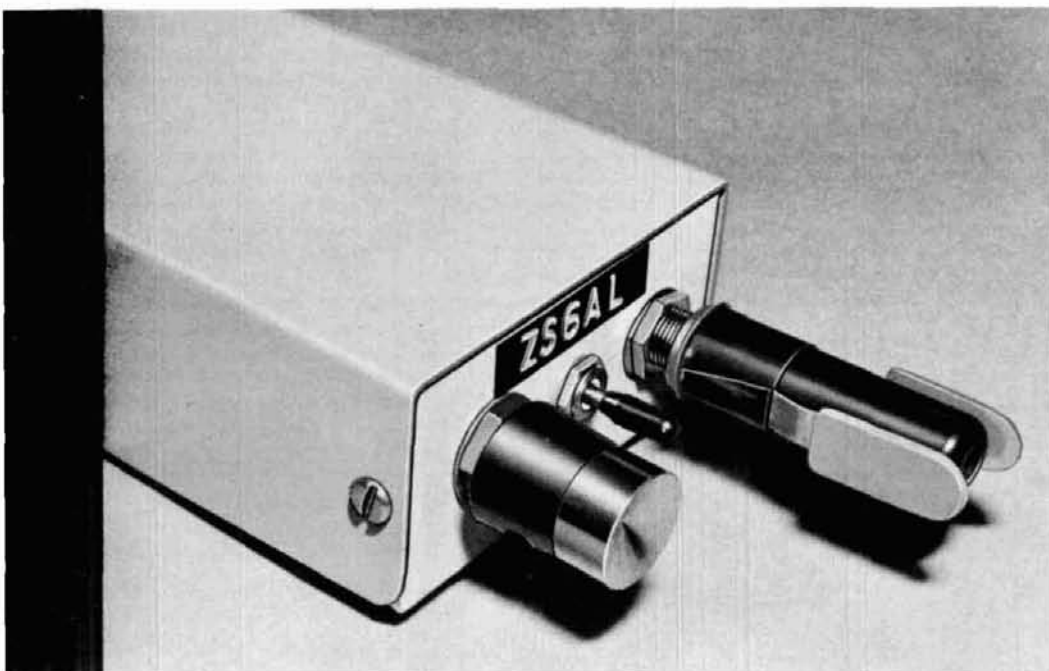

## simple paddle

### for electronic keyers

Construction details  
for the  
Ambidextrous Paddle  
for Electronic Keyers  
OR APEK

**The need may arise for** the serious CW operator to take a battery operated electronic keyer on a mobile trip or to environments where a heavy fixed station dual-lever paddle simply has to stay home. I have improvised several keying devices in the past which provide comfortable keying of the mobile or portable

rig under the varied conditions typical of such excursions. These devices were, however, all of the single lever variety that either had to be wedged, clamped, or clipped on to something, and moreover, had an extra lead going to the keyer — a nuisance at the best of times.

The keying paddle described here is essentially a dual-lever device which has proved to be so versatile that most of the problems typical of portable or mobile operation could be surmounted. As a matter of fact since inventing this Ambidextrous Paddle for Electronic Keyers, which I call APEK, the heavy dual-lever paddle at the fixed station has hardly been used at all.

The APEK is basically a three-contact jack plug with a few bits and pieces added, the total cost of which is hardly worth mentioning. Should a particular keyer, however, not be fitted with a jack type paddle socket, such a socket will have to be mounted on the front panel in a convenient position and connected in parallel with the existing socket. Since the

**By Vidi la Grange, ZS6AL, 3 Elgar Street,  
Vanderbijlpark, 1900 Republic of South Africa**

APEK plugs directly into the keyer, it can be rotated to have the dot lever at the right or left — a real ambidexter! As a matter of fact, it can be rotated into any convenient angle depending on the orientation of the keyer, which, during mobile or portable work can be just about anything imaginable.

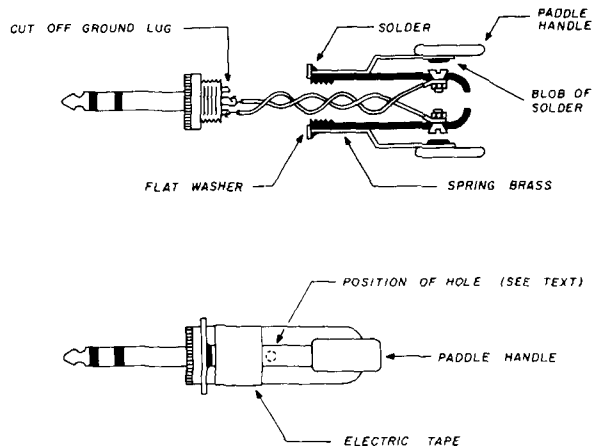


fig. 1. Construction of the Ambidextrous Paddle for Electronic Keyers or APEK. The paddle is built completely from junk-box parts, as described in the text.

The keyer shown in the photograph was built into a box which fits snugly into the car's door box. The APEK sticks out vertically so you can reach it without effort. Another attractive feature is the fact that the APEK is compatible with dual-lever keying devices. Squeeze keying features, if provided, don't have to be sacrificed when using the APEK, a feature impossible to achieve with single-lever keying devices.

### construction

Obtain a standard three-connector jack plug and remove the shell. Cut off the ground connection close to the jack body. Drill and countersink two opposing holes in the plug shell about 8 mm (5/6 inch) from the unthreaded end. The holes should be suited to take two 2.3 mm by 4 mm (3/56 x 5/32 inch) countersink machine screws.

Take two small solder lugs and connect about 60 mm (2-1/4 inch) of thin flexible hook-up wire to each. Fit one of these lugs to each screw on the inside of the shell and secure with a nut. Find a suitable flat washer which will fit over the threaded part of the jack body and having an outside diameter slightly larger than that of the shell.

Prepare two strips of spring brass approximately 0.5 mm (1/64 inch) thick, 5 mm (3/16 inch) wide and 40 mm (1-1/2 inches) long. De-burr the edges and bend them into the shape shown in fig. 1. Solder these strips to the rim of the flat washer in opposing

positions. This step can be simplified by temporarily assembling the plug. Mark off, on the underside of each strip, the positions of the screw heads fitted to the shell.


Disassemble the plug, clean and tin the positions marked off on the strips. Form a small blob of solder at these points and file them lightly to give a flat contact surface. Solder the two pieces of hookup wire, already connected to the screws on the shell, to the inner and outer lugs of the jack. Leave these wires long enough to survive the twist they will get when putting the jack together.


Shape two pieces of old PC board according to taste or as shown in fig. 1 to form the paddle handles. Fix them to the brass strips with a small amount of epoxy. Finally, one or two wraps of electric tape cut to the correct width should be wound onto the jack shell. This will provide the necessary damping of the otherwise too springy brass strips.

### final adjustment

Contact spacing and spring tension can be adjusted by means of long nosed pliers. If you find that the spring tension is too high, a small hole drilled through the spring at the position indicated should do the trick. Then determine by experiment which side of the APEK activates dots or dashes and mark it for your convenience.

### ham radio

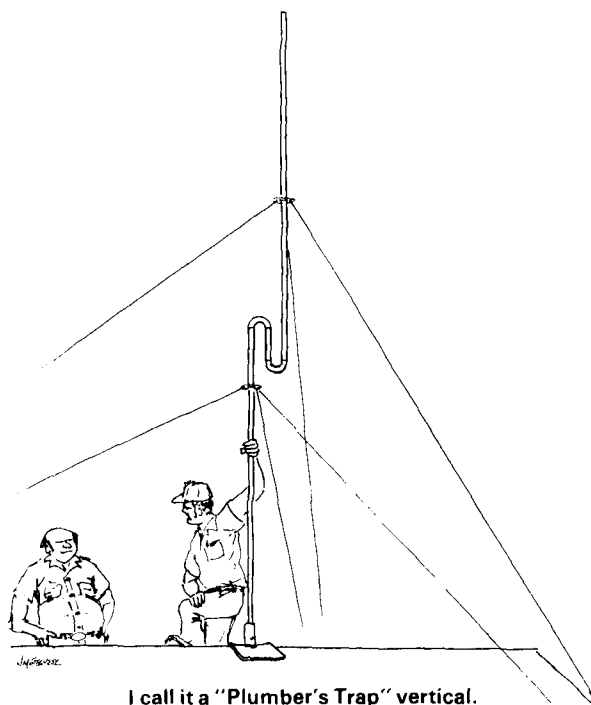

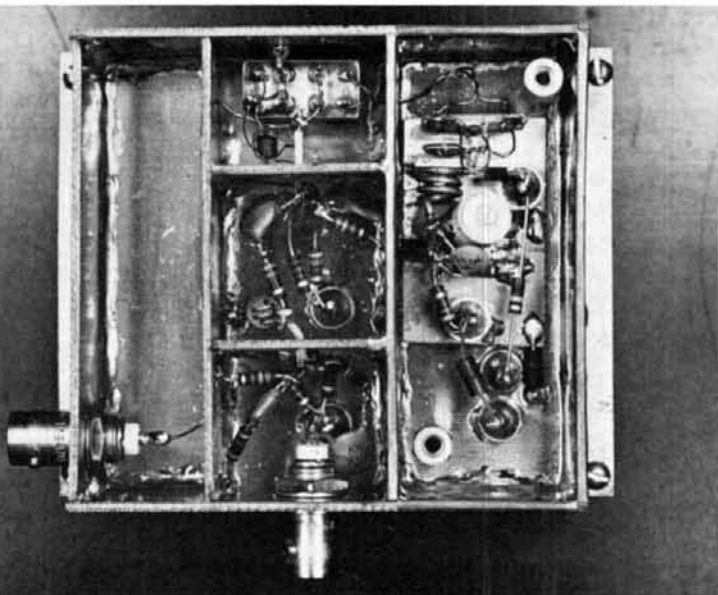

## spectrum analyzer tracking generator

**What is a tracking generator?** When used with a spectrum analyzer it generates a CW signal corresponding to the frequency at which the spectrum analyzer is tuned. It's useful for looking at filter response. Filter blowby and undesired responses can be readily observed.

The generator described here was built for use with the spectrum analyzer described in reference 1. A tracking generator identical to this one is now being used with a Hewlett-Packard 8554/141. The tracking generator can be used with almost any spectrum analyzer that provides first-local oscillator output and has a first i-f of  $200 \pm 20$  MHz.


Because of the tracking generator's oscillator instability, narrow-bandwidth measurements can't be made, such as the bandpass response of crystal filters. Nevertheless, it's useful for measuring responses at other frequencies (parasitic resonances) often found in crystal filters.

### circuit description

The schematic is shown in **fig. 2**. Q1 and Q2 provide some gain and isolation between the 200-MHz oscillator, Q3, and the first i-f amplifier of the spectrum analyzer. R1 provides fine tuning and should be located for easy access by the operator. MX1 mixes the 200-MHz output with the signal from the first local oscillator to provide the 100-kHz to 100-MHz tracking signal. An optional 130-MHz lowpass filter is shown. The lowpass filter attenuates the 400-500 MHz component generated by the mixer in the tracking generator.

The tracking generator is built in a box made from 1/16-inch thick (1.5mm) copper-clad board. The same board is used as separators between stages. Paper-thin copper, available from hobby shops, is wrapped over the surface where the cover for the 200-MHz oscillator attaches. The other stages do not have shield covers. A blank compartment is available for the optional 130-MHz lowpass filter. **Fig. 1** shows the layout.

The oscillator is built on a separate piece of copper-clad board, 7/8 x 1-1/2 inch (22x38mm) and

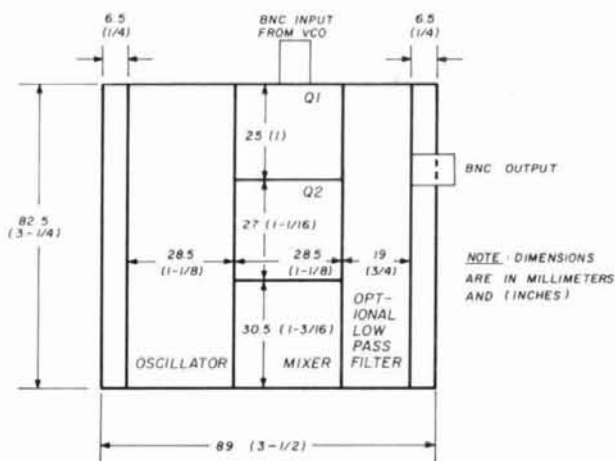

**fig. 1.** Circuit-board layout. Shielding is important for the 200-MHz oscillator compartment (see text).

By Wayne Ryder, W6URH, 115 Hedge Road, Menlo Park, California 94025

is held in place with double sticky-back tape. Two ferrite beads are strung on the ground wire that connects the oscillator ground to the compartment ground to minimize ground-loop currents, which can cause radiation from the oscillator. The mixer can be a standard mixer or the home-made mixer described in reference 1.

Dimensions shown inside are inside dimensions. The assembly is 1 inch (25.5mm) high. The 1/4 inch (6.5mm) overhang at each end is for mounting.

### operation

The spectrum analyzer vfo output is connected to the tracking generator input of the spectrum analyzer.

1. Set spectrum-analyzer bandwidth to 250 or 300 kHz and scan width to 100 MHz.
2. Set R1 to the center of its range.

3. Adjust C1 so that the baseline on the spectrum analyzer shifts up.

4. Move L2 away from L1 until the baseline starts to move down.

5. Install the shield on the 200-MHz oscillator and adjust R1 so that the baseline is as high as possible, consistent with a flat response. As the tracking generator is being used, the 200-MHz oscillator will drift, and some readjustment of R1 will be required.

### design considerations

One of the more challenging problems here is preventing the 200-MHz oscillator from radiating into the first i-f. If this happens, the baseline on the spectrum analyzer will shift up without a signal input. The signal from the oscillator will leak through MX1 backward through buffers in the tracking genera-

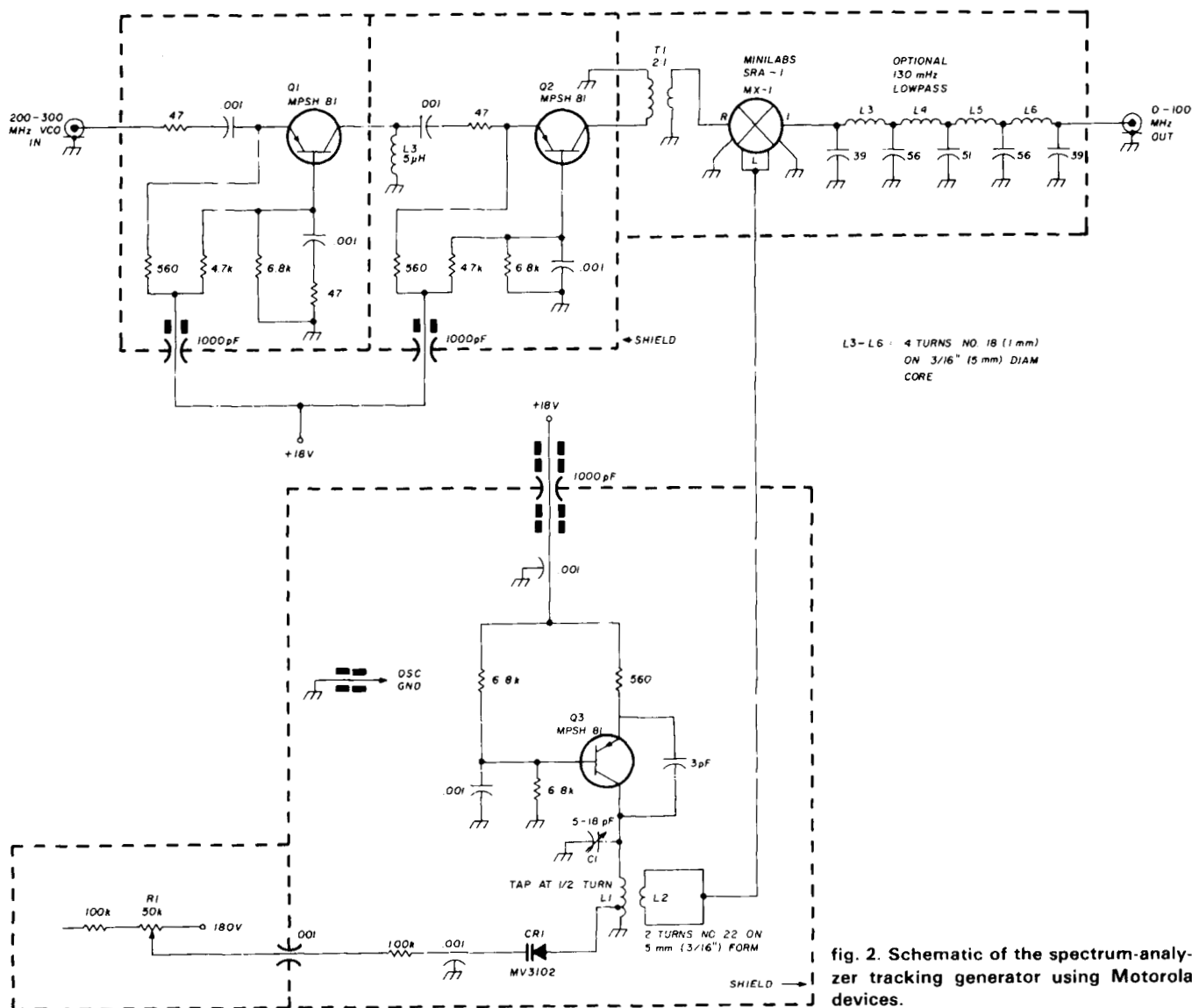


fig. 2. Schematic of the spectrum-analyzer tracking generator using Motorola devices.



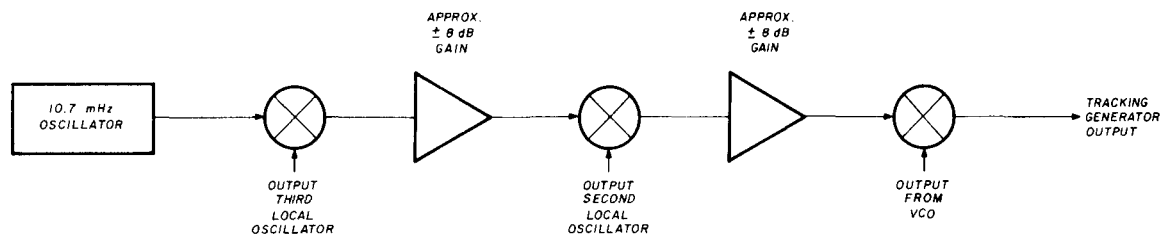


fig. 3. Suggestion for a tracking generator for measuring narrowband signals. Oscillators within the spectrum analyzer are used. A highly stable signal is provided.

tor, backward through any buffer in the vco and will follow the path of the vco to the first mixer in the spectrum analyzer and leak through the first mixer into the first i-f. This is not surprising, since the output from the oscillator is about 0.5 volt and the spectrum analyzer sensitivity is only a few microvolts. Also, the 200-MHz oscillator can radiate directly into the spectrum analyzer if both are not carefully shielded.

The tracking generator described here was mounted on the outside back of the spectrum analyzer to minimize coupling. If your spectrum analyzer has a

phase-locked vco, or if the vco is stabilized in some other way, you might consider a different form of tracking generator for measuring narrow bandwidth. This method uses the local oscillators within the spectrum analyzer and provides a more stable tracking-generator signal. The block diagram (fig. 3) assumes that the last i-f is 10.7 MHz.

### reference

1. Wayne F. Ryder, W6URH, "High-Performance Spectrum Analyzer," *ham radio*, June, 1977, pages 16-30.

**ham radio**

## zip-cord feedlines

Many years ago I watched as someone set up a rig in the desert. The power plant was set out, the rig was set up, and the antenna was strung out between two convenient cactus plants (cactus attain a respectable height here). The thing that caught my eye was the feedline. It consisted of a long length of garden variety zip cord. My funny look at it gained a quick assurance that lamp cord was a perfectly good feedline.

Everything seemed to work just fine and the operators had no trouble working out on the band of the day, which was 75-meter phone. In those days it was common to run 100 to 200 watts input with high level a-m.

After a recent move I decided to put up a 75-meter antenna at home and use the most economical feedline. In the process of getting on the air, intermediate forms of antennas were used. That means some wire of about the resonant length was thrown up on the roof, and the near end was run into the rig. It was somewhat of a disappointment to discover that the intermediate antenna worked better than the well elevated final installation. A little checking showed that when the feedline itself was loaded up, it worked better than the antenna it was supposed to be feeding. In short, it appeared that something was not quite right.

A little further investigation revealed some rather interesting facts. RG-8/U, RG-58/U, and lamp cord

were tested at 4 and 21 MHz. The rig was tuned up into a terminating type of wattmeter and the feedline under test was inserted between the rig and the meter. Power out with 60 cm (24 inches) of feedline vs power out with 9 to 18 meters (30 to 60 feet) of feedline was measured and the results were tabulated.

RG-58/U coax showed a 58 per cent loss at 21 MHz; it showed almost no attenuation at 4 MHz. RG-8/U gave about 12 per cent loss at 21 MHz.

Zip cord looked like it was best suited for use on the other end of a lamp or soldering iron. If you really want to know, it showed about a 60 per cent loss at 4 MHz. There was no need to measure it at 21 MHz!

About 20 meters (65 feet) of coax was used in the tests, and only 9 meters (30 feet) of zip cord (the rest of the zip cord was still attached to the antenna). Obviously, more lamp cord would have shown more loss. These tests were not conducted under laboratory conditions, but the variables were held to a reasonable level so that it was possible to reach a reasonable conclusion.

In any case, the zip cord came down and the RG-58/U went up. A crosstown telephone call got K7OXS on the air, again. Bill indicated that my 3-5 watt rig was back up to its normal signal strength at his location. He was almost as glad as I was that my antenna problems were finally resolved.

**Evert Fruitman, W7RXV**



Pictured  
with optional  
HD-1984 Micoder II™

# The HEATHKIT HW-2036A

...just that much better!

We'll give it to you straight! The HW-2036 was a great 2-meter transceiver – but our new HW-2036A is just that much better.

It boasts the same impressive specifications, but now gives you a full 4 MHz of coverage over any portion of its 143.5 to 148.5 MHz operating range.

But most startling of all is the price tag. At \$269.95\* in easy-to-build kit form, the HW-2036A is the lowest priced, synthesized 2-meter transceiver you'll find anywhere!

At Heath we're holding down the soaring cost of Amateur Radio. Look over our entire line of quality kit products. Then join the thousands of Radio Amateurs who've taken the sensible alternative – and built Heath!

**Heath Amateur Radio Gear...**  
**...the quality that measures up!**

More Details? CHECK – OFF Page 126

Send for your **FREE Heathkit Catalog** today!

Or you may obtain a catalog by bringing this coupon to one of the 50 Heathkit Electronic Centers coast-to-coast (units of Schlumberger Products Corp.). Where Heathkit products are displayed, sold, and serviced. Retail prices on some products may be slightly higher. See the white pages of your telephone directory.

Heath Company, Dept. 122-400, Benton Harbor, MI 49022



HEATH <b>Schlumberger</b>	Heath Company, Dept. 122-400, Benton Harbor, MI 49022
------------------------------	---

Please send me my FREE Catalog. I am not on your mailing list.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

\* Price is mail order, F.O.B. Benton Harbor, MI. Zip \_\_\_\_\_

Prices and specifications subject to change without notice.

AM-366

# constant-current battery charger for portable operation

Tired of pulling out  
your nicads for charging?  
Here's a neat method  
for keeping your batteries  
fully charged  
at all times  
in any location

The use of portable battery-operated equipment requires fully charged batteries to obtain maximum usefulness of the equipment. For handheld transceivers, keeping the batteries fully charged would normally require frequent overnight charging. If the handheld is operated in a mobile environment it must be removed often from the car to the battery charger. However, it's possible to charge the equipment's batteries while in use, thus always assuring a full charge and maximum lifetime from the batteries between charges.

A charging system has been developed that permits constant-current charging from an automobile electrical system to a 10-cell nicad battery pack, which is commonly found in handheld and similar portable transceivers. Since a 12-volt nicad battery is not easily charged from an automobile 12-volt system, a special circuit was designed to furnish a charging current to the nicads.

## nicad charging systems

The most obvious method of charging a nicad battery is shown in **fig. 1A**. A source potential,  $V1$ , delivers current into a battery pack whose potential is  $V2$ . Resistor  $R$  limits the charging current to a safe and maximum value. The charging current,  $I$ , is defined by

$$I = \frac{V1 - V2 - 0.6}{R}, \quad V1 > V2 \quad (1)$$

This simple circuit works only if  $V1$  is greater than  $V2$ , which may not be true in all instances. For example, if a nicad battery has a discharge potential of 10 volts, a 12-volt source can be used as a charging source. However, as the nicad battery becomes charged, its potential will increase to 13.5 volts, in which case the charging current would actually stop flowing during the charge cycle. In an automobile environment, source potential  $V1$  is not constant but may vary from 11 to 14 volts depending on the condition of the automobile battery and engine rpm. Although the worst-case maximum voltage condition can be assumed, and the maximum charge current

By Gene Hinkle, K5PA, I/O Engineering, 9503 Gambels Quail, Austin, Texas 78758

defined and limited, this simple circuit will not charge a nicad battery with a constant current all the time.

If a large value of  $V1$  is available, the circuit in **fig. 1B** works well. Since  $V1$  is much larger than  $V2$ , the battery potential, the change in  $V2$  versus charge time has little effect on the charging current. A lamp is used to decrease the voltage to the nicad at a specified current. This circuit is representative of many chargers on the market today. Its disadvantage is that the charging current is not exact and  $V1$  must be much greater than  $V2$ , which is not the case in an automobile system.

**Fig. 2** shows an excellent method of obtaining a constant-current from a common three-terminal voltage regulator. The three-terminal voltage regulator would normally have its common terminal grounded and would deliver a constant voltage between the output and common terminal. However, if the common line is not grounded, but left floating, and a fixed resistance is connected from the output to the common terminal, the regulator will try to furnish a fixed voltage across the resistance. The current through the resistor is given by Ohm's law:



$$I_{OUT} = V/R$$

where  $I_{OUT}$  is current through resistor  $R$ ;  $V$  is the voltage regulated by the device.

Once the circuit is completed between the three-terminal regulator's common and power return (ground connection), current will flow through this connection, even if a resistance or voltage exists in the path to ground. The only requirement is that the input voltage must be equal to or greater than the full charge battery potential plus 5 volts (for a 5-volt regulator) plus 2 volts (overhead voltage). Thus, for a 13-volt full-charge nicad potential and a 5-volt-type voltage regulator, the input voltage to the current regulator circuit must be greater than 20 volts.

In the circuit shown, a transformer and rectifier were used to provide 30 volts dc. A 50 mA, 6-volt lamp was used in series with the regulator to indicate when the 50 mA charge current was flowing; it also dropped the power-supply voltage to 24 volts dc.

**fig. 1.** Simple charging systems for nicads. In **A** a resistor is used to limit the current source; the current is not constant and is non-linear. Sketch **B** shows a lamp current-limited source. Voltage  $V1$  must be much larger than  $V2$  for good regulation. This is a very popular charging method.

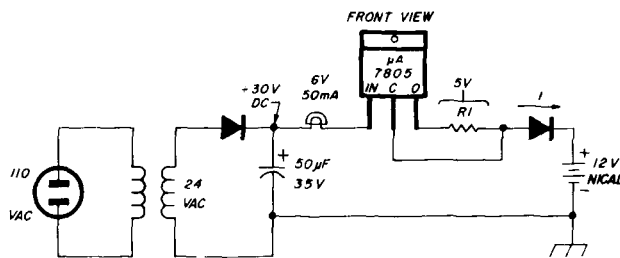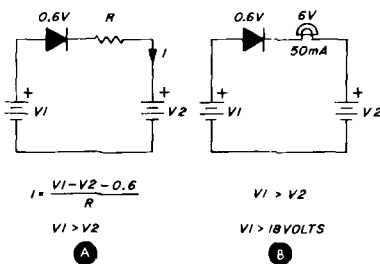

**fig. 2.** An excellent constant-current regulator using a popular 3-terminal voltage-regulator IC. Current source is determined by  $R1$ . For a 7805 IC,  $V$  is 5 volts. Thus for  $R = 50$  ohms,  $I = 50$  mA constant current.

The use of three-terminal regulators is an excellent technique for defining a constant current level. The current level is easily adjusted by changing resistor  $R1$  in the output circuit. The current is essentially constant regardless of the discharge state of the nicad battery.

### voltage-doubler circuit

To use a constant-current source as described it's necessary to provide an input source voltage of at least 20 volts. In an automobile situation, a 20-volt source is not available, so the circuit of **fig. 3** was designed. This circuit uses a NE-555 universal timer IC and two power transistors in a voltage doubling circuit. The output voltage is roughly twice the input voltage, minus any diode voltage drops. Thus, a 10-volt source will be converted to 19 volts and a 13-volt source to 25 volts. This doubled voltage is then used to drive a source current into a three-terminal current regulator.

The operation of the voltage doubler is as follows, referring to **fig. 3**.

The NE-555 is used in the common astable multivibrator configuration. The oscillation frequency is determined by  $R1$ ,  $R2$ , and  $C1$  and is equal to

$$F = \frac{1.44}{(R1 + 2R2) C1} \quad (2)$$

To have a near 50 per cent duty cycle the ratio of  $R1$  to  $R2$  should be around 1 to 4 as shown.

The 555 astable oscillator drives a pair of complementary transistors. High-current power transistors were used to switch the large charge and discharge currents. Transistor Q1 charges capacitor C2 to the input voltage during the first part of the astable cycle. During the second half of the cycle, transistor Q2 puts the fully charged capacitor C2 in series with the supply voltage. Typical values for C2 are

$$C2 = \frac{I_{OUT}}{F} \quad (3)$$

where  $F$  was defined earlier and  $I_{OUT}$  is the constant

output current required. A diode and capacitor (C3) filter the pulsating dc to a value nearly equal to two times the supply voltage. The value of C3 should equal C2.

Transistors Q1 and Q2 are plastic-cased power transistors. Power transistors are used because of the high peak currents during the charge and discharge cycle of C2. Although MJE 2955 and MJE 3055 types are shown, most common power transistors will work. The transistors are not heat sunk because both are operated in the saturated mode, thus power dissipation is held to a minimum. The diodes are 1-amp silicon types and may also be substituted with similar devices.

The current regulator operates as the one previously described. It may be attached to a heat sink, but is not mandatory. If the regulator's input terminal voltage is 25 volts, and the output terminal is at 17 volts, only 400 mW of heat must be dissipated in the worst case. The oscillation frequency of the voltage-doubling circuit can be increased, but transistor switching becomes less efficient with the increased switching speed. A too-low frequency requires larger values of capacitance for C2 and C3. A good compromise is to make the frequency between 1 and 10 kHz.

In the circuit shown the switching frequency was set to 1.4 kHz. Since ten 500 mA-hr nicads were being charged, the charging current ( $I_{OUT}$ ) was set to 50 mA. For an input voltage range of 10-15 volts, the charging current was a constant 50 mA.

### practical approach

To make these charging schemes work in a mobile charging system, charging current may be delivered

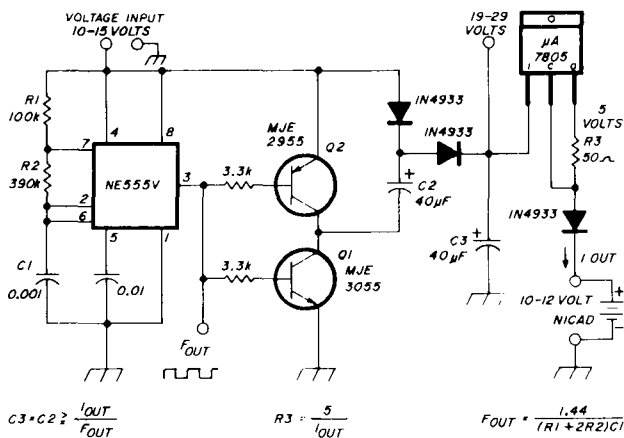


fig. 3. Voltage doubler circuit suitable for developing enough voltage from an auto battery to run the current regulator. Power transistors may be substituted for those shown.

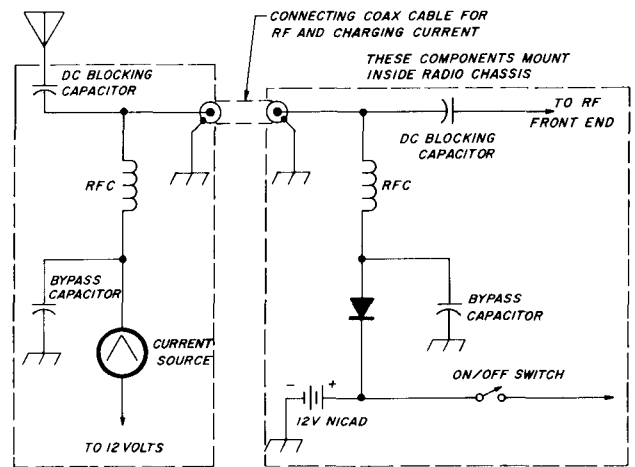


fig. 4. Use of the constant-current charging source requires only the connection of the antenna lead to the radio in a mobile or base station. The current source may be located inside your power amplifier or within an ac-operated charger. For 2 meters, the rf choke, RFC, is ten turns no. 26 AWG (0.3mm) copper wire on a 1-megohm 1/2-watt composition resistor.

to the portable unit through the antenna coaxial cable. This approach makes it easy to connect the handheld or other equipment to the charging source as well as to the antenna.

It's quite common to use small power amplifiers in a mobile system. This creates a convenient location for the current source circuits. Fig. 4 shows a typical mobile setup. The current source is located inside the amplifier housing. A small rf choke isolates the incoming and outgoing rf energy from the current-source circuits. A small capacitor in series with the antenna confines any charging potential to the inside of the automobile. The coax connecting the handheld to the amplifier or antenna carries the charging current to the batteries through an isolating rf choke. A dc blocking capacitor should be used in series with the rf circuitry. Most transceivers employ such a capacitor; check your schematic. The charging current source should be connected across the battery at all times.

### advantages

By charging the nicads through the coax line, the batteries can be maintained at full charge at all times.

By using the a-c operated charger and the automobile charger system, the nicads can be charged at any location. The current source could be switched to a lower trickle charge if desired. A 3-position switch could be used for this purpose and for turning off the regulator.

ham radio

# the super-compact ALDA 103

only 3 1/4" high x 9" wide x 12 1/2" deep • less than 8 1/4 pounds

ALDA 103, the trim little powerhouse with incredible performance for the price! ALDA 103 provides a full 250 watts PEP input for SSB operation, and 250 watts DC input for CW. And when it comes to performance, ALDA 103 is the hottest little transceiver going — all solid state, totally broadbanded and super-stable VFO.

Ideal first transceiver for brand new novices! You'll want a full-capability CW/USB/LSB unit with all the power and performance you can use. ALDA 103 gives you 250 watts DC input for CW, the maximum allowable power for your novice license. When you upgrade to technician, you've got 2 bands

for CW operation. And with your general license, just plug in your mic and use the ALDA 103's full 250 watts PEP on SSB!

Perfect second or mobile unit for seasoned hams! If you're looking for a super-sharp, compact unit to use in your car or boat, ALDA 103 will live up to your expectations. Absolute worst case sensitivity 0.5  $\mu$ V for 10 dB S+N/N — a must for mobile operation. Receiver audio output of 3 watts minimum — another must. Also, very low receiver power drain of only 5.5 watts — that's 0.4 amps at nominal 13.8 VDC including power for dial and meter lamps!



## GENERAL SPECIFICATIONS

**Semiconductors:** 39 diodes, 23 transistors; 11 integrated circuits

**Power Requirements:** Nominal 13.8 VDC input at 15 amps, negative ground only

**Power Consumption:** Receive — 5.5 watts (includes dial and meter lamps); Transmit — 260 watts

**Dimensions:** 3-1/4" high x 9" wide x 12-1/2" deep (82.55 mm x 228.6 mm x 317.5 mm)

**Weight:** 8-1/4 lbs. (3.66 kg)

## PERFORMANCE SPECIFICATIONS

**Frequency Range:** 80 meter band — 3.5 to 4.0 MHz  
40 meter band — 7.0 to 7.5 MHz  
20 meter band — 14.0 to 14.5 MHz

**Modes:** CW; USB; LSB

**RF Input Power:** SSB — 250 watts PEP nominal  
CW — 250 watts DC maximum (adjustable)

**Transmitter:**

Antenna Impedance: 50 ohm, unbalanced

Carrier Suppression: Better than -45 dB

Side-Band Suppression: Better than -55 dB at 1000 Hz

**Distortion Products:** Better than -26 dB

**AF Response:** 500 to 2500 Hz

**Spurious Radiation:** Harmonics better than -45 dB below 30 MHz; better than -60 dB above 30 MHz

**Frequency Stability:** Less than 100 Hz drift per hour (from a cold start at room temperature)

**Microphone:** High impedance 3000 ohm

**Receiver:**

**Sensitivity:** Better than 0.5 watts audio output for 0.5  $\mu$ V input

**Signal-to-Noise Ratio:** Better than 10 dB S+N/N for 0.5  $\mu$ V input

**Image Ratio:** Better than -60 dB (typical with respect to 0.5  $\mu$ V input: 80 meters — -130 dB; 40 meters — -100 dB; 20 meters — -75 dB)

**IF Rejection:** Better than -70 dB (typical with respect to 0.5  $\mu$ V input: 80 meters — 110 dB; 40 meters — 80 dB; 20 meters — 75 dB)

**Intermodulation Intercept Point:** Better than 10 dBm

**Selectivity:** 2.5 kHz — 6 dB; 5.0 kHz — 60 dB

**Audio Output Power:** More than 3 watts

**Audio Distortion:** Less than 5% at 3 watts

# \$495

including microphone and mobile mount, too.

## OPTIONS & ACCESSORIES

Noise Blanker — Model No. PC 701 ..... **\$29.95**

100 kHz and 25 kHz Dual Crystal Calibrator — Model No. PC 801 ..... **\$14.95**

Portable Power Supply — Model No. ALDA PS 115: average duty 15 amp unregulated; input — 115/230 VAC; 50/60 Hz; output — 13.8 V nominal at 15 amps .... **\$79.95**

Heavy Duty Power Supply — Model No. ALDA PS 130: output — regulated 30 amp at 13.8 VDC; input — 115/230 VAC, 50/60 Hz ..... **\$149.95**

alda communications, inc. 215 Via El Centro Oceanside, CA 92054 (714) 433-6123



# how to modify linear amplifiers for full break-in operation

With the introduction of the Ten-Tec *Triton IV*, which provides full break-in operation on CW, I needed a companion linear amplifier which also had this very desirable operating feature. At the present time, however, there is only one commercially produced amplifier on the market which meets this requirement — and it's priced at almost \$3000. The purpose of this article is to outline the theory and give some typical circuits which can be used to modify any power amplifier to provide full break-in capability. The circuitry is for use with grounded-grid triode linear amplifiers; class B or AB is assumed.

While class C might seem to be a better choice for a CW power amplifier, there are several reasons to maintain linear operation. First, and most important, since class C operation is not linear, the CW waveform supplied by the exciter will be distorted and the resulting output wave may produce serious key clicks and other unwanted spurious signals.

For the modification described here the grid of the amplifier tube must be at chassis ground, with a positive voltage applied as cutoff bias to the cathode. The classical biasing scheme, with the cathode at

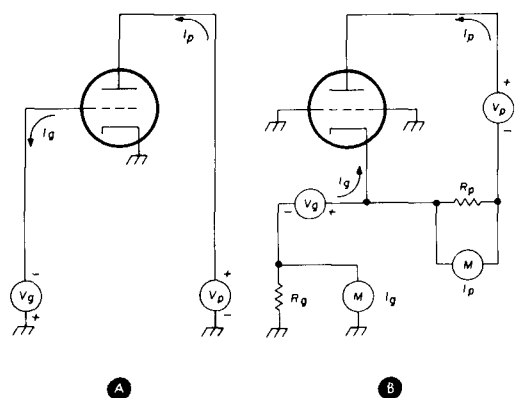


fig. 1. In the classical bias circuit, **A**, the cathode is grounded and a negative bias is applied to the grid; in the grounded-grid circuit a positive bias is applied to the cathode, **B**. In these circuits  $V_g$  is the bias supply,  $V_p$  is the plate supply,  $R_g$  is the grid meter shunt, and  $R_p$  is the plate meter shunt.

ground, **fig. 1A**, is rearranged to place the grid at both rf and dc ground, **fig. 1B**. The operating or cutoff bias is in the form of a positive voltage which is applied to the cathode; the high-voltage B+ plate supply is above ground by this potential.

When the amplifier is used for break-in operation, it is essential that the tube be biased to cutoff — with no plate current flowing — so the tube doesn't generate noise which would mask weak received signals.

## cutoff bias

Of the several types of tubes commonly used for linear amplifier service, there are two basic types: those with hot cathodes and those with indirectly heated cathodes (see **fig. 2**). For the purposes of this discussion the main difference is that the bias on a hot cathode is applied through the center tap of the filament transformer (**fig. 2A**); bias for indirectly heated tubes is fed directly to the cathode through an rf choke (**fig. 2B**).

**Figs. 3 and 4** show two common ways to bias rf power amplifiers to cutoff. The circuit in **fig. 3** (from the ARRL *Handbook*), uses a 10k resistor in series with the cathode circuit to develop self bias. It is the least acceptable method, however, because it requires a certain amount of plate current flow to provide the bias. Therefore, the tube is not completely cut off.

Another cutoff bias circuit is shown in **fig. 4**. It uses a +150 volt bias supply which cuts off all plate current and powers the T/R relay, K1. Actually, for B+ supplies up to about 3500 volts, 75 volts of bias is enough to cut off a pair of 3-500Zs — 75-volt relays, however, are hard to find.

**Fig. 5** shows a circuit which uses an rf-sensing transistor switch to remove the cutoff bias from the amplifier. Under standby conditions Q2 is an open circuit and 50 volts cutoff bias is applied to the cathode. When the drive signal is applied, Q2 turns on

By Dick Frey, K4XU, Chief Engineer, Ten-Tec, Inc., Sevierville, Tennessee 37862

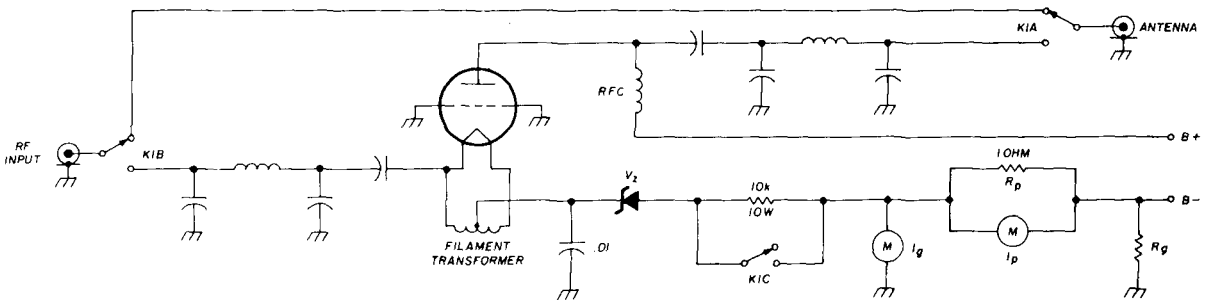


fig. 3. Typical linear amplifier bias and control using self bias developed across the 10k resistor in the B- line. Relay K1 is shown in the operating position with the amplifier on.

and the operating bias becomes the sum of the zener voltage,  $V_z$ , Q2's collector-emitter saturation voltage,  $V_{CE(SAT)}$ , and the voltage drop across the grid meter shunt,  $R_g$ .  $V_{CE(SAT)}$  for the specified 2N5321 resistor is 0.8 volt at 500 mA.

When selecting Q2, two criteria must be met: a low  $V_{CE(SAT)}$  because this adds to the operating bias, and a maximum collector-voltage rating that is greater than the applied voltage bias voltage. The Darlington configuration is used because transistors which meet the two voltage requirements seldom have the necessary current gain for this circuit. The power requirement for Q2 is quite low because the voltage impressed across it is low when it carries the grid current. A power dissipation rating of 10 watts is more than adequate. The resistance of the grid meter shunt resistor,  $R_g$ , should be as low as possible; usually 0.5 ohm is sufficient with a grid current meter which has a 1 mA movement.

The basic bias circuit of fig. 5, modified to accommodate the directly heated cathodes of two 3-500Zs, has been used successfully in a Heath SB-220. Note that the zener diode no longer has to pass the full plate current so it is permissible to use a less expensive 20-watt zener diode. An added feature of this circuit is that if any of the devices which supply operating bias fail open, cutoff bias will be applied to the tube — this prevents any damage that might otherwise occur.

The 1N4004 diode shown in the negative high-voltage line is a clamp which prevents the B- from going negative with respect to the chassis in case of bias supply failure.

When the linear amplifier is in the standby condition virtually no current is drawn from the bias supply. When Q2 turns on, resistor R1 limits the current flow. This current will show as grid current, so it's a good idea to keep R1 as large as possible. When testing this circuit I found it was useful to provide a means for turning on Q2 without applying rf drive power; S1 is a test button which does this.

In normal operation, the linear appears to be running class C because plate current is drawn only

when an rf drive signal is present. The amplifier is not operating class C, of course, but since quiescent class C, of course, but since quiescent plate current is no longer being drawn under no-signal conditions, the average power dissipated by the tube due to quiescent bias (200 to 600 watts in a typical class AB amplifier) is greatly reduced; this increases tube life, improves reliability, and results in a cooler ham shack.

### receiver switching

When the power amplifier can be operated without using relays to switch the bias, one step remains: receiver antenna switching. Electronic T/R switches have been available for years, but have never been widely accepted because, when the transmitter is tuned to resonance, the tank circuit acts as a "suck out" filter which reduces received signal strength. The electronic T/R switch was not the culprit — its placement in the system caused the problem. The solution is to place the electronic T/R switch at a high impedance point in the system. If you want to eliminate noisy relays which are slow and prone to failure and go to full break-in operation, the antenna

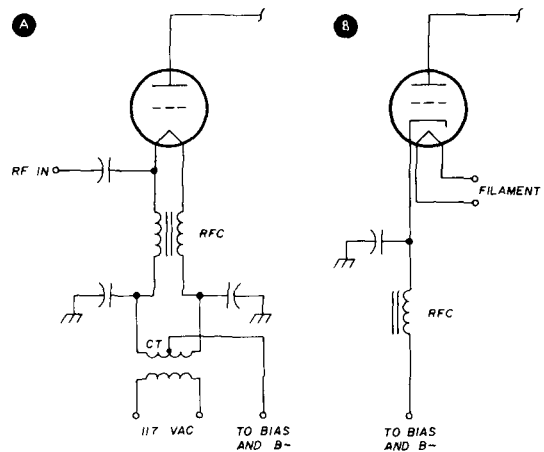


fig. 2. Grounded-grid biasing arrangements for hot cathode tubes, A, and indirectly-heated cathodes, B. Typical hot-cathode tubes are the 3-500Z, 3-1000Z, and 3CX1000; the 8877 and 8874 series of power amplifier tubes have indirectly-heated cathodes.

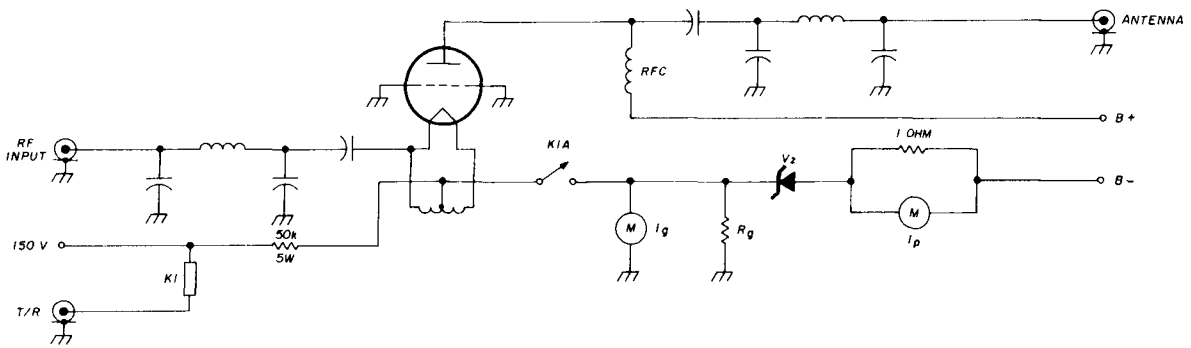


fig. 4. Linear bias and control using an external bias supply; this method provides better operation than the arrangement of fig. 3. Relay K1 is shown in the operating position with the amplifier biased to cutoff.

must be connected to the transmitter at all times. Thus, to find a high impedance point to connect an electronic T/R switch, the plate tank of the amplifier is a good choice.

Coupling to the plate tank is not without its problems, however. First of all, it's dangerous because of the high voltage that is present. Secondly, since there is a large amount of rf voltage present, the coupling capacitor C1 (fig. 6), must be small both to reduce its effect on the amplifier tuning and to assure that the T/R switch is not overdriven. This presents a problem because the optimum value of C1 for receiving purposes, about 5 pF, is too much capacitance when used at the kilowatt level on transmit. Therefore, a compromise is made on the side of safety and reliability.

The capacitor specified is made from RG-8/U

coaxial cable with the center conductor overlapping the braid for approximately 12 mm (1/2 inch). Two 25 mm (1 inch) square tabs, spaced 1 cm (3/8 inch), will also work if the mechanical layout of the amplifier will permit placement of this arrangement. Be sure that this capacitor is placed directly across the plate tuning capacitor *after* the plate blocking capacitor. This compromise results in a slight loss of gain on receive, but most transceivers have more than enough front-end gain to make up for the loss.

### construction

Since most modern kilowatt linears use some sort of input tuning, the placement of S1 in fig. 6 is not too difficult. The switch wafer can usually be added to an existing switch shaft, or the shaft can be extended to provide room for the wafer. When pur-

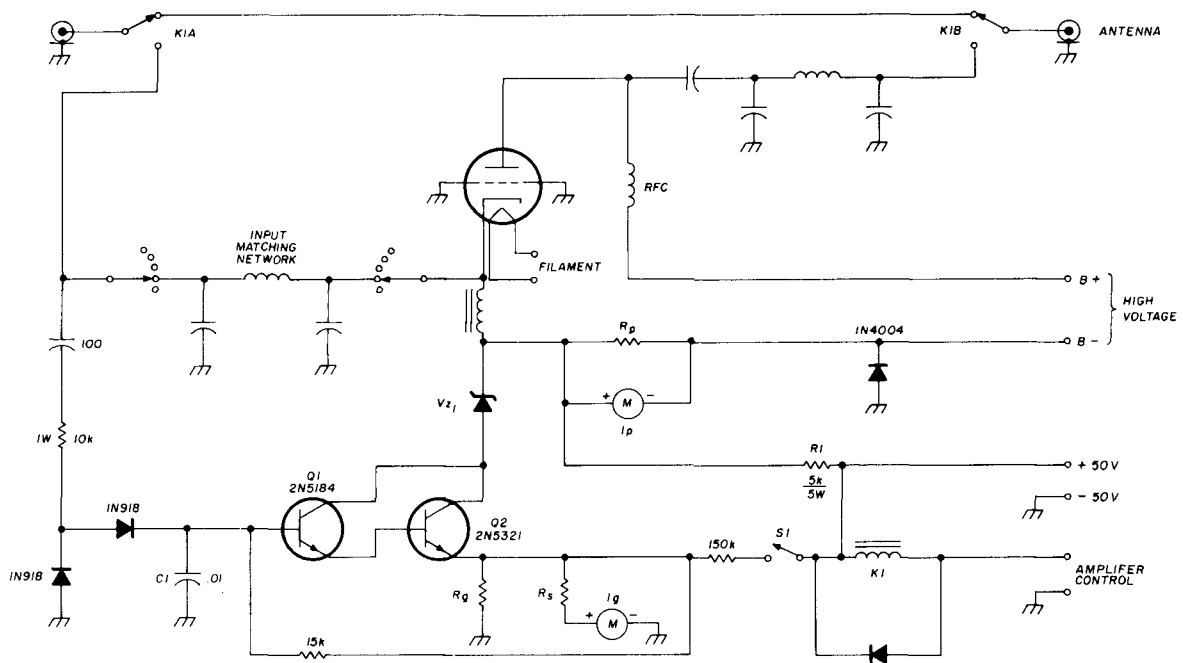


fig. 5. Cutoff bias circuit for a linear amplifier which uses an rf sensing transistor switch. The zener voltage,  $V_z$ , provides the proper operating bias and was part of the original amplifier circuit. Cutoff bias circuit operation is described in the text.


chasing the wafer switch for S1, be sure to note whether the amplifier uses 30, 45, or 60 degree indexing between switch positions.

The location of Q1 and its associated circuitry is not too critical except that it must be reasonably close to both C1 and S1 to minimize losses. It should be shielded if it is located inside the plate tank enclosure and all dc leads must be shielded. Since the dc current drawn is very small, the +18 volts can be obtained with a voltage doubler from the amplifier filament supply, or from a zener regulated drop from the positive bias supply. The switched coils form broadly resonant tuned circuits with the existing circuit capacitance, so some adjustment of the given values may be necessary.

### Triton IV modifications

There are also modifications to the Triton IV which will improve performance when using a linear amplifier. First is a simple change to eliminate the delay of the control relay while using ssb. As built at the factory, the time constant capacitor, C3 in **fig. 7** and page 3-34 of the manual, is tied directly to ground on the circuit board. By lifting the ground end of C3 and taking it to the unused center pin on the board, a wire can be run to the mode switch, S1E (CW1 and CW2 positions), which will activate the delay only when using CW. S1E is part of the rear wafer, closest to the chassis.

The second modification involves removal of the control relay, K1. This should be done only if the amplifier uses a positive voltage to key its control and

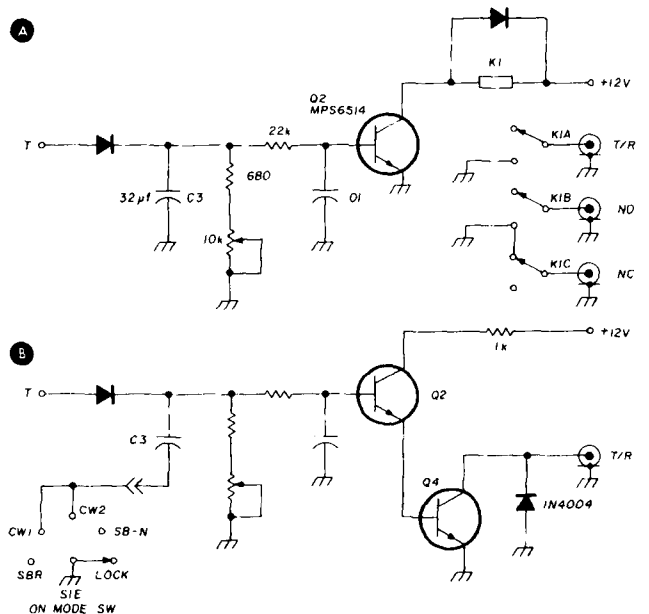

**fig. 7.** Modification of the Triton IV to remove the control relay and to eliminate unwanted delay times during CW break-in operation.


changeover relay. The reason for doing this is to eliminate the turn-on delay which is caused by using one relay to activate another. Relay K1 has no function in the operation of the Triton by itself. When the key is closed, it takes about 25 milliseconds for this relay to close, and perhaps another 23 ms for the amplifier relay to pick up, before the output of the Triton is amplified. This causes key clicks on the first dot. The transistor used for Q4 depends on the voltage used on the amplifier control relay and the relay current. With K1 removed, there is plenty of room for the added components on the board.

Some Triton users have complained of an ac hum in the receiver when using a linear amplifier — especially in the narrow CW-1 position. This is caused by ac ripple (or raw ac) on the relay control line. When attached to the Triton T/R relay's normally-open jack, unshielded wires going to K1 pass underneath the CW filter which picks up the hum. The solution is simple: reroute the wiring between K1 and T/R normally-open jacks on top of the chassis. This change has been incorporated in late production Tritons.

### conclusion

What has been presented here are notes and basic technical information needed to modify an existing rf power amplifier for full break-in operation with a Triton IV; the circuits can also be adapted to other transceivers. Ten-Tec in no way assumes responsibility for the use or misuse of this information, nor for any damage to other manufacturer's equipment resulting from implementation of these circuits.

ham radio

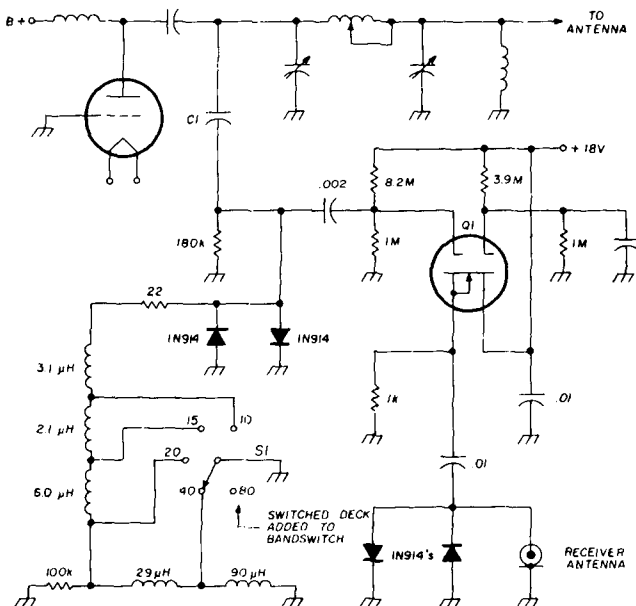

**fig. 6.** Electronic T/R switch for the receive antenna. The station antenna is connected to the linear at all times. Capacitor C1 is less than 1 pF and consists of 12 mm (1/2 inch) of RG-8/U coaxial cable (see text).



# DRAKE UV-3 multi-band



Optional  
Drake 1525EM  
Encoding  
Mike

*Designed and manufactured in the U.S.A.*

- Model 1346** Drake UV-3 (144-220-440) . . . . . \$795.00
- Model 1344** Drake UV-3 (144-440) . . . . . \$695.00
- Model 1343** Drake UV-3 (144-220) . . . . . \$695.00
- Model 1345** Drake UV-3 (220-440) . . . . . \$695.00
- Model 1340** Drake UV-3 (144) . . . . . \$595.00
- Model 1359** Drake UV-3E (144-430)\*

(Models above include factory installed modules for bands as listed, standard dynamic mike, and mobile mounting bracket.)

\* This model tuned for European fm bands.  
See your dealer for price details.

Add-on modules expand band coverage of models which may have been purchased in a single band or two band configuration. Prices include factory installation which is necessary to meet FCC receiver certification requirements.

- Model 1504** Drake PS-3 AC Power Supply . . . . \$ 89.95
- Model 1525** Drake 1525EM Encoding Mike . . . \$ 49.95
- Model 1330** UMK-3 Remote Trunk-Mount Kit . . \$ 69.95

**NOTE:** Certain of the above models will be available before others. Check with your dealer for specific availability.

# synthesized fm system

For the serious amateur who...

- considers fm a vital part of a total communication system
- needs multi-band coverage in a single transceiver
- needs to continuously scan-monitor a priority amateur repeater dedicated to public service, weather, or DX alerts
- needs extra programmed channels for quick selection, in addition to the synthesizer...

The Drake UV-3 provides it all!

- Continuous priority channel scan
- Remote trunk operation (optional)
- Four extra diode-programmed channels on each band
- All three bands in a single bandswitched unit, or start with basic models and add extra band-modules later
- Non-standard offsets available for each band


## The Priority Channel Scan

You can diode-program your priority channel in one of the fixed channel positions. It can be con-



tinuously monitored from any other synthesized or fixed channel. If you're operating on the priority channel, or another programmed fixed channel, you can scan-monitor any synthesizer frequency you choose.

## The Extra Diode-Programmed Channels

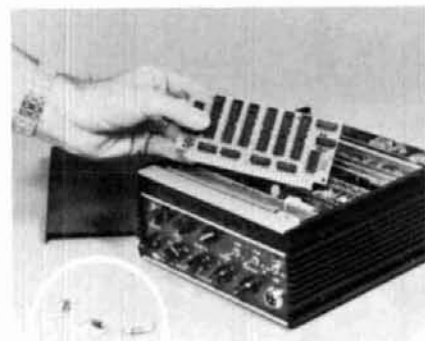


You can diode-program up to four fixed channels, with their offsets, for each band. This feature allows super-quick selection of favorite channels. The five-kHz synthe-

sizer operates independently of these programmed channels. And best of all, soldering is not necessary for programming. The program board has special sockets mounted on it for direct insertion of diodes. We even provide the diodes.
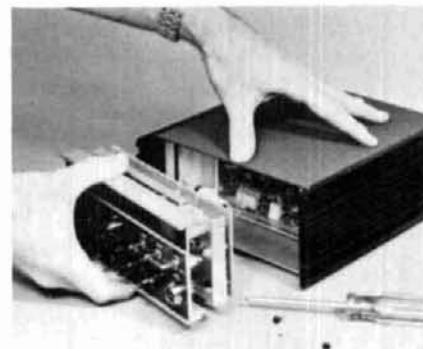
## Remote Trunk Mount Kit

The control panel of every UV-3 removes for installation in the UMK-3 Remote Kit. This provides for safety, as well as easy installation in small cars where under-dash space is limited.



Write for a fully illustrated brochure on the Drake UV-3 System.

**R. L. DRAKE COMPANY**



540 Richard St., Miamisburg, Ohio 45342  
Phone: (513) 866-2421 • Telex: 288-017

Western Sales and Service Center, 2020 Western Street, Las Vegas, Nevada 89102 • 702/382-9470



# how to design matching networks

Six basic impedance matching networks and how to design them for your own applications


Common L, T, and pi networks work well for impedance matching but they lack the selectivity required for amplifiers or frequency-multiplier chains. Adding a component to the network and rearranging allows it to be selective on both sides of band center. Presented here are six simple matching circuits and their design equations that allow adjustment of design  $Q$  for selectivity and different source or load impedances.

Fig. 1 shows the basic network with its source and load interfaces. The assumption is that  $R_i$  is less than  $R_o$ . Simply reverse the input, output, and the network if  $R_o$  is less than  $R_i$ . Both source and load are assumed to have shunt capacitances; this is usually true and will include stray capacitance as well.

The value of  $Q$  is the design  $Q$  of the network and determines selectivity. It is *not* component  $Q$  which should be at least five times design  $Q$ . Selectivity around band center is treated the same as a tuned circuit with a certain  $Q$ . Each of the six networks has

different attenuation far from center; examples of this are shown later.

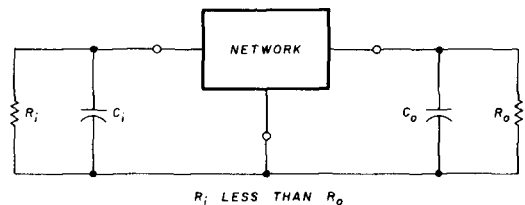The constants listed in fig. 1 reduce the size (and complexity) of the network equations, and will be used with all six networks. It must be emphasized that all capacitive reactances must calculate *negative*, inductive reactances *positive*. Any excep-



$R_i$  LESS THAN  $R_o$

#### CONSTANTS

$$X_i = -1 / (2\pi F C_i) \quad X_o = -1 / (2\pi F C_o)$$

$F$  = CENTER FREQUENCY

$$N = \frac{R_i X_i}{R_i^2 + X_i^2} \quad R_x = X_i N$$

$$Q_i = R_i + X_i Q \quad Q_o = R_o + X_o Q$$

fig. 1. The basic matching network. Constants shown here will be used in calculating the values for the six different networks discussed in this article.

tion to this rule with a network indicates that particular network cannot be used.

#### different sources and loads

Fig. 1 shows a parallel capacitive reactance across the input and output terminals. Sometimes the end impedances are given (or measured) in series form. This may be converted to parallel form either by impedance-to-admittance plus inversion of resulting conductance and susceptance. Any of the calculators with rectangular/polar conversion can handle this easily. The following conversion formula can be

By Leonard H. Anderson, 10048 Lanark Street, Sun Valley, California 91352

used if those functions are not available on your calculator:

$$R_p = R_s + (X_s^2/R_s)$$

$$X_p = X_s + (R_s^2/X_s)$$

where

$$R_s = \text{Series resistance}$$

$$X_s = \text{Series reactance}$$

$$R_p = \text{Parallel resistance}$$

$$X_p = \text{Parallel reactance}$$

Note that the sign of the reactance is preserved in conversion.

An inductive reactance is a special problem. Compensation of this is done by capacitive shunting so that the total reactance at the band center becomes capacitive. Some of the networks will have shunt inductors at the ends. This condition allows the physical inductor to be the parallel difference with stray capacitance (always present) forming  $C_i$  or  $C_o$ . If the end reactance changes rapidly around the band center, it is better to add a physical capacitor and use calculated inductance directly. In any case, end reactances must be capacitive.


## handling data from the spec sheet

Transistor data is invariably given in admittance or S-parameters. Admittance is already in parallel form so the conductance and susceptance values are taken directly and inverted to yield end resistance and  $X_i$  or  $X_o$  (watch the sign of susceptance, it is positive when capacitive).

S-parameters are a bit different and are found on Smith chart representations. These are normalized to 50 ohms or 0.02 mho and can be taken directly,

$$T_i = R_o - R_x \quad (\text{SEE TEXT IF NEGATIVE})$$

$$R_d = \sqrt{R_x T_i}$$

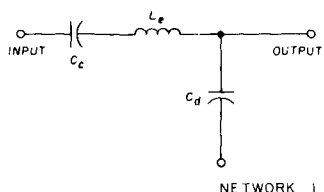


NETWORK 1

$$X_c = R_d - Q_i N$$

$$X_d = -\frac{R_o R_x X_o}{R_d X_o + R_o R_x}$$

$$X_e = R_x Q$$

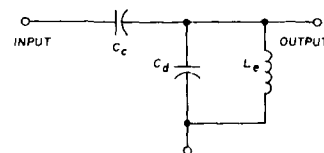

NETWORK 2

$$X_c = -(R_d + R_i N)$$


$$X_d = \frac{R_o R_x X_o}{R_d X_o - R_x Q_o}$$

$$X_e = R_o / Q$$

fig. 2. Networks 1 and 2.

$$T_i = R_o - R_x \quad (\text{SEE TEXT IF NEGATIVE})$$

$$R_d = \sqrt{R_x T_i}$$

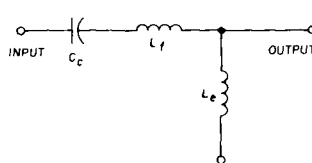

NETWORK 3

$$X_c = \left[ \frac{R_o R_x}{X_o} \right] - Q_i N$$

$$X_e = \frac{R_o X_o R_x}{R_d X_o - R_o R_x} \quad \text{for } L$$

$$X_e' = - \left[ \frac{R_o X_o R_x}{R_d X_o + R_o R_x} \right]$$

$$X_f = R_x Q - (R_o R_x / X_o) - R_d \quad \text{for } L$$

$$X_f' = R_x Q - (R_o R_x / X_o) + R_d$$


$$X_c = - \left[ \frac{R_o X_o X_i}{R_o X_i + X_o Q_x} \right]$$

$$X_e = R_d - R_i N \quad \text{for } L$$

$$X_e' = -(R_d + R_i N)$$

$$X_f = \frac{R_o R_x}{Q_i N - R_d} \quad \text{for } L$$

$$X_f' = - \left[ \frac{R_o R_x}{Q_i N + R_d} \right]$$

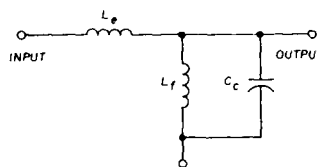

NETWORK 4

fig. 3. Networks 3 and 4.

then un-normalized.  $S_{11}$  is the input impedance while  $S_{22}$  is the output impedance; both are complex numbers. Knowledge of Smith chart interpretation is required.<sup>1</sup>

Data in admittance or S-parameter form is invariably frequency sensitive. They also represent the average data of a production run so individual devices can vary. Under such conditions it is well to keep the design  $Q$  relatively low. There may be an advantage to swamping the end with a parallel resistance (small carbon composition resistor) to reduce sensitivity of values. This has two cautions: power loss and about 2 pF extra capacitance with each resistor.

## examples

Numerical examples all assume matching a 50-ohm line to the input of a Motorola MC1590 amplifier IC (single-ended) at 7.15 MHz with a design  $Q$  of 20. Stray capacitance of 3 pF is assumed at each end; the MC1590 is insensitive with a parallel, single-ended impedance of 5k and 5 pF. The line is assumed perfect. Fig. 1 constants are then:

$R_i = 50$	$R_o = 5000$
$C_i = 3 \text{ pF}$	$C_o = 8 \text{ pF}$
$X_i = -7419.81$	$X_o = -2782.43$
$N = -6.73841 \cdot 10^{-3}$	$R_x = 49.9977$
$Q_i = -148346$	$Q_o = -50648.6$

An HP-25 calculator was used for these and following calculations.

## networks 1 and 2

These are shown in **fig. 2**. Variable  $T_1$  is a test value and is also used for Networks 3 and 4. If  $T_1$  results in a negative, none of the first four networks can be used with the given constants. Design  $Q$  and/or end resistances can be changed to make it positive. The negative situation only comes about with low  $R_o \cdot R_i$  ratios.

For the first four,  $T_1 = 4950$  so  $R_4 = 497.483$ . Values of Network 1 are then:

$$\begin{array}{ll} X_c = -502.135 & C_c = 44.33 \text{ pF} \\ X_d = -613.263 & C_d = 36.30 \text{ pF} \\ X_e = 999.555 & L_e = 22.26 \text{ } \mu\text{H} \end{array}$$

Note that all reactance signs are correct. Values for Network 2 are:

$$\begin{array}{ll} X_c = -497.146 & C_c = 44.77 \text{ pF} \\ X_d = -605.847 & C_d = 36.74 \text{ pF} \\ X_e = 250.000 & L_e = 5.565 \text{ } \mu\text{H} \end{array}$$

Reactance signs are correct here, too.

## networks 3 and 4

Test variable  $T_1$  and  $R_4$  apply here. Both inductors of both networks have two possible solutions. The reactance sign rule still applies so *both*  $X_e$  and  $X_f$  must be positive or *both*  $X'_e$  or  $X'_f$  must be positive. Do not mix  $X'_e$  and  $X_f$  or vice-versa; use either all non-prime or all prime values. Network 3 will have:

$$\begin{array}{ll} X_c = -1089.46 & C_c = 20.43 \text{ pF} \\ X_e = 425.637 & L_e = 9.474 \text{ } \mu\text{H} \\ X_f = 592.318 & L_f = 13.18 \text{ } \mu\text{H} \end{array}$$

Non-prime values obey the rules as do Network 4 values:

$$\begin{array}{ll} X_c = -274.782 & C_c = 81.01 \text{ pF} \\ X_e = 497.819 & L_e = 11.08 \text{ } \mu\text{H} \\ X_f = 497.853 & L_f = 11.08 \text{ } \mu\text{H} \end{array}$$

The inductors in Network 4 came out very close to the same value. This happened with this particular example, but is not true of other conditions.

## network 5

This one is shown in **fig. 4**. It must be noted that the two inductors have zero coupling and must be physically separate. The schematic may appear to be a conventional tapped-inductor circuit but such

would need a different set of equations plus measurement of mutual coupling. Networks 3 and 4 must also have separate inductors.

Test variable  $T_2$  cannot be negative. If  $T_2$  is negative design  $Q$  or end resistances, and possibly input capacitance, may have to be changed. Example conditions fit alright so we get:

$$\begin{array}{ll} R_5 = 22.0617 \cdot 10^9 & \\ T_2 = 827.815 \cdot 10^9 & R_4 = 64.3356 \cdot 10^6 \\ X_c = -274.782 & C_c = 81.01 \text{ pF} \\ X_e = 227.822 & L_e = 5.071 \text{ } \mu\text{H} \\ X_f = 28.7208 & L_f = 0.639 \text{ } \mu\text{H} \end{array}$$

Non-prime inductor values were correct in this example. Note that  $C_c$  is the same as for Network 4.

## network 6

**Fig. 5** shows this to be the tuned circuit often found in receiver front ends. The test variable is  $T_3$  and there is only one set of solutions. Our example condition results in:

$$\begin{array}{ll} R_5 = 2.57302 \cdot 10^9 & \\ T_3 = 89.9416 \cdot 10^9 & R_4 = 21.2063 \cdot 10^6 \\ X_c = -250.921 & C_c = 88.71 \text{ pF} \\ X_d = -32.9475 & C_d = 675.60 \text{ pF} \\ X_e = 250.000 & L_e = 5.565 \text{ } \mu\text{H} \end{array}$$

The inductor is the same value as in Network 2.

## wideband response

**Fig. 6** shows the frequency response over a two-decade range for the examples given. Voltage response has been calculated with constant end resistances. As such, it will be the same in either direction. Frequency is normalized to 7.15 MHz.

The joker in the deck is Network 3. The extra peak on the high side of resonance will vary in frequency and relative amplitude depending on the design  $Q$  and end impedances. A saving grace is that Network 3 has the best low-frequency attenuation. All networks will vary in other applications, primarily with different design  $Q$ ; the general shape of the response curve, however, will still be the same.

Choice of a network depends on the application. A frequency-multiplier chain should consider Networks 2, 5, or 6 because of their better low-frequency attenuation. The last stage could use Networks 1, 4, or 5 in the output to reduce unwanted harmonics. An amplifier chain such as an i-f strip could alternate Networks 5 and 6 between stages for best skirt attenuation.\*

\*There are better ways; this would only be for miniature construction or multiple stages with degeneration of gain.

**table 1. Design Q determination with fixed-value capacitors**

Network 1, Fixed  $C_c$ :  $Q_1 = \frac{R_4 - X_c - R_i N}{X_i N}$

Network 2, Fixed  $C_d$ :  $Q_2 = (R_4/R_i) - \left[ \frac{R_o(X_o + X_d)}{X_o X_d} \right]$

Network 3, Fixed  $C_c$ :  $Q_3 = \frac{R_o R_x - X_o(X_c + R_i N)}{X_i X_o N}$

Networks 4 and 5, Fixed  $C_c$ :  $Q_{45} = - \frac{R_o R_i (X_o + X_c) + X_c X_o R_i}{X_c X_o X_i}$

### impedances presented to the source

The impedance presented to the source can be easily calculated.<sup>2,3</sup> Networks 1 through 4 have variations far from band center that might cause stability problems. Network 1 is inductive from the band center to about 20.75 MHz from the example. Parallel resistance climbs abruptly to about a megohm while parallel reactance changes swiftly to capacitive reactance. Network 2 has a similar, less abrupt change at about 9.76 MHz. Network 3 is also similar with the changeover coinciding with the voltage response peak at about 24.3 MHz.

Network 4 becomes inductive below 4.9 MHz and capacitive above 28 MHz, resistance peaking to 4 megohms at that frequency. Networks 5 and 6 were much less susceptible to changes, and showed only slight variations at passband edges. All components were assumed lossless so a practical circuit would exhibit much less variation due to finite component  $Q$ .

The swamping-resistor method with transistor collectors works well from 6 meters and down with  $f_i$  of 150 MHz or greater. This increases a normally low-collector conductance but does have some power loss. A swamping resistor can also be used at the load since load changes reflect to the source. A

rule of thumb is to add 2 pF for every resistor, using only carbon composition types.

Mismatch loss will add out-of-band attenuation when used with receiver front ends. An exception is where the input impedance of the network matches the antenna impedance out of band. This is rare, but it happens. A similar condition occurs with different equipment connected with coax cable: the line length may cause a match out of band.


### non-standard component values

A cure for non-standard component values is to change design  $Q$  slightly to accommodate at least one standard, fixed value. The other two compon-

$$R_5 = X_o^2 + Q_o^2$$

$$T_3 = R_i R_o - R_o X_o^2 \quad (\text{SEE TEXT IF NEGATIVE})$$

$$R_4 = \sqrt{R_o T_3}$$

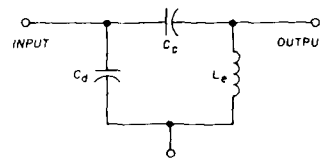

$$X_c = -(X_o/R_5)(R_4 + R_o Q_o)$$

$$X_d = \frac{R_o R_i X_o X_i}{R_4 X_i - R_o R_i X_o}$$

$$X_e = R_o / Q$$

NETWORK 6

fig. 5. Network 6.

ents can be trimmable. Table 1 is a tabulation of design  $Q$  for Networks 1 through 5 based on one specified reactance.

Our example for Network 2 gives a  $C_d$  value of 36.74 pF. A 39 pF mica is a standard value with a reactance of  $-570.755$  ohms at 7.15 MHz. This  $X_d$  value is used and gives a design  $Q$  of 20.5074. The  $X_c$  of Network 2 is unaffected by  $Q$  but  $X_e$  changes to 243.814 ohms or 5.427  $\mu$ H.

Network 6 is a bit difficult to solve for  $Q$  but it can be done by programming an HP-25 or similar calculator to solve either  $X_c$  or  $X_d$  with manual  $Q$  input. An approximation that works in some cases is:

$$Q_6 \cong (R_o + R_i) / X_c$$

The Network 6 example had  $C_c$  at 88.71 pF. A fixed 82 pF capacitor will have  $-271.456$  ohms so the approximate  $Q$  is 18.6034. Recalculating with  $Q$  gives:


$$\begin{array}{ll} X_c = -272.564 & C_c = 81.67 \text{ pF} \quad (\text{close!}) \\ X_d = -37.0998 & C_d = 599.99 \text{ pF} \\ X_e = 268.768 & L_e = 5.983 \text{ } \mu\text{H} \end{array}$$

$C_c$  is within 0.4 per cent of desired value so it should work well.

$$R_5 = X_i^2 + Q_i^2$$

$$T_2 = R_i R_o - R_o X_i^2 \quad (\text{SEE TEXT IF NEGATIVE})$$

$$R_4 = \sqrt{R_o T_2}$$

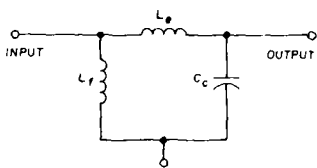

NETWORK 5

$$X_c = - \left[ \frac{R_o X_o X_i}{R_o X_i + X_o Q_i} \right]$$

$$X_e = (X_i / R_5)(R_o Q_i + R_4) \quad \text{volt}$$

$$X_e' = (X_i / R_5)(R_o Q_i - R_4)$$

$$X_f = - \frac{R_o R_i X_i}{R_4 + R_o R_i} \quad \text{volt}$$

$$X_f' = \left[ \frac{R_o R_i X_i}{R_4 - R_o R_i} \right]$$

fig. 4. Network 5.

Usual tolerances of fixed components are only 5 per cent. This will have little effect on matching when the other two components are trimmable. Lower design  $Q$  will show less sensitivity to tolerances.

### applications and variations

Some situations cannot be met with given end resistances. This can sometimes be cured by using

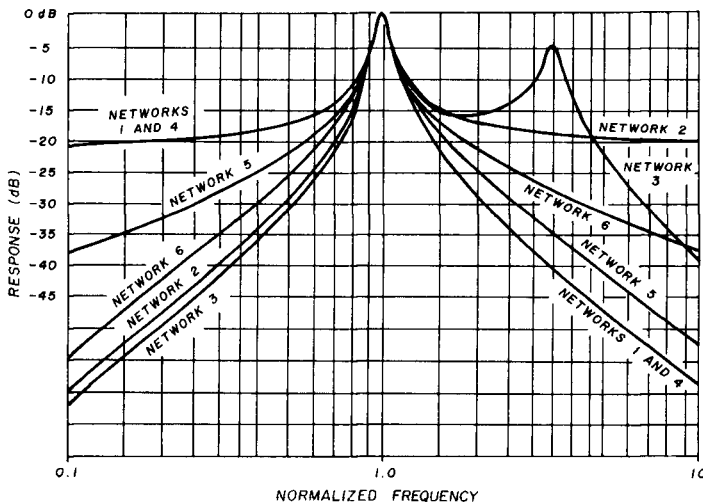


fig. 6. Frequency response of the six networks with the band center normalized to 7.15 MHz.

a broadband toroidal transformer.<sup>9</sup> Impedance changes of up to 16:1 are possible. Remember that parallel reactance is also changed by the same ratio in this application.

Good bypassing in active-device applications cannot be over-emphasized. A poor bypass and decoupling not only cause trouble between stages but also become networks. Resonance of bypass capacitors with lead length is common at higher frequencies; one cure is to double up several lower-capacitance bypasses. Short lead lengths and a large ground plane should always be used.

An interesting application is the replacement of the preselector tuning used in 1960-era receivers such as the Heath SB-300 series. These all have one band per bandswitch position so the front end can be stagger-tuned over the desired portion of the band. Fixed capacitors replace the variable and Networks 5 or 6 can be used at the antenna input. The Heath design has enough room to add a couple of bandswitch wafers to allow selection of other matching networks for other antennas such as a long-wire. The variable capacitor can be retained, insulated, and used as part of a Wien-bridge audio notch filter.

Antenna networks used in receivers should have a dc path to ground such as in Network 5. This avoids static build-up during electrical storms and potential arcing.

### other networks

End impedance frequency sensitivity may require simpler networks. An excellent treatment of L-networks is found in the first reference along with proper use of the Smith chart. Tabulated values are available<sup>4,5</sup> and theoretical aspects can be found in texts.<sup>6</sup>

Application of transistor amplifiers and matching is well covered in reference 7. Access to a computer that speaks FORTRAN can use the program of reference 8 to calculate other networks and also determine amplifier stability.

### references

1. Phillip H. Smith, *Electronic Applications of the Smith Chart*, McGraw-Hill, New York, 1969.
2. Leonard H. Anderson, "Admittance and Impedance, and Circuit Analysis," *ham radio*, August, 1977, page 76.
3. Leonard H. Anderson, "Calculator-Aided Circuit Analysis," *ham radio*, October, 1977, page 38.
4. *ARRL Electronics Data Book*, Chapters 3, 4, and 5, ARRL, Newington, Connecticut, 1976.
5. Frank Davis, "Matching Network Designs With Computer Solutions," Application Note AN-267, Motorola Semiconductor Products, Phoenix, Arizona.
6. Philip Cutler, *Electronic Circuit Analysis; Volume 1, "Passive Networks."*
7. Ralph S. Carson, *High Frequency Amplifiers*, John Wiley & Sons, New York, 1975.
8. Gunnar Richwell, "Design and Match RF Amplifiers," *Electronic Design* 10, May 10, 1969, page 106.
9. John J. Nagle, "Use Wideband Autotransformers," *Electronic Design* 3, February 2, 1976 (reprinted in *ham radio*, November, 1976, page 10).

### ham radio



"I DID clean up my desk . . . two years ago, just before I picked up that call from Russia."

# 600 MHZ. FREQUENCY COUNTER

±0.1 PPM TCXO

## OPTO-8000.1



This new instrument has taken a giant step in front of the multitude of counters now available. The Opto-8000.1 boasts a combination of features and specifications not found in units costing several times its price. Accuracy of ±0.1 PPM or better — *Guaranteed* — with a factory-adjusted, sealed TCXO (Temperature Compensated Xtal Oscillator). **Even kits require no adjustment for guaranteed accuracy!** Built-in, selectable-step attenuator, rugged and attractive, black anodized aluminum case (.090" thick aluminum) with tilt bail. 50 Ohm and 1 Megohm inputs, both with amplifier circuits for super sensitivity and both diode/overload protected. Front panel includes "Lead Zero Blanking Control" and a gate period indicator LED. AC and DC power cords with plugs included.

#### SPECIFICATIONS:

Time Base—TCXO ±0.1 PPM GUARANTEED!  
 Frequency Range—10 Hz to 600 MHz  
 Resolution—1 Hz to 60 MHz; 10 Hz to 600 MHz  
 Decimal Point—Automatic  
 All IC's socketed (kits and factory-wired)  
 Display—8 digit LED  
 Gate Times—1 second and 1/10 second  
 Selectable Input Attenuation—X1, X10, X100  
 Input Connectors Type—BNC  
 Approximate Size—3" h x 7½" w x 6½" d  
 Approximate Weight—2½ pounds  
 Cabinet—black anodized aluminum (.090" thickness)  
 Input Power—9-15 VDC, 115 VAC 50/60 Hz  
 or internal batteries  
 OPTO-8000.1 Factory Wired **\$299.95**  
 OPTO-8000.1K Kit **\$249.95**

#### ACCESSORIES:

Battery-Pack Option—Internal Ni-Cad Batteries and charging unit **\$19.95**  
 Probes: P-100—DC Probe, may also be used with scope **\$13.95**  
 P-101—LO-Pass Probe, very useful at audio frequencies **\$16.95**  
 P-102—High Impedance Probe, ideal general purpose usage **\$16.95**  
 VHF RF Pick-Up Antenna—Rubber Duck w/BNC #Duck-4H **\$12.50**  
 Right Angle BNC adapter #RA-BNC **\$ 2.95**

#### FC-50 — Opto-8000 Conversion Kits:

Owners of FC-50 counters with #PSL-650 Prescaler can use this kit to convert their units to the Opto-8000 style case, including most of the features.

FC-50 — Opto-8000	<b>Kit \$59.95</b>
*FC-50 — Opto-8000F	<b>Factory Update \$99.95</b>
FC-50 — Opto-8000.1 (w/TCXO)	<b>Kit \$109.95</b>
*FC-50 — Opto-8000.1F	<b>Factory Update \$149.95</b>

\*Units returned for factory update must be completely assembled and operational



### OPTOELECTRONICS, INC.

5821 NE 14 Avenue  
 Ft. Lauderdale, FL 33334  
 Phones: (305) 771-2050 771-2051  
 Phone orders accepted 6 days, until 7 p.m.



**TERMS:** Orders to U.S. and Canada, add 5% to maximum of \$10.00 per order for shipping, handling and insurance. To all other countries, add 10% of total order. Florida residents add 4% state tax. C.O.D. fee: \$1.00. Personal checks must clear before merchandise is shipped.



# overtone crystal oscillators without inductors

A discussion of  
overtone crystal  
oscillator circuits  
which don't  
require inductors

Until recently, all of the circuits for overtone crystal oscillators I've seen have included tuned LC circuits. It seemed necessary to have an LC resonator, tuned to the desired overtone frequency, to be sure the oscillator would operate at the proper overtone frequency and prevent operation at the crystal's fundamental frequency or some undesired overtone. It would be nice if the LC tuned circuit could be eliminated, of course, because it would simplify bandswitching of the crystal oscillator.

International Crystal has introduced a crystal oscillator circuit called the OF-1. Although the OF-1 circuit has no inductor, and thus no LC tuned circuit, it can be used with crystals operating in the third-

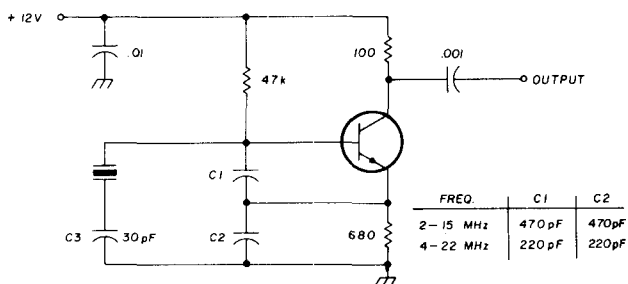


fig. 1. International Crystal OF-1 LO oscillator circuit for fundamental-mode crystals.

overtone mode. I found this quite interesting and did some relevant experimenting to satisfy my curiosity. My efforts are documented here for others who may share this interest.

## the circuit

International Crystal supplies two different kits of the OF-1 type. The OF-1 LO uses crystals operating in the fundamental mode from 2 to 22 MHz; fig. 1 is a schematic of the circuit. The OF-1 HI uses crystals

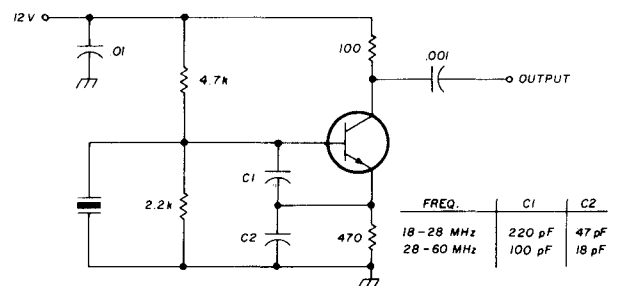


fig. 2. International Crystal OF-1 HI oscillator circuit for third-overtone crystals; note that no inductors are required.

operating in the third-overtone mode from 18 to 60 MHz; fig. 2 is a schematic of the OF-1 HI. Notice that in the latter circuit capacitor C3 has been omitted; in the overtone mode, the crystal operates near series resonance.

I breadboarded and tested both of these circuits using a 2N4996 transistor. The crystal I used in all of my tests was a 28.3 MHz third-overtone type originally purchased for use in International Crystal's older OX oscillator circuit (which has an inductor). Using this crystal, the circuit of fig. 1 had an output frequency at the crystal's fundamental, or about 9.43 MHz. The circuit in fig. 2 produced the third-overtone frequency of 28.3 MHz when the smaller values shown for C1 and C2 were used; using the larger values for C1 and C2 given in fig. 2 produced oscillation at the fundamental frequency of 9.43 MHz.

By Courtney Hall, WA5SNZ, 7716 La Verdura Drive, Dallas, Texas 75248

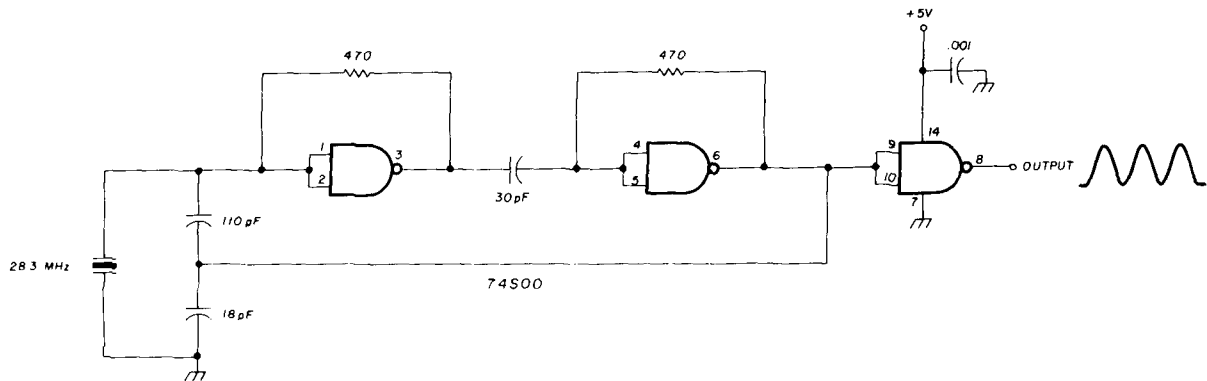


fig. 3. Third-overtone crystal oscillator which uses a 74S00 Schottky TTL gate; no inductors are required.

### TTL version

To obtain increased output amplitude I developed the circuit shown in **fig. 3**. The 74S00 quad NAND gate acts as both oscillator and output buffer. One of the gates in the IC is unused. A 74S00 is required because of the relatively high frequency; I don't believe the 7400, 74LS00, or 74H00 will work as well, if at all, at 28.3 MHz.

All wiring should be as short as possible, and the circuit should be shielded. The peak-to-peak output amplitude swings from about 0.4 to 3.5 volts, which are acceptable TTL levels. If the capacitor which couples the first two gates together (30 pF in **fig. 3**)

is too large (1000 pF), the circuit's output frequency will drop down to the crystal's fundamental. Some experimentation with the value of this capacitor may be required for different crystals.

### conclusion

The simplicity of these overtone crystal oscillators could make them desirable in many applications. I have not had the opportunity to investigate them to the degree I would like; therefore, I would welcome comments from interested readers on this type of overtone oscillator circuit.

ham radio

## simple method for making printed-circuit boards

I have developed a method of making printed-circuit boards that, while not professional in appearance, work well and beat the mess that results from using wire-wrap sockets and soldering them in place.

I use paint (enamel) in a K&E Leroy pen, inserted in a hole of a test probe. When using paint, do not use the insert for the pen, which is used to prevent the ink from running through. The paint is not thinned but just as it comes from the can; the result is a slow writing paint pen. I have found that a no. 2 or no. 3 Leroy pen is just about right. Cleaning is easy with pipe cleaners and paint thinner. I use an inking pen with paint for the long straight lines, and a small brush for the large areas.

To make a PC board, place the copper board under the layout, secure it so it won't slip, then use a sharp instrument such as a scribe and punch a prick hole through each place where there is a dot, or where there will be a hole. This gives the spacing you'll need to draw (free hand) the circuit on the board. After you have completed the hole punching (not

through the board), remove the layout. Note that this does not destroy your layout. Now you can fill your pen and draw the circuit on the copper board.




I recommend you practice with simple circuits before you jump into a complex layout. After the paint has dried naturally or in an oven heated to 150 to 160 degrees, check to see that your layout is as you want it. If two lines are touching, the scribe will allow you to make a fine line between them.

I have tried two types of etching solutions: ferric chloride and an etch solution from Vector Electronics. The paint stood up well in both. First I tried two types of paint, Sears acrylic enamel, and Ace Hardware quick-drying black enamel. There was no apparent difference.

Drilling the board can be done before painting the circuit or after etching. The little prick marks show you exactly where the hole belongs. Removing the paint after etching is done with trichloroethane or other solvent that will not contaminate the board.

Robert H. Kernan, W4MTD

# Super Terminals with Hidden Features

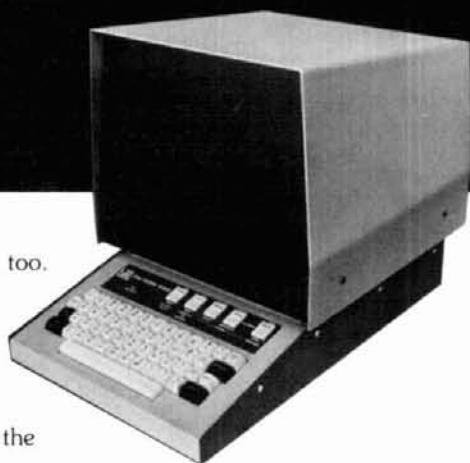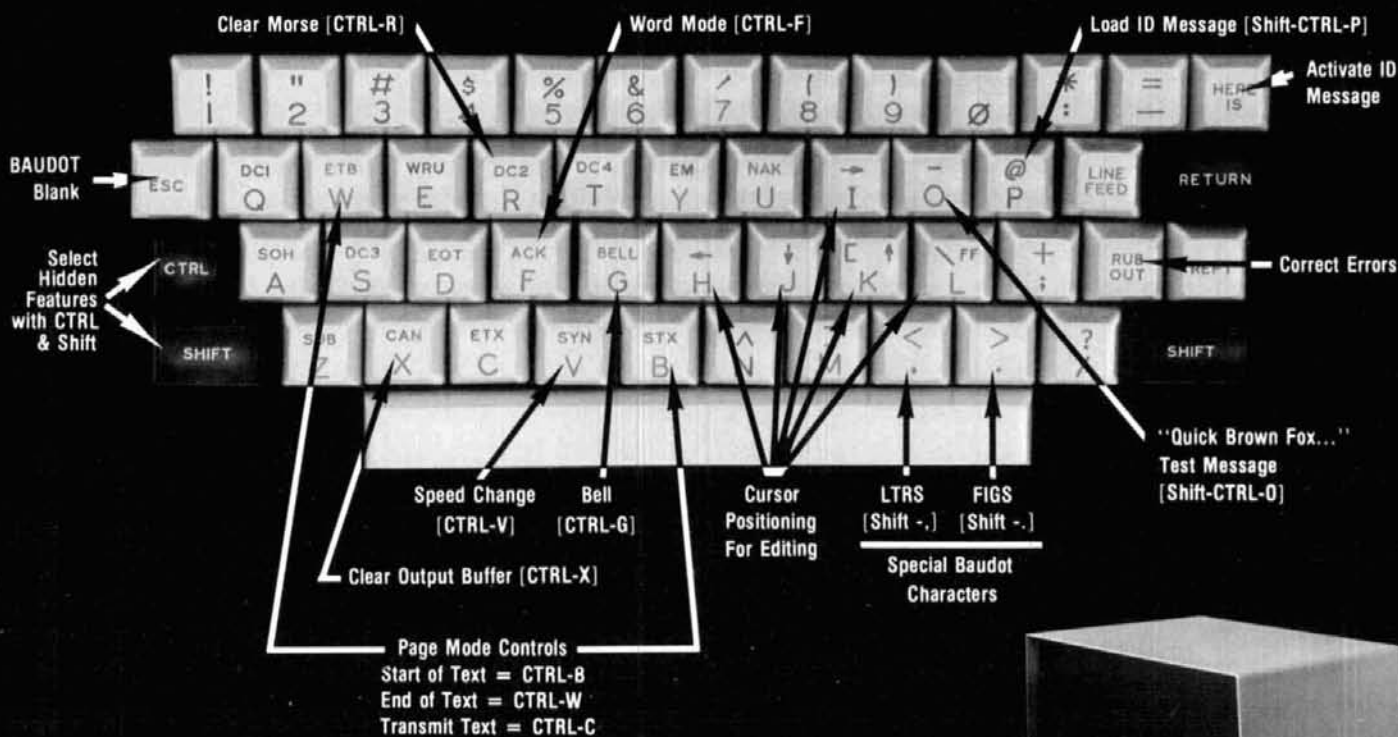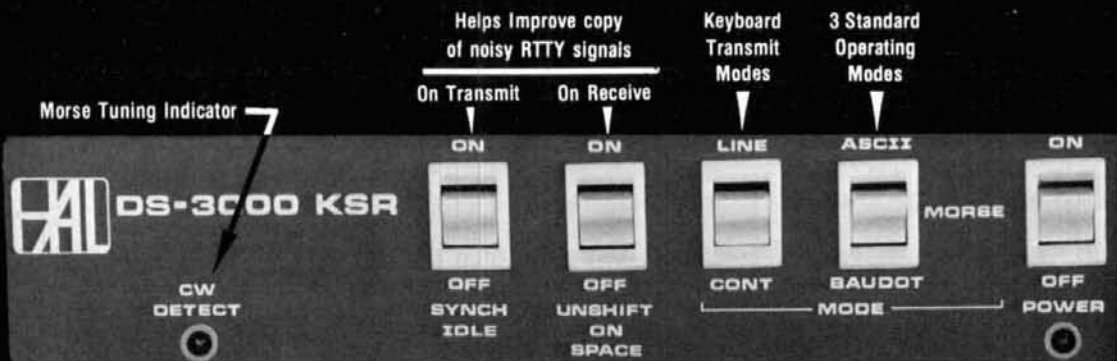

For super operator convenience, our keyboard works in MORSE, BAUDOT, and ASCII codes and controls the terminal, too. You can edit a message, program the HERE IS message, send the "QUICK BROWN FOX..." test message, change speeds, and change the terminal modes, all from the keyboard itself. In fact, the KOS (Keyboard Operated Switch) feature even turns the transmitter on and off from the keyboard. The DS-3000 KSR also features full-length 72 character lines (16 lines per screen), 5 speeds of BAUDOT and ASCII RTTY and Morse code from 1 to 175 wpm (Version 3), and word wrap-around to prevent splitting of words at the end of a line. When combined with the HAL ST-6000 Demodulator, you have the ULTIMATE in RTTY equipment.

DS-3000 KSR Version 3 (MORSE, BAUDOT, ASCII)..... \$1575.00  
 DS-3000 KSR Version 2 (BAUDOT & ASCII only) ..... \$1195.00

Write for our latest catalog & RTTY guide.



**HAL COMMUNICATIONS CORP.**  
 Box 365  
 Urbana, Illinois 61801  
 217-367-7373



For our Overseas customers:  
 see HAL equipment at:  
 Richter & Co.; Hannover  
 I.E.C. Interrelco; Bissone  
 Vicom Imports; Auburn, Vic., Australia

# Full Features and Superior Performance

## ST-6000 RTTY DEMODULATOR

Select Rx & Tx Shifts  
Accurately Tuned Rx Filters  
Crystal Controlled Tx Tones  
True Transceive Operation

Invert Both Rx Demod,  
and Tx Tones

Data Status Indicators  
Loop 1 Post-Autostart Pre-Autostart



Hard-Limiting [FM]  
or  
Non-Limiting [AM]  
Reception

Correct for  
Bias Distortion


Correct For  
Multi-Path Distortion

Local Loop Operation

Autostart with:  
◦ Motor Control  
◦ Mark Hold  
◦ Antispace

Tuning Oscilloscope  
[Front Panel Controls]  
Meter Indicator Option  
Also Available

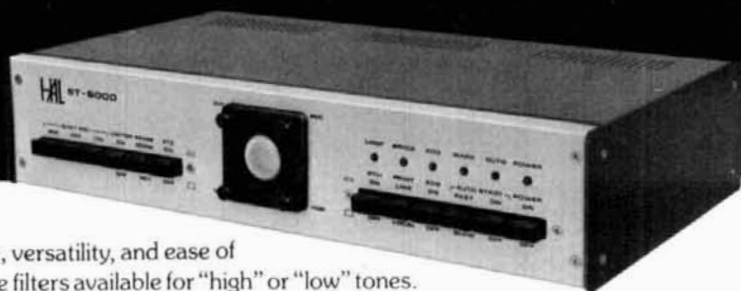Automatic Tx/Rx Station  
Control with Keyboard  
Operated Switch [KOS]



Why not have the best?

The HAL ST-6000 Demodulator offers outstanding performance, versatility, and ease of operation. The Receive Demodulator features multiple-pole active filters available for "high" or "low" tones. These filters are frequency-matched to the transmit tone crystals for true transceive operation. Input bandpass filters, discriminator filters, and post-detection filters are carefully designed and tested for optimum weak-signal recovery. The ST-6000 has an internal loop power supply, 2 loop keyers, RS-232, MIL-188C, and CMOS data I/O, and rear panel connections to data and control circuits for connection to UART and computer devices. Use it with the HAL DS-3000 KSR for the best in RTTY performance.

**\$595.00**

Write today for HAL's latest RTTY catalog.



**HAL COMMUNICATIONS CORP.**

Box 365  
Urbana, Illinois 61801  
217-367-7373



For our Overseas customers:  
see HAL equipment at:  
Richter & Co.; Hannover  
I.E.C. Interrelco; Bissone  
Vicom Imports; Auburn, Vic., Australia

# repeater interference: some corrective actions

Suggestions for  
repeater associations  
to minimize  
the ever-increasing  
interference problem

**Our local repeater**, WR4ADC, operating on the 146.34/146.94 pair, has been experiencing interference on both the input and output frequencies. This article covers the technical corrective actions which have been considered for this interference. Some of these are now being used or are being installed for future use.

## input channel anti-interference measures — lockout

Since repeaters operate on a fixed-frequency plan, one method of avoiding unnecessary call-up is to use a repeater lockout signal on transmissions not intended for repeaters. Technically, as in **fig. 1**, this would be simple. An NE-555 subaudible oscillator producing a small deviation would be required at the non-using transmitters. The repeater input receiver would need a tone detector and a relay contact in series with the carrier-operated relay (COR) to block operation when the tone is received.

While technically simple, this method of input interference prevention requires cooperation by the interfering stations. Lacking this, it is completely ineffective. It does seem to be a useful approach and could be adopted as a national standard. If done, the standard should include designation of the lockout tone frequency and of the deviation it produces.

While the lockout tone is not currently a useful technique, there are several technical anti-interference approaches available based on the characteristics of interfering signals. One of the most common of these is the frequency window, **fig. 2**, which locks

out transmission if the incoming signal is appreciably off frequency. While this is usually done to avoid excessive distortion, it is a powerful anti-interference method. In its simplest form, it may be a Schmidt trigger on the dc voltage at the discriminator, set to the value corresponding to the selected value of allowable frequency error, with the trigger interrupting the COR. Some filtering, on the order of a tenth-second time constant, is needed.

## signal characteristic measures

Other anti-interference measures based on the characteristics of interfering signals include:

1. a-m rejection
2. Wideband fm rejection
3. Non-voice modulation rejection

The purpose of a-m rejection, **fig. 3**, is to prevent operation of the repeater COR by an a-m carrier. In simple form this requires a pickoff from the receiver ahead of the limiters, feeding to an agc-controlled stage and an a-m detector. The lockout circuit would require presence of carrier in the fm section and in the a-m section, plus presence of a-m exceeding some percentage, say around 25 per cent. Some protection against noise pulses or unmodulated pauses would probably be required, at least several seconds time constant of filtering.

Rejection of wideband fm, **fig. 4**, would require a wideband receiver, and a form of detection of the out-of-band energy component. A simple form would be to compare audio levels of the narrow and wideband discriminator outputs: if they approach equality, the incoming signal would be wideband. Another wideband modulation detector would beat the limiter output against a local oscillator, followed by a highpass filter. The filter cutoff frequency would be set to the desired peak deviation.

A lockout system based on the absence of voice modulation, **fig. 5**, would be a powerful anti-interference technique. In principle, this is relatively simple — just measure the ratio of peak-to-average power in the audio. The ratio varies from 3 dB for pure sine waves, to 13 dB for noise, and to about 16 dB for voice. Noise-operated squelch makes the distinction between the last two easy.

However, in current fm practice, the approach is not this simple, since most fm transmitters use a

By **R. P. Haviland, W4MB**, 2100 South Nova Road, Box 45, Daytona Beach, Florida 32019

limiter to keep the deviation high, and this reduces the peak-to-average ratio. Because of this, a peak-to-average detector would have to be set to a lower ratio. About 6 dB, or 2:1 in voltage, with a time constant of about one-tenth second should be good and would provide appreciable protection against non-voice signals.

## wanted signal anti-interference measures

All of the above anti-interference measures are based on some characteristic of the unwanted signal. The other family of input frequency measures is based on characteristics of wanted signal. The two standard forms of this, **fig. 6**, are the subaudible tone, or *private line*, required continuously for access; and whistle-on, a single tone or a Touch-Tone signal giving access. Access may be for a definite time period or until the COR is dropped for a time period. Various other forms have been used, including carrier-formed Morse and two-band interlocking.

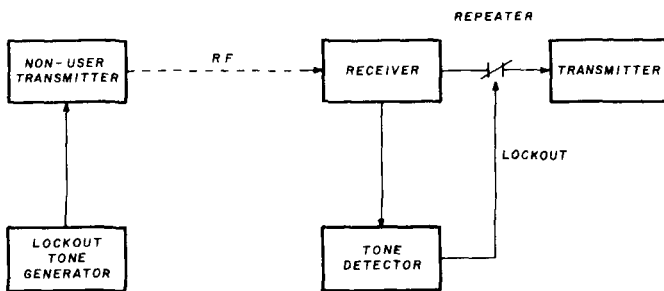


fig. 1. Elements of the repeater lockout system.

Most of these methods have the disadvantage of requiring additions to the using transmitter. This is not a severe problem for closed repeaters, where the number of users is small, but represents a serious drawback for open repeaters, especially those on the common frequencies or close to holiday areas or heavily traveled routes.

One method of partially overcoming this objection is to operate the repeater with carrier access only during no interference periods, and to switch to one of the other access methods when interference is experienced. This switch could be coupled with voice announcement on the identifier, giving instructions as to access method. A Touch-Tone access is probably best since such pads are common and since the signal should never be used in normal communication, except for signaling.

It would seem that this method would give good protection against incidental interference. Willful interference is another matter, since operation in ac-

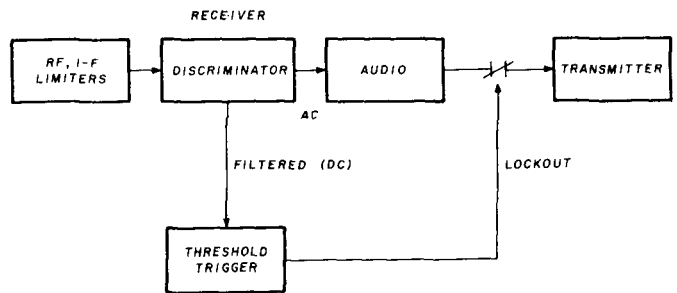


fig. 2. Elements of the frequency window, which locks out transmission if the incoming signal is appreciably off frequency.

cordance with the announcement instructions would turn the repeater on. However, malicious intent would seem to be proven if interference continues.

## output channel anti-interference measures — channel guards

Repeaters also cause interference, and some technique of guarding against the interference they cause may be desirable. Probably the best method of doing this is to guard the output channel, **fig. 7**, holding repeater operation in abeyance if the channel signal exceeds some predetermined value. To account for emergency operation, this guard could be combined with a timer identification announcement, giving instructions on the procedure to override the lockout.

The setting of the guard receiver would need to be based on a value of "signal to be protected," and a margin, or "protection ratio." These are common concepts in other radio services, but they have not been used in amateur operations. As a result, there are no accepted values for these quantities.

The closest other service is the Mobile Service, which includes land mobile. Since this was the source of many 2-meter repeater concepts and equipment, it should provide good guidance.

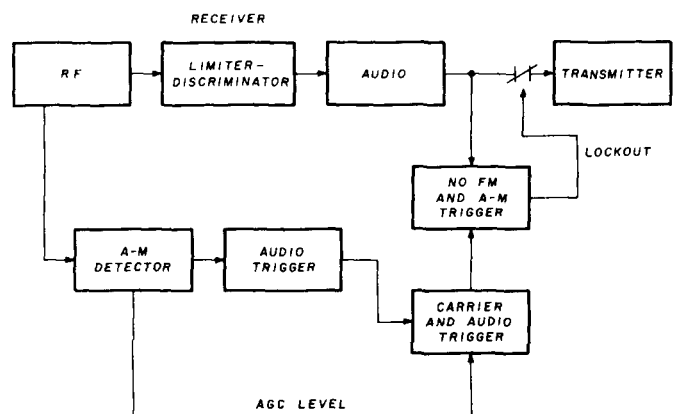


fig. 3. Principle of a-m lockout, which prevents operation of the repeater COR by an a-m carrier.



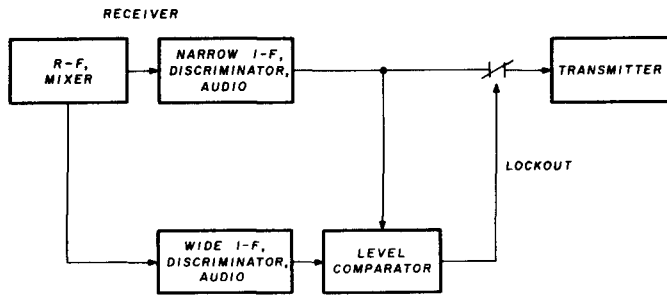


fig. 4. Principle of wideband fm lockout, which would require a wideband receiver and a form of detecting the out-of-band energy component.

The International Consultative Committee (CCIR) data which relates to this matter is in their Report 358. This report states that, not considering the effects of natural or man-made noise, the median signal levels to be protected for an average grade of mobile service are:

band (MHz)	signal (dB above 1 $\mu\text{V}/\text{m}$ )
30-50	8
50-100	14
100-200	20
400-470	28

The report also states that the protection ratio, based on degradation from 20 dB S/N to 14 dB S/I, should be 8 dB for fm with fm interference, or 7 dB for fm with a-m interference. The report lists other ratios, but it has not been necessary to consider these, since the 2-meter National plan is based on narrow-band fm.

The 1971 Special Joint Meeting of the CCIR gives the following noise values:

- typical urban noise, 150 MHz, + 35 dB (KTB)
- typical rural noise, 150 MHz, + 3 dB (KTB)
- maximum cosmic noise, 150 MHz, + 8 dB (KTB)

These figures are based on omnidirectional antennas.

Many repeaters are located in urban areas and will see full urban noise levels; others are remotely located and will see less noise. Assume that the cosmic value, 8 dB, represents typical noise. Then the value of signal to be protected becomes 20 + 8 or 28 dB above 1  $\mu\text{V}/\text{m}$  — about 25  $\mu\text{V}/\text{m}$ . (This signal would give 20 dB output signal/noise in the average mobile installation and in a typical location.) The allowable value of interference that would give protection for this signal is 28-8, or 20 dB above 1  $\mu\text{V}/\text{m}$  — just 10  $\mu\text{V}/\text{m}$ . (Presence of the interference would reduce the 20 dB S/N to 14 dB S/I.)

It is easy to see the effect of this protection level if the values are translated to power and distance relationships. For average terrain, the effective radiated transmitter power to just reach the 10  $\mu\text{V}/\text{m}$  signal, as a function of distance from the repeater, is approximately:

distance km (miles)	transmitter antenna height		
	100 ft (30m) or more	30 ft (9m)	10 ft (3m) or less
	transmitter power (W)	transmitter power (W)	transmitter power (W)
10 6.2	0.02	0.3	3.0
15 9.3	0.5	3.0	31.0
20 12.4	1.0	6.0	60.0
30 18.6	8.0	50.0	500.0
50 31.0	100.0	500.0	5000.0
100 62.1	3000.0	8000.0	—

The ERP is the product of the transmitter output and the antenna gain multiplied by 2.5 (to include the effect of ground reflection).

Stated another way, the 10-microvolt signal would be produced by a typical mobile at about 8 miles (13km) distance, by a typical base station at about 18 miles (29km), or by a DX station about 90 miles (144km) away and beaming toward the repeater. The signal would be the same as that of another typical repeater if it were some 50 miles (80km) away.

These values indicate that output channel guarding to the 10  $\mu\text{V}$  level would not eliminate *all* interference. However, it would prevent interference to simplex operation within reasonable distances, to the point that any resulting interference would hardly be considered harmful. Accordingly it would appear that repeater associations wishing to minimize interference problems should consider this approach.

Construction of an automatic protection system should not be difficult. The output-channel monitor-receiver antenna could be mounted on the repeater tower at a height of 30 feet (9m). (This level is used because the height gain is zero.) Assuming use of a

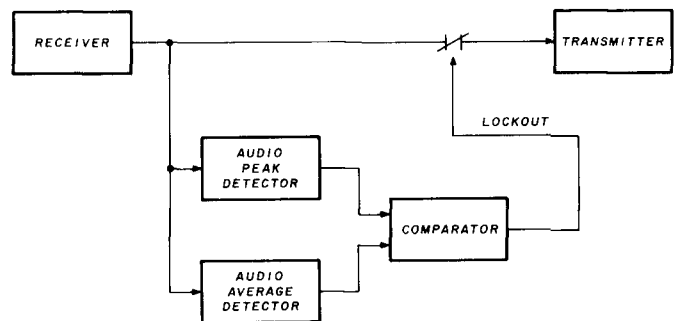


fig. 5. The non-voice lockout principle. Comparator measures peak-to-average power ratio in the audio, which varies from 3 dB for pure sine waves to about 16 dB for voice.

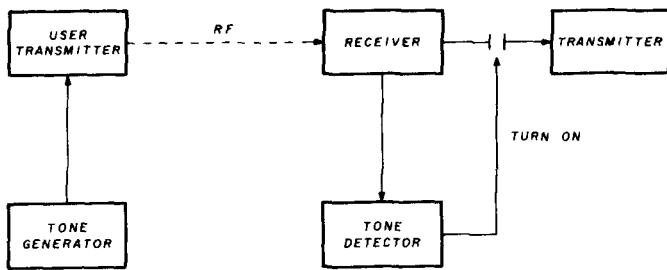


fig. 6. Elements of the tone-access system, which is based on characteristics of the wanted, rather than the interfering, signal.

dipole, its captive area is  $0.54 \text{ m}^2$  (free space), or  $1.35 \text{ m}^2$  over average ground. A signal of  $10 \mu\text{V}/\text{m} + 10 \text{ dB}$  above  $1 \text{ V}$  corresponds to a flux level of  $-136 \text{ dB W}/\text{m}^2$ , so the antenna captures about  $-133 \text{ dB}$  relative to  $1 \text{ watt}$ . Assuming  $3 \text{ dB}$  line loss, this becomes  $-136 \text{ dBW}$  at the receiver input, or about  $0.2$  microvolt.

Setting the squelch to operate at this signal level would allow use of the squelch circuit to produce the protect control signal. Suitable timers and desensitize circuits would have to be included. A five-minute delay after detection of the channel-occupied signal might be used. A voice announcement could be included to the effect that the output channel is occupied. Emergency over-ride instructions could also be included.

### auto-QSY

Probably the most important HF method of interference control is to QSY. This is not really practical in repeater operation. However, there is a partial step which seems possible, fig. 8, and one which would make QSY for the station on the repeater output channel easier. This is to shift the repeater output frequency by a small amount;  $5 \text{ kHz}$  would seem to be suitable.

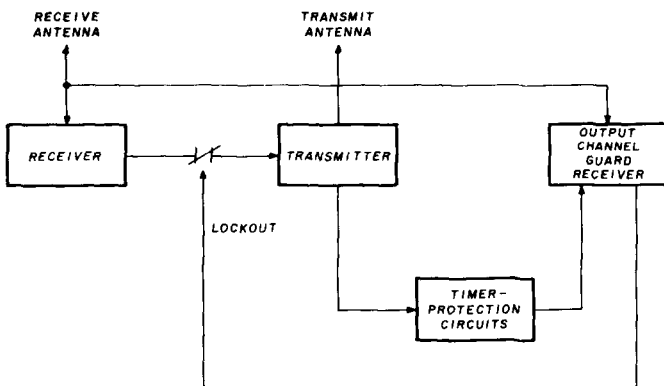


fig. 7. The output-frequency guard receiver principle, in which repeater operation is locked out if the channel signal exceeds some predetermined value.

A limited number of tests with this method indicate that the effect on normal repeater operation would be negligible — a small increase in distortion and a small decrease in range. With no other action, the effect on the other station on the channel would also be small. However, if the other station would also QSY by the same amount, but in the opposite direction, he would escape the interference completely. At the same time his operation would be affected only by a small amount. For the repeater users and the other stations involved, nearly full operation could be restored by retuning.

The signal for this scheme can be generated by the circuitry used for transmit lockout. (If desired, the channel-occupied receiver could be widened out a bit to give better detection of these slightly offset signals.)

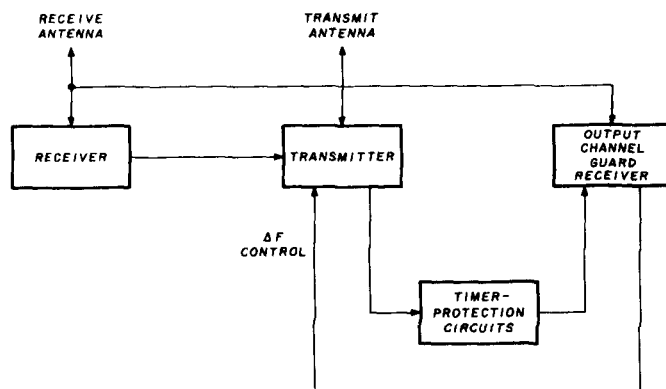



fig. 8. Principle of channel-occupied QSY method, which would make it worthwhile for the station on the repeater output to change frequency slightly.

It may be noted that this offset method is used in vhf television to reduce co-channel interference and to allow closer station spacings. It is a powerful anti-interference technique.

A number of other anti-interference measures have been considered with respect to WR4ADC interference problems. The other technical ones considered did not seem attractive and so are not reported. There were several operational ones of value, and these have been discussed along with the technical solutions above.

With increasing numbers of amateurs on the air, and especially with the continued expansion of repeater operation, interference is going to increase. It seems to be time for the repeater associations to consider the steps that should be taken to minimize those interference problems. This should include recommendation of standard techniques and of protection ratios.


ham radio

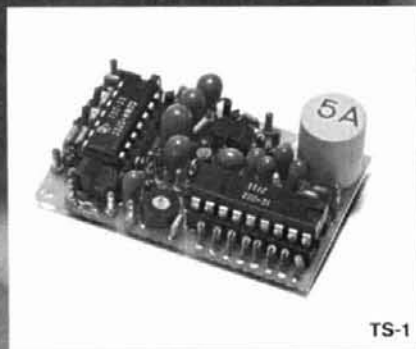


TS-1



TS-1JR

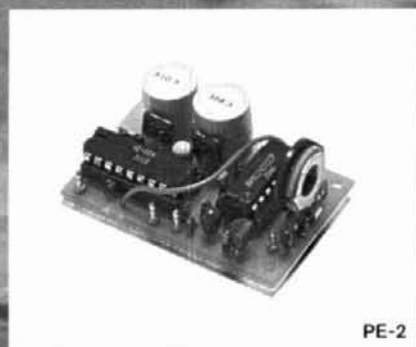

PE-2

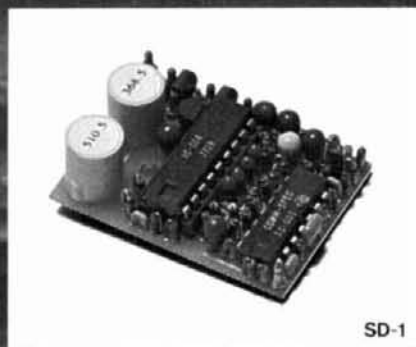


SD-1
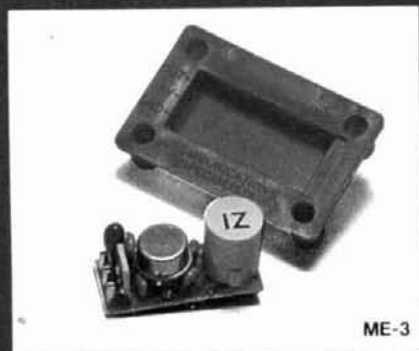
# THE DAWNING

The age of tone control has come to Amateur Radio. What better way to utilize our ever diminishing resource of frequency spectrum? Sub-audible tone control allows several repeaters to share the same channel with minimal geographic separation. It allows protection from intermod and interference for repeaters, remote base stations, and autopatches. It even allows silent monitoring of our crowded simplex channels.


We make the most reliable and complete line of tone products available. All are totally immune to RF, use plug-in, field replaceable, frequency determining elements for low cost and the most accurate and stable frequency control possible. Our impeccable 1 day delivery is unmatched in the industry and you are protected by a full 1 year warranty when our products are returned to the factory for repair. Isn't it time for you to get into the New Age of tone control?




ME-3



TE-8

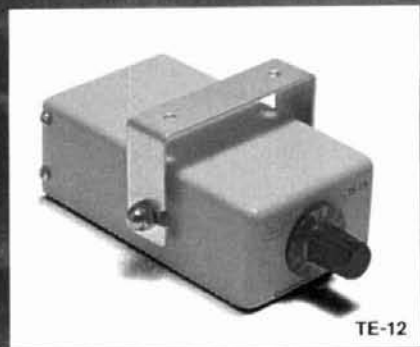

TE-12

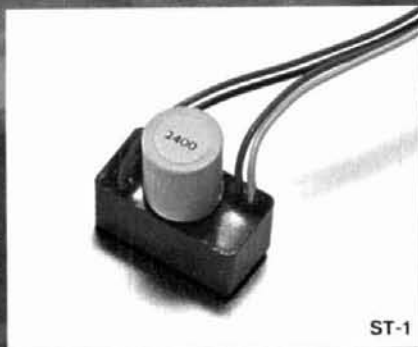

ST-1

# OF A NEW AGE.

**TS-1** Sub-Audible Encoder-Decoder • Microminiature in size, 1.25" x 2.0" x .65" • Encodes and decodes simultaneously • **\$59.95** complete with K-1 element.

**TS-1JR** Sub-Audible Encoder-Decoder • Microminiature version of the TS-1 measuring just 1.0" x 1.25" x .65", for hand-held units • **\$79.95** complete with K-1 element.

**ME-3** Sub-Audible Encoder • Microminiature in size, measures .45" x 1.1" x .6" • Instant start-up • **\$29.95** complete with K-1 element.

**TE-8** Eight-Tone Sub-Audible Encoder • Measures 2.6" x 2.0" x .7" • Frequency selection made by either a pull to ground or to supply • **\$69.95** with 8 K-1 elements.

**PE-2** Two-Tone Sequential Encoder for paging • Two call unit • Measures 1.25" x 2.0" x .65" • **\$49.95** with 2K-2 elements.

**SD-1** Two-Tone Sequential Decoder • Frequency range is 268.5 - 2109.4 Hz • Measures 1.2" x 1.67" x .65" • Momentary output for horn relay, latched output for call light and receiver muting built-in • **\$59.95** with 2 K-2 elements.

**TE-12** Twelve-Tone Sub-Audible or Burst-Tone Encoder • Frequency range is 67.0 - 263.0 Hz sub-audible or 1650 - 4200 Hz burst-tone • Measures 4.25" x 2.5" x 1.5" • **\$79.95** with 12 K-1 elements.

**ST-1** Burst-Tone Encoder • Measures .95" x .5" x .5" plus K-1 measurements • Frequency range is 1650 - 4200 Hz • **\$29.95** with K-1 element.



**COMMUNICATIONS  
SPECIALISTS**


426 W. Taft Ave., Orange, CA 92667  
(714) 998-3021


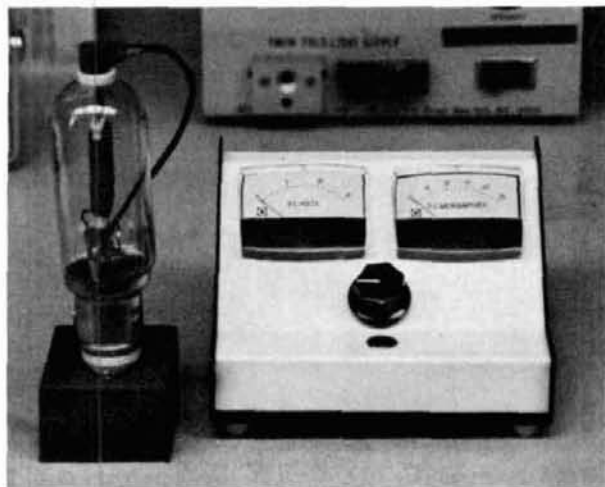
## Joe Carr, K4IPV testing power tubes

Several months ago a reader of this column wrote me asking the question, "How do you test rf power tubes?" Not long afterward a close friend of mine, about to build a linear amplifier for 80 through 10 meters, bought a box full of used 4X150 power tetrodes at a hamfest. After building the amplifier he found that none of the tubes were good and that he would have been better off using another type of tube from his collection that was known to be good. He naturally wanted to know if there was a better way available to amateurs than testing by trying.

In my work, medical electronic servicing, we repair *electrosurgical generators*, which are rf power oscillators that produce up to several hundred watts in the 500-2500-kHz range. Some old but still perfectly good *electrosurgical generators* use the type UXCV-11 power triodes in a push-pull pair. These tubes cost about \$120 each (\$240 per pair!) unless you are clever enough to know about United Electronics in Newark, New Jersey. The cost makes stocking a number



Final project built by the author for testing high-power vacuum tubes.

large enough to permit routine testing by substitution too costly — especially in a shop with a limited budget. Again, there "has to be a better way!"

Three times within the past six months people and situations have forced the issue of testing transmitting tubes, so perhaps it is time that we covered that point in this column. But before we answer the question posed originally, let's recap a little about elementary vacuum tubes.

A vacuum tube consists of an electron emitter called a cathode, several grids, and an electron collector called either a plate or an anode. The cathode can be either an incandescent filament, or an indirectly heated metal cylinder that has a heated filament at its center. The plate surrounds the cathode but is insulated from it. The various grids are placed in the space between the cathode and the plate.

The plate will have an electrical potential that is positive with respect to the cathode. Grid no. 1, the *control grid*, is given a negative potential with respect to the cathode so it can control the flow of electrons between cathode and plate. The second grid is called the screen grid or accelerator grid and is given a positive potential with respect to the cathode. The third grid, that nearest the plate (G3), is called the *suppressor grid* and may be either biased negative with respect to the cathode or (more commonly) tied directly to the cathode either internally or externally, as shown in **fig. 1**.

Variations in the grid voltage will produce variations in the plate current, which by Ohm's law, become variations in the voltage drop across the load resistor,  $R_L$ .

Several vacuum tube parameters are of interest when trying to ascertain overall quality. These are: amplification factor ( $\mu$  or  $\mu$ ), plate resistance ( $R_p$  from the spec sheet or data book), and the transconductance ( $g_m$ ).

The amplification factor is defined as the change in output voltage caused by a given change in grid no. 1 (input) voltage. In fact, the amplification factor of any amplifying device can be given by:

$$\text{amplification} = \frac{E_{out}}{E_{in}} \quad (1)$$

But for vacuum tubes specifically we can use the notation:

$$\mu = \frac{\Delta E_b}{\Delta E_c} \quad (2)$$

where:

$\Delta E_b$  is the change in plate voltage  
 $\Delta E_c$  is the change in plate current

The transconductance rating relates a change in plate current ( $I_p$ ) for a small change in grid voltage,



with the plate *voltage* held constant. In other words:

$$gm = \left. \frac{\Delta I_p}{\Delta E_c} \right|_{E_b = \text{constant}} \quad (3)$$

where:

$\Delta I_p$  is the change in plate current expressed in amperes

$\Delta E_c$  is the small change in grid bias voltage expressed in volts

$gm$  is the transconductance expressed in mhos

This relationship will lead us to a method for testing tubes easily and quickly.

### tube tester configurations

Fig. 2 shows the basic circuit for a short-circuit tester. This will give only limited information but is useful when screening a large number of hamfest specials. Why perform a more time-consuming test on a tube that has a high resistance short between the filament and cathode, for example?

The tester circuit is nothing more than a series of several continuity testers arranged to ascertain the existence of any resistance paths between adjacent elements. Each continuity tester consists of a low-current filament transformer (*i.e.*, rated at less than 1 ampere) and a compatible lamp. I was tempted to specify the use of light emitting diodes instead of lamps but was quickly persuaded to use lamps because the LEDs made the device too sensitive. This problem causes apparent shorts, when all we are reading is electrons flowing from the heated filament to the electrode on half cycles when the ac is positive-going.

It is best to test for shorts after allowing the tube to warm up for a few minutes. Some shorts do not be-

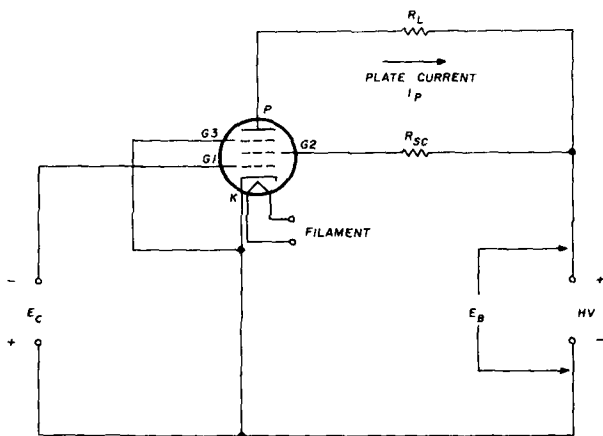


fig. 1. Fundamental vacuum-tube circuit.

come apparent until after the tube has reached operating temperature. This is also the reason why the use of an ohmmeter is not recommended in this case.

The simplest tester circuit that gives us a qualitative insight into the worth of any given tube is the *emission tester* of fig. 3. This circuit tests the tube for the emission of electrons from the cathode. Notice that the tube is connected in a diode configura-

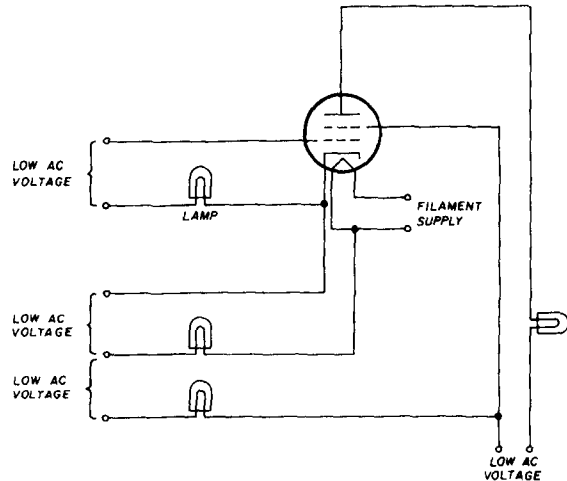


fig. 2. Short-circuit tester.

tion in which all elements except the cathode and filaments are connected to the plate.

The tube in a circuit such as fig. 3 acts very much like the classic diode. The *emission current* is defined as the saturation current of the tube. If the plate voltage is increased from near zero, we find that the plate current will also increase in a nearly linear manner (except at very low plate potentials). But once a certain critical plate voltage is reached, we find that the plate will attract all the electrons that the cathode produces. Any further increase in plate voltage will produce very little, if any, increase in plate current. The current level at which this occurs is the *saturation* or *emission current*.\*

The emission-type tube tester checks for this current, and if the current is low, it will indicate "reject." Some tubes cannot be tested at the actual saturation current either because it is inconvenient to do so, or because the current is too high and may damage the tube. These tubes are tested at a specific plate potential, at which a given current is expected. If the tube will not produce at least a certain predetermined percentage of that current (usually 80 to 90 per cent), then it is rejected. The emission tester can spot a grossly bad tube, but there are certain problems with

\*An interesting variation of the emission tester, which does not require high voltage but uses a low-voltage bias source, is described in reference 1. editor.



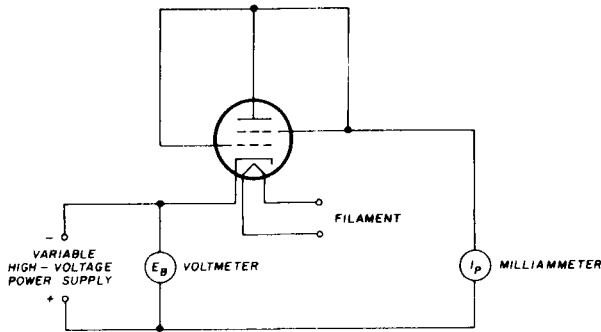


fig. 3. Circuit for simple emission-type tube tester.

this type. Note that most drug-store tube testers are emission types.

Defects that will prevent the tube from operating normally will not always show up on a simple emission tester, so some better means is necessary. The type of tester preferred by most professional servicers is the *mutual conductance* or *transconductance* tester. Examples of this type of circuit are given in fig. 4. The circuit shown in fig. 4A is a static transconductance tester using the *grid-shift* method, also called *grid-level shift*.

Switch S1 is in position 1 at the beginning of the test, making grid voltage  $E_c$  equal to  $E_2$  alone. Both  $E_1$  and  $E_2$  are adjusted to produce a convenient (safe!) plate current. It is usually wiser to begin with the plate voltage ( $E_1$ ) at some level well within the range that can be tolerated by the particular tube being tested, and have the grid voltage at some value in excess of cutoff for that tube. This may be unnecessary much of the time but could save you some grief often enough to make it a good standard practice. You may then adjust the grid voltage downward until the plate current is at a convenient level. When this adjustment is completed, make a note of the values of  $E_b$ ,  $I_p$ , and  $E_c$ .

To perform the test, place switch S1 in position 2. This operation makes grid voltage  $E_c$  equal to  $(E_2 + E_3)$ . The plate voltage is then measured and the supply readjusted if a change has been noted. The plate voltage at this point must be equal to the plate voltage that existed initially.

Now read the plate current, and find the *difference* between this reading and the initial reading. Plug the difference current into the formula:

$$gm = \frac{\Delta I_p}{1.5} \quad (4)$$

where:

$\Delta I_p$  is in amperes

$gm$  is in mhos

This answer is given in *mhos*, but most vacuum tube spec sheets list the transconductance in *micro-mhos*. 1 mho = 1-million  $\mu$ mhos, so multiply the answer by  $10^6$ .

A *dynamic* transconductance tube tester is shown in fig. 4B. This circuit is the basis for most commercial tube testers. A low voltage ac transformer is connected in series with the grid bias power supply, so that the transformer secondary voltage forms the "*delta- $E_c$* ." Actual transconductance is measured on the plate ac milliammeter, which is calibrated in units of conductance.

Fig. 5 and the photo show a test jig I built to test power tubes at work. It will serve equally well for amateurs. The circuit is the simple grid-shift method for finding the transconductance of the tube being tested. Note that it is not a real tube tester construction project because it lacks power supplies. Almost all amateurs can jury-rig adequate power supplies to make this test or can borrow bench supplies. Note also that it is not strictly necessary to use the full operating voltage of the tube to obtain meaningful results.

Please, be very careful when using this jig; high voltages will be exposed! If there is any doubt, place the tube socket subassembly inside an insulated or *grounded* metal enclosure. I may seem to harp on

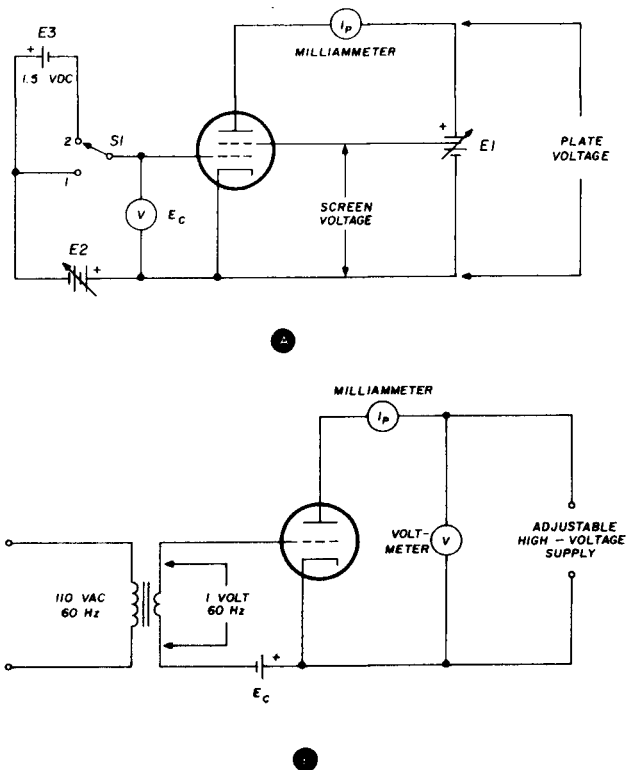


fig. 4. Static transconductance tester, A, and dynamic transconductance tester, B.

safety an awful lot, but it is so very important. Recall the note on one of my past articles which pointed out that an editor almost canded himself while working on a 4000-volt final amplifier power supply.

The test jig is built in two main parts, a main assembly and a tube-socket subassembly. A multiconductor cable connects the two parts of the jig. This design was selected so that the same mainframe can be used to accommodate a larger number of different tube types.

Jacks J1-J8 are heavy duty banana-jack binding posts, while J9/P1 are a mating pair of multipin connectors such as the circular MS or AN series. I used a high-voltage power supply that delivered 500 Vdc, but if greater potentials are needed (I doubt that they will) it would be wise to change J1-J4 to high-voltage chassis connectors.

Meter M1 is an appropriate high-voltage meter, although in my case a voltmeter was made from a suitable multiplier resistor (a pot and a fixed resistor) and an available 0-50- $\mu$ A meter movement. Meter M2 is a dc voltmeter with a range suitable for the range of grid voltages expected.

Resistors R1-R3 were selected so that varying R2 produced approximately 1 volt of grid voltage change. R1 is used to allow precision trimming of that change. In my case,  $E_c$  was 25 Vdc, but if your voltage is different, use the normal voltage divider equation to find appropriate resistor values.

Resistor R4 is made approximately equal to the plate resistance of the tube being tested, which in this case was about 3000 ohms.

I used an external plate current milliammeter

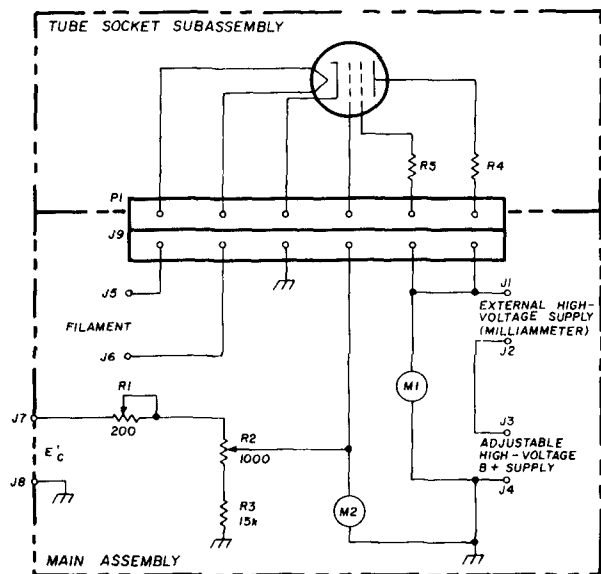


fig. 5. Schematic for a practical static (grid-shift) transconductance tube tester.

table 1. Transconductance measurements of type UXCV-11 tubes made by the author on the test jig shown in fig. 5.

bad tubes	$\Delta E_c$ (volts)	$\Delta I_p$ (amps)	$g_m$ (micromhos)
1	1	0.0013	1300
2	1	0.0015	1500
3	1	0.0014	1400
good tubes			
1	1	0.0045	4500
2	1	0.0039	3900
3	1	0.0043	4300

because there was a digital multimeter available that would measure current very accurately.

Table 1 lists the values of transconductance actually measured for both known good and known bad tubes. The UXCV-11 has a  $\mu$  of 14 and a plate resistance of 3220 ohms. The spec sheet does not give the transconductance, but we may compute it from:

$$g_m = \frac{\mu}{R_p} \quad (5)$$

$$g_m = \frac{14}{3220}$$

$$g_m \approx 0.00435 \text{ mhos}$$

$$g_m \approx 4350 \mu\text{mhos}$$

(Note that all the bad tubes had grossly lowered  $g_m$  readings.)

This tester is not "scientifically" designed but is intended to allow amateurs to test power tubes on an occasional basis. Its saving grace is that it can be built inexpensively! Note that I defined "bad tube" by saving from my own work those tubes that had been found to produce customer complaints similar to, "It seems to work, but has low output." These observations were confirmed by an rf ammeter in series with my 500-ohm (not 50-ohm; these were medical rf generators) dummy load. The real value of this tester is that it will allow you to test hamfest specials or perform preventive maintenance on your equipment. Of course, if you have an rf power meter or rf ammeter in your feedline, then a low-power output coupled with seemingly normal drive will point the finger to the final amplifier tubes. But the thought of that poor guy building an entire linear amplifier around a whole box full of bad tubes seems to justify doing a little testing — at five minutes per tube, how could he have gone wrong?

## references

1. Neil Johnson, W2OLU, "Testing High-Power Tubes," *ham radio (The Ham Notebook)*, March, 1972, page 64.

ham radio

**KENWOOD**  
*...pacesetter in amateur radio*

The TS-820S... still the Pacesetter. It has proven itself to be the performer we promised, proven itself through thousands of hours of operating time, world wide and under the most difficult conditions. Unique features, superb specifications and top quality construction... all hallmarks of Kenwood amateur products are eminently displayed in the TS-820S. But then, you've probably heard all that on the air by now.

The TS-820S puts out probably the cleanest signal on the bands. The third order products are at least -35 dB due to Kenwood's unique RF Negative Feedback (RFNFB) circuit. State-of-the-Art PLL and single conversion design are combined for superb spurious characteristics far exceeding today's FCC requirements... the non-harmonic spurious emissions are better than -60 dB and the harmonic spurious are better than -40 dB. The receiver boasts outstanding sensitivity... better than .25 uV for 10 dB S/N. And when it comes to dynamic range, it's tough to beat the TS-820S. These are impressive numbers. That's why so many prominent DXers are using the Kenwood Pacesetter... the TS-820S.

The man to see... your local Authorized Kenwood Dealer. He can give you all the information you need and the best deal.

# TS-820S



**TS-820S VFO-820S SP-820**

Kenwood's unbeatable combination. The VFO-820 solid state remote VFO adds greatly to the versatility of your TS-820S. It has its own RIT circuit, control switch and is a perfectly matched accessory. The SP-820 deluxe external matching speaker includes audio filters for added versatility on receive and two audio inputs.

The TS-520S provides full coverage on all amateur bands from 1.8 to 29.7 MHz. It provides 160 meter capability, WWV on 15.0 MHz and an auxiliary band position for maximum flexibility. With the addition of the DG-5, you have an easy to read, accurate readout of your operating frequency while transmitting and receiving. The TS-520S is solid state except for the driver and the two final tubes. It also incorporates a 3SK35 dual gate MOSFET for outstanding cross modulation and spurious response characteristics.

The TS-520S is completely self-contained with a rugged AC power supply built in. The addition of the DS-1A DC-DC converter (option) allows for mobile operation. Additional features of the TS-520S include: A new improved speech processor • An extremely effective noise blanker • A built in 20 dB attenuator • Convenient jacks for PHONE PATCH IN and PHONE PATCH OUT • Amplified type AGC circuit RIT control • 8-pole crystal filter • Built-in 25 KHz calibrator • Front panel carrier level control • Semi-break-in CW with sidetone • VOX/PTT/MOX • TUNE position for low power tune up • Built in speaker • Built in cooling fan • Provision for 4 fixed frequency channels • Heater switch.

The man to see... your local Authorized Kenwood Dealer. He can give you all the information you need and the best deal.


The TS-520S... still the most popular transceiver in the world, is a solid foundation for an expanding series designed to please any ham... from Novice to Extra.
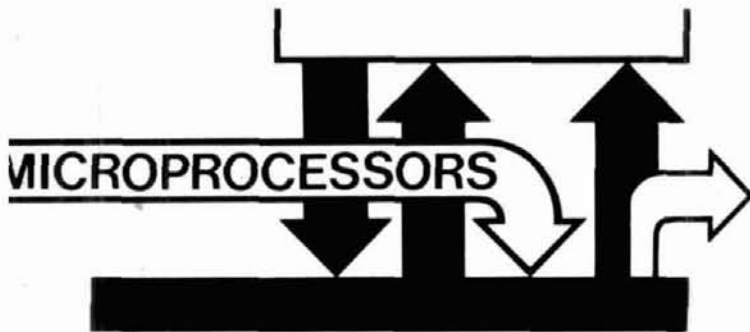
# TS-520S



A great station... at an affordable price! The TS-520S with its companion accessories... including two new units. The AT-200 antenna tuner provides a versatile tool in any station. The other is the TV-520S, Kenwood's 2 meter transverter for SSB and CW operation from 146 to 148 MHz.

TRIO-KENWOOD COMMUNICATIONS INC.  
1111 WEST WALNUT/COMPTON, CA 90220



## microcomputer interfacing: interfacing a 10-bit DAC

A **Digital-to-Analog Converter** or DAC is an electronic device that converts digital signals into analog signals. A typical converter consists of an arrangement of "weighted" resistors, each controlled by a single bit of input data, that develops varying output analog voltages or currents in accordance with the digital input code.<sup>1</sup> You could use a DAC to provide a small analog error signal from a microcomputer used in a feedback circuit, to convert a sequence of bytes in memory into analog-vs-time data and thus simulate the output from an analog instrument such as a rotator control box for tracking OSCAR; to provide analog data for the two channels of an x-y recorder, or in general, to operate any device that requires an analog voltage or current and is interfaced to a digital device, such as a microcomputer.

For a general discussion of the principles of analog/digital conversion, you should read the excellent

Reprinted with permission from American Laboratory, February, 1977, copyright © International Scientific Communications, Inc., Fairfield, Connecticut, 1977.


By **Peter R. Rony, Jonathan A. Titus, Christopher Titus, and David G. Larsen, WB4HYJ**

Mr. Larsen, Department of Chemistry, and Dr. Rony, Department of Chemical Engineering are with the Virginia Polytechnic Institute and State University, Blacksburg, Virginia. Mr. Jonathan Titus, and Dr. Christopher Titus are with Tychon, Inc., Blacksburg, Virginia.

Analog Devices conversion handbook<sup>1</sup> or the series of small pamphlets distributed by National Semiconductor Corporation.<sup>2</sup> Important terms and concepts associated with DACs include resolution, accuracy, scale error, gain error, offset error, linearity, differential linearity, settling time, slew rate, overshoot and glitches, temperature coefficient, supply rejection, conversion rate, and output drive capability. A few of the terms have been summarized in **table 1**.

To help understand how you'd interface a DAC to an 8-bit microcomputer, **fig. 1** shows the connections between an Analog Device AD7522 and an 8080A-based microcomputer. An important feature of this specific DAC is the fact that it is double buffered; this means that there exist within the device

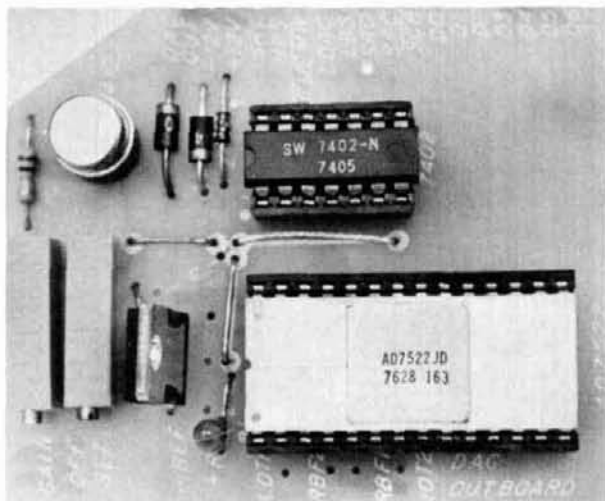The DAC *Outboard* circuit board contains all the circuitry shown in **fig. 1**. A copy of the board layout is available from the authors.






two independent 10-bit registers, the DAC register and the two-bit and eight-bit shift registers (**fig. 2**).

A DAC is an output device for a microcomputer, and thus data is strobed from the microcomputer data bus into the internal registers or latches, of the DAC. In **fig. 1**, are shown the connections to the 8-bit bidirectional data bus, D0 through D7, the 8080A control signals OUT or MEMW, which are used with accumulator I/O or memory I/O data transfers,<sup>3</sup> and the channel select outputs 003 through 005 that are generated by a decoder tied to the microcomputer address bus.<sup>4</sup>

Since the AD7522 is a 10-bit DAC, it is not possible to simultaneously load all ten bits from an 8-bit microcomputer. The sequence that actually occurs can be summarized as:


1. The DAC input bits DB0 through DB7 are first strobed into the 8-bit shift register/latch using a positive device select pulse applied at pin 24, (LBS or Low Byte Strobe).
2. The most significant two bits, DB8 and DB9, are then strobed into the 2-bit shift register via the use of a device select pulse applied at pin 25 (HBS or High Byte Strobe).
3. Finally, a device select pulse applied at pin 22 (LDAC or Load DAC) transfers the ten bits of input data, DB0 through DB9, into the second buffer within the DAC chip, the DAC register.

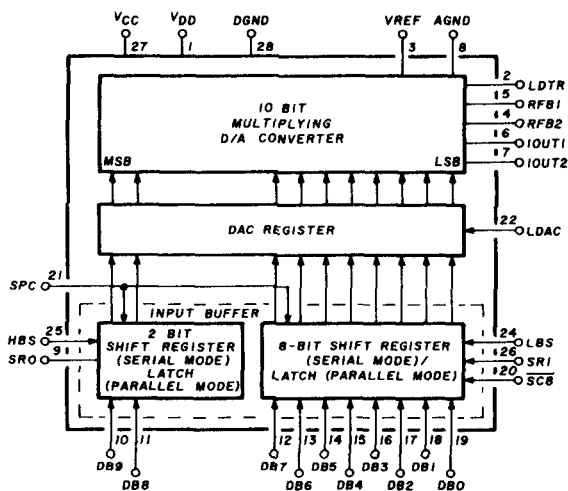

**fig. 2.** Functional diagram of the AD7522 IC. This figure is courtesy of Analog Devices.

The output current appears at IOUT1 and IOUT2 and is converted into a voltage with the aid of a 741 operational amplifier. The two most significant bits are loaded from the eight-bit microcomputer bus using any two bits. Generally bits D0 and D1 are chosen since it makes data formatting easier. Thus, the ten bits are transferred as eight bits D0 to D7 and as two additional bits, D0 and D1.

A simple program that exercises the DAC over its full operating range is provided in **table 2**. The program generates a slow linear ramp at the analog out-

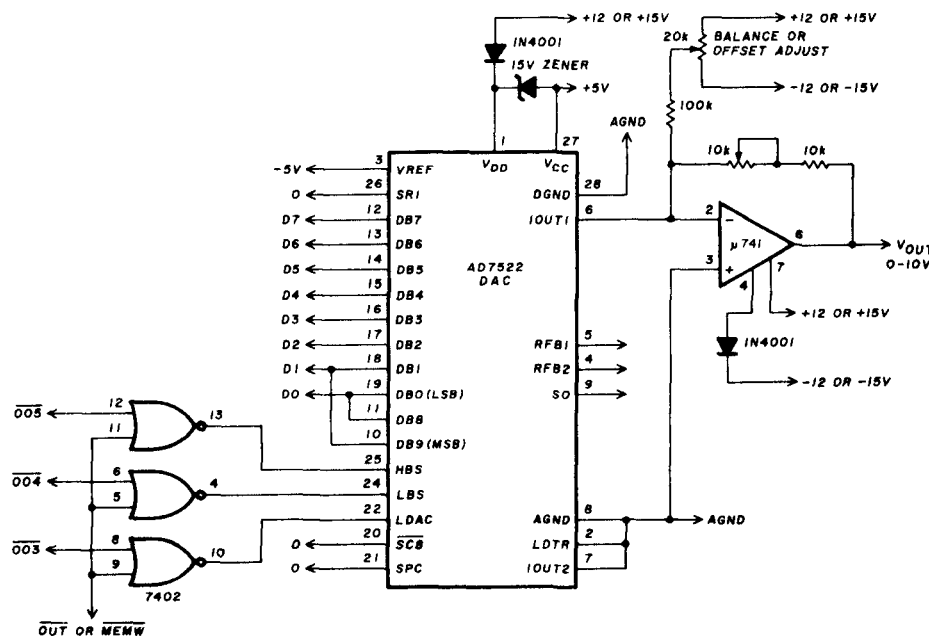

**fig. 1.** Schematic diagram of an interface circuit between an 8080A-based microcomputer and an Analog Devices AD7522 digital-to-analog converter.



**table 1. Important concepts and terms associated with digital-to-analog converters.**

Resolution	The smallest standard incremental change in output voltage of a DAC. A converter with $n$ input bits can resolve one part in $2^n$ .
Accuracy	Describes the worst case deviation of the DAC output voltage from a straight line drawn between zero and full scale; it includes all errors.
Settling time	The elapsed time after a code transition for a DAC output to reach a final value within specified limits.
Conversion rate	The speed at which a DAC can make repetitive data conversions.
Nonlinearity	Error contributed by a deviation of the DAC transfer function from a best straight line function. Normally expressed as a percentage of full scale range.
Monolithic chip	An integrated circuit chip in which both active and passive elements are simultaneously formed in a single small silicon wafer via the use of diffusion and epitaxial processes. Metallic stripes are evaporated onto the oxidized surface of the silicon to interconnect the elements.
Multiplying DAC	A digital-to-analog converter in which the output analog signal is the product of the number represented by the digital input code and the input analog reference voltage, which may vary from scale to zero, and in some cases, even to negative values.

**table 2. Memory I/O program that generates a slow linear ramp. Execution starts at HI = 003 and LO = 000.**

LO address byte	instruction byte	mnemonic	comments
START: 000	042	SHLD	Strobe ten bits of digital data into the AD7522 DAC shift registers. The ten input data bits are contained in register pair H. The address select code for the LBS input is HI = 200 and LO = 004; the address select code for the HBS input is HI = 100 and LO = 005.
001	004	004	
002	200	200	
003	062	STA	Strobe ten bits of digital data from the input buffer into the DAC register within the AD7522 DAC. The address select code for the LDAC input is HI = 200 and LO = 003.
004	003	003	
005	200	200	
006	043	INX H	Increment register pair H
007	315	CALL*	Call 10 ms time delay routine, DELAY
010	277	277	LO address byte of DELAY
011	000	000	HI address byte of DELAY
012	303	JMP	Unconditional jump to START, where the input of new data into the DAC occurs
013	000	000	LO address byte of START
014	003	003	HI address byte of START

\*On the 8080-based microcomputer that we use in our courses, a 10 millisecond time delay subroutine is located in EPROM starting at HI = 000 and LO = 277. Such a routine can be located anywhere in memory.

put of the AD7522. This can be observed on a Vom, digital multimeter, or oscilloscope. The ramp is subdivided into 1024 small steps, each step being approximately 5 mV in magnitude. The total time required to change from 0.0 volts to +5.12 volts is 10.24 seconds. The SHLD <B2> <B3> instruction outputs two data bytes in succession, from register pair H, into the input buffer registers of the DAC. The contents of register L are transferred into the 8-bit shift register, while the least significant two bits in register H go into the 2-bit shift register. Note that the address is automatically incremented, and a second MEMW control pulse generated by the 8080A when the SHLD instruction is executed. The STA <B2> <B3> instruction provides only a strobe pulse at the LDAC input to the DAC; no data transfer occurs between the accumulator and the DAC.

Other small monolithic and hybrid DAC systems are available from different manufacturers. The Analog Devices converter was chosen because of the on-the-chip latches and double buffering registers. The use of a reference potential is common to many DAC modules. Perhaps in the future it, too, will be included in the module.

### references


1. *Analog-Digital Conversion Handbook*, Analog Devices, Inc., Norwood, Massachusetts 02062.
2. "Specifying A/D and D/A Converters," AN-156, and "Data Acquisition System Interface to Computers," AN-159. National Semiconductor Corporation, Semiconductor Division, 2900 Semiconductor Drive, Santa Clara, California 95051.
3. Peter R. Rony, et al, "Microcomputer interfacing: Accumulator I/O vs memory I/O," *ham radio*, June, 1976, page 64.
4. *Introductory Experiments in Digital Electronics, 8080A Microcomputer Programming, and 8080A Microcomputer Interfacing*, Bugbook V, E & L Instruments, Inc., Derby, Connecticut, 1976.

**ham radio**

# King of the Road
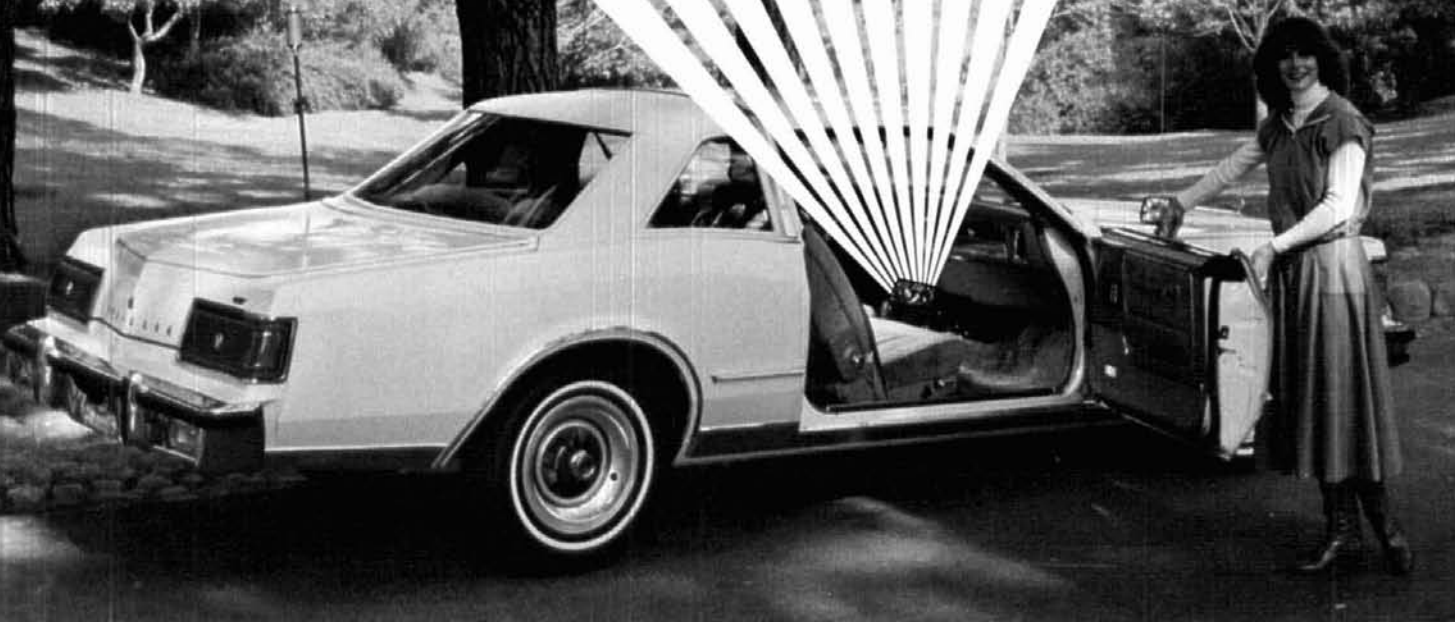
## ATLAS 210x/215x

5 BAND—200 WATT—ALL SOLID STATE  
HF SSB CW TRANSCEIVER



## The Perfect Mobile Rig

With its exclusive PLUG-IN-AND-GO MOBILE MOUNT, its light weight (7 pounds), and compact size (3½" high X 9½" wide X 9½" deep) the Atlas 210x/215x is the perfect mobile rig.

To go mobile just slip the 210x into its mobile mount and all connections are made automatically.

In just 10 seconds you're on the air mobile!



**ATLAS 210x or 215x \$679**  
with noise blanker \$719



417 Via Del Monte, Oceanside, CA 92054  
Phone (714) 433-1983  
Special Customer Service Direct Line  
(714) 433-9591

**MADE IN AMERICA**

# ATB-34

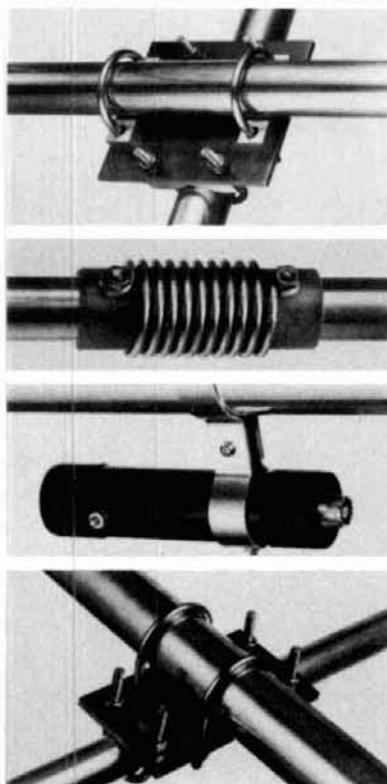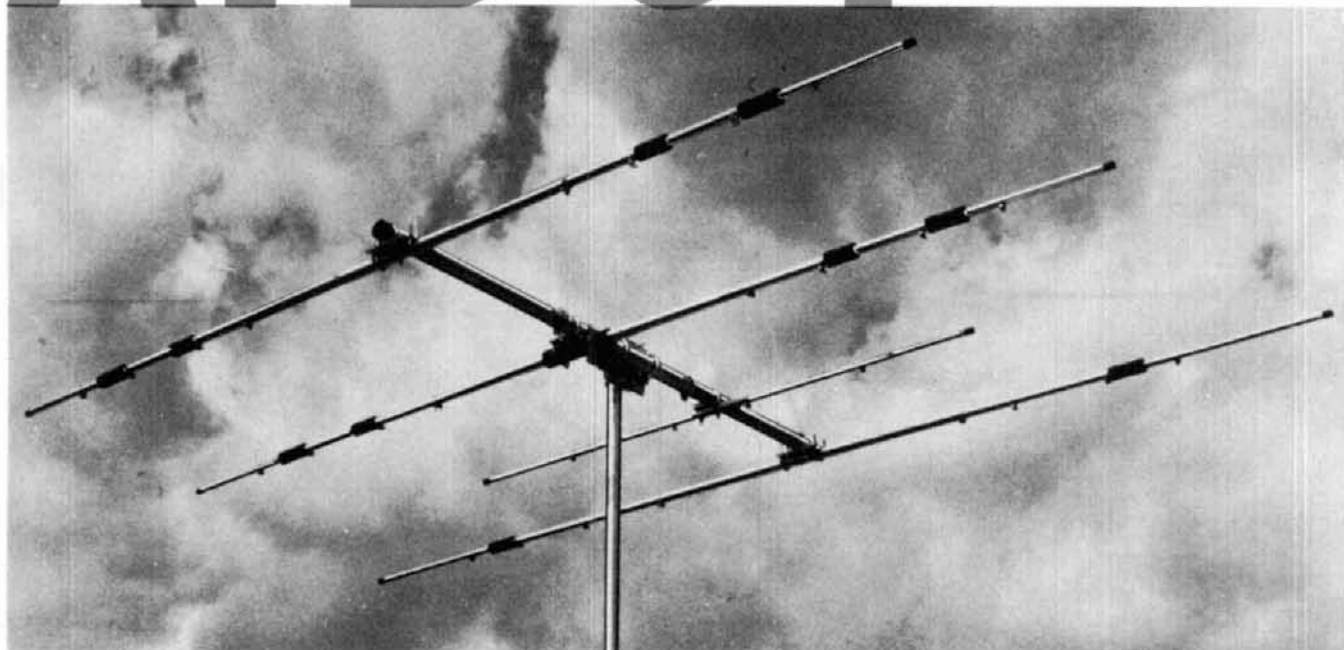

## 4 ELEMENT-3 BAND 10-15-20 METER BEAM

Cushcraft engineers have incorporated more than 30 years of design experience into the best 3 band HF beam available today. ATB-34 has superb performance with three active elements on each band, the convenience of easy assembly and modest dimensions. Value through heavy duty all aluminum construction and a price complete with 1-1 balun.

Enjoy a new world of DX communications with ATB-34!

### SPECIFICATIONS

FORWARD GAIN -	7.5 dBd	WIND SFC -	5.4 Sq.Ft.
F/B RATIO -	30 dB	WEIGHT -	42 Lbs.
VSWR -	1.5-1	WIND SURVIVAL -	90 MPH.
POWER HANDLING -	2000 WATTS PEP		
BOOM LENGTH/DIA. -	18' x 2 1/8"		
LONGEST ELEMENT -	32'8"		
TURNING RADIUS -	18'9"		

**UPS SHIPPABLE**  
**IN STOCK WITH DISTRIBUTORS WORLDWIDE**

**COMPLETE**  
**NO EXTRAS TO BUY**




# cushcraft

CORPORATION

BOX 4680, MANCHESTER, N.H. 03108

# VHF DX


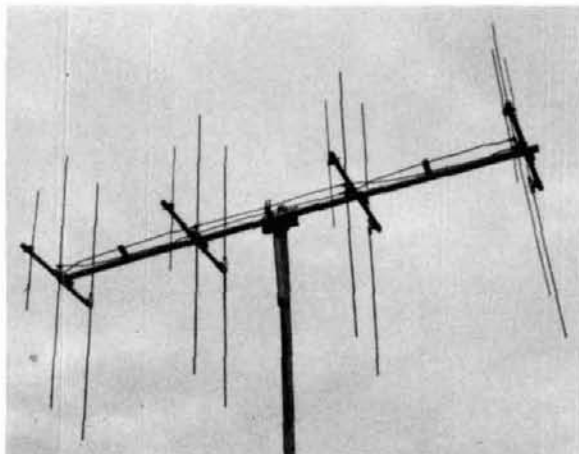


## FM —

Enjoy the thrill of dependable long distance contacts on simplex or thru remote repeaters. The 20 element col-linear DX-Array offers a precise pattern with large capture area. This vertically polarized, horizontally stacked array provides a narrow beamwidth for the discriminating FM user. Wide impedance and gain bandwidths make the DX-Array a natural choice for the serious FM'er. A vertical polarization bracket, model DX-VPB, is required (support boom and mast not supplied). Seek out new horizons with DX-Array!
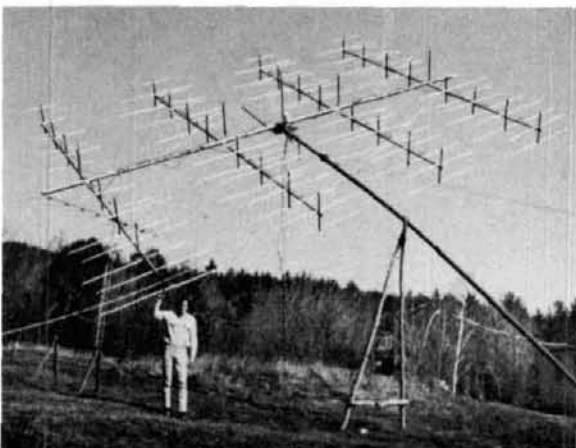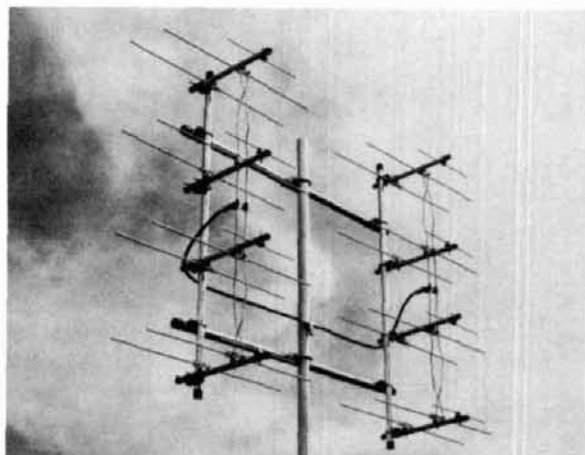
## SSB/CW —

Discover reliability in long-haul communications with VHF SSB and CW. The Cush Craft DX-Array also gives low angle, high gain performance for many exotic propagation modes — tropo, aurora, sporadic-E, and meteor scatter. Horizontally polarized DX-Arrays may be used singly or combined in pairs (twice Effective Radiated Power) or quads (4 x ERP). Each DXK stacking kit is complete with stacking frame and phasing harness (vertical mast not supplied). This year has seen some spectacular VHF band openings — Don't miss the next one!



Dave Olean, K1WHS, with his 160 Element DX-Array and Polar Mount EME System

## EME —

Many VHF experimenters have found excitement in conquering the formidable Earth-Moon-Earth (EME) path. 2-meter moonbouncers have achieved outstanding success using eight stacked DX-Arrays. Impedance and gain characteristics of this antenna permit stacking without the critical detuning problems inherent in large arrays of Yagis. Enlarging system size will yield a more uniform gain increase with DX-Arrays than with many other large antennas. The physical configuration alleviates mounting and phasing/tuning problems. EME enthusiasts are setting new records — So can you!

**DX-ARRAY LEADS THE WAY!**

Description:	144 MHz.		220 MHz.		432 MHz.	
	Model:	Price:	Model:	Price:	Model:	Price:
20 Element DX-Array	DX-120	\$42.95	DX-220	\$37.95	DX-420	\$32.95
Frame & Harness (40 E.)	DXK-140	\$59.95	DXK-240	\$54.95	DXK-440	\$39.95
Frame & Harness (80 El.)	DXK-180	\$109.95	DXK-280	\$89.95	DXK-480	\$79.95
1-1 52-ohm Balun	DX-1BN	\$12.95	DX-2BN	\$12.95	DX-4BN	\$12.95
Vert. Pol. Bracket (20 El.)	DX-VPB	\$9.95	DX-VPB	\$9.95	DX-VPB	\$9.95

IN STOCK WITH  
DISTRIBUTORS WORLDWIDE



**cushcraft**  
THE ANTENNA COMPANY  
P. O. BOX 4680, MANCHESTER, N. H. 03108

# let's reduce audio pollution in the vhf bands

How's your  
audio quality  
over the repeater?  
Here are  
some ideas  
for improvements

**Much has been written** about the control and power output of vhf fm equipment. But little has been written, that I can discover, about the input part — audio signal generation — particularly the how and why of obtaining audio quality throughout the entire chain of repeater operation.

As a one-time audiophile I have paid close attention, the past several months, to the audio quality of signals being retransmitted by amateur repeaters. It's been a pretty sad experience, but there's a glimmer of hope. I've also been hearing others commenting on the situation, and steps are being taken to remedy it.

Other than from equipment electrical malfunctions, bad audio is caused mostly by *close talking* into the dynamic microphone that usually comes with the radio. A couple of years ago I wrote an article on the subject of proximity effect for my club paper. The article was subsequently published in *ham radio*.<sup>1</sup> It pointed out that all conventional moving-coil microphones (including speakers used as microphones) accentuated the bass tones by a factor of 3 to 4 dB at 200 Hz (fig. 1). Such response can easily cause the first audio amplifier stage to overload and feed this signal into the transmitter.

I've heard many reasons why amateurs don't remain at least 5 cm (2 inches) from their microphones, none of which are valid. Many old wives' tales have sprung up regarding the use of microphones. The most ridiculous is that foreign equipment manufacturers have "set the audio stages of their radios for their countrymen." Sheer nonsense! It's usually not necessary to touch any internal controls in any radio, regardless of its origin, foreign or domestic. This statement is qualified by reminding you that, in most transceivers, audio is set using one audio frequency at a time from an audio oscillator, and that the radio and microphone are packaged in a carton as the equipment goes out the door.

## talking across the microphone

The next fallacious theory to be laid to rest is the "talk-across-the-microphone" nonsense. *All* micro-

**By Budd Meyer, K2PMA, 6505 Yellowstone Blvd., Forest Hills, New York 11375**



phones are designed for speaking directly into the active element (fig. 2). The sound waves should impinge onto the element perpendicularly; the microphone element should be in the same plane as your mouth. The microphone element is designed to react to, or transduce, all frequencies pretty much equally.

Unfortunately, microphone designers have a problem in that the higher audio frequencies are more directive. The further from a straight line access to the microphone element, the greater will be the loss of the higher audio frequencies reaching the microphone element. Fig. 3 gives an idea of what happens when an audio signal (your voice) impinges indirectly onto the microphone element. Audio frequencies above about 800 Hz travel almost directly toward the element, whereas lower audio frequencies have much less directivity and much more power per unit bandwidth.

So if you talk *across* the microphone, the bass voice frequencies can overload the audio chain in the radio; and the high frequencies, which are essential to intelligibility, are attenuated. I'd like to emphasize that the information above applies to *all* microphones whether crystal, dynamic, ceramic, or whatever. If you talk across the microphone, you're going to sacrifice the higher audio frequencies.

### over-deviation

Another situation that should be remedied is the idea that increasing the fm deviation will increase power output. More nonsense! The rf output of an fm transmitter is constant, and no amount of "dinking" with the deviation control will increase power



Test setup used by K2PMA to check VU meter readings with a calibrated audio power meter.

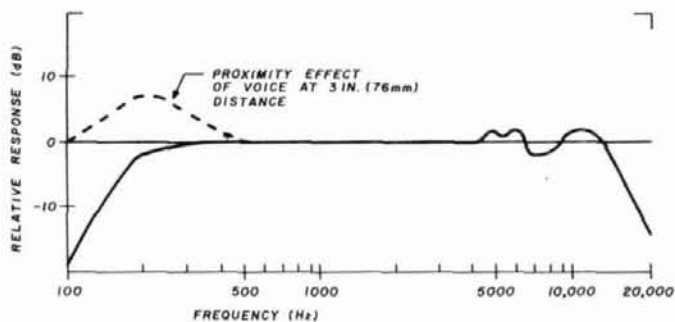


fig. 1. Generalized response curve of the dynamic microphone. Note the accentuated bass tones at 200 Hz (reference 1).

output. If you adjust the deviation control so that the radio is over-deviating, all you will do is increase distortion, since the transmitted signal bandwidth will be increased.

Most amateur repeaters have some form of deviation limiting control to prevent their signals from spreading out. If your radio's deviation setting is above this predetermined limit, you'll probably experience the phenomenon of "popping out the repeater." You won't gain anything but shrugs from other repeater users who know better. You may even get an admonishment to clean up your signal.

### some answers to the problem

How do you obtain good audio quality through the repeater? Much of the answer lies in the desire to do so. A standard answer you'll get, as I have, when you mention to someone who is over-deviating that perhaps he might try backing away from the microphone, is "You're the first to complain." Don't let this answer put you off. Most amateurs will back away from the microphone if asked to do so. Of course, if you tell him he sounds better at *that* distance from the microphone, and he realizes he's a half-meter (2 feet) away, he just *might* consider adjusting his microphone gain control!

### simple tests

Some time ago I came across a good buy in volume unit (VU) meters for my stereo system. I purchased an additional meter and connected it to the output of my vhf transceiver, which uses an 8-ohm speaker. I now had a reference of sorts — the fact that it was qualitative rather than quantitative served my purpose. At a comfortable listening level, the VU meter indicated average and peak audio output. To get quantitative values, I connected a calibrated audio-power meter to the output, which proved the validity of my VU-meter measurements.



Being aware that most amateurs don't have VU or audio-power meters, I connected a Simpson 260 Vom to the speaker output. Lo and behold — the VU-meter and Simpson 260 Vom readings matched! Such instrumentation can be used to advise the fel-

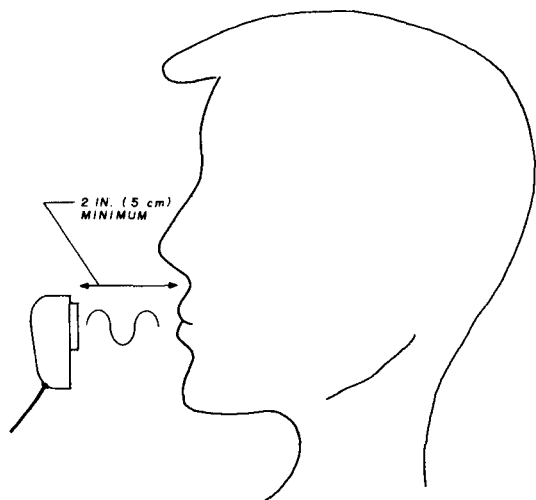


fig. 2. Most fm problems with poor audio can be remedied by speaking at least 5 cm (2 inches) from the microphone. Loud speech doesn't improve power output.

low on the other end that he's over-deviating, and you can prove it by comparison.

As a rough approximation, I suggest to the other fellow that he adjust his level to cause my VU meter, which has 300 ohms rather than the standard 600-ohm impedance, to average  $-7$  VU and peak at  $-4$  VU. (A correction factor of 15.75 dB must be added to the reading.) This comes out to about 7.5 mW average and 15 mW peak. These numbers are only guides; you can set your own standards based on your own equipment.

### measurement problems

Audio measurements are subjective, which means that all such measurements obtained by instrumentation are subject to individual taste and hearing characteristics. I've listened to rigs set up by deviation meters and oscilloscopes and note that this method just doesn't accomplish the job. There are resolution problems with oscilloscopes and frequency problems with deviation meters. Personal habits and voice characteristics color the tests. Obviously an oscilloscope presentation will show clipping; however, by the time the clipping is discernible the distortion will probably be very high.

How can we obtain good audio? Probably 90 per cent of the distortion heard on repeaters can be elimi-

nated if we all talked at least 5 cm (2 inches) away from the microphone. Also, accepting the fact that talking loudly does not equate to more output power will eliminate the other major culprit causing distortion, as noted previously.

I've no recommendation for setting up metered standards since an infinite number of variables must be considered. And no matter what one could come up with, we still must contend with the subjective aspect of audio measurements. I've heard many amateurs with unbearable distortion access a repeater and ask for an audio check, only to be told that they sound good. The smartest thing to do would be to listen to your favorite repeater for awhile and learn which people give accurate reports. If one fellow consistently *improves* the audio of others with honest reports, then he's your man.

### level setting

Here are some ideas for setting the level of your radio. As an example of the typical imported fm transceiver, I've provided a couple of sketches showing where to find the deviation and microphone gain control (fig. 4).

First, you must have someone listen to your signal over a period of time, preferably on a simplex frequency, so that the repeater doesn't affect your audio. Start by practicing the technique of talking at least 5 cm (2 inches) from the microphone. Once you get the hang of it, this procedure will become second

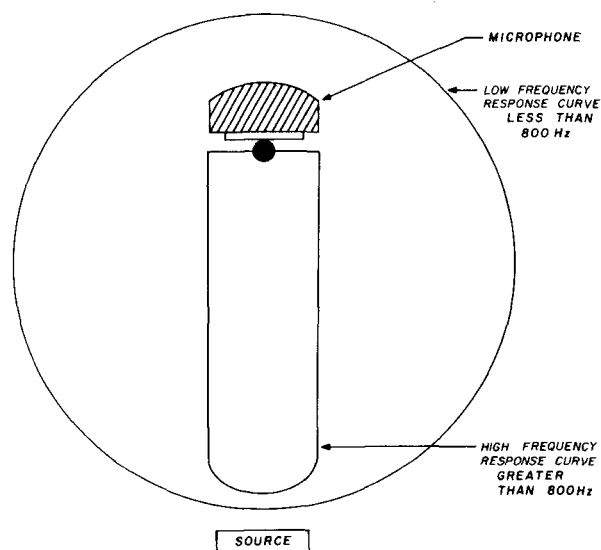


fig. 3. Response patterns of dynamic microphones. Higher audio frequencies, which convey intelligence, are more directional than the lower frequencies — a case supporting the theory for talking directly into the microphone rather than across it.

nature. Chances are you won't have to touch the radio's innards.

If you have to reduce the audio, locate the microphone gain control (not the deviation control), and turn it in small increments until your listener agrees

## the microphone

As a final attempt to clean up your signal, you can always buy a new microphone. Perhaps yours is out of spec, or you dropped it once too often. The thing to look for here is not so much impedance match

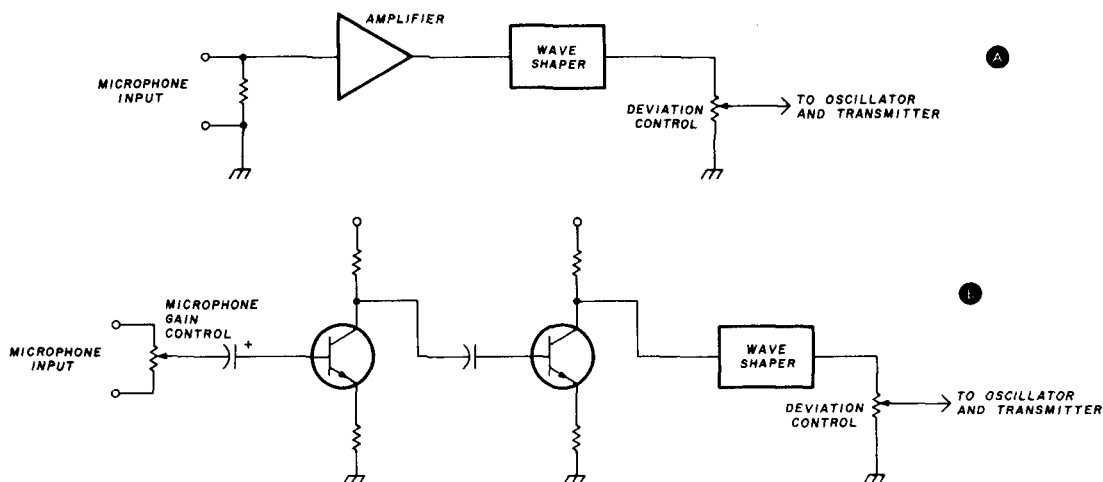


fig. 4. Generalized sketch of most fm vhf radios showing where to find the deviation control, A, and the microphone gain control, B.

that your audio is sufficient and clean — no rough edges. I don't believe that these tests can be done in committee fashion — stay with one man!

Only rarely is it necessary to touch the deviation control. What procedure do you use if there's only one control in your radio? Not much, really. The situation then becomes a tradeoff between microphone talking distance and level. Make every attempt to keep your audio clean. If your radio has only one control, not eating the microphone is bound to improve your signal quality. Some hand-held radios use the speaker as a microphone; not much can be done here.

If your radio has a deviation control but no microphone gain control, it's easy to adjust the deviation control so that your signal isn't two barn doors wide. As I've mentioned previously some repeaters are deviation limited, and if your fm signal swing is beyond the preset standard set by the repeater, the machine will pop out when you try to talk.

Locate the deviation control, which is generally near the end of the speech amplifier and audio chain. Ask your friend to listen to your signal while you adjust the deviation control for minimum swing with clean audio. Keep in mind that excessive deviation *does not* increase talk power or rf output. You can adjust the deviation control so that your signal will deliver all the talk power you can use without objectionable distortion.

(since most dynamic microphones will work with most transistorized amplifiers) but the microphone output level — somewhere in the vicinity of 10-50 mV across 2000 ohms. How do you ascertain this without meters? Buy it with return privileges.

## closing remarks

Let us not forget that your transmitter is only one-third of the communications chain. Repeater operators should also get into the loop. Someone in the group should listen to the average quality of the repeater audio. Sad to say, many repeaters have all kinds of added exotic features, but repeated audio is poor because no one has taken the time to check it.

We have autopatch, beeps, timers, tone-encoded outputs, frequency checks, automatic signal reports, welcoming speeches, and the like, but bad audio in many cases. I earnestly believe that control stations should absolutely and positively comment on bad audio coming into the repeater.

I hope this article will help improve a long-neglected aspect of amateur radio. I've found most hams to be cooperative in helping to rid the airwaves of audio pollution.

## reference

1. "Dynamic Microphones," *ham radio*, (Circuits & Techniques), June, 1976, page 49.

ham radio

**DSI****Be the one who's on FREQUENCY!!**

With your *DSI Counter*. . . save the shop cost of tweaking xtals. . . know your frequency. . . from 160 meters through 450 MHz. Now *DSI* offers *the most* counter for your dollar. Latest state-of-the-art technology. . . *DSI* advanced LSI design far exceeds outdated TTL. Go with the leader . . . buy a *DSI FREQUENCY* counter and **SAVE TIME & MONEY!!**

**NOT A KIT****MODEL 3500 \$139.95****500 MHz Frequency Counter**

- Includes 500 MHz Prescaler — Not an add-on
- 7 Large bright — 1/2 inch LED Readouts
- Temperature compensated crystal timebase
- Accuracy 1 PPM Typ
- Sensitivity 50 MvRms 150 & 250 MHz 150 MvRms 450 MHz
- Gate time light
- No direct RF connection Required
- AC or DC operation
- 50 Hz to 500 MHz typ
- Comprehensive owners manual with complete accurate schematics
- Factory assembled & tested

**MODEL 3600A \$189.95**

Includes oven timebase

**600 MHz Frequency Counter**

- Includes oven compensated crystal timebase
- Includes built-in 600MHz Prescaler-Not an add-on
- 8 Large bright — 1/2 inch LED Readouts
- Two timebases 0.1 sec & 1. sec
- Resolution 1 Hz Direct 10 Hz Prescaled
- Sensitivity 20 MvRms @ 150 & 220 MHz 100 MvRms 450 MHz
- Accuracy .5 PPM over temperature
- Oven light & Gate time light
- Automatic Decimal point placement
- NO DIRECT RF CONNECTION Required.
- Comprehensive owners manual with complete accurate schematics
- AC or DC operation
- 50 Hz to 600 MHz Typ.
- Factory assembled & tested

Use it in the car or on the bench. . . take it to the repeater site. . . high-impact case. . . light weight—but rugged. . . Designed with the latest readily available LSI, CMOS, Schottky, Mecl-integrated circuits.

**NEW PRODUCTS**

- 250 MHz 7 Digit Battery operated hand held counter \$109.95
- 3 1/2 Digit Bench Digital Multi-meter AC or Battery operated \$99.95

Visit us at the DAYTON HAMVENTION — APRIL 28, 29, 30

Strongest Warranty in the Counter Field. ONE Year Parts and Labor we pay the return shipping plus . . . satisfaction guaranteed . . . Dennis Romack . . . WA6OYI.  
VP-MARKETING, DSI

**TO ORDER CALL COLLECT (714) 565-8402**

Name \_\_\_\_\_ Call \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Phone: \_\_\_\_\_

Order: \_\_\_\_\_

 Check enclosed  Please send more information on your full line of Instruments and Accessories.  
 BankAmericard  MasterCard  VISA  R.E.

Credit card # \_\_\_\_\_ Card expiration date \_\_\_\_\_ Signature \_\_\_\_\_

**DSI INSTRUMENTS INC.**  
 Div. Diversified Security Ind, Inc.

We pay shipping charges anywhere in the U.S.A. UPS Brown or P.P. — CA Residents please add 6% state sales tax.

- American Express
- Bank of America
- MasterCard
- VISA

**7914 Ronson Road No. G, San Diego, CA 92111**

# DSI

DSI INSTRUMENTS INC.


## 250MHZ FREQUENCY COUNTER BATTERY OPERATED HAND-HELD

**ALL NEW! Unparalleled** DSI quality hand-held counter at a price that is affordable for any budget. Remember the 3240 is factory assembled and ready to use. GO with the leader and order your counter today.

**MODEL 3240HH**

**\$109.95**

**Made in USA  
Not A Kit**

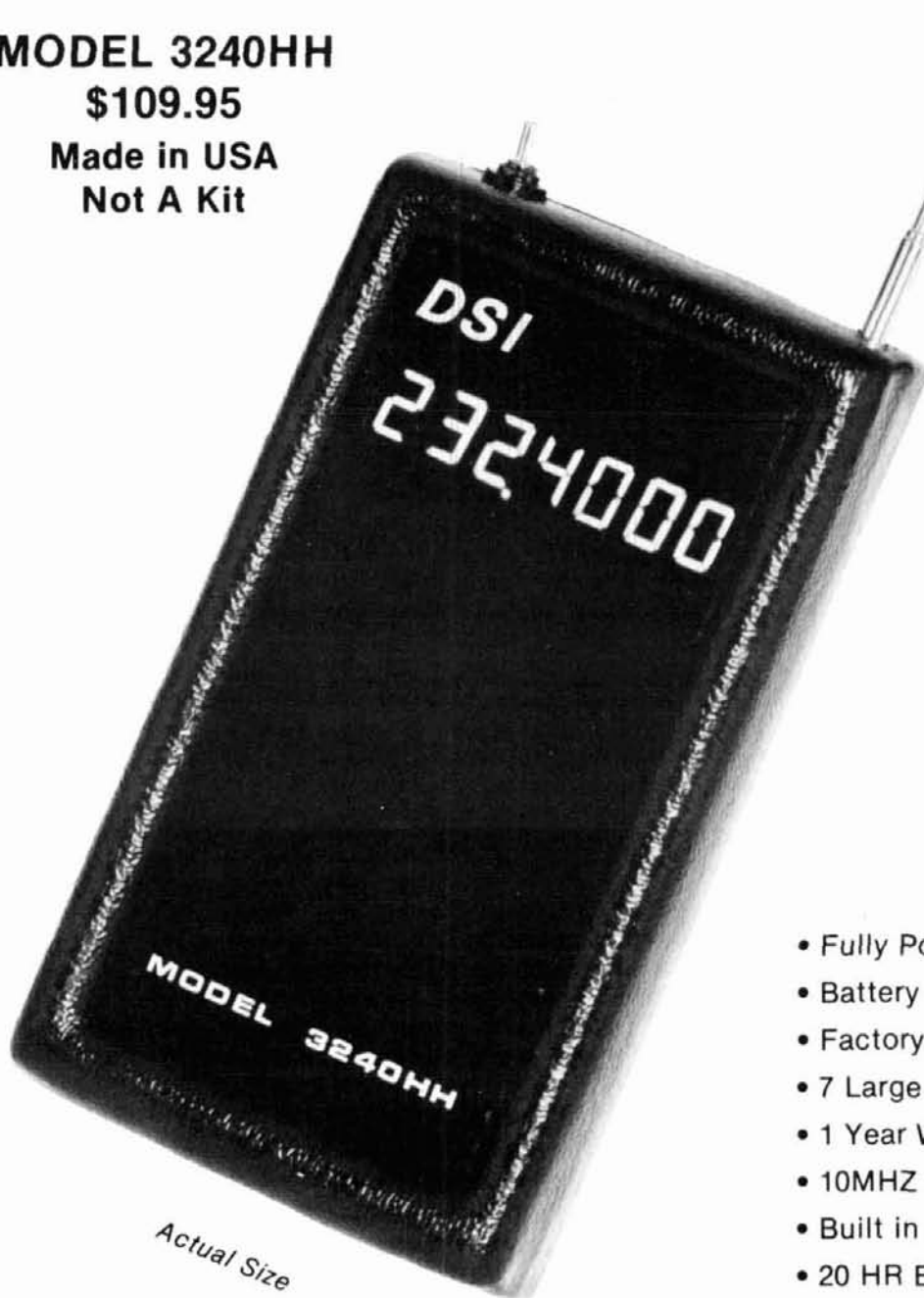

*Actual Size*

- Fully Portable.
- Battery Operated.
- Factory Assembled.
- 7 Large .4" LED Readouts.
- 1 Year Warranty.
- 10MHZ to 250MHZ.
- Built in Ant.
- 20 HR Batt. Life.
- Uses H AA Batteries.

7914 Ronson Road No. G, San Diego, CA 92111

# You have your own calculator. Why not a DMM?



Finally, a digital multimeter that's yours, just like your pocket calculator, and more useful. Only \$169.\*

You pack only 13 ozs. in your pocket or service kit, but size is deceptive. The 8020A has more useful features than any other multimeter available—at any price! Features like 26 ranges and seven functions, including *conductance*. 2000-count resolution. Hi/lo power ohms.

And it's rugged. The high-impact case protects a minimum number of component parts (47 in all), and they're all readily available from any of the worldwide Fluke service centers. Your 8020A is factory calibrated by NBS traceable equipment. And we guaran-

tee it'll live up to published specs for a full year.

The 8020A is a true field instrument, designed with a highly readable LCD display, and inexpensive 9V transistor battery power for continuous use up to 200 hours. Reliability, quality and value: *that's* Fluke tradition.

To get your hands on one, call (800) 426-0361, toll free. Give us your charge-card number and we'll ship an 8020A the same day. Or, we'll tell you the location of the closest Fluke office or distributor (where you can save by buying a ten-pack of 8020As for only \$1521\*).

\*U.S. price only.

## The DMM for Home Electronics Experts.

**FLUKE**®

2507-7104

# BIG back issue DEAL

It's simple. Order a set of **ALL AVAILABLE** Ham Radio back issues for the bargain price of just \$65.00.

Ham Radio guarantees you a **minimum** of 50 issues. Right now we have many more for you than that — from 1968 to 1978 — but obviously with this unbelievable deal they won't last long!

Single issues of **HAM RADIO** are still available for \$2.00 each or 3 for \$4.95. For a full listing of all back issues send for our free brochure.

Complete your collection, replace lost issues, discover new ones — or — get everything with Ham Radio's back issue **BIG DEAL**. Order Now.

The BIG DEAL — send me all available back issues right away. Enclosed is \$65.00.

I want \_\_\_\_\_ back issue(s).  
\$2.00 each or 3 for \$4.95.  
(specify month and year)

\_\_\_\_\_ 19 \_\_\_\_\_  
\_\_\_\_\_ 19 \_\_\_\_\_  
\_\_\_\_\_ 19 \_\_\_\_\_  
\_\_\_\_\_ 19 \_\_\_\_\_  
\_\_\_\_\_ 19 \_\_\_\_\_

Send a free Back Issue brochure.

Check or money order enclosed.  
Charge my  Master Charge  
 BankAmericard/VISA

Acct # \_\_\_\_\_

Ex. Date \_\_\_\_\_ Bank # \_\_\_\_\_ (MC only)

Name \_\_\_\_\_ Call \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Mail to:  
**HAM RADIO Magazine**  
Greenville, NH 03048



# SAVE UP TO 50% ON PARTS.

Hobbyist or professional, there are probably a lot of circuits you build just for the fun of it. And a lot you'd *like* to build, but never get around to.

One reason is the cost of parts. Parts you buy for one project, but can't re-use... because you haven't time to take them carefully apart. Or because of heat and mechanical damage that occur when you do.

Now, there's an easier way that can save you big money on parts *and hours on every project*, as well: *Proto-Board® Solderless Breadboards*.

Now, assembling, testing and modifying circuits is as easy as pushing in—or pulling out—a lead. IC's, LED's, transistors, resistors, capacitors... virtually every kind of component... connect and interconnect instantly via long-life, nickel-silver contacts. No special patch cords or jumpers needed—just

lengths of ordinary #22-30 AWG solid hookup wire.

Circuits go together as quickly as you can think them up. And parts are re-usable, so as your "junk box" builds, you build more and more projects for less and less money.

Before you invest in your next project, invest in a CSC breadboard.

Order today. Call 203-624-3103 (East Coast) or 415-421-8872 (West Coast): 9 a.m.-5 p.m. local time. Major credit cards accepted. Or see your CSC dealer. Prices slightly higher outside USA.

MODEL	NO. OF TIE-POINTS	14-PIN DIP CAPACITY	SUGG. LIST *	OTHER FEATURES
PB-6	630	6	\$15.95	Kit—10-minute assembly
PB-100	760	10	19.95	Kit—with larger capacity
PB-101	940	10	29.95	8 distribution buses, higher capacity
PB-102	1240	12	39.95	Large capacity, moderate price
PB-103	2250	24	59.95	Even larger capacity, only 2.7¢ per tie-point
PB-104	3060	32	79.95	Largest capacity, lowest price per tie-point
PB-203	2250	24	80.00	Built-in 1% regulated 5V, 1A low-ripple power supply
PB-203A	2250	24	129.95	As above plus separate 1/2-amp +15V and -15V internally adjustable regulated outputs

\*Manufacturer's suggested list  
Prices and specifications subject to change without notice.

CONTINENTAL SPECIALTIES CORPORATION



70 Fulton Terrace, Box 1942, New Haven, CT 06509  
203-624-3103 TWX 710-465-1227  
WEST COAST: 351 California St., San Francisco, CA 94104,  
415-421-8872 TWX 910-372-7992  
GREAT BRITAIN: CSC UK LTD.  
Spur Road, North Feltham Trading Estate,  
Feltham, Middlesex, England.  
01-890-8782 Int'l Telex: 851-881-3669

© 1978, Continental Specialties Corporation





## NEW! ALDA 103 HF TRANSCEIVER



Please write for Special Package Prices

- Superb Commercial Grade Quality and Construction Second to none!
- Superior Audio Quality!
- Totally Solid State
- 250 Watts
- Modular Plug-in Circuit Board Assembly
- Dual Speed VFO Dial-Vernier
- Semi-Break In CW with Sidetone

## NEW! SIGMA MODEL AF250L DEVIATION/MODULATION METER

Introductory Price

**\$169**



**FEATURES:** Extremely stable local oscillator for easy measurement of HF, VHF, and UHF bands employing negative feedback, to insure extremely high stability ● Easy to read, accurate linear scale ● Direct off the air signal measurement capability. **OPTIONAL 12v DC Power Kit - \$12. FULLY CERTIFIABLE FOR COMMERCIAL USE.**

**SPECIFICATIONS:** Frequency: 1.8MHz-520MHz/3 range select (A,B,C,EXT), A range: 26.5 MHz-40MHz, B range: 48MHz-60MHz, C range: 140MHz-156MHz (generous overranges), EXT. range: 1.8 MHz-520MHz (Need Signal Generator) ● Input level: (1) Through type input level: 1W-200W (RF Input Terminal), (2) Direct input level: More than 80db/50ohm impedance ● Amplitude modulation: 0-100% ● Frequency deviation: 0-20KHz ● Accuracy: +/- 3% of full scale ● Intermediate frequency: 10.7MHz ● RF Attenuator: 0-60db variable ● Audio Signal oscillator: (1) Audio Frequency—1,000Hz (1 KHz), (2) Output level—More than 1V RMS (variable) ● Power Source: AC117 ● Dimensions: H-5½" (140mm), W-10¼" (260mm), D-7¼" (184mm) ● Wt.: 7 lbs.

## SIGMA XR3000D LINEAR AMPLIFIER

INTRODUCTORY PRICE

**\$789**

2 Day Air Shipment Anywhere in U.S.  
Airport to Airport \$35  
Alaska and Hawaii Slightly Higher



### SPECIFICATIONS:

- Full band coverage 160-10 meters including MARS.
- 2000 watts P.E.P. SSB input. 1000 watts input continuous duty, CW, RTTY & SSTV.
- Two Eimac 3-500Z conservatively rated finals.
- All major HV and other circuit components mounted on single G-10 glass plug in board. Have a service problem? (Very unlikely) Just unplug board and send to us.
- Heavy duty commercial grade quality and construction second to no other unit at any price!
- Weight: 90 lbs. Size: 9½" (h) x 16" (w) x 15¼" (d)

## NEW! SIGMA MODEL AF250L DEVIATION/MODULATION METER

Introductory Price

**\$169**



**FEATURES:** Extremely stable local oscillator for easy measurement of HF, VHF, and UHF bands employing negative feedback, to insure extremely high stability ● Easy to read, accurate linear scale ● Direct off the air signal measurement capability. **OPTIONAL 12v DC Power Kit - \$12. FULLY CERTIFIABLE FOR COMMERCIAL USE.**

**SPECIFICATIONS:** Frequency: 1.8MHz-520MHz/3 range select (A,B,C,EXT), A range: 26.5 MHz-40MHz, B range: 48MHz-60MHz, C range: 140MHz-156MHz (generous overranges), EXT. range: 1.8 MHz-520MHz (Need Signal Generator) ● Input level: (1) Through type input level: 1W-200W (RF Input Terminal), (2) Direct input level: More than 80db/50ohm impedance ● Amplitude modulation: 0-100% ● Frequency deviation: 0-20KHz ● Accuracy: +/- 3% of full scale ● Intermediate frequency: 10.7MHz ● RF Attenuator: 0-60db variable ● Audio Signal oscillator: (1) Audio Frequency—1,000Hz (1 KHz), (2) Output level—More than 1V RMS (variable) ● Power Source: AC117 ● Dimensions: H-5½" (140mm), W-10¼" (260mm), D-7¼" (184mm) ● Wt.: 7 lbs.


## SUPERB NEW WANZER Z-4 TRANSMATCH

- Roller Inductor
- Switchable Double-L or Pi
- In/Out Switch
- Commercial Grade Construction
- 160-10 Meters
- 3KW

Introductory  
Price  
**\$129**



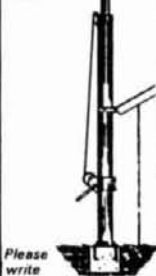NEW!  
TRISTAO'S  
40 foot Self-  
Supporting  
Crank-up  
Mast



Please  
write  
for Special  
Package Price

**DSI**

Fully Certifiable  
for commercial  
use



COMPARE!

**\$189**

factory assembled  
not a kit

## 600 MHZ FREQUENCY COUNTER WITH CRYSTAL OVEN TIMEBASE

- Sensitive—No Direct RF Connection Required
- Accurate—5PPM ● Selectable Resolution



## SIGMA RF-2000 SWR & POWER METER




Cal PWR Scales 200W-2000W Freq Range 3.5-150 MHz. Please do not confuse the RF2000 with similar appearing lower priced units. RF2000 is an individually calibrated professional quality instrument. Unequaled at many times the price. Size 7" (w) x 2 1/3" (d).

**\$29**

Introductory Price

SHIPPING ANYWHERE U.S. - \$1
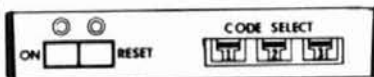
## GO PRIVATE! on 2 meters with the FMTD-1\*



SPECIAL INTRODUCTORY PRICE \$75.00

Touch tone pad (encoder) actuated. Quiets your receiver until other station sends private 3 digit code, selected from front panel. 999 Channels. Receiver can be muted or opened manually or remotely with a touch tone pad. Bright led's indicate muting and reset. State of the art digital circuitry. Works with the KDK FM2015R or any 2-meter rig. 5 pin pin plug supplied. Size 5½" D x 6½" W x 1½" H. Wt. 12 oz.

FM2015R Accessories		KDK SPECIAL SALE FM144 Accessories	
FMSS SUPER SCANNER 1000 Total Scanning Capability .....	\$99	FMOF-1 Offset Option Kit - 2 Extra Positions, Crystals Required ..	\$5
FMPS-4R Regulated AC/PS .....	\$39.95	FMOF-2 1 MHz Offset Option Kit (No Crystals to Buy) .....	\$5
FMCC-1* Microphone with Built-in Touch Tone Pad .....	\$49.95	MARS-CAP Option Kit - Any Frequency Any Split .....	\$12
FMTD-1* Private Call Decoder for use with and Programmed by any Touch Tone Pad .....	\$75		
MARS-CAP and Multiple Offset Kit* - Any Frequency, Any Split, No Crystals .....	\$5		
FMAT-1 ½ Wave Portable Antenna for Hotel, Motel or Apartment .....	\$7.95		
Extra DC Cord & Plug .....	\$4.00		
Service Manual .....	\$4.00		
Mounting Bracket (Extra) .....	\$6.00		

NEW!! ADD 5 CHANS (TOTAL 10) TO SRC-146A

- Simple 10 min. installation
- Same color and quality as SRC-146A
- Completely WIRED & TESTED
- ALSO usable with most other hand fields

Price \$29

## New Standard 2 Meter FM Transceivers Model SRC 146A



Special  
Package

\$314  
NC  
\$47  
\$12  
\$10  
\$30  
Reg \$413

NEW!!! Touch Tone pad completely wired and ready to plug in - \$59.95

Our Price **\$289**  
COMPARE!

## FLUKE Model 8020A Professional DMM

**\$169**

Please write for details



NEW CDE HAM III ROTATORS—  
Reg. \$159.95—\$125

# AMATEUR-WHOLESALE ELECTRONICS

8817 S.W. 129th Terrace, Miami, Florida 33176

COURTEOUS PERSONAL SERVICE—SAME DAY SHIPMENT - Prices subject to change without notice.  
Telephone: (305) 233-3631 • Telex 51-5628 • Store Hours: 10-5 Mon.-Fri.



## SUPERB NEW ICOM IC-701 HF TRANSCEIVER

Please write for detailed information



# NEW! THE FUTURE NOW! FM2015R



Does Your Unit Cover The New  
Sub-band 144.5 - 145.5 MHz?  
The FM2015R Does, PLUS MARS-CAP!\*

All Solid State-CMOS PL digital synthesized - No Crystals to Buy! 5KHz steps - 144-149 MHz-LED digital readout PLUS MARS-CAP and MULTIPLE OFFSET.\*

● 5 MHz Band Coverage - 1000 Channels (instead of the usual 2MHz to 4MHz-400 to 800 Channels) ● 4 CHANNEL RAM IC MEMORY WITH SCANNING ● MULTIPLE FREQUENCY OFFSETS ● ELECTRONIC AUTO TUNING - TRANSMIT AND RECEIVE ● INTERNAL MULTIPURPOSE TONE OSCILLATOR ● RIT ● DISCRIMINATOR METER - 15 Watts Output - Unequaled Receiver Sensitivity and Selectivity - 15 POLE FILTER, MONOLITHIC CRYSTAL FILTER AND AUTOMATIC TUNED RECEIVER FRONT END, COMPARE! ● Superb Engineering and Superior Commercial Avionics Grade Quality and Construction Second to None at ANY PRICE.

INTRODUCTORY  
PRICE

**\$419<sup>00</sup>**

Regulated AC/PS  
Model FMPS-4R . . . \$39.95



FMMS-1\* Micro-  
phone with Built-in  
Touch Tone Pad.

WHY BUY LESS?  
THE FMMS-1  
HAS IT ALL!

- New! Auto key up
- Snap-Action Keyboard
- Adj. level and tone balance
- Use with any transceiver
- Only 3 1/4" x 2"

\$49<sup>95</sup>

- **FREQUENCY RANGE:** Receive and Transmit: 144.00 to 148.995 MHz, 5KHz steps (1000 channels) INCLUDING NEW BAND 144.5-145.5MHz + MARS-CAP and MULTIPLE OFFSET.\*
- **LED DIGITAL READOUT.**
- **4 CHANNEL RAM SCANNER WITH IC MEMORY:** Program any 4 frequencies and reprogram at any time using the front panel controls—search for occupied (closed) channel or vacant (open) channels. Internal Ni-Cad included to retain memory (no diode matrix to wire or change).
- **MULTIPLE FREQUENCY OFFSETS:** Three positions A,B,C, provided for installation of optional crystals: EXAMPLE - 1 MHz offset. Duplex Frequency Offset Built in - 600 KHz PLUS or MINUS 5 KHz steps, plus simplex, any frequency.
- **INTERNAL MULTIPURPOSE TONE OSCILLATOR BUILT IN:** 1750Hz tone burst for "whistle on operation" and sub-audible tone operation possible by simply adding a capacitor across the terminals provided. Internal 2 position switch for automatic and manual operation, tone burst or sub audible tone PL - adjustable 60-203Hz (100 Hz provided).
- **AIRCRAFT TYPE FREQUENCY SELECTOR:** Large and small coaxially mounted knobs select 100KHz and 10KHz steps respectively. Switches click-stopped with a home position facilitate frequency changing without need to view LED's while driving and provides the sightless amateur with full Braille dial as standard equipment.
- **FULL AUTOMATIC TUNING OF RECEIVER FRONT END AND TRANSMITTER CIRCUITS:** DC output of PLL fed to varactor diodes in all front end RF tuned circuits provides full sensitivity and optimum intermodulation rejection over the entire band. APC(AUTO POWER CONTROL) - Keeps RF output constant from band edge to band edge. NO OTHER AMATEUR UNIT AT ANY PRICE has these

- features which are found in only the most sophisticated and expensive aircraft and commercial transceivers.
- **TRUE FM:** Not phase modulation - for superb emphasized hi-fi audio quality second to none.
- **RIT CONTROL:** Used to improve clarity when contacting stations with off frequency carrier.
- **MONITOR LAMPS:** 2 LED's on front panel indicate (1) incoming signal-channel busy, and (2) Transmit.
- **FULLY REGULATED INTEGRAL POWER SUPPLY:** Operating voltage for all 9v circuits independently regulated. Massive Commercial Hash Filter.
- **MODULAR COMMERCIAL GRADE CONSTRUCTION:** 6 Unized modules eliminate stray coupling and facilitate ease of maintenance.
- **ACCESSORY SOCKET:** Fully wired for touch tone, phone patch, and other accessories. Internal switch connects receiver output to internal speaker when connector is not in use.
- **MULTI-PURPOSE METER:** Triple Function Meter Provides Discriminator Meter, "S" Reading on receive and Power Out on Transmit.
- **RECEIVE:** Better than .25uv sensitivity, 15 POLE FILTER as well as monolithic crystal filter and AUTOMATIC TUNED LC circuits provide superior skirt selectivity - COMPARE!
- **HIGH/LOW POWER OUTPUT:** 15 watts and 1 watt, switch selected. Low power may be adjusted anywhere between 1 and 15 watts. Fully protected-short or open SWR.
- **OTHER FEATURES:** Dynamic Microphone built in speaker, mobile mount, external 5 pin accessory jack, speaker jack, and much, much more. Size 2 1/2 x 7 x 7 1/2. All cords, plugs, fuses, microphone hanger, etc. included. Weight 5 lbs.

Manufactured by one of the world's most distinguished Avionics manufacturers, Kyokuto Denshi Kaisha, Ltd.  
First in the world with an all solid state 2 meter FM transceiver.



## AMATEUR-WHOLESALE ELECTRONICS

8817 S.W. 129th Terrace, Miami, Florida 33176  
Telephone (305) 233-3631 • Telex: 51-5628  
U.S. DISTRIBUTOR

DEALER INQUIRIES INVITED.

PLEASE ORDER FROM YOUR LOCAL  
DEALER OR DIRECT IF UNAVAILABLE.

### Regional Sales & Service Centers

**East:** Sanford Communications, Inc.  
Colonia, N.J.  
(201) 574-3003  
**Northwest:** Buzzards Bay Electronics  
Buzzards Bay, Mass.  
(617) 759-3376  
**West:** The Radio Shop  
Riverton, Utah  
(801) 254-0991  
**Northwest:** Action Supply, Inc.  
Boise, Idaho  
(208) 344-5084  
**Midwest:** Universal Service  
Columbus, Ohio  
(614) 221-2335  
**South:** Electronic Communications  
Highland Springs, Virginia  
(804) 737-5100



For literature on any of the new products, use our *Check-Off* service on page 126.

### DenTron Jr. monitor antenna tuner



DenTron's newest tuner, called the *Jr. Monitor*, has power-handling capability of 300 watts, and can handle balanced, coaxial and random-wire-fed antennas. It also includes a relative-power-output meter and a mobile-mounting bracket. The *Jr. Monitor* measures a mere 5½-inches wide, by 2¾-inches high, by 6-inches deep (14x7x15cm). This size makes it ideal for portable, mobile, or fixed operation. Designed to handle virtually any transceiver or receiver-transmitter combination, the *Jr. Monitor* is priced at \$79.50 and is available at DenTron dealers throughout the United States and the world. For more information, write DenTron Radio Company, 2100 Enterprise Parkway, Twinsburg, Ohio 44087.

### OSCAR amateur radio satellites

For most amateurs, obtaining information about any of the Oscar satellites has been somewhat of a piecemeal process. Almost every area of interest was covered in a

separate publication or source, and some information just did not seem to be available at all.

Author and engineer Stratis Caramanolis has written a very useful book, *OSCAR Amateur Radio Satellites*, that ties it all together in one place. The original was published in German, and now an English-language version is being distributed by the Radio Society of Great Britain, and by Ham Radio's Communications Bookstore.

Almost any question that you may have about amateur radio satellites can be answered by consulting *OSCAR Amateur Radio Satellites*. It shows a high degree of competence in presenting the technical and theoretical facts of satellite operation, but at the same time these facts are covered in language that the non-engineer can understand and work with. The author uses just enough mathematics to prove whatever theory or point is being discussed, but not so much as to scare away any neophyte to amateur radio or satellite communications.

The book starts out with a discussion of the solar system from the first misconceptions that placed the earth at the center of the universe, and brings you right through the changes in scientific thinking into the current period of knowledge, which was started by Johannes Kepler. The first three laws formulated by Kepler are essential in understanding the mechanics of orbiting bodies, no matter what size they are. The book uses this Keplerian foundation to build a subsequent discussion of satellite orbital mechanics starting with a simple explanation of the trajectory of a projectile and then developing this into a trajectory that has no terminus, thus being an orbit.

Once the essential mechanics of orbits and satellite theory are taken care of, the author gets into a good explanation of satellite types, systems, control, power requirements, and structures. This is followed by a chapter on the fundamentals of telecommunications by means of satel-

lites, which includes such areas as free-space loss (of signal strength) and receiver sensitivity — both important considerations if you plan to use a satellite system.

All of this groundwork material takes up a good portion of the book, but it is interesting and essential reading if you are to really understand what makes any satellite behave the way it does. Chapter seven is the first one that is devoted entirely to amateur radio satellites, and it starts with the background of amateur work in planning, building, and launching the first OSCAR. It continues with a history of each amateur satellite right through to the current OSCARs 6 and 7.


This chapter is followed by one that, logically, devotes many pages to detailed descriptions of all the systems that go to make up an OSCAR satellite package — transponders, telemetry, antennas, receivers, modes, decoding, and much more. It explains how you can calculate orbital information, how you can interpret the telemetry data that indicates the condition of the spacecraft systems, and what you need at your home (ground) station to work with satellites.

The last chapter is devoted to the subject of learning with satellites. It is a section designed to acquaint educators with the possibilities of classroom use of amateur satellite signals and experiments. The author points out some of the uses that have been made of this material, and provides names and addresses where those interested can obtain more information. Some samples of techniques useful in classrooms are given, such as measurement and explanation of Doppler effects, orbital data, and transmission of amateur television and weather satellite pictures through the OSCAR spacecraft. Future satellites are discussed, but because of the many variables in timing of launch vehicles, satellite construction, and the like, this coverage can be only tentative at best.



All-in-all, the book is recommended as an excellent reference for the amateur (or anyone else) who is curious about any phase of satellites, or who is seriously contemplating the use of OSCAR for communication or educational purposes. *OSCAR Amateur Radio Satellites*, by Stratis Caramanolis, is 194 pages, paperback, and is \$8.50 postpaid from Ham Radio's Communications Bookstore, Greenville, New Hampshire 03048; order RS-O.

## active filter design

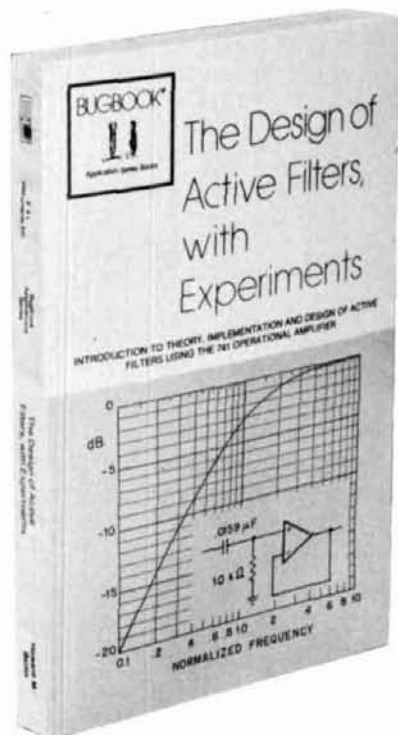

*The Design of Active Filters and Experiments* by Howard M. Berlin, published by E&L Instruments, is an introduction to theory, implementation, and design of active filters. The text includes descriptions and schematic diagrams of designs for the various lowpass, highpass, bandpass, and notch filters based on the 741 operational amplifier IC. Recommended for the experimenter and hobbyist who want to learn the basics of active filters, the book is complete enough to serve as a college-level laboratory manual. It is also an excellent reference for the practicing circuit designer.

# Antenna Baluns



1 Kw CW, 3 Kw PEP input. For dipoles, inverted Vees, beams, quads.

Dependable. Takes temporary overloads in stride.

Specify 1:1 or 4:1 ratio.

**Model 1K \$16.95**



2 Kw CW, 6 Kw PEP input. Far more rugged than any other balun made for amateur use.

Specify 1:1 or 4:1 ratio.

**Model 2K \$32.50**



2 Kw CW, 6 Kw PEP input. Our heavy duty balun with mounting bracket for 2" mast or boom.

Specify 1:1 or 4:1 ratio.

**Beam Balun \$37.50**

### Only Palomar Baluns Have All These Features

- RF toroidal core for highest efficiency.
- Teflon insulated wire.
- Stainless steel hardware. Won't rust.
- Epoxy filled case. Waterproof.
- Wideband 1.7 to 30 MHz.
- White case to reflect the sun.
- Lightning protection built in.

Free brochure sent on request

How many lightweight baluns have you burned out already? Install the balun that will stay up there working year after year.

**Order direct. Add \$2 shipping/handling. California residents add sales tax.**

# Palomar Engineers

Box 455, Escondido, CA. 92025 • Phone: [714] 747-3343

AMECO • ARRL BOOKS • ASTATIC • B & W • BEARCAT  
 • CALLBOOK • CDE HAM III • CUSHCRAFT • DENTRON  
 • HALLICRAFTERS • HY-GAIN • KLM • LARSEN  
 • MALLORY • J. W. MILLER • MOSLEY • SAY POWER  
 SUPPLIES • SHURE • W2AU BALUN • MORE TO COME!

Orlando's Most Complete Stock of Electronic Hardware

Transistors • Diodes • Integrated Circuits • Variable Capacitors • Connectors • Audio Cables  
 • Variable Resistors • Antenna Wire • RG-8/U Coax (foam) • Rotor Cable • Steel Mast  
 • Ceramic Insulators • and much more

## LAFAYETTE RADIO ELECTRONICS

1811 N. HWY 17-92, MAITLAND, FL. 32751

(Near Orlando)

305-831-2271

ASSOC.  
STORE



# NEWS Update

from **DRAKE**

## UV-3 PRICE REDUCTION

In this day of rising prices on almost everything, it is not only refreshing but even remarkable to be able to announce a significant price reduction on the Drake UV-3 System.

How can this be? Well, considering that no one has ever produced a 144-220-440 MHz multi-band fm system before, at the time it was priced we could only use our best estimate on materials, labor, etc. Now that we are shipping the first UV-3 units, we refigured our costs on the entire system and are pleased to announce that we can pass along these substantial savings to you:

<b>Model 1346</b> Drake UV-3 (144-220-440) .....	<del>\$995.00</del>	\$795.00
<b>Model 1344</b> Drake UV-3 (144-440) .....	<del>\$795.00</del>	\$695.00
<b>Model 1343</b> Drake UV-3 (144-220) .....	<del>\$795.00</del>	\$695.00
<b>Model 1345</b> Drake UV-3 (220-440) .....	<del>\$795.00</del>	\$695.00
<b>Model 1340</b> Drake UV-3 (144) .....	<del>\$595.00</del>	no change
<b>Model 1359</b> Drake UV-3E (144-430) European Model ..		see dealer

(Prices above include factory installed modules for bands as listed, standard dynamic mike, and mobile mounting bracket.)

*144 Add-on Module .....	<del>\$250.00</del>	\$175.00
*220 Add-on Module .....	<del>\$250.00</del>	\$175.00
*440 Add-on Module .....	<del>\$250.00</del>	\$175.00
<b>Model 1504</b> Drake PS-3 AC Power Supply .....	\$ 89.95	no change
<b>Model 1525</b> Drake 1525 EM Encoding Mike .....	\$ 49.95	no change
<b>Model 1330</b> Drake UMK-3 Remote Trunk-Mount Kit .....	\$ 69.95	no change

\*Add-on modules expand band coverage of models which may have been purchased in a single band or two band configuration. Prices includes factory installation which is necessary to meet FCC Type Certification requirements.

To receive a FREE Drake Full Line Catalog, please send name and date of this publication to:

**R. L. DRAKE COMPANY**



540 Richard Street, Miamisburg, Ohio 45432 • Phone (513) 866-2421 • Telex 288-017

Western Sales and Service Center, 2020 Western Street, Las Vegas, Nevada 89102 • 702/382-9470

Mathematical equations and techniques are held to a minimum; the filter design characteristics are conveyed primarily by means of tables, graphs, and illustrative examples. The subjects covered include the basics of operational amplifiers and filters, first order lowpass and high-pass active filters, and second and higher order active filters. Other topics described are bandpass and notch filters as well as the state-variable filter. Twenty-six experiments demonstrate active-filter characteristics.

*The Design of Active Filters and Experiments* sells for \$8.50 and is available from Ham Radio's Communications Bookstore, Greenville, New Hampshire 03048; order BB-AF.

### flex-i-pak instrument case

A flexible instrument housing system has just been designed by the Buckeye Stamping Company of Columbus, Ohio. This case, tradenamed *Flex-i-pak*, is supplied in a basic unit/frame configuration with a variety of chassis and brackets to choose from. This allows custom designing of prototype units at a minimum cost, without tooling. It's also a sturdy, economical case for production run equipment.

Since *Flex-i-pak* extrusions, brackets, and panels contain a pattern of holes on 1/2 inch (12.5cm) centers, an almost infinite number of configurations is possible. Card guides may be installed spaced for popular connector lengths.

The basic case features vinyl covered top and bottom, with side rails and perimeter frame of extruded aluminum. The standard case width is 17 inches (43cm) with 13-inch (33cm), 16-inch (41cm), or 20-inch (51cm) depths. Heights are 3-1/2, 5-1/4, 7, 8-3/4, 10-1/2, and 12-1/4 inches (8.9, 13.3, 17.8, 22.2, 26.7, and 31.1cm).




For complete specifications, contact The Buckeye Stamping Company, 555 Marion Road, Columbus, Ohio 43207.

# WHERE RELIABILITY & ACCURACY COUNT

## INTERNATIONAL CRYSTALS

70 KHz to 160 MHz

### HOLDER TYPES

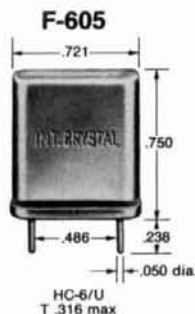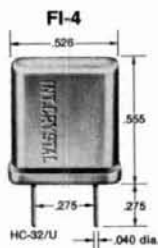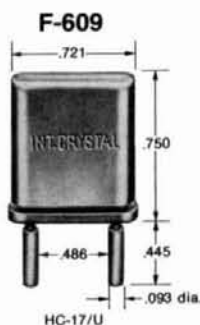



**International  
Crystal Manufacturing Co., Inc.  
guarantees  
every crystal against defective  
materials and workmanship for  
an unlimited time, when used in  
equipment for which they were  
specifically made.**

### CRYSTAL TYPES

(GP) for "General Purpose" applications  
 (CS) for "Commercial" equipment  
 (HA) for "High Accuracy" close temperature  
 tolerance requirements

International Crystals are available from 70  
 KHz to 160 MHz in a wide variety of holders.

WRITE FOR INFORMATION

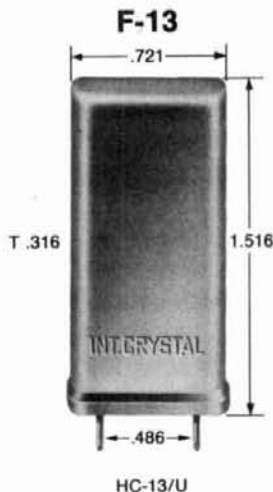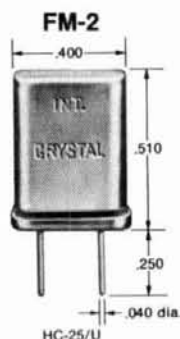

**INTERNATIONAL CRYSTAL MFG. CO., INC.**  
 10 North Lee, Oklahoma City, Oklahoma 73102  
 405/236-3741



# HIRAM PERCY MAXIM



"Hiram Percy Maxim" will be a featured book among the several hundred book titles awaiting you at Ham Radio's exciting exhibit at the Dayton Hamvention.

Inventor, author, technological pioneer — the life story of the "Father of Amateur Radio" details this outstanding American's unique contributions. You can use this special show savings coupon or purchase the book directly from HRPBG for just \$4.50.

Visit Ham Radio — and "Hiram Percy Maxim" at the Dayton Hamvention.

**See you there!**

**HAM RADIO PUBLISHING GROUP  
GREENVILLE, NH 03048**

## HIRAM PERCY MAXIM goes to DAYTON

### with the HAM RADIO PUBLISHING GROUP

save 10%

**SPECIAL  
SAVINGS COUPON**

save 10%

Visit the Ham Radio Publishing Group's exhibition at the Dayton Hamvention and present this coupon for a 10% discount on the cover price of **Hiram Percy Maxim**.

This coupon is good only at the Dayton Hamvention on April 28th, 29th, and 30th, 1978.

save 10%

save 10%

## This is easy- anyone can solder- WITH KESTER SOLDER

**KESTER  
SOLDER**



## Handymen! Hobbyists! DO-IT-YOURSELFERS!

Let Kester Solder aid you in your home repairs or hobbies. For that household item that needs repairing — a radio, TV, model train, jewelry, appliances, minor electrical repairs, plumbing, etc. — Save money — repair it yourself. Soldering with Kester is a simple, inexpensive way to permanently join two metals.

When you Solder go "First Class" — use Kester Solder.

For valuable soldering information send self-addressed stamped envelope to Kester for a FREE Copy of "Soldering Simplified".



**KESTER SOLDER**

Litton 4201 WRIGHTWOOD AVENUE/CHICAGO, ILLINOIS 60639

## NEW FROM GLB

A complete line of **QUALITY 50** thru 450 MHz **TRANSMITTER AND RECEIVER KITS**. Only two boards for a complete receiver. 4 pole crystal filter is standard. Use with our **CHANNELIZER** or your crystals. Priced from \$69.95. Matching transmitter strips. Easy construction, clean spectrum, **TWO WATTS** output, unsurpassed audio quality and built in **TONE PAD INTERFACE**. Priced from \$29.95.

**SYNTHESIZER KITS** from 50 to 450 MHz. Prices start at \$119.95.

Now available in **KIT FORM** — **GLB Model 200 MINI-SIZER**.

Fits any HT. Only 3.5 mA current drain. Kit price \$159.95 **Wired and tested. \$239.95**

Send for **FREE 16 page catalog**. We welcome Mastercharge or VISA

**GLB ELECTRONICS**  
1952 Clinton St., Buffalo, N. Y. 14206

**TEN-TEC 540/544**—the transceivers that almost seem like an extension of yourself. Following your every command, easily, simply — because we did our homework. They are designed with the same out-front thinking that characterizes all Ten-Tec equipment — super-sophisticated to make things simple for you.

**TAKE BAND CHANGING. IT'S SIMPLE!** No more peak and dip, peak and dip. Just snap a switch and there you are. Anywhere you want to be, in any part of a band segment—and always at full efficiency without danger of out-of resonance damage to the final amplifier. Thanks to the Ten-Tec broadband design, and thanks to the leadership of Ten-Tec engineers in solid-state high power HF design.

**FREQUENCY READOUT. IT'S SIMPLE!** The 544 has big easy-to-read numerals with significant figures in red for instant recognition. No more studying a dial or misreading, and no more lag in readout — you instantly know where you are on the band. Even the 540 has an optional add-on digital readout, in case you change your mind later. More operating simplicity from Ten-Tec.

**THE SMART "S"-METER. IT MAKES THINGS SIMPLE FOR YOU.** It's electronically switched to read SWR when you are transmitting so that without throwing switches you know at a glance that the correct antenna is in use. Simple for you, extra effort for us.

**SIGNAL HANDLING OF ALL SIZES. IT'S SIMPLE!** From the "down under" DX to the KW next door, the 540/544 series' dynamic range goes a long way in minimizing front-end overload. And that's important in today's growing amateur radio population. So is the 8-pole i-f filter. It gives you State-of-the-Art signal separation in those crowded bands — to make your operating simpler, more enjoyable

**SUPERIOR SPEECH QUALITY. IT'S SIMPLE!** Ten-Tec rigs are known for their crisp articulation — the kind that brings compliments and satisfaction. Articulated, shaped speech for maximum penetration, yet smooth and clean, with less than 2% distortion to reduce fatigue and enhance the quality of both transmitted and received signals. The signal that's easy to listen to is the one

everyone wants to work. And it's yours in the sophisticated simplicity of the 540/544.

**CW CONVERSATION. IT'S SIMPLE!** The CW buffs used to speak in monologs. Now they carry on conversations, thanks to Ten-Tec's full break-in. It provides a constant window on the band to check for QRM, to save useless calling, to allow conversations that are natural, easier, and a lot more fun. And no more clattering relays! Simply sophisticated.

**FAST, EASY, LOW-COST SERVICING. IT'S SIMPLE!** The thoughtful modular design of the 540/544 makes any trouble-shooting simple and fast, resolving itself down to one of 22 circuit boards, any of which are readily replaced or serviced in the field! Or give the Ten-Tec service people a shout — they will have an exchange on its way to you the same day.

But, best of all, little if any service will be needed because while your 540/544 is sophisticated, complex equipment, it also is designed to conservative ratings with high standards of American craftsmanship. Simply durable.

**FEATURES** — • Instant Band Change (no xmtr. tune-up) • Covers 3.5 to 30 MHz (plus One-Sixty with option) • 200 Watts Input — all bands • Receiver Sensitivity 0.3  $\mu$ V • VFO changes less than 15 Hz per  $F^\circ$  after 30 min. warm-up • 8-pole Crystal IF Filter • Direct Readouts — choose LED digital model or 1 kHz dial model • 150 Hz CW filter • Offset Tuning • WWV at 10 & 15 MHz • Separate Receive Capability • Automatic Sideband Selection, Reversible • Sidetone Level and Pitch control • Pre-Settable ALC • 100% Duty Cycle • S Meter and SWR Bridge • LED indicators for ALC and OFFSET • Modular Plug-In Circuit Boards • Broad Accessory Line

544 Digital — \$869 540 Non-digital — \$699

To make your operating simple, simply see your Ten-Tec dealer, or write for full details.

**TEN-TEC, INC.**  
SEVIERVILLE, TENNESSEE 37862  
EXPORT 5705 LINCOLN AVE., CHICAGO, ILL. 60648

# SIMPLICITY OF OPERATION, SOPHISTICATION OF DESIGN



# YOUR **TEN-TEC** HEADQUARTERS



**ENCORE! ENCORE!**

**TEN-TEC'S 540  
GOES 544!**

REQUEST FURTHER DETAILS


**ELECTRONIC DISTRIBUTORS, INC.**

*Communications Specialists for over 39 Years*

1960 PECK STREET  
TELEPHONE (616) 726-3196

MUSKOGON, MICHIGAN 49441  
TELEX 22-8411
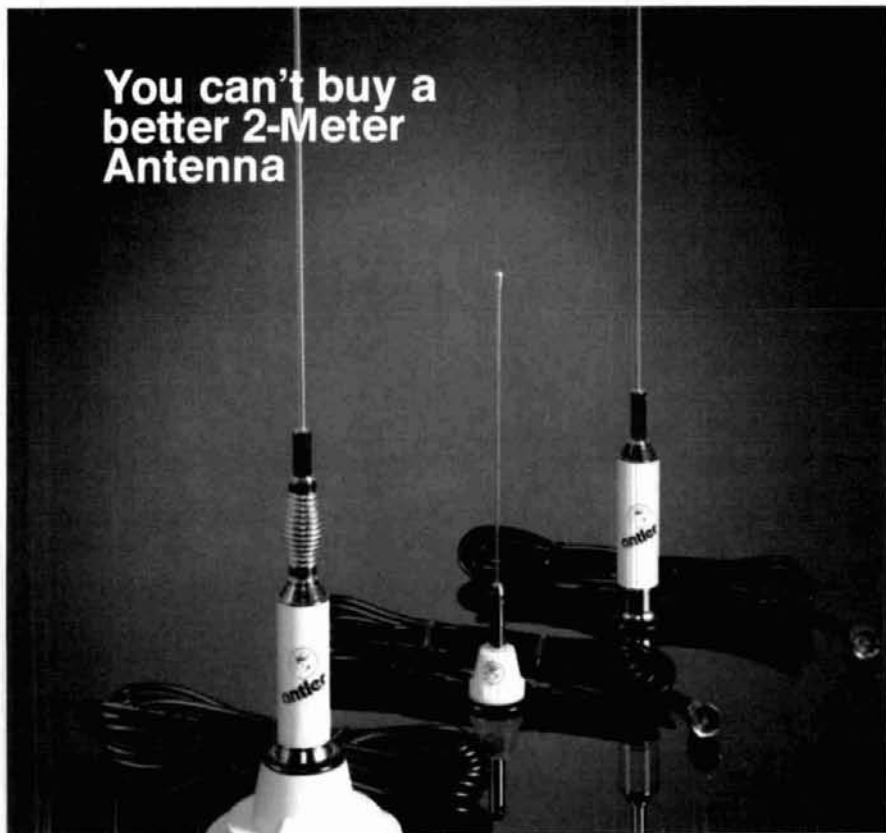
## You can't buy a better 2-Meter Antenna



### Make the best of fine equipment

Take full advantage of the potential of fine radios with Antler. The famous Antler  $\frac{5}{8}$ -wave "Posi-Grip" magnetic mount . . . or the easy-to-install roof or trunk mount that snaps into a  $\frac{3}{8}$ " hole.

There's also a new snap-in "shorty"  $\frac{1}{4}$ -wave. Ideal for repeater use and in-town driving with overhead obstruction problems. You can rely on precision engineering and craftsmanship with "made in U.S.A." quality. Antler . . . you can't buy a better antenna.

\* $\frac{5}{8}$ -wave antennas

at Leading  
Dealers or  
write factory  
for technical  
data and  
prices

**antler<sup>®</sup>  
antennas**



MCM Mfg. Co. / 6200 So. Freeway / Fort Worth, Texas 76134 / Out-of-State Orders 800/433-2524 Toll Free

Foreign Distributors:

EMBEE ELECTRONIC AGENCIES, LTD. Downsview, Ontario M3J264 WILLIAMSON PRODUCT 7000 Stuttgart 50, West Germany

**JAN CRYSTALS HOLD  
THE FREQUENCY**



- CB
- CB standard
- 2 meter
- Scanners
- Amateur Bands
- General
- Communication
- Industry
- Marine VHF
- Micro processor crystals

**easy  
to  
charge**



Send 10\* for our latest catalog  
Write or phone for more details

2400 Crystal Drive  
Ft. Myers, Florida 33901  
all phones (813) 936-2397



### Oak Hill Academy Amateur Radio Session

19th Year — July 29 thru August 11, 1978

We have moved our location just 15 miles from our previous site to the Oak Hill Academy, Mouth of Wilson, Virginia.

Our accommodations are now the finest one could hope for, suites in a beautiful Dorm with bath for each four students. Lovely spacious lobby and fine recreation room in the lower level of the dorm.

Oak Hill Academy in the Appalachian Mountains of Virginia offers an intensive two week Radio Session in code and theory starting at your level.

Expert instructors, some of whom have been on the staff for the past 18 years are the same. Only the location has been changed. Close association with fellow amateurs offers an opportunity for Saturation Learning that has been very successful since its conception.

Novices upgrade to General, Techs to General & Advanced, and Advanced become Extras. Golf privileges, canoeing on the New River & many other recreation activities are offered. Make your vacation a "Vacation with a Purpose" and upgrade your license at a beautiful school in the cool mountains of Virginia.

Formerly Glade Valley School Radio Session

C. L. PETERS, K4DNJ, Director  
Oak Hill Academy Amateur Radio Session  
Mouth of Wilson, Virginia 24363

Name \_\_\_\_\_ Call \_\_\_\_\_

Address \_\_\_\_\_

City/State/Zip \_\_\_\_\_



# SUBSCRIBE NOW

## TO AMATEUR RADIO'S JAM-PACKED TECHNICAL MAGAZINE

# YOURS FREE!



"Hiram Percy Maxim" is the life-saga of the fascinating American who contributed more to Amateur Radio than any other individual. This unique story documents Maxim's accomplishments as an inventor, author and pioneer in many fields during an era of unprecedented technological progress. Includes fascinating excerpts from Maxim's "The Old Man" editorials that appeared in early issues of QST. This \$4.50 value, yours **FREE** by subscribing now.

Yes, HAM RADIO, I'll take you up on your offer, let me save up to 45% off the newsstand cost. Send me my **FREE** biography of Hiram Percy Maxim and start my subscription with the next available issue. I understand I may cancel my subscription at any time and receive a refund for all undelivered copies and the book is mine to keep in any case.

## SAVE UP TO \$24 OFF THE NEWSSTAND PRICE.

**ham  
radio**

GREENVILLE, NH 03048

- 1 Year . . . 12 issues . . \$12.00  
 2 Years . . . 24 issues . . \$22.00  
 3 Years . . . 36 issues . . \$30.00  
(US only)

New  Renew

Master Charge  Visa (BankAmericard)  Check or MO Enclosed

Acct. No. \_\_\_\_\_ Exp. Date \_\_\_\_\_ Bank # \_\_\_\_\_

(MC only)


Name \_\_\_\_\_ Call \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

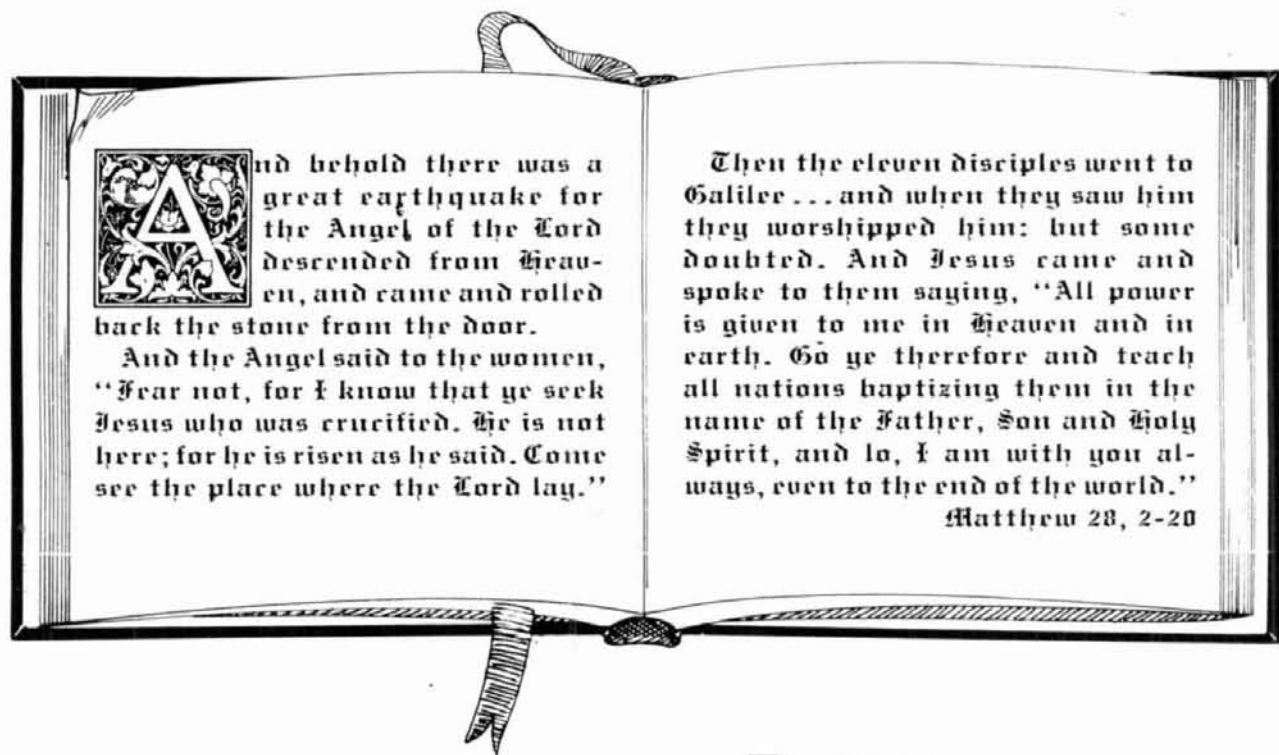Please allow 4-6 weeks for first issue to arrive.





**A**nd behold there was a great earthquake for the Angel of the Lord descended from Heaven, and came and rolled back the stone from the door.

And the Angel said to the women, "Fear not, for I know that ye seek Jesus who was crucified. He is not here; for he is risen as he said. Come see the place where the Lord lay."

Then the eleven disciples went to Galilee . . . and when they saw him they worshipped him: but some doubted. And Jesus came and spoke to them saying, "All power is given to me in Heaven and in earth. Go ye therefore and teach all nations baptizing them in the name of the Father, Son and Holy Spirit, and lo, I am with you always, even to the end of the world."

Matthew 28, 2-20


We would like to share the message and joy of Christ risen this Easter.

**Dentron**  
Radio Co., Inc.

2100 Enterprise Parkway  
Twinsburg, Ohio 44087  
(216)425-3173

## PEOPLE WHO KNOW QUALITY AND NEED RELIABILITY (Military, Industry, RCC's) Demand
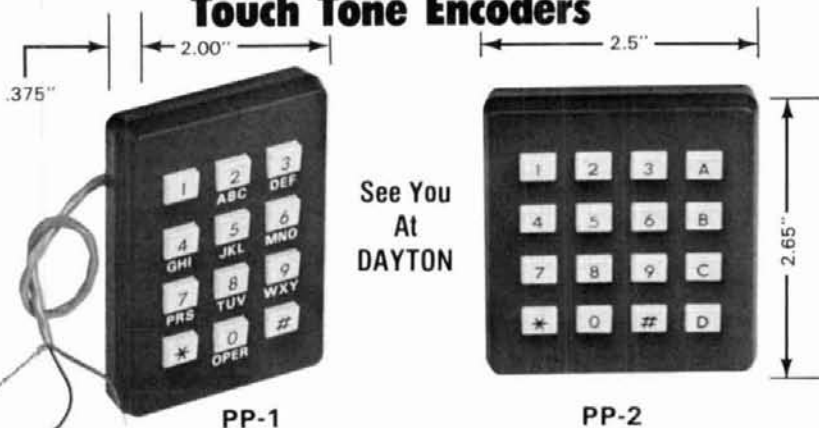
### Pipo Communications For Trouble Free Touch Tone Encoders



See You At DAYTON

## WANT TO KNOW WHY?

Send for Descriptive Brochure and Complete Dealers List  
P.O. Box 3435, Dept. B, Hollywood, CA 90028

# Pipo Communications



Radio Amateurs Reference Library of Maps and Atlas

**WORLD PREFIX MAP** — Full color, 40" x 28", shows prefixes on each country . . . DX zones, time zones, cities, cross referenced tables  
**\$1.25**

**RADIO AMATEURS GREAT CIRCLE CHART OF THE WORLD** — from the center of the United States! Full color, 30" x 25", listing Great Circle bearings in degrees for six major U.S. cities; Boston, Washington, D.C., Miami, Seattle, San Francisco & Los Angeles.  
**\$1.25**

**RADIO AMATEURS MAP OF NORTH AMERICA!** Full color, 30" x 25" — includes Central America and the Caribbean to the equator, showing call areas, zone boundaries, prefixes and time zones, FCC frequency chart, plus useful information on each of the 50 United States and other Countries  
**\$1.25**

**WORLD ATLAS** — Only atlas compiled for radio amateurs. Packed with world-wide information — includes 11 maps, in 4 colors with zone boundaries and country prefixes on each map. Also includes a polar projection map of the world plus a map of the Antarctica — a complete set of maps of the world. 20 pages. Size 8 3/4" x 12"  
**\$2.50**

Complete reference library of maps — set of 4 as listed above  
**\$3.75**

See your favorite dealer or order direct.  
Mail orders please include \$1.25 per order for shipping and handling.

RADIO AMATEUR **callbook** INC.

WRITE FOR FREE BROCHURE!



Dept. E 925 Sherwood Drive  
Lake Bluff, Ill. 60044

# THINKING ABOUT OSCAR?

Here are some helpful suggestions -

## FAMOUS HAMTRONICS PREAMPS let you hear the weak ones!

Great for OSCAR, SSB, FM, ATV. Over 10,000 in use throughout the world on all types of receivers.

**P9 Kit \$12.95**  
**P14 Wired \$24.95**

Deluxe vhf model for applications where space permits.



- 1-1/2 x 3" • Covers any 4 MHz band • 12 Vdc
- Ideal for OSCAR • Diode protection • 20dB gain

MODEL	RANGE
P9-LO	26-88 MHz
P9-HI	88-172 MHz
P9-220	172-230 MHz
P14 Wired	Give exact band

**P8 Kit \$10.95**  
**P16 Wired \$21.95**

- Covers any 4 MHz band
- 20 dB gain • 12 Vdc

Miniature VHF model for tight spaces - size only 1/2 x 2-3/8 inches.

MODEL	RANGE
P8-LO	20-83 MHz
P8-HI	83-190 MHz
P8-220	220-230 MHz
P16 Wired	Give exact band

**P15 Kit \$18.95**  
**P35 Wired \$34.95**

- Covers any 6 MHz band in UHF range of 380-520 MHz
- 20 dB gain • Low noise



## FM/CW TRANSMITTER KITS

BUILD UP YOUR OWN GEAR FOR OSCAR CW OPERATION, FM REPEATERS, CONTROL LINKS

- Professional Sounding Audio • Free of Spurs
- Completely Stable • Built-in Testing Aids



T40 11 Channel 200 MW Exciter Kit for 2M or 6M band..... \$39.95  
T20 Tripler/Driver Kit. Use with T40 for operation on 432-450 MHz band..... \$19.95




T80 RF POWER AMPLIFIER MODULES FOR ABOVE

- No tuning • VSWR Protected • Wired and Tested
  - Rated for Continuous Duty - Great for Repeaters
- T80-150; 140-175 MHz, 20-25W output \$79.95  
T80-450; 430-470 MHz, 13-15W output \$79.95

# AT LAST! A 2 METER SSB TRANSVERTER
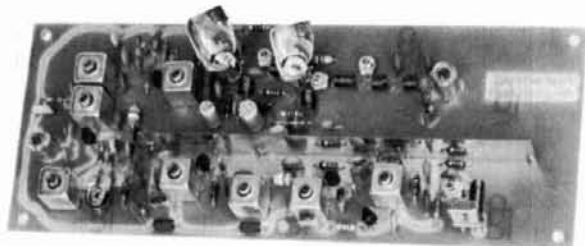
## At a price you can afford

Use inexpensive recycled 10 or 11 meter ssb exciter on 2 meters.



### FEATURES:

- Linear Converter for SSB, CW, FM, etc.
- A fraction of the price of other units
- 2W p.e.p. output with 5 MW of drive
- Use low power tap on exciter or attenuator pad
- Easy to align with built-in test points

### Frequency Schemes Available:

VX2-4	28-30 = 144-146	□	Other frequency
VX2-5	28-29 = 145-146	□	ranges available
VX2-6	26-28 = 144-146	□	on special order

### 2M LINEAR POWER AMPLIFIERS:

LPA 2-15 Kit	15 W p.e.p.	\$69.95
LPA 2-70 Kit	70 W p.e.p.	\$139.95

**VX2-( ) TRANSVERTER KIT \$59.95**  
**A25 Optional Cabinet for Xverter & PA \$20**

## New VHF&UHF Converter Kits

let you receive OSCAR signals and other exciting SSB, CW, & FM activity on your present HF receiver.



either one  
**- ONLY \$34.95**  
including crystal



MODEL	RF RANGE (MHZ)	I-F RANGE
C50	50-52	28-30
C144	144-146	28-30
C145	145-147 (OSCAR)	28-30
C146	146-148	28-30
C110	Aircraft	28-30
C220	220 band	28-30
Special	Other i-f & rf ranges available	

MODEL	RF RANGE (MHZ)	I-F RANGE
C432-2	432-434	28-30
C432-5	435-437 (OSCAR)	28-30
C432-7	427.25	61.25
C432-9	439.25	61.25
Special	Other i-f & rf ranges available	
A9 Extruded Alum Case/Connectors		\$12.95

## VHF/UHF FM RCVR KITS

- ★ NEW GENERATION RECEIVERS
- ★ MORE SENSITIVE ★ MORE SELECTIVE (70 or 100 db)
- ★ COMMERCIAL GRADE DESIGN
- ★ EASY TO ALIGN WITH BUILT-IN TEST CKTS
- ★ LOWER OVERALL COST THAN EVER BEFORE



R70 6-channel VHF Receiver Kit for 2M, 6M, 10M, 220 MHz, or com'l bands..... \$69.95  
Optional xtal filter for 100 dB adj chan 10.00



R90 UHF Receiver Kit for any 2 MHz segment of 380-520 MHz band..... \$89.95

## \* FREE 1978 CATALOG \*

40 PAGE CATALOG IS YOURS FOR THE ASKING!

### IT'S EASY TO ORDER!

- ☛ CALL OR WRITE NOW FOR FREE CATALOG OR TO PLACE ORDER!
- ☛ PHONE 716-663-9254. (Answering service evenings and weekends for your convenience. Personal service 9-5 eastern time.)
- ☛ Use credit card, c.o.d., check, m.o.
- ☛ Add \$2.00 shipping & handling.

IN CANADA, send to Comtec; 5605 Westluka Ave; Montreal, Que H4W 2N3 or phone 514-482-2640. Add 28% to cover duty, tax, and exchange rate.

# hamtronics, inc.

182-C Belmont Rd; Rochester, NY 14612



8-POLE 350-Hz FILTER FOR SIGNAL/ONE TRANSCEIVERS \$120.00

### Finally! Superior 8-Pole CW Selectivity for Drake TR-4, TR-4C, TR-4Cw

350 Hz at -60dB, 850 Hz at -60dB. Cuts QRM. More selective than 6-pole CW filter in new TR-4Cw which is 500 Hz at -60dB, and 2000 Hz at -60dB. CF-350/B \$100.00. Switch and mounting kit \$10.00

### At Last! Superior 8-Pole CW Selectivity for Kenwood TS-820

MINIMAL LOSS IN SET. GOOD SIGNAL-TO-NOISE. 350 Hz at 60dB, 850 Hz at 60dB. Cuts QRM. More selective than standard YG-88C 6-pole CW filter which is 500 Hz at 60dB, and 1800 Hz at 60 dB. CK-350/B \$100.00

### 600 Hz 6-Pole First-IF Filter for Drake R-4C

Improve the early stage selectivity. Eliminate those high-pitched beat notes from signals that leak around the switchable second-IF filter. Minimize the chance of strong signals overloading the second mixer, causing intermodulation and desensitization. Both the existing filter and our CF-600/B can be mounted in the receiver and relay switched to retain phone capabilities. CF-600/B \$80.00. Relay switch kit \$33.00

### 125 Hz 8-Pole Second-IF Filter for Drake R-4C

Still the sharpest available! 300 Hz at -60dB! Cuts QRM. Ideal for DX and contest work. Unexcelled under crowded band conditions. Does what no audio filter can do. More selective than audio filters. Puts selectivity in AGC loop. Unlike with audio filters, receiver gain not reduced by QRM outside passband. Yet works well with an audio filter to improve receiver performance. Plugs directly into an accessory filter socket of the R-4C. CF-125/B \$130.00

**CW Operators!**  
**Attention:**  
*These crystal filters*  
**are for you!**

All filters contain specially-treated high-Q crystals.

**Sherwood Engineering Inc.**

1268 South Ogden St.  
Denver, Colo. 80210  
(303) 722-2257

Money back if not satisfied

Add \$3 per order shipping;  
\$6 overseas air

Dealer Inquiries Welcome



## FT-101 OWNERS

Does your rig have a fast/slow/no AGC control? Compare it with these other fine sets:

Make/Model	Fast/Slow/No AGC Control	
	Yes	No
Yaesu FT-101 Series		✓
Yaesu FR-101, FT-301, FT-901	✓✓	
Kenwood TS-520, TS-820, R-599	✓✓	
Heath SB-104	✓	
Drake R-4C, TR-4C	✓✓	
Tempo 2020, etc., etc., etc.	✓✓	

Your FT-101 should have this control, like the others, to improve CW/SSB reception under difficult conditions. Our new kit makes it easy and inexpensive. No holes to drill, only two soldered connections to rig, complete easy-to-follow instructions. Includes all parts — even solder!



\$5.00

AIRMAIL POSTPAID  
US & CANADA.  
OVERSEAS ADD \$1.

Another winning idea from the International Fox Tango Club. Money back guarantee.

### FT ACCESSORIES

DIVISION OF FOX TANGO CORPORATION  
BOX 274, BRONX, N. Y. 10463

## HAVE YOU WORKED THE NEW OSCAR 8 SATELLITE? IT'S UP THERE NOW, AND READY FOR USE. AND LUNAR PUTS YOU THERE!

# NEW FROM LUNAR OSCARBOX "J"

Dual frequency receiving Model J. down converter for reception of the new Oscar 8 satellite.

Use your Mode A receiver for Mode J. 435.1-2 converts to 29.4-5

432.0 converts to 28.0 by use of front panel selector switch for normal 432 reception capability.

#### SPECIFICATIONS:

NF 3 dB Nominal. Conversion Gain 27 dB, Nominal. Power required: 11 to 14 volts DC, 50 mil amps nominal.

Available with three connector configurations:



SO 239 input, RCA output. \$99.95

Type N input, BNC output.

BNC input, BNC output.

Don't forget Lunar's Preamp line includes the Model PA-28 which will add new life to your Mode A receiver.

\$34.95

### In Line Switching PREAMPLIFIERS Newest addition to the preamplifier line from Lunar In Line RF Actuated PREAMPLIFIER

For use external to your transceiver.

Same high quality as all Lunar preamplifiers. Available for 28 through 220 MHz Bands. Maximum allowable input: 25 watts. Small, compact.

Connector configurations available include:

SO 239 input, RCA output.



Type N input, BNC output.

BNC input, BNC output.

Additional models available soon.

\$49.95

Also new from Lunar:

PREAMPLIFIER PAE432-4.

Under 1.0 dB NF, 16 dB Gain.

\$69.95


#### SEE LUNAR'S NEW PRODUCTS AT THESE LUNAR DEALERS

DEALERS: Ron Com, 820 Whittier Drive, Beverly Hills, CA 90210 • Ham Radio Outlet, 2620 W. La Palma Avenue, Anaheim, CA 92801 • Buddy Sales, 18552 Sherman Way, Reseda, CA 91335 • Help Radio, 1055 Liberty Street, Jacksonville, FL 32206 • Burbank Electronics, 23088 Magnolia Avenue, Burbank, CA 91506 • C. W. Electronics, 18618 24 Parthenia, Northridge, CA • Ing Hanes Bauer KG, Hornthalstraße 8, Postfach 2387, 86 Bamberg, West Germany • Emona Electronics, Room 208/861 George Street, Sydney, New South Wales, Australia • Hobby All, 14 Country Club Road, Norwalk, CN 06851 • Radio West, 3417 Purer Road, Escondido, CA 92025 • Germans Bog & C.A., Av. Fernao de Magalhães, 860 Porto, Portugal • D-P Electronic, Logfinkvej 7 Kraghøve, 4800 Nykøbing Fl. Denmark • C & G Industries, 1040 Pryor Street, Amarillo, TX 79104 • Spectronics, Inc., 1009 Garfield Street, Chicago, IL 60604 • Will Go Shops, Inc., 500 Bluff View Drive, Bellaire Bluffs, FL 33540 • Yucca Associates, Inc., 1605 Beech, Suite G, El Paso, TX 79925 • Henry Radio, 11240 W. Olympic Blvd., Los Angeles, CA 90064 • Bonneville Saw Co., 302 S. Lake Street, Bonneville, MS 38829 • Srepro Electronics, 314 Lee Street, Dayton, Ohio 45404 • The Walt Shop, 410 Hilda Street, Oregon City, OR 97045 • Multiphase Electronics, 116 Haddon Avenue, Collingswood, NJ 08108 • Spectrum International, Inc., P.O. Box 1084, Concord, MA 01742 • Mohr Electronics, 7515 Geyer Springs Road, Little Rock, AR 72209 • George J. Croze, 1317 Gordon Street, Lansing, MI 48910 • M-Tron, 2611 Telegraph Ave., Oakland, CA 94609 • C. Comm., 6115 15th Ave. NW, Seattle, WA 98107 • P.A.C.C., 1720 W. Wetmore, Tucson, AZ 85705 • Erickson Communications, 5935 N. Milwaukee Ave., Chicago, IL 60646 • Bellaire Electronics, 5200 Bellaire Blvd., Bellaire, TX 77401

• Henry Radio, 931 N. Euclid, Anaheim, CA 92801 • Ham Radio Outlet, 999 Howard Ave., Burlingame, CA 94010 • Ham Radio Outlet, 13754 Victory Blvd., Van Nuys, CA 91401 • John Allen, RFD 1, Bowling Green, MO 63334 • Henry Radio, Butler, MO 64730 • Universal Amateur Radio, Inc. 1280 Ada Drive, Reynoldsburg, Ohio  
Area Distributors: Amplifiers West, 2292 Sycamore Drive, Simi Valley, CA 93065 • Panamericana de Comunicaciones C.A., P.O. Box 76 093, Caracas Venezuela • Tycol Communications, Route 3, Mt. Airy, MD 21771 • Slade Communications, 22 Barnmeadow Road, Gateacre, L25 4 UG, U.K. • Radios Unlimited, 86 Balch Avenue, Piscataway, NJ 08854 • Apache Auto Machine, 8825 N. Central, Phoenix, AZ 85022 • C. Comm. 6115 15th Ave., N.W. Seattle, WA 98107



#### FULLY AUTOMATIC C.W. IDENTIFIER

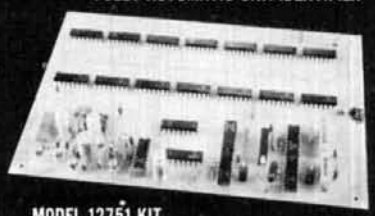

MODEL 12751 KIT

REGULAR \$59.50 VALUE, NOW ONLY \$35.95\*

MODEL 12751 — connects in line between mic. and transmitter requiring no modification to transceiver • automatic 1 to 10 min. timer • 5 to 40 wpm adjustable code speed • built-in squelch tail • auto or manual modes • ideal for repeaters • 5" x 7" PCB and 20-page manual.

#### FACTORY PROGRAMMED MEMORY Ider KITS

MODEL 11764 — semi-auto. MCW Ider • adjustable audio level • programmable code speed, tone and repeat interval • 1.7" x 3" PCB. \$29.95/kit\*

MODEL 97710 — manual CW Ider • programmable code speed • IDs upon request • ideal for contesting or repeated messages • 1.5" x 2.2" PCB. \$24.95/kit\*

MODEL 11765 — beacon CW Ider • programmable code speed • great for 1750-meter band • 1.3" x 2" PCB. \$19.95/kit\* (additional pre-programmed memory elements available)

\*Include \$3 shpg/hdlg., \$5 foreign. CA res. add 6% tax. CODs accepted. Send check or MO, allow 3 weeks on personal checks. Write for additional information  
Phone (408) 294-8383

**SECURITRON Co.**  
P. O. Box 24899  
San Jose, Ca 95154



**Wilson  
Electronics  
Corp.**



**SPECTRONICS, INC.**

1009 Garfield St., Oak Park, Illinois • 60304

**(312) 848-6777**

**THE FIRST NAME IN AMATEUR "HAND-HELD" RADIOS**

**FAMOUS Mark II & Mark IV  
2-METER HAND-HELDS**

**Mark II  
2½-Watt**

**Mark IV  
4-Watt**

**\$219<sup>95</sup> \$249<sup>95</sup>**

Mark IV shown with  
optional TTP  
Auto Patch Pad




- Built-in Microswitch Speaker-Mike
- 6-Channel Operation • Flex Antenna

Wilson's Mark II and Mark IV—the smallest size hand-held two-meter transceivers ever marketed. These high-performing, high-quality, American-made radios are designed for the Amateur who demands the ultimate in dependability, durability, ease of servicing—and value. Both models feature excellent adjacent channel selectivity and intermod/image rejection (60 dB). Individual trimmers on all TX/RX crystals. Microswitch control of Transmit/Receive. Can be modified for MARS or CAP operation. Easily accessible circuitry for simplified servicing. Powered by inexpensive rechargeable Ni-Cad battery pack. Includes rubber flex antenna and one pair of crystals (146.52/.52 MHz). BNC type antenna connector. Attractive and rugged blue-gray Lexan® outer case. Double conversion receiver with sensitivity of 0.3 uV or less for 20 dB quieting. Freq. Range: 144-148 MHz. Size: 6" x 1.77" x 2.44". Weight: 1 lb.

Wilson Mark II. 2.5-watt RF output. . . . . \$219.95  
Wilson Mark IV. 4-watt RF output . . . . . \$249.95

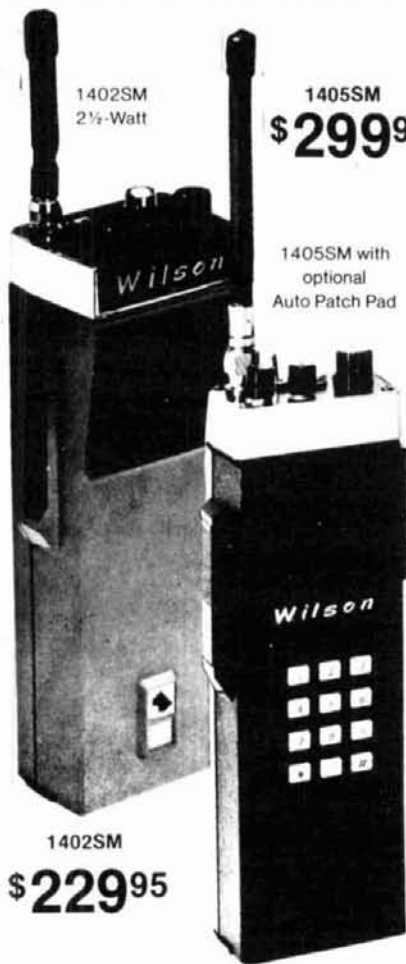**ACCESSORIES**

Model BC-2 Desk Battery Charger. ½ lb. . . . . \$39.95  
Model BP-4 Rechargeable Battery Pack. ½ lb. . . . . \$20.95  
Model LC-3 Leather Carrying Case. 1 lb. . . . . \$18.95  
Model SM-3 Speaker Mike. Wt. 1 lb. . . . . \$30.95  
Model TTP Auto Patch Pad. Factory installed at time of purchase only. Add to price of radio. . . . . \$61.95



1402SM  
**\$229<sup>95</sup>**

1405SM  
**\$299<sup>95</sup>**

1405SM with  
optional  
Auto Patch Pad

**2-METER HAND-HELD RADIOS**

Three top-performing, pocket-size 144-148 MHz radios. Six-channel operation. Individual trimmers on plug-in TX/RX crystals, microswitch TX/RX control. Rubber flex antenna. Powered by rechargeable Ni-Cad battery pack. With 146.52/.52 MHz crystals. 8-7/8x2¼x1-13/16". 1½ lbs.

Model 1402SM. Delivers 2.5-watt RF output. . . . . \$229.95  
Model 1405SM. Switchable 1 or 5 watt RF output . . . . . \$299.95  
Model 1407SM. 7-W . . . . . \$349.95

**UHF HAND-HELDS**

Same construction as above.  
Model 2202SM. 1/2.5 watt. With 223.50/.50 xtals. . . . . \$249.95  
Model 4502SM. 1/1.8-watt. With 446.00/.00 xtals. . . . . \$389.00

**ACCESSORIES**

Model BP-1 Rechargeable Battery Pack. For 1402/1405 . . . . . \$18.95  
Model BP-7 Rechargeable Battery Pack. For 1407SM . . . . . \$24.95  
Model BC-1 Desk Battery Charger. 110 VAC. Wt. 1 lb. . . . . \$40.95  
Model BC-12 Cigarette Lighter Mobile Power Plug . . . . . \$14.95  
Model LC-1 Leather Carrying Case. For 1402SM . . . . . \$18.95  
Model LC-2 Leather Carrying Case. For others above . . . . . \$18.95  
SM-2 Speaker Mike . . . . . \$30.95  
Model TTP Auto Patch Pad. Factory installed only. . . . . \$61.95  
Model BT-2 Battery Tray. Brown, for 1402SM . . . . . \$7.95  
Model BT-3 Battery Tray. Black, for 1402/1405/2202/4502 . . . . . \$7.95

**MOBILE/PORTABLE 2-METER 800-CHANNEL SYNTHESIZED RADIO**



Model WE-800  
**\$459<sup>00</sup>**

All-purpose 2-meter rig operates on 800 channels from 144.000 to 147.995 MHz in 5 kHz steps—up or down 600 kHz for local repeater. Provision for pre-programming five frequencies or changing to two optional offsets. Detachable rubber flex antenna, S-meter/output indicator. With plug-in speaker-mike, mobile bracket/handle. Powered by 13.6 VDC negative ground; takes optional rechargeable battery pack. 8¼ x 6¾ x 1-7/8". Wt. 3 lbs.  
Model WE-800. . . . . \$459.00

- 1 or 12 Watt RF Output
- 800 Channels in 5 kHz Steps
- Base/Mobile/Portable

PRICES AND SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE

**NEW!****DAVIS ELECTRONICS****600 MHz Mini Counter**

- NOW . . .
- Completely PORTABLE with Ni-Cad Batteries
  - Crystal Oven Available



See You at the Dayton Show

Pre-Amp PROBE  
10-500 MHz  
Only \$49.95

General Purpose Low Cost Counter Without the Sacrifice of Basic Performance  
"Check the features we have that some other low cost counters don't have."

- All Metal Cabinet
- Sensitivity < 10 MV
- Completely Auto Decimal Point
- 8 Digit 4" LED Display
- 115V or 12V Operation
- Selectable Gate Times (1 sec & .1 sec)
- Input Cable Included
- Push Button Controls
- State of the Art LSI Circuitry
- 12V Input Jack
- Gate Light
- Crystal Time Base (1 ppm after cal.)

7208K 600 MHz Kit . . . \$149.95 7208A Assembled . . . \$199.95

OPTIONS . . .

- 01) Portable w/Ni-Cad Battery (Built-in Charger) . . . \$39.95  
02) Crystal Oven (1 ppm 0 to 60°C) \$37.95 03) Handle . . . \$5.00



DAVIS ELECTRONICS 636 Sheridan Dr., Tonawanda, NY 14150 716/874-5848

## QUALITY KENWOOD TRANSCEIVERS . . . from KLAUS RADIO

The TS-820S is the rig that is the talk of the Ham Bands. Too many built-in features to list here. What a rig and only \$1098.00 ppd. in U.S.A. Many accessories are also available to increase your operating pleasure and station versatility.



TS-820S  
160-10M TRANSCEIVER

Super 2-meter operating capability is yours with this ultimate design. Operates all modes: SSB (upper & lower), FM, AM and CW. 4 MHz coverage (144 to 148 MHz). The combination of this unit's many exciting features with the quality & reliability that is inherent in Kenwood equipment is yours for only \$729.00 ppd. in U.S.A.



TS-700S  
2M TRANSCEIVER

Guess which transceiver has made the Kenwood name near and dear to Amateur operators, probably more than any other piece of equipment? That's right, the TS-520S. Reliability is the name of this rig in capital letters. 80 thru 10 meters with many, many built-in features for only \$739.00 ppd. in U.S.A.



TS-520S  
80-10M TRANSCEIVER

This brand new mobile transceiver (TR-7400A) with the astonishing price tag is causing quite a commotion. Two meters with 25W or 10W output (selectable), digital read-out, 144 through 148 MHz and 800 channels are some of the features that make this such a great buy at \$399.00 ppd. in U.S.A.



TR-7400A  
2M MOBILE TRANSCEIVER

Send SASE NOW for detailed info on these systems as well as on many other fine lines. Or, better still, visit our store Monday thru Friday from 8:00 a.m. thru 5:00 p.m. The Amateurs at Klaus Radio are here to assist you in the selection of the optimum unit to fulfill your needs.

# KLAUS RADIO Inc.

8400 N. Pioneer Parkway, Peoria, IL 61614  
Jim Plack W9NWE — Phone 309-691-4840

## COLLINS & MORE

### Ham Gear

Collins 180S1, Antenna tuner \$325  
Collins 30L1, Linear amp. \$595  
Collins 312B4, Sta. Cntl., rd., exc. \$250  
Collins 312B5, Vfo Console, vy gd \$550  
Collins 312B5, Vfo Console, new, orig. box \$795

Collins 32S3, Transmitter, rnd., exc. \$895  
Collins MP-1, DC supply, new \$175  
Collins R-388/51J3, rcvr., vy gd \$425  
Collins 75S3, Ham receiver, vy gd \$425  
Collins 75S3B, Ham receiver, vy gd \$695  
Collins 75A4, Ham receiver, vy gd \$425  
Collins 51S1, 2-30MHz rcvr Special \$395  
Hammarlund SP-600JX, .5-50MHz rcvr \$195

Collins CP-1 Crystal Pack \$195  
Johnson KW Matchbox, w/SWR meter \$225  
National NCL 2000, Linear amp., vy gd \$550

Racal 6217E, .5-30MHz receiver Special \$350  
New R390A receivers available. Call for quote.

### Test Gear

HP-302A Wave Analyzer \$495  
HP RM 608D, 10-420MHz sig. gen. \$595  
Measurements Model 65B, LF sig. gen. \$365  
Measurements Model 80, 2-400 MHz sig. gen. \$350  
Tektronix 585A, scope, 80-MHz bandwidth \$595

We stock good, used equipment from Collins, Drake, Heath and other manufacturers. Hundreds of test items also available. Call for specific requirements, or

write for free catalog.

**DAMES COMMUNICATION SYSTEMS**  
201-998-4256  
10 SCHUYLER AVENUE  
NORTH ARLINGTON, N. J. 07032

All equipment sold checked and realigned

## PCP™ TYPE-A PATENT PENDING

SEE POPULAR ELECTRONICS  
FEB '78 ISSUE!

FINALLY you can make HIGH QUALITY printed circuit boards directly from magazine construction articles! Can also be used to make specialized meter faces, front panel decals, component placement decals & others.

Small Pkg. 6pcs 4x6 \$5.49  
Med. Pkg. 4pcs 6x9 \$6.95  
Large Pkg. 3pcs 9x12 \$7.95



PRINTED CIRCUIT PRODUCTS CO.  
P.O. BOX 4034  
MELLEN, MT 59601

### GROTH-Type

COUNTS & DISPLAYS  
YOUR TURNS

- 99.99 Turns
- One Hole Panel Mount
- Handy Logging Area
- Spinner Handle Available

Case: 2x4"; shaft ¼"x3"

PRICES	POST PAID	
TC 2	—	\$8.00
TC 3	—	\$8.75
Spinner (S)	—	\$1.00
Add \$0.75 for Air or UPS		
Model TC2:	Skirt 2-1/8";	Knob 1-5/8"
Model TC3:	Skirt 3";	Knob 2-3/8"


**R. H. BAUMAN SALES**

P.O. Box 122, Itasca, Ill. 60143



# Pound for pound. there is no match for the

## Vhf engineering PS-25M Power Supply

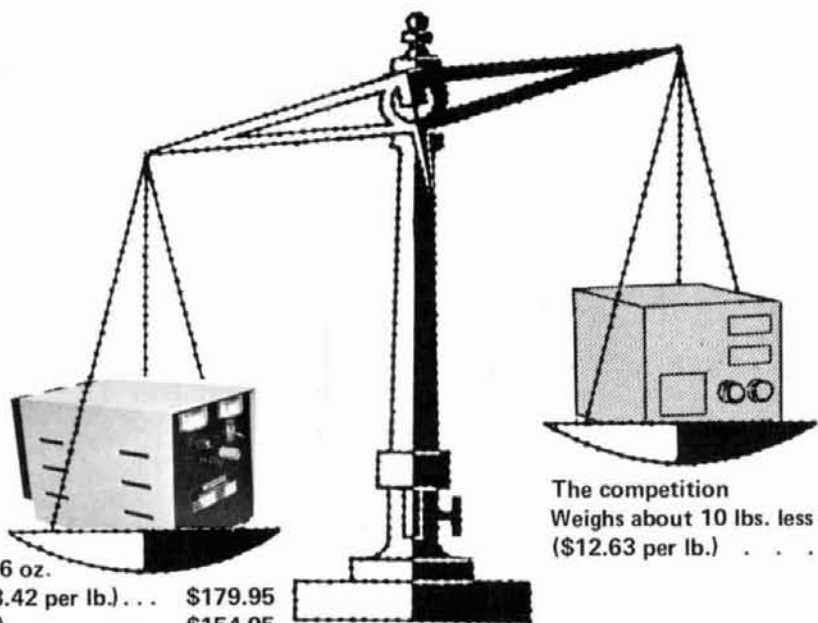

PS-25M — 21 lb. 6 oz.  
Wired & tested (\$8.42 per lb.) . . . \$179.95  
Kit ( \$7.25 per lb.) . . . . . \$154.95

The competition  
Weighs about 10 lbs. less than the PS-25M  
(\$12.63 per lb.) . . . . . \$139.00

**25 Amp regulated power supply with fold back current limiting, over voltage and transient protection. Also, output voltage and current meters.**

You might find a cheaper power supply, but you can't find one as well built with top quality components. Other power supplies with lighter weight transformers and components are no match for the VHF Engineering PS-25M. It is rated at 14 amps continuous duty (not 10 amps). This power means extra dependability and versatility when you need it.

Compare VHF Engineering's quality and specifications.

### FEATURES

- Over-voltage protection crowbar.
- Electrostatic shield for added transient surge protection.
- A foldback output limiter operates for loads outside of the operating range.
- Isolation from ground. The circuit is isolated from the case and ground.
- 115/220 volt input — 50/60 cycle.
- Units are factory wired for 110 volt AC, 50/60 cycle power. A simple jumper will reconfigure the input for 220 volt AC, 50/60 cycles.
- Temperature range—operating 0 to +55 C.
- Black anodized aluminum finish.

### SPECIFICATIONS

Voltage Output:  
adjustable between 10-15V  
Load Regulation:  
2% from no load to 20 amps  
Current Output:  
25 amps intermittent  
(50% duty cycle)  
14 amps continuous  
Ripple:  
50 mV at 20 amps  
Weight:  
25 pounds  
Size:  
12¼" x 6¾" x 7¾"



DIVISION DIVISION OF BROWNIAN ELECTRONICS CORP.

320 WATER STREET / BINGHAMTON, NEW YORK 13901 / PHONE 607-723-9574

F.O.B. Binghamton / Prices and specifications subject to change without notice. / Export prices slightly higher.

1-800-432-1234

1-800-233-0250

1-800-647-8660

1-800-527-4634

1-800-645-9187

1-800-228-4097

1-800-432-1234

# Don't play the numbers!

## Just call us... Toll Free!

# 1-800-325-3636

**FOR NEW OR USED AMATEUR RADIO GEAR**... we're specialists and carry *in stock* most of the famous-brand lines. Or, we will talk trade.

**FOR FAST, DOOR-STEP DELIVERY**... give us a call. You'll be amazed; for we guarantee we'll ship your equipment the same day. Plus, most shipments are **PRE-PAID**.

**TO SAVE MONEY**... join thousands of our satisfied customers who buy from us as easily as from their local supplier. So, remember your call is **Toll Free**.

We welcome your Master Charge or VISA/BankAmericard.

## HAM RADIO CENTER

8340-42 Olive Blvd. P.O. Box 28271 St. Louis, MO 63132



## Look what's new from Whitehouse:



### DX-ARRAYS 20 ELEMENTS

	List	OUR PRICE
DX-120 144 MHz	\$42.95	\$39.95

### OSCAR ANTENNAS

A144-10T 145 MHz 10 El. Twist	\$34.95
A432-20T 430-436 MHz 20 El. Twist	\$49.95
A14T-MB Twist Boom & Bracket	\$15.95

Total List Price **\$108.85**  
OUR PRICE **\$94.95**

### RINGO RANGER for FM

Model	Frequency	YOUR CHOICE
ARX 2	135-170 MHz	<b>\$30.00</b> Delivered in USA Reg. List \$32.95
ARX 220	220-225 MHz	
ARX 450	435-450 MHz	


Make 2 Meters all the fun you had hoped for... put more signal into the other guy's receiver with a new Cushcraft 2 meter antenna.

A147-4	146-148 MHz	4 El. Yagi	\$19.95
A147-11	146-148 MHz	11 El. Yagi	\$29.95
A147-22	146-148 MHz	22 El. Yagi	\$84.95
AFM-4D	144-148 MHz	Four Pole (9dB over 1/2 wave dipole)	\$59.95
A144-10T	145 MHz	10 El. Twist	\$34.95
A144-20T	145 MHz	20 El. Twist	\$54.95
A147-20T	146 & 147 MHz	20 El. Twist	\$54.95

Prices subject to change without notice.

G.R. WHITEHOUSE & CO.  
10 Newbury Drive, Amherst, N. H. 03031

SEND FOR CATALOG with First Class Stamp

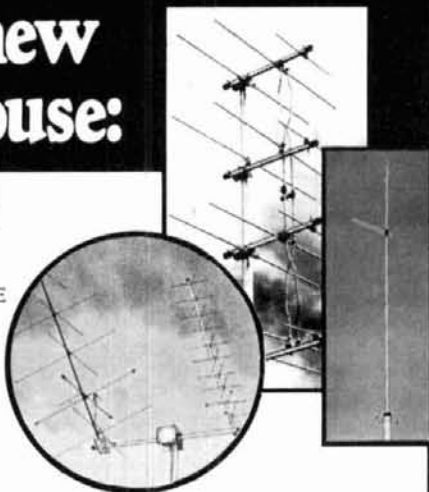

Move those 220 and 430 MHz signals in and out with the quality you deserve. A Cushcraft antenna from G.R. Whitehouse & Co.

A220-7	220-225 MHz	7 El.	\$21.95
A220-11	220-225 MHz	11 El.	\$27.95
A220-20	220-225 MHz	22 El.	\$74.95
AFM-24D	220-225 MHz	Four Pole	\$57.95
AFM-44D	440-450 MHz	Four Pole	\$54.95
A432-20T	430-436 MHz	20 El.	\$49.95

### CUSHCRAFT HF ANTENNAS

ATB-34	Tri-band	4 El.	\$224.95
A14-3	14 MHz	3 El. Monoband	\$125.95
A21-4	21 MHz	4 El. Monoband	\$107.95
A28-4	28 MHz	4 El. Monoband	\$71.95

## SUB-AUDIBLE GENERATOR for FM

- Inexpensive multi tone encoder
- Compatible with PL-CG-QC
- Low distortion sinewave
- Input 8-18 VDC unregulated
- Rugged, plastic encased with leads
- Adjustable frequency (98-250 Hz), Lower available
- Excellent stability



Price **\$19.95**

Freq. set at factory **\$5.00 extra**

Calif. res. add 6%

Send for more info **lyle Products**  
Dept. hr P.O. Box 2083 Santa Clara, CA. 95051

## BUILD-IT-YOURSELF AVIONICS FOR HAM PILOTS

Free catalogue describes high technology, low cost avionics and test equipment offered in kit form. Product line includes audio panel, aircraft band two-channel transceiver, digital chronometer, navigation and communications test equipment, bench power supply, and more. Shoot us the coupon for details.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

(916) 272-2203

**Radio Systems Technology, Inc.**


RR 5, GRASS VALLEY, CA 95945

# YOUR BEST BUY IN KITS

# FREQUENCY COUNTERS

## 6 GOOD REASONS FOR BUYING A HAL-TRONIX FREQUENCY COUNTER

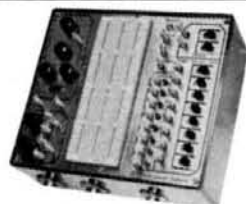(1) 100% COMPLETE KIT, (2) EASY ASSEMBLY, (3) COMPLETELY ENCLOSED IN METAL CABINET, (4) IC SOCKETS USED THROUGHOUT FOR EASY TTL REPLACEMENT (5) EASY ON YOUR POCKET BOOK, AND (6) NO EXPENSIVE CHIPS TO REPLACE (EXAMPLE — IF YOU LOSE A DECODER, LATCH OR DRIVER IN A HAL-TRONIX COUNTER, THE AVERAGE COST OF REPLACEMENT OF THE LOW-COST TTLS IS LESS THAN \$1.00 EXCLUDING THE PRE-SCALE CHIP. IN SOME OF THE NEWER COUNTERS NOW BEING MARKETED BY MY COMPETITION, THEY ARE USING THE EXOTIC SINGLE CHIP AND WOULD COST YOU CLOSE TO \$30.00 TO REPLACE). THIS IS SOMETHING YOU SHOULD CONSIDER.



### ANALOG-DIGILAB KIT \$139.50

DESIGNED BY HAL-TRONIX AND MIKE GOLDEN OF R.E.T.S. ELECTRONICS SCHOOL OF DETROIT. FOR RUGGED CLASSROOM USE.

FOR THE RADIO AMATEUR, STUDENT, EXPERIMENTER OR DESIGNER. SPECIFICATIONS: OUTPUT VOLTAGES: +5V, +12V, -12V; USABLE CURRENT: 750mA; % Regulation at 500mA: 0.2%; Short-circuit limited at 1.0 amp; Thermal overload protected. Power requirements: 117VAC, 60HZ, 40 Watts. Function Generator: Frequency range: 1HZ to 100 HZ in 5 bands. Amplitude adjustable from 0 to 10 VPP. DC offset adjustable from 0 to  $\pm$  10V. Waveforms: Sine, square, triangular and TTL Clock. TTL Clock 0 to +5V level, 200 ns rise and fall time. Frequency determined by Function Generator. Output impedance 1.2K ohm.

Most of all, it's easy to construct and service. PC boards are predrilled, plated thru and solder flowed. Over 1000 units sold to schools.

## NEW FROM HAL-TRONIX FIRST TIME OFFER

**SIX-DIGIT ALARM CLOCK KIT** for home, camper, RV, or field-day use. Operates on-12-volt AC or DC, and has its own 60-Hz time base on the board. Complete with all electronic components and two-piece, pre-drilled PC boards. Board size 4" x 3". Complete with speaker and switches. If operated on DC, there is nothing more to buy.

**PRICED AT \$16.95**  
Twelve-volt AC line cord for those who wish to operate the clock from 110-volt AC. \$2.50

\*Fits clock case advertised below.

### 6-DIGIT CLOCK 12/24 HOUR

COMPLETE KIT CONSISTING OF 2 PC G10 PRE-DRILLED PCB BOARDS, 1 CLOCK CHIP, 6 FND 359 READ-OUTS, 13 TRANSISTORS, 3 CAPS, 9 RESISTORS, 5 DIODES, 3 PUSH-BUTTON SWITCHES, MOLDED POWER TRANSFORMER CORD AND INSTRUCTIONS. DON'T BE FOOLED BY PARTIAL KITS WHERE YOU HAVE TO BUY EVERYTHING EXTRA.

**PRICED AT \$12.95**

### ATTENTION RADIO CLUBS

For club or group projects, request FREE information about our DISCOUNTS on any of the HAL-TRONIX kits. Discounts range from 10-25%, depending upon the quantity needed.

We are experienced in supplying kits in volume quantities to schools, laboratories, clubs, and common-interest groups. Nobody beats HAL-TRONIX quality and price. Just try us and see for yourself.

**CLOCK CASE** Available and will fit any one of the above clocks  
Regular Price... \$6.50 But Only \$4.50 when bought with clock

#### 60-HZ TIME BASE

CRYSTAL TIME BASE KIT. WILL ENABLE MOST ALL DIGITAL CLOCKS TO OPERATE FROM 12 VDC. LOW PROFILE UNIT, EASY 3-WIRE HOOKUP. ACC 2PPM, ADJUSTABLE.  
COST ONLY \$5.95 EACH OR 2 FOR \$10.00 — OR ONLY \$4.50 WITH CLOCK PURCHASE.

#### 10-MHZ CRYSTALS

HI-QUALITY CRYSTALS, DESIGNED FOR FREQUENCY CONTROL AND ELECTRONIC TIME PIECES; AGING FACTOR 5PPM. MEETS OR EXCEEDS MIL-C-3098 SPECS. MADE ESPECIALLY FOR HAL-TRONIX BY SENTRY.  
PRICE \$5.95 OR 2 FOR \$10.00

## NEW FROM HAL-TRONIX FIRST TIME OFFER

**DELUXE 12-BUTTON TOUCH-TONE ENCODER KIT** utilizing the new ICM 7206 chip. Provides both VISUAL AND AUDIO indications! Comes with its own two-tone anodized aluminum cabinet. Measures only 2 3/4 x 3 3/4". Complete with Touch-Tone pad, board, crystal, chip and all necessary components to finish the kit.


**PRICED AT \$29.95**  
For those who wish to mount the encoder in a hand-held unit, the PC board measures only 9/16" x 1 3/4". This partial kit with PC board, crystal, chip and components.

**PRICED AT \$14.95**

DISTRIBUTOR FOR A P PRODUCTS, INCORPORATED



SUPER STRIP SS-2 #923252 PRICE \$17.00

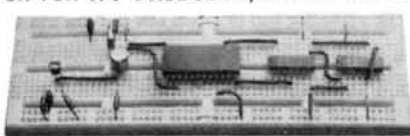

BY POPULAR DEMAND — we are continuing to offer

**FREE** with any purchase of \$99 or more from ad or flyer, a Fairchild clock module FCS-8100A (suggested retail price \$20).



**COMPLETE KITS:** CONSISTING OF EVERY ESSENTIAL PART NEEDED TO MAKE YOUR COUNTER COMPLETE. **HAL-600A** 7-DIGIT COUNTER WITH FREQUENCY RANGE OF ZERO TO 600 MHz. FEATURES TWO INPUTS: ONE FOR LOW FREQUENCY AND ONE FOR HIGH FREQUENCY; AUTOMATIC ZERO SUPPRESSION. TIME BASE IS 1.0 SEC OR .1 SEC GATE WITH OPTIONAL 10 SEC GATE AVAILABLE. ACCURACY  $\pm$ .001%. UTILIZES 10-MHz CRYSTAL 5 PPM.

**COMPLETE KIT \$149.00**

**HAL-300A** 7-DIGIT COUNTER WITH FREQUENCY RANGE OF ZERO TO 300 MHz. FEATURES TWO INPUTS: ONE FOR LOW FREQUENCY AND ONE FOR HIGH FREQUENCY; AUTOMATIC ZERO SUPPRESSION. TIME BASE IS 1.0 SEC OR .1 SEC GATE WITH OPTIONAL 10 SEC GATE AVAILABLE. ACCURACY  $\pm$ .001%. UTILIZES 10-MHz CRYSTAL 5 PPM.

**COMPLETE KIT \$124.00**

**HAL-50A** 8-DIGIT COUNTER WITH FREQUENCY RANGE OF ZERO TO 50 MHz OR BETTER. AUTOMATIC DECIMAL POINT, ZERO SUPPRESSION UPON DEMAND. FEATURES TWO INPUTS: ONE FOR LOW FREQUENCY INPUT, AND ONE ON PANEL FOR USE WITH ANY INTERNALLY MOUNTED HAL-TRONIX PRE-SCALER FOR WHICH PROVISIONS HAVE ALREADY BEEN MADE. 1.0 SEC AND .1 SEC TIME GATES. ACCURACY  $\pm$ .001%. UTILIZES 10-MHz CRYSTAL 5 PPM.

**COMPLETE KIT \$124.00**

### HAL-TRONIX BASIC COUNTER KITS

#### STILL AVAILABLE

THE FOLLOWING MATERIAL DOES NOT COME WITH THE BASIC KIT: THE CABINET, TRANSFORMER, SWITCHES, COAX FITTINGS, FILTER LENS, FUSE HOLDER, T-03 SOCKET, POWER CORD AND MOUNTING HARDWARE.

**HAL-600X** (Same Specifications as HAL-600A) \$124.00

**HAL-300X** (Same Specifications as HAL-300A) \$99.00

**HAL-50X** (Same Specifications as HAL-50A) \$99.00

### PRE-SCALER KITS

**HAL-0-300PRE** (Pre-drilled G10 board and all components) \$19.95

**HAL-0-300P/A** (Same as above but with preamp) \$29.95

**HAL-0-600PRE** (Pre-drilled G10 board and all components) \$39.95

### PRE-BUILT COUNTERS AVAILABLE

(HAL-600A — \$229.00) (HAL-300A — \$199.00) (HAL-50A — \$199.00). ALLOW 4- TO 6-WEEK DELIVERY ON PRE-BUILT UNITS.

See you in Dayton

**HAL-TRONIX**

P. O. BOX 1101

"HAL" HAROLD C. NOWLAND W8ZXH

SOUTHGATE, MICH. 48195

PHONE (313) 285-1782

**SHIPPING INFORMATION:** ORDERS OVER \$15.00 WILL BE SHIPPED POSTPAID EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES ARE REQUESTED. ON ORDERS LESS THAN \$15.00 PLEASE INCLUDE ADDITIONAL \$1.00 FOR HANDLING AND MAILING CHARGES.

SEND SASE FOR FREE FLYER



# THE BIG STEAL

"PART 2"

Featuring the

## Bearcat 210

Frequency Reception Range  
 Low Band 32-50 MHz  
 "Ham" Band 146-148 MHz  
 High Band 148-174 MHz  
 UHF Band 431-470 MHz  
 "T" Band 470-512 MHz  
 \*Also receives UHF from 416-450 MHz

REG. \$349.95

NOW  
**\$269**

The Bearcat 210 is a sophisticated scanning instrument with the ease of operation and frequency versatility you've dreamed of. Imagine, selecting from any of the public service bands and from all local frequencies by simply pushing a few buttons. No longer are you limited by crystals to a given band and set of frequencies. It's all made possible by Bearcat space-age solid state circuitry. You can forget crystals forever.

Automatic search lets you scan any given range of frequencies of your choice within a band. Push button lockout permits you to selectively skip frequencies not of current interest. The decimal display with its exclusive "rolling zeros" tells you which channels you're monitoring. When the Bearcat 210 locks in on an active frequency the decimal display shows the channel and frequency being monitored.

Offer good to licensed hams only.  
 Include call with order.

Freight prepaid in continental U.S.

No COD's



1401 Blake Street  
 Denver, Co. 80202



electronics

303-893-5525



## RTTY for ALL Systems



ELECTROCOM® "SERIES 400"  
 FREQUENCY SHIFT CONVERTERS

Professionally engineered for outstanding performance, stability, and reliability, the Electrocom® Models 400 and 402 add new dimensions of compatibility between radio and teletypewriter systems. Manufactured to highest quality standards—an Electrocom tradition for nearly two decades—these units are ideal for military, government, commercial, civil defense and amateur applications. The Model 400 front panel digital knob accurately selects shifts up to 1000 Hz., while two such knobs on the Model 402 independently set the mark and space frequencies. Both models may also be preset with any tone pair between 1000 and 3200 Hz.

Optimum performance with FSK or AFSK

systems is assured by matched filters, precision linear detectors, baud rate selector, bias compensation, and semi-diversity circuitry. Operation is enhanced by a CRT monitor, autostart with solid-state motor switching, antispacer, markhold, EIA/MIL output voltages, and a constant current loop supply. In addition, various options are available including rack mounting and polar current output.

Write or call us for complete product details and specifications. Learn why Electrocom® "400" Converters are designed not only for today's communication environment, but ultimately to fulfill RTTY requirements for years to come.

## TRANSFORMERS

American made, 115V Primaries:

12 volt 1/2 amp.	\$2.05 ea.
12V 1.2 amp	\$2.84 ea.
12V 3 amp	\$4.48 ea.
12V, 250 mils for P.C. board	\$1.66 ea.
36VCT, 1A; 14VCT, 400Ma	\$4.20 ea.
44VCT, 1A; 6.3V 1/4 amp tap	\$3.47 ea.
48VCT, 1A, 6.3V, 1/4 amp tap	\$3.46 ea.
6.3V, 1 amp shielded	\$1.80 ea.

UNPOTTED TOROIDS — Center tapped,  
 88 MHY - 5 oz. 5/\$2.95; 9 oz. - 5/\$3.49  
 44 MHY - 5/\$3.95

NEW — LINE CORDS — US — 7 AMP  
 6' — Blk — 50¢ ea. 4/\$1.50 ppd.  
 8' — Gray — 60¢ ea. 4/\$1.90 ppd.

EDGEVIEW METERS 250 µa 'S' METERS  
 NEW — \$2.65 ea. 3/\$7.25 ppd.

8 PIN "T05" IC Socket, gold plit. 6/\$1.08

**m. weinschenker**  
 electronic specialties-BOX 353, IRWIN, PA 15642

## BIRD WATCHERS

Don't be absurd, buy a BIRD!  
 ... from your Bird distributor

MODEL  
 43



\$120

ALL ITEMS AND ELEMENTS  
 ORDINARILY IN STOCK  
 Prepaid Shipment in Continental USA Only

MADISON  
 ELECTRONICS SUPPLY, INC.

1508 MCKINNEY HOUSTON, TEXAS 77002  
 713/658-0268 Nites 713/497-5683

**Electrocom**® INDUSTRIES  
 1105 N. IRONWOOD DRIVE, SOUTH BEND, INDIANA 46615  
 Telephone: (219) 232-2743

# SST T-1 RANDOM WIRE ANTENNA TUNER



All band operation (160-10 meters) with any random length of wire. 200 watt **output** power capability—will work with virtually any transceiver. Ideal for portable or home operation. Great for apartments and hotel rooms—simply run a wire inside, out a window, or anyplace available. Toroid inductor for small size: 4-1/4" X 2-3/8" X 3." Built-in neon tune-up indicator. SO-239 connector. Attractive bronze finished enclosure.

only **\$29.95**

THE ORIGINAL Random Wire Antenna Tuner. . . in use by amateurs for 6 years.

## sst t-2 ULTRA TUNER

Tunes out SWR on any coax fed antenna as well as random wires. Works great on all bands (160-10 meters) with any transceiver running up to 200 watts power output.

Increases usable bandwidth of any antenna. Tunes out SWR on mobile whips from inside your car.

Uses toroid inductor and specially made capacitors for small size: 5 1/4" x 2 1/4" x 2 1/2." Rugged, yet compact. Attractive bronze finished enclosure. SO-239 coax connectors are used for transmitter input and coax fed antennas. Convenient binding posts are provided for random wire and ground connections.



only **\$39.95**

## sst t-3 IMPEDANCE TRANSFORMER

only  
**\$19.95**




Matches 52 ohm coax to the lower impedance of a mobile whip or vertical. 12 position switch with taps spread between 3 and 52 ohms. Broadband from 1-30 MHz. Will work with virtually any transceiver—300 watt output power capability. SO-239 connectors. Toroid inductor for small size: 2-3/4" X 2" X 2-1/4." Attractive bronze finish.

### GUARANTEE

All SST products are guaranteed for 1 year. In addition, they may be returned within 10 days for a full refund (less shipping) if you are not satisfied for any reason. Please add \$2 for shipping and handling. Calif. residents, please add sales tax. COD orders OK by phone.

## SST A-1 VHF AMPLIFIER KIT

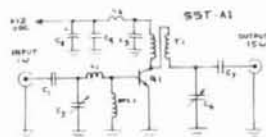

1 watt input gives you 15 watts output across the entire 2 meter band without re-tuning. This easy to build kit (approx. 1/2 hr. assembly) includes everything you need for a complete amplifier. All top quality components. Compatible with all 1-3 watt 2 meter transceivers.

Kit includes:

- Etched & drilled G-10 epoxy solder plated board.
- Heat sink & mounting hardware. All components — including pre-wound coils.
- Top quality TRW RF power transistor.
- Complete assembly instructions with details on a carrier operated T/R switch.

only **\$29.95**

**\$49.95** wired & tested

# BULLET ELECTRONICS

P. O. BOX 19442 DALLAS, TEXAS 75219

\* No COD'S  
\* Send check or MO  
\* MasterCard or VISA accepted.  
\* Texas Residents add 6% sales tax.  
\* Foreign orders add 10% (20% airmail)  
\* Catalog included with each order  
\* Orders over \$50. take 10% discount.

PHONE ORDERS (214/823-3240) ON MASTERCARD & VISA

## PS-14 12V, 15A Power Supply Kit

If its **POWER** you need, than look no further. The PS-14 gives you a highly regulated power supply with features only the commercial units offer at a fraction of the cost. Compare our specs with any other unit on the market and then compare our price!

**SPECS:**  
Output: 11.5-14.5 adjustable  
Current: 15A continuous; 20A int.  
Current Limit: Adjustable Foldback type  
Ripple: Less than 1% @ 15A  
Regulation: Better than 200 millivolts from no load to full load  
Thermal: Adjustable thermal shut down protects series pass.

**YOU GET:**  
\* Heavy duty 12 lb. transformer  
\* 2 large finned heatsinks  
\* Regulator PC board with all parts.  
\* Huge 34,000 mfd computer grade filter cap.  
\* 40 amps of series pass transistors  
\* Wire, transistor mounting kits, line cord.

**\$39.95**

Less Case & Meters

## THE LAST CHANCE!


THAT'S RIGHT! THE LAST CHANCE TO BUY OUR SUPER POPULAR MK-05 MINI MOBILE SIX DIGIT CLOCK KIT at this super low price. The response has been great but supplies are starting to run low. So order NOW!

Features:

- \* Quartz crystal timebase
- \* Toroid & zener noise & over-voltage protection.
- \* Magnified .15", 6 digit LED readout
- \* Complete with presettable 24 hr. alarm.
- \* 9-14 VDC @ 40 to 50 ma.
- \* Readouts can be suppressed
- \* EASY, QUICK ASSEMBLY!
- \* All components required included (you supply the speaker).
- \* Top quality drilled & plated PC Boards
- \* Clock board: 2.6" x 2"
- \* Readout board: 2 3/8" x .75"

Small enough to mount in the instrument panel.

**\$12.95**

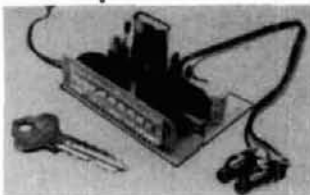

**METERS:** Quality 3/2" meters for PS-14. 0-15VDC. 0-25 ACD matched set. Individually packaged. **NOT SURPLUS!**

**12.50/set**

### OVERVOLTAGE PROTECTION KIT: \$6.95

Provides cheap insurance for your expensive equipment. Trip voltage is adjustable from 3 to 30 volts. Overvoltage instantly fires a 25A SCR and shorts the output to protect equipment. Should be used on units that are fused. Directly compatible with the PS-12 and PS-14. All electronics supplied. Drilled & plated PC board. (Order OVP-1)

**2N6028**  
Programmable uni- junction super for oscillators, timers, time delay etc. **50c**



**SPECIAL!**  
Limited Qty!  
LM567 Tone Decoders while they last! **99c**



**2N6111**  
PNP Transistors 40Watt 3A TO 220 case **2/\$1.00**

**ROCKER SWITCHES**  
DPDT Rocker Switches **5/\$1.00**

**220mfd @25V**  
Axial Cap **7/\$1.00**

**500mfd @35V**  
Axial Cap **5/\$1.00**

**741 Amps**  
8 pin mini dip **5/\$1.00**  
**1458 Dual 741's**  
8 pin mini dip **3/\$1.00**

**Heatshrink Tubing**  
A very good asst. of 3/32", 1/8", 3/16", 1/4" & 7/16" 6" lengths **12 pcs. 75c**

**Above item FREE!**  
with \$15.00 purchase or more!

**MICRO TRIMMER CAPS**  
Tiny 4.40 pfd trimmer used originally in watches! **3/\$1.00**

**MJ900; MJ1000**  
Complimentary Darlington. PNP. NPN power transistor. 8 amps. pair for **\$3.**

**Multicolored 26 Conductor Ribbon Cable**  
No. 28 wire with a woven binder. Super Flexible!  
10' roll - **\$2.95**  
50' roll - **\$9.95**

**1100mfd @ 35**  
Axial Capacitor **4/\$1.00**  
Sprague

**WESTON MICRO**  
PC mount trim pots. Single turn 1K. **3/\$1.00**



**BULLET LUCKY NUMBER FOR MAR.**  
IS: 159943 (Number worth \$100.; numbers are in catalogs.)

**MC1469R**  
500ma positive regulator. 3 to 30 volts. with complete specs and applications. **\$1.25 - house no.**

**MC1351P FM IF AMP.** 14 pin IC. Complete FM sound subsystem, similar to LM2111. house no. **5/\$1.00**

**2N3569 NPN**  
epoxy TO-5 case, VCEO=60; Hfe=300 800MW power **6/\$1.00**

**No. 30 Wirewrap Wire.** Kynar jacket. 4 colors. 100 ft. of each color. **\$4.00 (400')**

**CA3011 Wideband IC** **50c**

**FANTASTIC NEW SOUND SYNTHESIZER IC \$3.95 each**  
Make any sound under the sun with this 28 pin marvel! Single IC contains: Noise generator, super low frequency OSC, VCO, one shot, mixer envelope control and amp. works from a single 5 to 9 VDC source. With 8 page manual.

### Mini Grandfather Clock Kit - \$39.95

Just in case you have spent the last six months in Siberia, we will tell you one more time that **Bullet** has the **ONLY** Completely Electronic Grandfather Clock Kit in the world that has all the below listed features. The biggest problem we have is to try and describe how unique and fascinating this clock really is! The Swinging LED Pendulum and Matching Tick-tock sound are available only on our clock. In addition the electronic chime notes each hour (ie: 3 times for 3 o'clock). Housed in the optional Solid Hardwood Case, the unit makes a beautiful addition to any room as well as a great gift.

- \* 1/4" 4 digit LED readout
- \* Adjustable tone & duration on chime
- \* Simulated swinging pendulum uses LEDs
- \* All CMOS construction
- \* All electronics, switches and transformer included
- \* Quality plated PC boards (2) 6.5" x 4.5"

**BEAUTIFUL HARDWOOD CASE FOR MG-01:** Case is cut, grooved and finished for clock. Includes ruby front filter. Quick, easy assembly requires only 4 screws (inc.) **\$19.95**

You've read the reviews on our MK-03 clock/Timer Kit. Wait till you see the new MK-03A 6 Digit Clock/Timer Kit:

- \* Separate 24 hour clock and 24 hour elapsed timer functions.
- \* Presettable alarms on both clock and timer
- \* Smaller more compact kit is 2 1/2" wide x 3 5/8" long x 1 1/2"
- \* Super revised manual makes assembly easy
- \* Many options available by adding switches.
- \* Sold less case & switches.

**\$28.95** (Will fit standard 3 1/8" instrument case)

## MK-06 Clock/Calendar Auto Home Clock Kit

We designed this to be a **SUPER CLOCK** with ALL the features you want. Quality double sided PC boards make assembly easy. Mobile (12VDC) or home (12VAC)

- \* Large 1/2" LED Readout
- \* AM/PM Indication
- \* 28/29/31 day calendar displays automatically or manually
- \* Display can be dimmed or blanked
- \* Flashing Colon counts the seconds
- \* Interval Timebase is adjustable
- \* Presettable Alarm with Snooze Feature.
- \* Noise and voltage protection circuits
- \* Single front mounted rotary switch selects all functions



**21.50**

# flea market



**RATES** Non-commercial ads 10¢ per word; commercial ads 60¢ per word both payable in advance. No cash discounts or agency commissions allowed.

**HAMFESTS** Sponsored by non-profit organizations receive one free Flea Market ad (subject to our editing). Repeat insertions of hamfest ads pay the non-commercial rate.

**COPY** No special layout or arrangements available. Material should be typewritten or clearly printed (not all capitals) and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** cannot check each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue

**DEADLINE** 15th of second preceding month.

**SEND MATERIAL TO:** Flea Market, Ham Radio, Greenville, N.H. 03048.

**COLUMBUS AMATEUR RADIO CLUB** Annual Hamfest April 8-9, 1978. Columbus Municipal Auditorium fairgrounds. Spacious, air-conditioned exhibit area, prizes, flea market, Saturday night banquet, FCC exams, and a luncheon at the Hamfest site. Contact Eddie Kosobucki, K4JNL, 5525 Perry Ave., Columbus, GA 31904.

**EZ** does it best. Deals, that is, on Yaesu, ICOM, Drake, Swan, Cushcraft, Larsen, KLM, DenTron, VHF Engineering and Wilson. For new or used gear call, see or write **W0EZ**, Bob Smith Electronics, 12 So. 21st St., Fort Dodge, Iowa 50501. (515) 576-3886.

**AUTHORIZED DEALER** for DenTron, KLM, Larsen, Bearcat, etc., Big Catalog 201-962-4695 Narwid Electronics, 61 Bellot Road, Ringwood, N.J. 07456.

**RECONDITIONED TEST EQUIPMENT** for sale. Catalog \$ .50. Walter, 2697 Nickel, San Pablo, Ca. 94806.

**HAM RADIO HORIZONS**, a super new magazine for the Beginner, the Novice and anyone interested in Amateur Radio. . . What it's all about, How to get started, The fun of ham radio. It's all here and just \$12.00 per year. **HURRY! HURRY!** Ham Radio HORIZONS, Greenville, NH 03048.

## Foreign Subscription Agents for Ham Radio Magazine

Ham Radio Austria  
Karin Ueber  
Postfach 2454  
D-7850 Loerrach  
West Germany

Ham Radio Belgium  
Sterehouse  
Brusselsesteenweg 116  
B-9218 Gent  
Belgium

Ham Radio Canada  
Box 114, Goderich  
Ontario, Canada N7A 3Y5

Ham Radio Europe  
Box 444  
S-194 04 Upplands Vasby  
Sweden

Ham Radio France  
Christiane Michel  
F-89117 Parly  
France

Ham Radio Germany  
Karin Ueber  
Postfach 2454  
D-7850 Loerrach  
West Germany

Ham Radio Holland  
MRL Electronics  
Postbus 88  
NL-2204 Delft  
Holland

Ham Radio Italy  
STE Via Maniago 15  
I-20134 Milano  
Italy

Ham Radio Switzerland  
Karin Ueber  
Postfach 2454  
D-7850 Loerrach  
West Germany

Ham Radio UK  
P.O. Box 63, Harrow  
Middlesex HA3 6HS,  
England

Holland Radio  
143 Greenway  
Greenside, Johannesburg  
Republic of South Africa

**TECHNICAL MANUALS** — send 50¢ stamps for 30 page list. Jim Cooper, W2JC, Box 73, Paramus, NJ 07652.

**MOBILE IGNITION SHIELDING** provides more range with no noise. Available most engines. Many other suppression accessories. Literature, Estes Engineering, 930 Marine Dr., Port Angeles, WA 93862.

**MUST SELL.** Johnson Invader 2,000 and power supply. Mint condition. Pickup — no shipping. \$425 W8HXC, 198 Shipherd Circle, Oberlin, Ohio 44074 (216) 774-7762.

**WANTED:** 62S-1 Collins VHF Transverter. Please include age, condx. and price. WA1MMD Box 355, Camden, ME 04843.

**QUAD BUILDERS** — Blizzard/Hurricane proof your antenna. Fiberglass vaulting poles. Incredible strength. Guaranteed new, 8-for \$240.00. S.A.S.E. for info. K5WSE, Box 20-AA, San Antonio, Texas 78201. (512) 699-9260.

**CANADIANS** 1,000,000 surplus parts. Bargains galore. Free catalog. Etco-HR, Box 741, Montreal, H3C 2v2.

**PORTA PAK** the accessory that makes your mobile really portable. \$67.50 and \$88.00. Dealer inquiries invited. P.O. Box 67, Somers, Wisc. 53171.

**QUAGI/YAGI BUILDERS** — Insulated fiberglass booms to 16-feet. Straight, strong, vaulting poles. S.A.S.E. for info. Guaranteed new \$30.00 K5WSE, Box 20-AA, San Antonio, Texas 78201. (512) 699-9260.

**PC BOARDS** — Ham Radio articles. Synthesized Converter 12/77 \$16.00; 2-Meter Scanner 2/78 \$8.50; 11C90 Prescaler \$3.00; Capacitor Checker 4/75 \$3.50. Glass, Plated, Drilled, Instructions and Parts Source. RTC Electronics, Box 2514, Lincoln, Nebraska 68502.

**LARGE S.A.S.E.** Brings list of new and used gear for sale. Good prices. W9POC, 725 College Way, Carmel, IN 46032.

**WANTED** — April 1977 issue of Ham Radio Magazine to complete collection. W7JHQ, Sam Lewbel, 10901 Saratoga Circle, Sun City, Arizona 85351.

**MOTOROLA U54HHT** — \$195, Mocom 30 vhf \$125, U43HHT-3100 cherry \$250, HT200 hi-band \$150, HT220 hi-band \$350, HT220 uhf pl remote speaker mike \$350, HO4BNC uhf pager \$120, L44BBB uhf base \$200. Jim Stephens K6UZP 714-278-9832 eves.

**SCHEMATICS** needed for Megason VI ultra sound instrument. Model 106-5 manufactured by The Bircher Corporation, Los Angeles, CA. Contact Harold Morse, W9TFZ, 4025 26th Avenue, Moline, IL 61265.

**ANYONE FOR CW SKED?** Any Novice Frequency. QSL 100%! Write: Dolores — W3JBD, 36 Quarter Turn Road West, Levittown, PA 19057.

**B&K TEST EQUIPMENT.** Free catalog. Free shipping. Dinosaur discounts. Spacetrion-CD. 948 Prospect, Elmhurst, IL 60126.

**MOTOROLA HT220, HT200,** and Pageboy service and modifications performed at reasonable rates. WA4FRV (804) 320-4439, evenings.

**TEKTRONIX SCOPES** — 543 with CA plugin, DC to 30 MHz \$425. Also 585 with 80 plugin, DC to 100 MHz \$475. Phone 215-933-8183. D. Shavney, 5 Flintlock Lane, Phoenixville, PA 19460.

**DUPLEXER** for sale, 6 cavity, 600 kHz spacing. 2M, per Jan. 1972 QST. Isolation better than 100dB. In service 5 years. Selling; Upgraded. \$250 contact Chesapeake Bay Radio Assn. 301-287-5211.

**CDE HAM X ROTORS.** \$249 USA. \$289 any Foreign QTH with 220/110V external transformer supplied. W9ADN in any call book since 1926.

**RTTY — NS-1A PLL** demodulator. Board \$3.50; Parts \$15.00; W/T \$24.95, all postpaid. SASE for info. Nat Stinnette Electronics, Tavares, Fl. 32778.

**SAVE \$\$\$.** Build your own: LINEAR AMPLIFIERS, 50-100 watt solid state. FREQUENCY COUNTER, 300 MHz, 7 digit, crystal accuracy, portable/mobile, memory! BASE ANTENNA, omnipolarized! Omnidirectional! VOX-COMPRESSOR AND MORE! Construction plans \$3.00 each, 3 up/\$2.50 each. Specify desired band. PANAXIS, Box 5516-AS-5, Walnut Creek, CA 94596.

**TELETYPE EQUIPMENT** for beginners and experienced operators. RTTY machines, parts, supplies. Beginner's special: Model 15 Printer and demodulator \$139.00. Dozen black ribbons \$6.50; case 40 rolls 11/16 perf. tape \$17.50 FOB. Atlantic Surplus Sales, 3730 Nautilus Ave., Brooklyn, N. Y. 11224. Tel: (212) 372-0349.

**TECH MANUALS** for Govt. surplus gear — \$6.50 each: SP-600JX, URM-25D, OS-8A/U, TS-173/UR. Thousands more available. Send 50¢ (coin) for 22-page list. W3IHD, 7218 Roanne Drive, Washington, DC 20021.

## SMOKE DETECTOR



Protect your family — home — and business. These U.L. Approved, ALL METAL units were removed from large apartment complex being torn down. 115 Volt AC input. Sensitivity to smoke is 2% per ft. max. Paint may be scratched but all units tested before shipment. Buy now — Don't delay longer. **\$8.95 ea. ppd.**

Transformer: 115V AC Primary, Secondary 17-0-17V @ 7 Amps. We tested and find good for 10 Amps intermittent duty. Ideal for 2M rigs! **\$8.00 ea. ppd.**

2N3055 xsitors TO-3 case **60c ea.**

12 Amp 100 Volt stud mount diodes **75c ea.**

6 foot AC Line Cords. 2 conductor heavy duty. Color white. **40c ea. ppd.**

Pilot Lite — red neon 115 VAC pilot lite. Single hole mount. Hardware supplied **50c ea. ppd.**

Mini-Toggle. DPDT Cutler-Hammer wire-wrap terminals but can also be soldered. Gold plated. A very high quality unit. Hardware supplied. **\$1.50 ea. ppd.**

Computer Grade Capacitor. 5100 mfd @ 50 volts. Size: 2" dia. x 2-1/4" high. **\$1.90 ea. ppd.**

Fuse Holder — Single hole mount **85c ea. ppd.**

Standard Binding posts. Single hole mount. Your choice Red or Black **25c ea.**

High-gain 8 watt audio amp. 20 mV will drive it to 8 watts out. Rectifiers and filter cap on the board. Size approx. 3" x 4" x 3" high. All you need is 24-0-24 volts ac. Of course we supply schematic. **\$3.25 ppd.**

S0239 Coax Fittings . . . . . **50c ea.**  
PL259 Coax Fittings . . . . . **50c ea.**

88 mHy unpotted toroids **5 for \$3.50**

2N3391A NPN plastic transistors **7c ea.**

3579.545 XTAL **\$1.30**

8.0000 XTAL **\$3.50**

MA1003 Clock Module **\$18.95**

ALL ITEMS PPD USA  
SEND STAMP FOR LIST OF BARGAINS  
PA RESIDENTS ADD 6% SALES TAX  
FONE 412-863-7006



**Gull Electronics**  
12690 ROUTE 30  
NORTH HUNTINGDON, PA 15642



# MADISON

## BIG SIGNAL BUYS

**NEW** OMNI-J 2-meter mobile or portable antenna, 3/4" thread, 5dB gain (1.5dB gain over conventional 3/4-wave mobile whip antenna) \$29.95; 220 MHz \$27.95; 450 MHz \$27.95. Guaranteed results.

**KLM: Antennas, Linears, Accessories All In Stock**

**FREE balun w/2 meter base antenna.**  
**BIRD 43 Wattmeter plus slugs, in stock, prepaid freight.**

**PREMAX 4-foot ground rod plus clamps \$4.50**

**YAESU FT-301D plus FREE FP-301 AC \$935.00**

**YAESU FT-301 plus FREE FP-301 AC \$750.00**

**HY GAIN 18AVT/WB + 100 feet RG8 coax \$100.00**

**HY GAIN 18V vertical \$19.95**

**Model 214 2m Yagi \$21.50**

**Hy-Gain 208 2M Yagi \$15.95**

**VHF SPECIAL: Kenwood TS700S List \$679 Call for quote**

**JANEL PREAMPS: In Stock. Technical Books (ARRL, Sams, Tab, RCA, T.I., etc.)**

**HAM X ROTOR (New Model) Turns 28 sq. ft. of antenna. List \$325. In Stock. Your Price \$249**

**CDE HAM-III \$129.00**

**BIRD 43 WATTMETERS plus slugs in stock.**

**SWAN METERS: WM 6200 VHF Wattmeter \$49.95; SWR 3 Mobile \$9.95.**

**TELEX HEADSETS: In Stock**

**CETRON 572B \$24.95 ea.**

**ADEL nibbling tool, \$6.45; punch \$3.50**

**CABLE 5/32", 6-strand, soft-drawn guy cable. For mast or light tower, 3c foot.**

**BELDEN COAX CABLE: 9888 double shield RG8 foam coax, 100% braid, suitable for direct bury 39' ft., 8237 RG8 21c ft., 8214 RG8 foam 25c ft., 8448 8-wire rotor cable 16c ft., 8210 72 ohm kw twinlead \$19/100 ft., 8235 300 ohm kw twinlead \$12/100 ft., Amphelol PL-259, silver-plated 59c, UG175 adapter 19c, PL-258 dbi female \$1.00, BNC female chassis mount 59c ea; MICRO RG-8/U same size as RG-59, 2 KW PEP @ 30 MHz 16c/ft.**

**BELDEN 14 gauge copper stranded antenna wire. \$5.00/100 ft.**

**22 gauge plastic covered ant. wire for long wire, radials. \$3.50/1000 ft.**

**KESTER SOLDER 1 lb. 60/40, .062 \$6.50**

**Leader — Amateur Test Equip. — 10% off list.**

**Mallory 2.5A/1000PIV epoxy diode 19c ea. .001 MFD 20KV CAP. \$1.95**

**Raytheon 811A, sealed cartons. \$16.00 pr.**

**GE receiving tubes. 50% off list**

**GE6146B, 8950 \$7.95 ea.**

**CALL FOR QUOTES ON: YAESU FT301D, FT301, FT-227R, KENWOOD TS520S, TS820S, TS600A, TR7400A, TR7500A & ETO-ALPHA. ALL IN SEALED CARTONS. CALL FOR QUOTES ON ITEMS NOT LISTED. THIS MONTH'S SPECIAL: BEARCAT 210 SCANNER \$249.**

**We will NOT be at Dayton so call NOW for Madison's stay-at-home prices.**

**TERMS: All prices FOB Houston. Prices subject to change without notice. All Items Guaranteed. Some items subject to prior sale. Send letterhead for Amateur dealers price list. Texas residents add 5% tax. Please add postage estimate.**

# MADISON

## ELECTRONICS SUPPLY, INC.

1508 MCKINNEY HOUSTON, TEXAS 77002  
 713/658-0268 Nites 713/497-5683

# flea market

**TELETYPEWRITER PARTS WANTED:** for all machines manufactured by: Klien Schmidt Corp., Teletype Corp. and Mite. Any quantity, top prices paid send list for my quote. Phil Rickson, W4LNW, Rt. 6, Box 1103G2, Brooksville, FL 33512.

**VERY in-ter-est-ing!** Next 4 issues \$1. "The Ham Trader", 2435 Fruitville, Sycamore, IL 60178.

**QSL CARDS 500/\$10.** 400 illustrations, sample. Bowman Printing, Dept. HR, 743 Harvard, St. Louis, MO 63130.

**HOMEBREWERS:** Stamp brings component list. CPO Surplus, Box 189, Braintree, Mass. 02184.

**CHANNEL ELEMENTS NEEDED KXN1024A,** Motorola for Micor Radio. Need several. WA6COA, 4 Ajax, Berkeley, CA 94708. (415) 843-5253.

**WANTED: Hallicrafters HA-20 VFO.** Write or call W1QUT, 22 Woodridge Road, Wayland, MA 01778. 617-358-4953.

**HAM RADIO HORIZONS,** a super new magazine for the Beginner, the Novice and anyone interested in Amateur Radio... What it's all about, How to get started, The fun of ham radio. It's all here and just \$12.00 per year. HURRY! HURRY! Ham Radio HORIZONS, Greenville, NH 03048.

**ATLAS 180...** Excellent condition, with manual: \$340. Morrie Goldman, WA9RAQ, 5815 N. Christiana, Chicago, Illinois 60659 (312) 583-2990.

**2MTR PREAMP** — size 1 cubic inch, fit inside your transceiver. 18 dB gain, 2 dB NF, \$14.95. Macassey, Apt. 39, 1939, N. Argyle Ave., L.A. CA 90068. SASE for lists other VHF goodies.

**PROP PITCH gasket sets** for smaller prop pitch series. Same material as original. \$5.00/set. H. Landskov, N7RT, 1050 So. Stanley, #40A, Tempe, AZ 85281.

**TOP BAND converter,** IF out 14 MHz, \$50, SASE for info. Macassey, Apt. 39, 1939, N. Argyle Ave., L.A. CA 90068.

**CLEANING OUT SHACK:** Scopes, Xmters, Recvrs, Generators, Counters, Antennas, Tubes, Racks, Meters, etc. 15 yr. collection, price right, SASE for list. WA8GFR 3358 West 130th, Cleve, Ohio 44111.

**CERTIFICATE** for proven two-way radio contacts with Amateurs in all ten USA call areas. Award suitable to frame and proven achievements added on request. SASE brings TAD data sheet from W6IS, 2814 Empire, Burbank, CA 91504.

**THE "CADILLAC" of QSL's!** New! Samples: \$1.00 (Refundable) — MAC'S SHACK; Box #1171-D; Garland, Texas 75040.

**TELETYPEWRITER PARTS,** gears, manuals, supplies, tools, toroids. SASE list. Typetronics, Box 8873, Ft. Lauderdale, FL 33310. N4TT Buy parts, late machines.

**EXCLUSIVELY HAM TELETYPE** 24th year, RTTY Journal, articles, news, DX, VHF, classified ads. Sample 35c. \$3.50 per year. 1155 Arden Drive, Encinitas, Calif. 92024.

**FIGHT TVI** with the RSO Low Pass Filter. For brochure write: Taylor Communications Manufacturing Company, Box 126, Agincourt, Ontario, Canada MIS 3B4.

**HEWLETT PACKARD G382A Attenuator** with pair of Type N adapters. Excellent condition. Copy of last commercial certification provided. \$200.00 W00ZG Rt. 5, Box 113, St. Charles, MO 63301.

**MANUALS** for most ham gear made 1937/1970. Send only 25c coin for list of manuals, postpaid. HI, Inc., Box H864, Council Bluffs, Iowa 51501.

**NEED CK1905 Nixies,** John Strubank, 36525 Grove, Livonia, Mich. 48154.

**QSL FORWARDING SERVICE** — 30 cards per dollar. Write: QSL Express, 30 Lockwood Lane, West Chester, PA. 19380.

## Coming Events

**MASSACHUSETTS:** The Wellesley Amateur Radio Society is conducting its annual auction on Saturday, April 15, 1978, beginning at 11:00AM at the Wellesley High School Cafeteria on Rice Street, Wellesley, Massachusetts. Talk-in on — 96:36, 04-64 and 52. Doors open at 10:00AM. Contact Kevin P. Kelly, WA1YHV, 7 Lawnwood Place, Charlestown, Massachusetts 02129.

# ALUMA TOWERS

60 Ft. Ham Crank-Up Model T-60-H

40 Ft. Crank-Up Ham Model T-140

HIGHEST QUALITY

MADE IN ALUMINUM

★ TELESCOPING (CRANK UP)

★ GUYED

★ TILT OVER MODELS

QUALITY MADE

*Excellent for*

## HAM


## COMMUNICATIONS

MANY MODELS MFG.

Towers to 100 feet. Specials designed & made. See dealer or send for free catalog.

**ALUMA TOWER CO.**  
 BOX 2806HR  
 VERO BEACH, FLA. 32960  
 PHONE (305) 567-3423
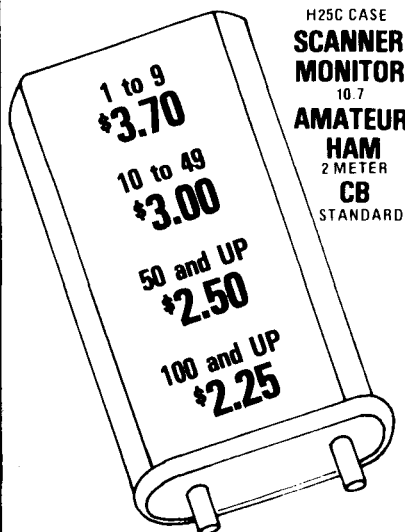
## 10's OF THOUSANDS OF CRYSTALS IN STOCK!



*Immediate delivery on most frequencies!*  
 OTHERS ARE SPECIAL ORDER

**CRYSTAL BANKING SERVICE**  
 P.O. BOX 683  
 LYNNFIELD, MASSACHUSETTS  
 01948






# CHICAGO

Area Amateurs

Know
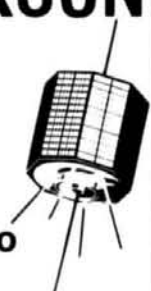
# ERICKSON

Can Provide  
All Their  
Amateur Radio  
needs!



**WB9JKT, WB9ZRA  
and WN9ANF**  
serving you with...

- Ameco • ASP • Atlas
- Belden • Bird • CDE • CIR
- CES • Collins • Cushcraft
- Dentron • Drake • HAL
- Hy-Gain • Icom • KLM
- Kenwood • Larsen • MFJ
- Midland • Mosley • NPC
- Newtronics • Nye
- Regency • Shure • Swan
- Standard • TPL • Tempo
- Ten-Tec • Wilson • Yaesu



Hours: 9:30-5:30 Mon., Tues., Wed. & Fri.  
9:30-9:00 Thurs.  
9:00-3:00 Sat.



**ERICKSON  
COMMUNICATIONS**

5935 N. Milwaukee Ave.  
Chicago, IL 60646  
(312) 631-5181

# flea market

**RARS SIXTH ANNUAL HAMFEST**, April 23, Crabtree Valley Mall, US 70 West, Raleigh, NC. Big, big flea market — all under cover. Fantastic prizes. Ladies activities, meetings. Walk to nearby motels, restaurants, shopping. More info? Write RARS, Box 17124, Raleigh, NC 27609.

**ZERO DISTRICT QSO PARTY**, organized by the Mississippi Valley Radio Club; 2000Z, Saturday, April 22nd to 0200Z, Monday, April 24th. Stations outside of zero district work zero stations only, while zero stations may work any station. Same station once each band, each mode, except for special mobile stations which may be worked each time they change counties. All stations exchange QSO number and ARRL section; all zero stations must send county. Suggested frequencies are, Phone: 3900, 7270, 14300, 21370, 28570; CW: 3560, 7060, 14060, 21060, 28060; Novice: 3725, 7125, 21125, 28125. Awards to high scorer in each ARRL section and DX country. Also top Novice/Technicians and special mobile stations. For information/log forms (S.A.S.E.) WB0UUA, 3518 W. Columbia, Davenport, Iowa 52804.

**HOLIDAY — IN — DIXIE FESTIVAL** sponsored by ARCOS (Amateur Radio Club of Shreveport, LA) from 1800Z, April 21st, through 2400Z, April 30th, 1978. Contact a station within 75 miles of Shreveport, exchange RS(T), power, ARRL section or country. ARCOS members will be on air as a group from 1800Z, April 22nd, to 2400Z, April 23rd, but QSOs can be made anytime during the ten-day festival. Suggested CW: 3555, 3710, 7055, 7110, 14055, 21130, and 28130; Phone: 3935, 3975, 7235, 14280, 21380, and 28575; VHF: 50.110 +/- SSB, and 52.525 +/- simplex FM; 145.100 +/- SSB, and 145.015 +/- simplex FM. Local contacts for demos on 07/67 and 16/76. Locals work each other. For extra points ask members for their Holiday-in-Dixie number. Info and logs to Holiday-in-Dixie QSO Party, P.O. Box 1485, Shreveport, LA 71164.

**MOUTRIE AMATEUR RADIO KLUB**, 17th annual hamfest, April 23, 1978 at Wyman Park, Sullivan, Illinois. Heated indoor, and large outdoor, fleamarket. No charge to vendors. Info from M.A.R.K., Box 327, Mattoon, IL 61938. Talk in on .94.

**ALABAMA FORESTRY FESTIVAL** — April 22, 1978. The Twin Base Amateur Radio Club station WA4PRY will be operating on site in conjunction with the Alabama Forestry Festival at the State Fair Grounds, Montgomery, Alabama. Any ARS completing a two-way contact will receive a special certificate in exchange for a QSL card and SASE. Operations will be conducted from 1600 hours to 2300 hours UTC on frequencies 14.300 MHz and 3.950 MHz normal SSB; slow C.W. (5 to 10 WPM) on 7.125 MHz during even hours UTC and 21.150 MHz during odd hours UTC. QRM frequency adjustments will be up band.

**MIDWEST SPRING CONVENTION** — Saturday, April 1, 1978, Holiday Inn-Holidome, Kearney, Nebraska sponsored by the Midway Amateur Radio Club. Flea market, auction, technical symposiums, ARRL Forum, State MARS Meeting, State QCWA meeting, special "Ladies Day", and evening banquet. Over \$2,500.00 worth of door prizes up for grabs with a Wilson Mark II with touchtone presented to a ham and, for the lucky "Lady" — a microwave oven. Over 200 other prizes to be given away. For registration and further details contact Chuck, W0CRK, Midwest Spring Convention, 3605 Third Avenue, Kearney, Nebraska 68847.

**ARIZONA:** Tucson Hamfest, April 28-30, 1978 Ramada Inn (just off North I-10) Technical session with demonstrations, Microprocessors, Solar Poser, QRP, Fast/Slow Scan, RTTY, Remote Base, etc. Prizes, Ladies Programs, Banquet, Exhibits, Swap Meet. Sponsored by Old Pueblo Radio Club. Write OPRC, 1361 E. Edlin, Tucson, AZ 85711.

**ATLANTIC CITY AREA HAMFEST** Sunday, April 16th. Rain or Shine. 200 Indoor, 400 Outdoor table spaces; Stockton State College Campus, Pomona NJ; Lots of dealers; \$1 advance, \$1.50 gate; Door prizes; More info SPARC, P.O. Box 142, Absecon, NJ 08201.

**27TH DAYTON HAMVENTION** at Hara Arena, April 28, 29, 30, 1978. More room this year! Technical forums, exhibits and huge flea market. Program brochure mailed March 6th to those registered within past three years. For accommodations or advance flyer, write Hamvention, P.O. Box 44, Dayton, OH 45401 or call 513-854-4126.

**THE 4TH ANNUAL NORTHWESTERN PENNSYLVANIA HAMFEST**, May 6th, Crawford County Fairgrounds, Meadville, PA. Gates open at 8:00 \$2 prize ticket required for admission — \$1 to display. Children FREE. Hourly door prizes, refreshments, commercial displays welcome. Indoors if rain. Talk-in 04/64 and 52. Details CARS, P.O. Box 653, Meadville, PA. 16335.

## ALDELCO ELECTRONICS COMPANY

We've Done It Again! Our Battery Operated Frequency Counter and Digital Clock Kit NOW available Assembled and Tested at the KIT Price



**ONLY \$99.95**

Frequency Range 100 Hz to 40 MHz Typical. (prescaler for 600 MHz coming soon) Six Big 0.4 LED Displays. Clock can be 12 or 24 Hour, 4 or 6 Digits, 12 VDC Operation or 8 AA Nicads can be used. Clock runs when counter is in use and when switch is in off position.

8 Size AA Nicad Batteries \$17.50  
110 Volt AC Plug in Power Supply & Charger 5.95

**ACCUKEYER KIT.** Similar to Handbook version. Includes PC Board, IC's, Sockets & all parts \$19.95

**ACCUKEYER MEMORY KIT.** Matches our Accukeyer and many other keyers. Two memories of 30 Characters each. (2 1101 Memory Chips). Includes PC Board, IC's, Sockets and all parts \$19.95

**Dual digital 12 or 24 HOUR CLOCK KIT.** NOW WITH A NEW WALNUT WOOD GRAIN CABINET. Model ALD 5-W. Six Big 0.5 Displays. Only \$49.95 12 or 24 Hour Operation — Each Clock controlled separately Freeze Feature for Time Set — Easy assembly for clock and Cabinet.



Model ALD 5-P. Same Kit as above but with unassembled Black Plastic Cabinet with Red Filter. ONLY \$44.95

**ALARM CLOCK KIT.** Six 0.5 LED Display Readouts. Elapsed Time indicator. 12 Hour Format with 24 Hour Alarm Snooze feature, AM PM Indicator, Power Supply power failure indicator. ONLY \$19.95 12 or 24 Hour Clock Kit. 0.5 Display LED's 18.95  
Wood Grain Cabinet 4.95

**TUNABLE AMATEUR TV CONVERTER**  
Receive Fast Scan ATV in the 420 MHz Band with any TV Set. Low noise high gain Amplifier stage with Varactor Tuned input and output. Built-in 110 VAC Supply. Two Tone Walnut & Beige Cabinet measuring 1-7/8" x 4-1/4" x 4-1/8"  
Factory Wired & Tested. 2 Year Warranty Only \$49.95  
Kit (Critical circuits prewired) Only \$39.95

**Adjustable Power Supply Kits.** 500 MA  
5 to 15 Volts \$6.95 12 to 20 Volts \$6.95  
Power Supply Kit of Parts. 5 Volt 6 Amp 17.95  
(add \$1.00 per Power Supply shipping)

Add 5% for Shipping. Min. Order \$10.00 out of USA send Certified Check or Money Order. Include Postage.

# ALDELCO

2281H Babylon Turnpike, Merrick, N. Y. 11566  
(516) 378-4555

Send 1st class stamp for our catalog.

## WE STOCK

### ICOM & WILSON

**WILSON WE800**  
IN STOCK . . . \$459

**WILSON MARK II**  
ON THEIR WAY . . . \$199

**WILSON MARK IV**  
ON THEIR WAY . . . \$239

### DAVIS

**DAVIS COUNTER**

**NEW** TO 600 MHz!  
MODEL 7208

We have it! . . . \$199.95

Guess who's got your **BIRD**



**EEB DOES**, and here's why . . .  
• We pay the AIR FREIGHT on all prepaid or credit card orders.  
• Call our order desk collect: 703-938-3511.  
• We stock in depth: Bird 43 Thru-line, All Table 1 elements, CC-1 & EC-1 cases.

**\$120.00**

**AUTHORIZED BIRD DISTRIBUTOR**  
All Prepaid & Charge Orders  
Shipped NO CHARGE To You.  
Sales tax 4% to Virginia residents only.

## ELECTRONIC EQUIPMENT BANK, INC.

516H Mill St., Vienna, VA 22180  
Call COLLECT 703-938-3511

# NEW

## Frequency Counter

### \$79<sup>95</sup> kit



UTILIZES NEW MOS-LSI CIRCUITRY

You've requested it, and now it's here! The CT-50 frequency counter kit has more features than counters selling for twice the price. Measuring frequency is now as easy as pushing a button, the CT-50 will automatically place the decimal point in all modes, giving you quick, reliable readings. Want to use the CT-50 mobile? No problem, it runs equally as well on 12 V dc as it does on 110 V ac. Want super accuracy? The CT-50 uses the popular TV color burst freq. of 3.579545 MHz for time base. Tap off a color TV with our adapter and get ultra accuracy — .001 ppm! The CT-50 offers professional quality at the unheard of price of \$79.95. Order yours today!

- CT-50, 60 MHz counter kit ..... \$79.95
- CT-50 WT, 60 MHz counter, wired and tested ..... 159.95
- CT-600, 600 MHz prescaler option for CT-50, add ..... 29.95

#### SPECIFICATIONS

- Sensitivity: less than 25 mv.
- Frequency range: 5 Hz to 60 MHz, typically 65 MHz
- Gatetime: 1 second, 1/10 second, with automatic decimal point positioning on both direct and prescale
- Display: 8 digit red LED .4" height
- Accuracy: 10 ppm, .001 ppm with TV time base!
- Input: BNC, 1 megohm direct, 50 Ohm with prescale option
- Power: 110 V ac 5 Watts or 12 V dc @ 1 Amp
- Size: Approx. 6" x 4" x 2", high quality aluminum case
- Color burst adapter for .001 ppm accuracy available in 6 weeks.
- CB-1, kit ..... \$14.95



#### CLOCK KIT

##### 6 digit 12/24 hour

Want a clock that looks good enough for your living room? Forget the competitor's kludges and try one of ours! Features: jumbo .4" digits, Polaroid lens filter, extruded aluminum case available in 5 colors, quality PC boards and super instructions. All parts are included, no extras to buy. Fully guaranteed. One to two hour assembly time. Colors: silver, gold, black, bronze, blue (specify).

- Clock kit, DC-5 ..... \$22.95
- Alarm clock, DC-8, 12 hr only ..... 24.95
- Mobile clock, DC-7 ..... 25.95
- Clock kit with 10 min ID timer, DC-10 ..... 25.95

Assembled and tested clocks available, add \$10.00

#### VIDEO TERMINAL KIT \$149.95

A compact 5 x 10-inch PC card that requires only an ASCII keyboard and a TV set to become a complete interactive terminal for connection to your microprocessor asynchronous interface. Its many features are single 5 volt supply, crystal controlled send and load rates (up to 9600 baud), 2 pages of 32 characters by 16 lines, read to and from memory, computer and keyboard operated cursor and page control, parity error display and control, power on initialization, full 64 character ASCII display, block type set thru cursor, keyboard/computer control backspace, forward space, line feeds, rev. line feeds, home, returns cursor. Also clears page, clears to end of line, selects page 1 or 2, reads from or to memory. The card requires 5 volts at approx. 900 ma and outputs standard RS 485 composite video.

- TH3216 Kit ..... \$149.95
- TH3216, Assembled and Tested ..... 239.95
- VD-1, Video to RF Modulator Kit ..... 6.95

#### CAR CLOCK KIT \$27.95



- 12/24 Hour 12 Volt AC or DC
- High Accuracy (1 minute/month)
- 6 jumbo .4" LED readouts
- Easy, no polarity hook-up
- Display blanks with ignition
- Case, mounting bracket included
- Super instructions
- Complete Kit, DC-11 ..... \$27.95

#### AUTO DIMMER \$2.50

Automatically adjusts display brightness according to ambient light level. For DC-11 Car Clock.

#### CHEAP CLOCK KIT \$8.95

- DC-4 Features: Does not include board or transformer ..... \$2.95
- 6 digit .4" LED ..... \$1.49
- 12 or 24 format ..... \$1.49

#### 600 MHz PRESCALER



Extend the range of your counter to 600 MHz. Works with all counters. Less than 150 mv sensitivity. Specify 10 or 100. Wired, tested, PS-1B ..... \$59.95

Kit, PS-1B ..... \$44.95

#### 30 watt 2 meter Power Amp

The famous RE class C power amp now available mail order! Four Watts in for 30 Watts out, 2 in for 15 out, 1 in for 8 out, incredible value, complete with all parts, instructions and details on T-R relay. Case not included.

Complete Kit, PA-1 ..... \$22.95

#### CALENDAR ALARM CLOCK

Has every feature one could ever ask for. Kit includes everything except case, build it into wall, station or even car!

- 6 Digits, 5" High LED
- 12/24 Hour Format
- Calendar shows mo./day
- Snooze button
- True 24 Hour Alarm
- 7001 chip does all!
- Battery back up with built in on chip time base

Complete Kit, less case, DC-9 ..... \$34.95

LINEAR		REGULATOR		TRANSISTORS	
5314 Clock	\$2.95	555	\$ .50	78MG	\$1.49
74500	.35	556	.75	309K	.89
74S112	.75	566	1.49	309H	.99
7447	.79	567	1.49	340K-12	.99
7473	.35	1458	.50	7805	.89
7475	.50	LED DRIVER	.7812	7812	.89
7490A	.55	75491	.50	7815	.89
74143	3.50	75492	.50	7818	.89

DIODES: 1KV.2.5A ..... 5/\$1.00    100V.1A ..... 10/\$1.00    1N914A type ..... 50/\$2.00

#### LED DISPLAYS

FND 359	.....	.75
FND 510	.....	1.25
DL 707	.....	1.25
HP 7730	.....	1.25

Red Polaroid Filter ... 4.25" X 1.125" ... \$9

#### 741 OP-AMP SPECIAL

Factory prime mini dip with both Xerox and 741 part numbers

10 for \$2.00

SOCKETS	FERRITE BEADS
14 PIN	5/\$1.00
16 PIN	5/\$1.00
24 PIN	2/\$1.00
40 PIN	3/\$2.00

with info and specs  
6 hole Balun Beads  
5/\$1.00

## MINI-KITS

#### TONE DECODER KIT

A complete tone decoder on a single PC Board. Features: 400-5000 Hz adjustable frequency range, voltage regulation, 567 IC. Useful for touch-tone decoding, tone burst detection, FSK demod, signaling, and many other uses. Use 7 for 12 button touchtone decoding. Runs on 5 to 12 volts.

Complete Kit, TD-1 ..... \$4.95

#### SUPER SLEUTH AMPLIFIER

A super-sensitive amplifier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or as a general purpose test amplifier. Full 2 watts of output, runs on 6 to 12 volts, uses any type of mike. Requires 8-45 ohm speaker.

Complete Kit, BN-9 ..... \$4.95

#### FM WIRELESS MIKE KIT

Transmit up to 300' to any FM broadcast radio, uses any type of mike. Runs on 3 to 9 V. Type FM-2 has added super sensitive mike preamp.

FM-1 ..... \$2.95    FM-2 ..... \$4.95

#### COLOR ORGAN/MUSIC LIGHTS

See music come alive! 3 different lights flicker with music or voice. One light for lows, one for the mid-range and one for the highs. Each channel individually adjustable, and drives up to 300 watts. Great for parties, band music, nite clubs and more.

Complete Kit, ML-1 ..... \$7.95

#### LED BLINKY KIT

A great attention getter which alternately flashes 2 Jumbo LEDs. Use for name badges, buttons, or warning type panel lights. Runs on 3 to 9 volts.

Complete Kit ..... \$2.95

#### POWER SUPPLY KIT

Complete triple regulated power supply provides variable 315 volts at 200 mA and +5 volts at 1 Amp. 50 mV load regulation good filtering and small size. Kit less transformers. Requires 6-8 V at 1 Amp and 18 to 30 VCT.

Complete Kit, PS-3LT ..... \$6.95

#### SIREN KIT

Produces upward and downward wail characteristic of police siren. 5 watts audio output, runs on 3-9 volts, uses 8-45 ohm speaker.

Complete Kit, SM-3 ..... \$2.95

#### DECADE COUNTER PARTS

Includes: 7490A, 7475, 7447, LED readout, current limit resistors, and instructions on an easy to build low cost frequency counter.

Kit of parts, DCU-1 ..... \$3.50

# ramsey electronics

TELEPHONE ORDERS WELCOME

P.O. Box 4072 Rochester NY 14610

(716) 271-6487



Minimum Order \$6.00



## SLEP SPECIALS

### ALPHA LINEARS

PA-76R 2 Tubes	\$1,195.00
PA-76R 3 Tubes	\$1,495.00
PA-76C 3 Tubes 2.4 KVA Hipersil Xmftr	\$1,695.00
PA-77DX 4.4 KVA Xmftr	\$3,295.00
PA-775X Two 8877 Tubes	\$3,895.00
PA-374, No tune-up for amateur band operation	\$1,595.00

Alpha/Vomax SBP-3C Speech Processor \$179.50

### ATLAS

350XL 10-160 350W Solid State Transceiver	\$995.00
350 PS 110/220V Console P/S	\$229.00
305 Plug-in Auxiliary VFO	\$155.00
311 Plug-in Crystal Oscillator	\$135.00
DD6XL Plug-in Mobile Mounting Kit	\$65.00
210X 10-80M Solid State Transceiver	\$679.00
210X with Noise Blanking	\$719.00
220CS 110/220 AC Console P/S	\$149.00
220 CX/VX-5 with VOX/Semi-Break-in CW	\$195.00
200PS 110/220 Portable AC/PS	\$100.00
206 Auxiliary VFO with extended freq. coverage for all Atlas transceivers	\$299.00
MT-1 Mobile Antenna Matching Transformer	\$27.00
10X Crystal Oscillator	\$59.00
PC-120 Noise Blanking Kit	\$52.00
DMK Plug-in Mobile Mounting Kit	\$48.00
DL-200 Dummy Load 200W	\$9.00
MBK Mobile Bracket	\$6.00

### ICOM

IC-22S FM 10W Transceiver	\$259.00
IC-24S FM 10W Synthesized	\$499.00
IC-245/SSB Transceiver	\$599.00
IC-211 Multi-Mode Transceiver	\$749.00
IC-202 2M Portable SSB	\$259.00
IC-502 6M Portable SSB	\$249.00
IC-215/BC-20 2M Portable FM	\$249.00
IC-30A 450 MHz FM 10W	\$399.00
IC-3PA Power Supply with speaker	\$99.00
IC-701 HF Transceiver all solid state 1.8-30 MHz The Ultimate	\$1,495.00

### TEN TEC

509 Argonaut 5W SSB/CW	\$369.00
210 P/S 1 Amp	\$34.00
405 Linear Amplifier 100W	\$169.00
251 P/S 9 Amp 509/405	\$95.00
206 Crystal Calibrator 509	\$29.00
208 CW Filter 509	\$29.00
540 Transceiver 200W SSB/CW	\$699.00
544 Transceiver Digital 200W SSB/CW	\$869.00
252 Power Supply 540/544	\$119.00
262 Power Supply with VOX 540/544	\$145.00
240 160 Converter 540/544	\$110.00
241 Crystal Oscillator 540/544	\$35.00
242 Remote VFO 540/544	\$179.00
244 Digital Read-out 540	\$197.00
245 CW Filter 540/544	\$25.00
249 Noise Blanking 540/544	\$29.00
215P Microphone with plug	\$29.50
207 Ammeter 251, 252, 262	\$14.00
570 Century 21 70W CW Transceiver	\$299.00
574 Century 21 Digital	\$399.00
276 Crystal Calibrated 570/574	\$29.00
670 Single Paddle Keyer 570/574	\$29.00
KR-20A Single Paddle Keyer	\$69.50
KR-50 Ultrasonic Keyer Dual Paddle	\$110.00

### KLM

Echo 70CM UHF Transceiver	\$495.00
Model-2700 All Mode 2M Transceiver	\$756.00
KLM 661 6 Meter SSB, CW, NBFM, AM Transceiver	\$695.95

### TEMPO

Tempo One SSB Transceiver	\$399.00
Tempo AC/One AC/PS	\$99.00
Tempo VF/One External VFO	\$119.00
Tempo 2020 Deluxe SSB Transceiver 115/12V	\$759.00
Tempo 8120 Ext. Speaker	\$29.95
Tempo 8010 Ext. VFO	\$139.00
DM-20 Dual Impedance Desk Mike	\$39.00
RBF-1A Dual Meter SWR/Wattmeter	\$42.95
DD-1T Digital Display Tempometer	\$169.95
Tempo VHF/Plus One 2 meter FM Transceiver 25W	\$399.00
Tempo SSB/One Adaptor SSB 2M	\$199.00
Tempo FMH-2 Hand Held	\$219.00
Tempo FMH-5 Hand Held 5W	\$299.00

WE PAY SHIPPING Via U.P.S. or best way on all advertised items to 50 states and APO/FPO on mailable items. Export orders shipping extra. We accept Master Charge. N. C. residents add 4% sales tax. Phone Bill Slep (704) 524-7519.

**SLEP ELECTRONICS CO.**

P. O. Box 100, Highway 441, Dept. HR-4  
Otto, North Carolina 28763

# flea market

**20TH ANNUAL S.E.M.A.R.A. HAMFEST** April 9th, 1978, 8:00 A.M. until 3:00 P.M. at South Lake High School, 21900 E. Nine Mile Road at Mack Ave., St. Clair Shores, Michigan (in the Detroit Michigan metropolitan area).

**TRI-COUNTY ARC ANNUAL HAMFEST** May 7, 9:00 A.M. to 4:00 P.M. Rain or Shine — Indoors at Stirling, NJ Youth Center, just off Valley Road. Tables \$5.00 Buyers \$1.00. Door Prize — Bird Wattmeter. Talk-in on 146.52 and 147.855-147.255. Info from Tri-County ARC P.O. Box 412, Scotch Plains, NJ 07076 or call Herb W2CHA 201-647-3461.

**HOSSTRADERS NET:** Fifth annual Tailgate Swapfest Saturday, May 13th at Deerfield, New Hampshire Fairgrounds. (Covered buildings in case of rain.) Admission one dollar, no commission or percentage. Commercial dealers welcome at same rate. Excess revenues benefit Boston Burns Unit of Shriners' Hospital for Crippled Children. Last year we donated \$430.80. Talk-in 52, 146.40-147.00, 3940 kHz. Questions: S.A.S.E. to Joe Demaso K1RQG, Star Rt. Box 56, Bucksport, ME 04416 or Norm Blake WA1IVB, P.O. Box 32, Cornish, ME 04020 or Check Hosstraders Net on Sundays 4 PM 3940 kHz.

**KENTUCKY HAM-O-RAMA** — Sunday, May 28 (Memorial Day Weekend), 7 minutes south of Cincinnati. Erlanger Lions Park, Erlanger, Kentucky. Donaldson Road exit, I-75 South. Prizes, exhibits, flea market. NKARC, Box 31, Ft. Mitchell, Kentucky 41017.

**THE RADIO CLUB DE PUERTO RICO** announces its 1978 Annual Convention and Hamfest at the famous Hotel El Conquistador in Fajardo, P.R., the weekend of April 28-30. For details, GPO Box 693, San Juan, PR 00936.

**RADIO SOCIETY OF BERMUDA CONTEST, 0001 GMT** April 22nd to 2400 GMT April 23rd, 1978; operate 36 hours of 48, single operator only; 3.5, 7.0, 14.0, 21.0 and 28.0 MHz bands. Top scorer in each state, county, province to receive printed award. Top scorer in each country to receive trophy presented in Bermuda at RSB Annual Dinner in October. For full information, send large S.A.S.E. plus 13¢ postage to Bernie Swandic, K3DHF, 7417 Mill Run Drive, Derwood, MD 20855.

**F.M. B\*A\*S\*H, DAYTON, OHIO,** April 28, 1978, Friday night of DAYTON HAMVENTION. Social evening for hams and friends, 8 P.M. til midnight. **NEW LOCATION:** Downtown Dayton Convention Center, Main @ Fifth. Admission is free. Sandwiches, beverages, snacks and C.O.D. bar available. Live entertainment by TV personality Rob Reider (WABGFF) and his group. Fabulous prize drawing featuring a complete Drake UV-3, including 144, 220 & 440 MHz synthesized modules, power supply, encoder mike and antenna plus other prizes. Winner of first prize need not be present. For further information contact: Miami Valley F.M. Assn. c/o Sue Hagedorn, WB8GWQ, 1340 Brainard Woods Drive, Dayton, Ohio 45459.

**ROCHESTER REPEATER SOCIETY HAMFEST,** April 15th, from 9:00 A.M., at St. John's Grade School, 420 West Center Street, Rochester, Minnesota. Door prize donation \$1; admission \$1; Children under 12 FREE. Tables \$2.50; plenty of parking. Talk-in 2282 WR0AFT, and 52 simplex. Take I-90 to route 52 or 63 and go north. Advance ticket sales and information from K0TS, Joe Fishburn, 2514 4th Ave., N.W., Rochester, MN 55901; tel: (507) 288-2676; or Gary Sharp, WB8AMA, 1610 34th St., N.W., Rochester, MN 55901; tel: (507) 282-5119.

**6TH ANNUAL MADISON SWAPFEST,** Sunday, April 9th, Dane County Expo Center — Youth Building — Madison, Wisconsin. Doors open at 8:00 A.M., rain or shine; indoor facilities; food; movies; family fun; overnight camping accommodations. Tickets: \$1.50 Advance; \$2 at door; Tables: \$2 Advance; \$3 at door. Featuring electronic equipment and components for hams, hobbyists, computer & experimenters. Follow Coliseum highway signs from I-90/12-18 "beltline" interchange to "MC" 10 miles exit. Talk-in on 16/76. Write M.A.R.A., Box 3403, Madison, WI 53704. Reservations must be in by April 1st!

**LAKE SHORE RADIO FEST,** sponsored by Sheboygan County ARC; Saturday, April 8th, 9 A.M. to 5 P.M., Wilson Town Hall, Sheboygan, Wisconsin. Ham, marine, CB gear on display; door prizes; food; special YL-XYL section. Adults \$2, children w/family FREE. Talk-in 66/06 and 40 meters. Take I-43 to business exit — Route 141. For information, call (414) 452-7570.

**FRAMINGHAM, MASSACHUSETTS ARC Flea Market,** April 29th, doors open 9 A.M. for setup, public at 10 A.M. Location Framingham police drill shed; take Route 9 to Route 126, go south on 126 about 2.5 miles. Drill shed is behind Civic League building. Table \$5. Half-tables also available. Contact F.A.R.C., Box 3005, Framingham, MA; or K1AZE, (617) 879-7456, or WA1UEH, (617) 653-6398.

## TEST EQUIPMENT

All equipment listed is operational and unconditionally guaranteed. Money back if not satisfied — equipment being returned must be shipped prepaid. Include check or money order with order. Prices listed are FOB Monroe.

**BOONTON 190A Q mtr 30-300MHz** ..... \$425  
**BOONTON 250A RX mtr bridge meas**  
 res. cap. ind. 500kHz-250MHz ..... 625  
**FLUKE 803B Diff ac dc vtvm** ..... 295  
**GR1001A LF sig gen 5kHz-50MHz** ..... 385  
**HP120B 450kHz gen pur scope** ..... 215  
**HP160B (USM105) 15mHz scope with**  
 reg horiz, dual trace vert plugs ..... 375  
**HP166B (Mil) Delay sweep for above** ..... 130  
**HP170A (USM140) 30mHz scope with**  
 reg horiz, dual trace vert plugs ..... 475  
**HP175A 50mHz scope with reg**  
 horiz, dual trace vert plugs ..... 565  
**HP202B LF Osc 50kHz 10v out** ..... 75  
**HP205AG Lab audio gen .02 20kHz** ..... 195  
**HP212A Pulse gen .06 5kHz PRR** ..... 65  
**HP524D Freq counter-basic range**  
 10Hz-10MHz extends w-plug-ins ..... 195  
**HP540B Trans osc to 12.4GHz for**  
 use w-HP524 tyoe counters ..... 145  
**HP616 Sig gen 1.8 4GHz FM-CW** ..... 365  
**HP686 Sweep gen 8.2-12.4GHz sweep**  
 range 4.4mHz-4.4GHz ..... 495  
**HP803A VHF Ant bridge 50-500MHz** ..... 135  
**HP2801A Prec dig thermometer**  
 -80 to 250 deg Cels with 1  
 osc. less sensors ..... 1295  
**Tek181 Time-mark scope calib.** ..... 55  
**Tek190 Sig gen(const ampli) 50MHz** ..... 125  
**Tek 545(mil vers by Hickok-Lavoie)**  
 33MHz gen pur scope less plugin ..... 495  
**Tek565 Dual beam 10mHz scope**  
 less plug ins (3 series) ..... 625  
**Tek585 80MHz gen pur scope less**  
 plugin ..... 645  
**URM25 Mil stand sig gen 10kHz-50MHz**  
 calib atfn ..... 225

For complete list of all test equipment send stamped, self-addressed envelope

## GRAY Electronics

P.O. Box 941, Monroe, Mich. 48161  
Specializing in used test equipment.

## FACSIMILE

### COPY SATELLITE, PHOTOS, WEATHER MAPS, PRESS!

The Fax Are Clear — on our full size (18-1/2" wide) recorders. These commercial-military units now available at surplus prices. Learn how to copy with our FREE Fax Guide. Tel: (212) 372-0349

### ATLANTIC SURPLUS SALES

3730 NAUTILUS BROOKLYN, N.Y. 11224

## See our HAM MART

listings to find the  
Amateur Radio  
dealers nearest you.

## GOING 2 OR 220?

### GET ON WITH THE BEST:



Midland 13-510

- Synthesized
- 144-148 MHz
- 1 or 25 watts
- Reg. \$399.95

OUR PRICE \$348<sup>99</sup>



Midland 13-513

- Synthesized
- 220-225 MHz
- 1, 10, 20 watts
- Reg. \$499.95

OUR PRICE \$438<sup>99</sup>

Master Charge and VISA welcome.



**burbank electronics, inc.**  
2308 MAGNOLIA BOULEVARD  
BURBANK, CALIFORNIA 91506  
(213) 843-1647

**DIODES/ZENERS**

1N914	100v	10mA	.05
1N4005	600v	1A	.08
1N4007	1000v	1A	.15
1N4148	75v	10mA	.05
1N753A	6.2v	z	.25
1N758A	10v	z	.25
1N759A	12v	z	.25
1N4733	5.1v	z	.25
1N5243	13v	z	.25
1N5244B	14v	z	.25
1N5245B	15v	z	.25

**SOCKETS/BRIDGES**

8-pin pcb	.25	ww	.45
14-pin pcb	.25	ww	.40
16-pin pcb	.25	ww	.40
18-pin pcb	.25	ww	.75
22-pin pcb	.45	ww	1.25
24-pin pcb	.35	ww	1.10
28-pin pcb	.35	ww	1.45
40-pin pcb	.50	ww	1.25
Molex pins	.01	To-3 Sockets	.45
2 Amp Bridge	100-prv		1.20
25 Amp Bridge	200-prv		1.95

**TRANSISTORS, LEDS, etc.**

2N2222A	NPN (2N2222 Plastic .10)	.15
2N2907A	PNP	.15
2N3906	PNP (Plastic)	.10
2N3904	NPN (Plastic)	.10
2N3054	NPN	.35
2N3055	NPN 15A 60v	.50
T1P125	PNP Darlington	.35
LED Green, Red, Clear, Yellow		.15
D.L.747	7 seg 5/8" High com-anode	1.95
XAN72	7 seg com-anode (Red)	1.25
MAN71	7 seg com-anode (Red)	1.25
MAN3610	7 seg com-anode (Orange)	1.25
MAN82A	7 seg com-anode (Yellow)	1.25
MAN74A	7 seg com-cathode (Red)	1.50
FND359	7 seg com-cathode (Red)	1.25

**C MOS**

4000	.15
4001	.15
4002	.20
4004	3.95
4006	.95
4007	.35
4008	.95
4009	.45
4010	.45
4011	.20
4012	.20
4013	.40
4014	.95
4015	.90
4016	.35
4017	1.10
4018	1.10
4019	.50
4020	.85
4021	1.00
4022	.85
4023	.25
4024	.75
4025	.30
4026	1.95
4027	.50
4028	.95
4030	.35
4033	1.50
4034	2.45
4035	1.25
4040	1.35
4041	.69
4042	.95
4043	.95
4044	.95
4046	1.75
4049	.45
4050	.45
4066	.95
4069	.40
4071	.35
4081	.70
4082	.45
MC 14409	14.50
MC 14419	4.85

7400	.15
7401	.15
7402	.20
7403	.20
7404	.15
7405	.25
7406	.35
7407	.55
7408	.25
7409	.15
7410	.10
7411	.25
7412	.30
7413	.35
7414	1.10
7416	.25
7417	.40
7420	.15
7426	.30
7427	.45
7430	.15
7432	.30
7437	.30
7438	.35
7440	.25
7441	1.15
7442	.45
7443	.65
7444	.45
7445	.65
7446	.95
7447	.95
7448	.65
7450	.25
7451	.25
7453	.20
7454	.25
7460	.40
7470	.45
7472	.40

7473	.25
7474	.30
7475	.35
7476	.40
7480	.55
7481	.75
7483	.95
7485	.75
7486	.25
7489	1.35
7490	.55
7491	.95
7492	.95
7493	.35
7494	.75
7495	.60
7496	.80
74100	1.15
74107	.35
74121	.35
74122	.55
74123	.55
74125	.45
74126	.35
74132	1.35
74141	.90
74150	.85
74151	.65
74153	.75
74154	.95
74156	.95
74157	.65
74161	.85
74163	.85
74164	.60
74165	1.50
74166	1.35
74175	.80

74176	1.25
74180	.75
74181	2.25
74182	.95
74190	1.75
74191	1.05
74192	.75
74193	.85
74194	1.25
74195	.95
74196	1.25
74197	1.25
74198	2.35
74221	1.00
74367	.85
75108A	.35
75110	.35
75491	.50
75492	.50
74H00	.15
74H01	.25
74H04	.20
74H05	.20
74H08	.35
74H10	.35
74H11	.35
74H15	.45
74H20	.30
74H21	.25
74H22	.40
74H30	.20
74H40	.25
74H50	.25
74H51	.25
74H52	.15
74H53J	.25
74H55	.20

74H72	.45
74H101	.75
74H103	.75
74H106	.95
74L00	.25
74L02	.25
74L03	.30
74L04	.30
74L10	.30
74L20	.35
74L30	.45
74L47	1.95
74L51	.45
74L55	.65
74L72	.45
74L73	.40
74L74	.45
74L75	.55
74L93	.55
74L123	.85
74S00	.35
74S02	.35
74S03	.30
74S04	.30
74S05	.35
74S08	.35
74S10	.35
74S11	.35
74S20	.35
74S40	.20
74S50	.20
74S51	.25
74S64	.20
74S74	.35
74S112	.60
74S114	.65

74S133	.40
74S140	.55
74S151	.30
74S153	.35
74S157	.75
74S158	.30
74S194	1.05
74S257 (8123)	1.05
74LS00	.25
74LS01	.35
74LS02	.35
74LS04	.30
74LS05	.45
74LS08	.25
74LS09	.35
74LS10	.35
74LS11	.35
74LS20	.25
74LS21	.25
74LS22	.25
74LS32	.40
74LS37	.35
74LS40	.45
74LS42	1.10
74LS51	.50
74LS74	.65
74LS86	.65
74LS90	.95
74LS93	.95
74LS107	.85
74LS123	1.00
74LS151	.95
74LS153	1.20
74LS157	.85
74LS164	1.90
74LS367	.75
74LS368	.75
74C04	.25
74C151	2.25

**9000 SERIES**

9301	.85	95H03	1.10
9309	.35	9601	.45
9322	.75	9602	.45

**MICRO'S, RAMS, CPU'S, ETC.**

74S188	3.00
1702A	4.50
MM5314	3.00
MM5316	3.50
2102-1	1.45
2102L-1	1.75
TR1602B	4.50
TMS 4044-45NL	14.50
8080AD	12.00
8T13	1.50
8T23	1.50
8T24	2.00
8T97	1.00
2107B-4, A	4.00
2708	11.50

**LINEARS, REGULATORS, etc.**

MCT2	.95	LM320T5	1.65	LM340K15	1.25	LM723	.50
8038	3.95	LM320T12	1.65	LM340K18	1.25	LM725N	2.50
LM201	.75	LM320T15	1.65	LM340K24	.95	LM739	1.50
LM301	.45	LM324N	.95	78L05	.75	LM741 (8-14)	.25
LM308 (Mini)	.95	LM339	.95	78L12	.75	LM747	1.10
LM309H	.65	7805 (340T5)	.95	78L15	.75	LM1307	1.25
LM309K (340K-5)	.85	LM340T12	1.00	78M05	.75	LM1458	.95
LM310	1.15	LM340T15	1.00	LM373	2.95	LM3900	.50
LM311D (Mini)	.75	LM340T18	1.00	LM380 (8-14 PIN)	.95	LM75451	.65
LM318 (Mini)	.95	LM340T24	.95	LM709 (8, 14 PIN)	.25	NE555	.50
LM320K5 (7905)	1.65	LM340K12	1.65	LM711	.45	NE556	.95
LM320K12	1.65					NE565	.95
						NE566	1.75
						NE567	1.35

**INTEGRATED CIRCUITS UNLIMITED**

7889 Clairemont Mesa Boulevard, San Diego, California 92111  
(714) 278-4394 (Calif. Res.)

All orders shipped prepaid No minimum  
Open accounts invited COD orders accepted

Discounts available at OEM Quantities California Residents add 6% Sales Tax  
All IC's Prime/Guaranteed. All orders shipped same day received.

**SPECIAL DISCOUNTS**

Total Order	Deduct
\$35 - \$99	5%
\$100 - \$300	10%
\$301 - \$1000	15%
\$1000 - Up	20%

24 Hour Toll Free Phone 1-800-854-2211 American Express / BankAmericard / Visa / MasterCard



# KLM Transceivers Amplifiers Antennas



Force 5 80-10m 200w PEP Xcvr ..... 1095 00  
F5PS AC power supply ..... 249 95  
F5SC Station console ..... 379 00



Multi-2700 2m FM/SSB/CW Xcvr ..... \$756 00  
Multi-2700 Service Manual ..... 10 00  
TVX0432 432 MHz OSCAR transverter ..... TBA  
Multi-11 23 ch 10w 2m FM Xcvr/4 ch scan ..... 325 95  
661 6m SSB/FM/CW Xcvr ..... 695 00  
Multi-U11 23 ch 10w 450 FM Xcvr/4 ch scan ..... 379 95  
Echo 70 CM 432 MHz SSB/CW Xcvr ..... 449 95



Amplifier	Freq.	Input	Output	
PA2-25B	2m FM	2w	25w	\$ 69 95
PA4-70BL	2m FM/SSB	4w	70w	189 95
PA15-40BL	2m FM/SSB	15w	40w	109 95
PA15-80BL	2m FM/SSB	15w	80w	179 95
PA15-160BL	2m FM/SSB	15w	160w	259 95
PA45-140BL	2m FM/SSB	45w	140w	219 95
PA4-70BC	220 FM	4w	70w	189 95
PA15-60BC	220 FM	15w	60w	164 95
PA45-120BC	220 FM	45w	120w	209 95
PA4-40C	450 FM	4w	40w	169 95
PA15-35CL	450 FM/SSB	15w	35w	154 95
PA15-110CL	450 FM/SSB	15w	110w	279 95

**ANTENNAS**

144-148-4 2m, 4 element	\$ 18 95
144-148-8 2m, 8 element	28 95
144-148-12 2m, 12 element	43 95
144-148-14 2m, 14 element	49 95
144-148-16 2m, 16 element	54 95
144-150-12C 2m circular, 12 element	54 95
144-150-16C 2m circular, 16 element	67 95
432-16LB 432 MHz 16 element	45 95
144-148-50 2m 1:1 sleeve balun	14 95
144-148-50N As above, with type N connectors	15 95
140-150-2N 2m coupler/power divider - 2 ants	19 95
140-150-4N 2m coupler/power divider - 4 ants	26 95

All other KLM products not listed here are available on special order.



## AMATEUR ELECTRONIC SUPPLY®

4828 West Fond du Lac Avenue  
Milwaukee, Wisconsin 53216  
Phone (414) 442-4200

### BRANCH STORES:

28940 Euclid Avenue; Wickliffe, Ohio 44092  
Phone: (216) 585-7388

621 Commonwealth Ave.; Orlando, Fla. 32803  
Phone: (305) 894-3238

Note: Branch Stores are set-up to handle Walk-in business or telephone orders only. They do not have facilities to respond to written inquiries.

## THIS IS IT



MODEL 4431 THRU LINE®

RF DIRECTIONAL WATTMETER  
with VARIABLE RF  
SIGNAL SAMPLER - BUILT IN

AUTHORIZED **BIRD** DISTRIBUTOR

**Webster**  
associates

115 BELLARMINE  
ROCHESTER, MI 48063  
CALL TOLL FREE  
800 - 521-2333

IN MICHIGAN 313 - 375 0420

## NEW 1978 EDITION



The most complete directory of Amateur Radio Equipment ever published. The all new 1978 Edition includes specifications, pictures, and prices of transceivers, transmitters, receivers, amplifiers, power supplies, transverters, antennas, tuners, towers, meters, microphones, keys, VFO's, preamps, test gear, etc. etc. No ham library will be complete without a copy of the 1978 Amateur Radio Equipment Directory.

\$4.00 Postpaid (U.S.)

Canada \$5.00, Foreign (Air) \$7.00

KENGORE CORP. Dept. HR  
9 James Avenue  
Kendall Park, N. J. 08824

SEND FOR YOUR COPY TODAY

PHIL  
WB4WLM

EXPERIENCE the Ultimate  
in Scanners

BOB  
W4YYS



**The Touch.™**

by **Regency**

\$329 LIST

our price  
**\$279 00**

- Over 15,000 frequencies at your fingertips
- Scans the Channels in 1.3 Seconds
- Special Weather Alert® and Priority Scan features

**LAFAYETTE RADIO ELECTRONICS**

ASSOC.  
STORE

1811 HWY 17-92, MAITLAND, FL. 32751

305-831-2271



## ALL BAND TRAP ANTENNAS!



ALL 5 BAND OPERATION - ONLY ONE NEAT SMALL ANTENNA. FOR CONGESTED HOUSING AND APARTMENT DWELLERS! LIGHT, NEAT - ALMOST INVISIBLE!

FOR ALL MAKES AMATEUR HF TRANSMITTERS - TRANSCEIVERS - GUARANTEED FOR 2,000 WATTS PEP POWER. FOR NOVICE AND ALL CLASS AMATEURS!

COMPLETE Ready to put up with 30 ft. Dacron end support cords! Wt. 3 lbs., 1"X5" MOLDED RESONANT TRAPS - just switch your transmitter to desired band for EXCELLENT PERFORMANCE! NO TUNERS OR BALUNS NEEDED! CAN BE USED IN ATTICS, TOPS OF BUILDINGS, INVERTED V's IN MINIMUM SPACE. NO CENTER SUPPORT NEEDED, NO HAYWIRE HOUSE APPEARANCE COMPLETELY ASSEMBLED. No tuning - cutting - soldering - measuring - JUST HANG IT, AND USE IT! SWR IS 1.2 AT RESONANCE THOUSANDS IN USE - EASIEST INSTALLATION!

80-40-20-15-10 meter bands---102 ft. with 90 ft. RG58U coax - connector - Model 998BU. . . \$49.95  
40-20-15-10 meter bands---54 ft. with 90 ft. RG58U coax - connector - Model 1001BU. . . \$48.95  
20-15-10 meter bands---26 ft. with 90 ft. RG58U coax - connector - Model 1007BU. . . \$47.95

Send only \$5.00 (cash, ck., mo.) and pay postman balance plus COD postage OR SEND FULL PRICE FOR POST PAID DEL. IN USA (Canada is \$5.00 extra) or order by MAIL OR PHONE with BankAmericard VISA - MASTER CHARGE - OR AM EXP. Give number and ex. date. Ph 1-308-236-5333 week days. We ship in 2-3 days. INFLATION? PRICES MAY INCREASE - SAVE - ORDER NOW! INFO. AVAILABLE FROM. WESTERN ELECTRONICS Dept. AH-4 Kearney, Nebraska, 68847

**NEW!**

# Synthacoder 509



Ask about Group Purchases

ONLY  
**\$129<sup>95</sup>**  
postpaid

## Take Command of 220 MHz!

The Synthacoder 509 represents the first of a totally new generation of frequency synthesizers, based on the latest advances in CMOS-LSI techniques. "Matrix Modules", which contain programming diodes, make adding new channels a cinch. Simply snip the leads on the diodes not needed, plug it in, and you are **On The Air!** Our unique interface design allows you to use your existing crystal positions even though the synthesizer has been installed. The Synthacoder is also easily adapted for **Scanning** and **External Frequency Control**. To sum it up—We are sure that you will find the new Synthacoder 509 **Everything You Want** in a 220 MHz synthesizer—And at a **Price Comparable to Crystals!**

- \* SIMPLE TO INTERFACE - Three wires and no holes!
- \* FULL COVERAGE - 220-225 MHz in 20 KHz steps
- \* MATRIX PROGRAMMABLE - No more crystals
- \* EXCLUSIVE "MATRIX MODULES" - Program in seconds
- \* FULL MODE CONTROL - Simplex, Repeater, Reverse
- \* LOW POWER CMOS - Draws only 60 ma
- \* FULLY ASSEMBLED AND CALIBRATED - Not a kit
- \* FITS MIDLAND, COBRA, and CLEGG 220 MHz transceivers

### Engineering Specialties

P.O. BOX 2233  
1247 COMMERCIAL AVENUE  
OXNARD, CA 93030  
(805) 486-0817

- I'LL BITE! Please send more info.  
 I'M HOOKED! Please RUSH my Synthacoder.

YES, I would like to purchase a Synthacoder for my 220 radio. Enclosed please find my \$129.95 (Price includes postage and handling). California residents add 6% sales tax.

\$ \_\_\_\_\_ enclosed.  Check  Money Order  
Please charge my  Master Charge  BankAmericard  
Credit card # \_\_\_\_\_  
Interbank # \_\_\_\_\_  
Expiration date \_\_\_\_\_  
Signature \_\_\_\_\_

Name \_\_\_\_\_ Call \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



# Rochester HAMFEST

# MAY 20, 21, 1978

OFFICIAL  
N. Y. STATE  
ARRL  
CONVENTION

**Monroe County Fairgrounds**  
Route 15A and Calkins Road  
Rochester, New York

**HUGE INDOOR  
AND OUTDOOR  
FLEA MARKETS**

**OUTDOOR  
FLEA  
MARKET  
RUNS  
CONTINUOUSLY  
FROM FRI. NOON.  
\$1.00 PER SPACE**

**SEE LATEST  
EQUIPMENT BY  
THE NATION'S  
LEADING  
MANUFACTURERS**

**FCC EXAMS  
FORUMS, SEMINARS  
LADIES' PROGRAMS  
AWARDS BANQUET**

Hotel Headquarters

**ROCHESTER  
MARRIOTT INN**  
(Route 15 at Thruway  
Exit 46)

P.O. BOX 9912  
ROCHESTER, NY 14623  
716-359-1800

Call or Write Hotel  
Direct for Reservations


**Hamfest Admission:**  
\$3.50 in advance.  
\$4.00 at the door.

**combination Registration  
and banquet**  
only \$12.00 in advance.  
Advance sale closes May 13

Exhibitors call Ash Palmer,  
K2EAW at 716-338-2180 days  
only. For other info call  
716-424-1100 days only, or  
write: Rochester Hamfest, Box  
1388, Rochester,  
NY 14603.
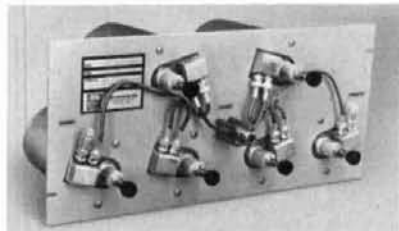
## DUPLEXERS

**NEW! VARI-NOTCH™** A state of the art design  
for the suppression of transmitter noise. A combination  
of the deepest notch, lowest loss, best passband roll-off.



The first 8 1/4" high rack mount that provides  
90 db at 0.5 MHz frequency separation,  
144-174 MHz band at 125 watts.



5 1/4" high rack mount models for 144-174 MHz,  
220 MHz, 406-512 MHz, 890-960 MHz. Frequency  
spacings to 0.5 MHz and power to 400 watts VHF.




85+ db at 0.5 MHz, 100 db at  
1.0 MHz separation for 1.5 db loss on  
models covering 132-174 MHz.

Band Pass, Notch, and Mobile duplexers are also available.

Write for detailed specifications, and for information on our convertible filter and expandable multicoupler lines



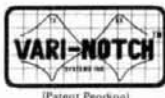**TX RX SYSTEMS, INC.,**  
P.O. Box 105,  
8625 Industrial Parkway, Angola, N.Y. 14006  
Phone: 716-549-4700



(Patent Pending)

## WANTED FOR CASH



4CX150	4CX1000	4-65	4-250
4CX250	4CX1500	4-125A	4-400
4CX300A	4CX3000		4-1000
4CX350A	4CX5000		304TL
	4CX10,000		
	5CX1500		

Other tubes and klystrons also wanted.  
See last month for other items available.

**The Ted Dames Company**

308 Hickory St. Arlington, N.J. 07032  
(201) 998-4246 Evenings (201) 998-6475

## SYNTHESIZERS

We have the worlds largest selection  
of synthesizers for receivers,  
transmitters and transceivers. For  
complete details see our 1/3 page  
ad in the April 1976 issue of this  
magazine or call or write for additional  
information. Phone orders  
accepted between 9 AM and 4 PM  
EDT. (212) 468-2720

**VANGUARD LABS**

196-23 JAMAICA AVENUE  
HOLLIS, N. Y. 11423



# THE BIG SIGNAL

UNADILLA  
"W2AU" BALUN



**\$1495**

- "UNADILLA ORIGINATED!"**
- World Famous Among Hammers
  - Awarded 7 Prices, Commendative
  - Radio Industry Why?
  - Each BALUN, Free PEP
  - Insulated
  - Lightning Arrestor
  - 500+ Pull-In Insulator
  - Needed

# THE OLD RELIABLE

REYCO  
"W2VS" ANTENNA COILS



**\$2195**

- "FREQUENCY-MATCHED PAIRS!"**
- Turn Your Antenna Into A Multi-Band Professional
  - Designed Receptor Why?
  - Precision Matched
  - Frequency Matched Pairs
  - Only 610 and 510 x 1 1/4 diameter
  - Rugged Over 300+ Pull
  - Weatherized
  - Models for 10, 15, 20, 40 Meters
  - Complete Instructions
  - Multi-Band Length-Tuning Data

DEALERS WANTED—NOW OVER 200 WORLD-WIDE

# the indispensable BIRD 43



Power Range	Frequency Bands (MHz)				
	2-30	25-50	100-250	200-500	400-1000
5 watts	—	5A	5C	5D	5E
10 watts	—	10A	10C	10D	10E
25 watts	—	25A	25C	25D	25E
50 watts	50H	50A	50C	50D	50E
100 watts	100H	100A	100C	100D	100E
250 watts	250H	250A	250C	250D	250E
500 watts	500H	500A	500C	500D	500E
1000 watts	1000H	1000A	1000C	1000D	1000E
2500 watts	2500H	—	—	—	—
5000 watts	5000H	—	—	—	—

THRULINE  
WATTMETER

MODEL	PRICE
43	\$120
Elements (Table 1) 2-30 MHz	42
Elements (Table 1) 25-1000 MHz	36
Carrying case for Model 43 & 6 elements	26
Carrying case for 12 elements	16

**Read RF Watts Directly.** (Specify Type N or SO239 connectors)  
0.45-2300 MHz, 1-10,000 watts ±5%, Low Insertion VSWR — 1.05.  
Unequaled economy and flexibility: Buy only the element(s) covering your present frequency and power needs, add extra ranges later if your requirements expand.



# BOMAR TWO METERS

Crystal Company  
Motorola HT 220 Crystals  
in Stock!

Novice Crystals (Specify Band Only)

In Stock: Standard / Icom / Heathkit / Ken / Clegg / Regency / Wilson / VHF Eng. / Drake — and others! \$4.50 @ Lifetime Guarantee; indicate make/model, xmit. frequency, rec. frequency.

Why Waste Watts? SWR - 1A \$29.95



**SWAN ELECTRONICS**  
A Division of Labco Corporation

SWR-1 guards against power loss! If you're not pumping out all the power you're paying for, our little SWR-1 combination power meter and SWR bridge will tell you so. You read forward and reflected power simultaneously, up to 1000 watts RF and 1:1 to infinity VSWR at 3.5 to 150 MHz.

Got it all tuned up? Keep it that way with SWR-1. You can leave it right in your antenna circuit.

**HF VERTICALS 10 through 80 METERS**

EFFICIENT TOP RING  
FIBERGLASS TRAP FORMS  
ENAMELED WIRE COILS  
SOLID ALUMINUM CAPACITORS  
NO TUNING REQUIRED  
FULL COMPRESSION CLAMPS  
OMNIDIRECTIONAL COVERAGE  
REINFORCED BASE  
MAST OR GROUND MOUNTING  
PRE-MARKED SECTIONS  
EASY ASSEMBLY  
SUPERIOR QUALITY

3 BAND 20-15-10 METERS MODEL 317-3 \$49.95  
4 BAND 40-20-15-10 METERS MODEL 317-4 \$69.95  
5 BAND 80-40-20-15-10 METERS MODEL 317-5 \$109.95

**Cushcraft**

# TELEX PROFESSIONAL HEADPHONES & HEADSETS

MODEL	C-610	SWL-610	C-1210	C-1320	CM-610	CM-1210	CM-1320	CM-1320S
Headphone Sensitivity	103dB SPL	103dB SPL	103dB SPL	105dB SPL	103dB SPL	103dB SPL	105dB SPL	105dB SPL
Ret. 0002 Dynes/cm <sup>2</sup> @ 1mW input, 1kHz	±5dB	±5dB	±3dB	±5dB	±5dB	±3dB	±5dB	±5dB
Headphone Impedance	32 ohms	2000 ohms	32 ohms	20 ohms	32 ohms	20 ohms	32 ohms	20 ohms
Microphone Frequency Response	—	—	—	—	50-8000 Hz	50-8000 Hz	50-8000 Hz	50-8000 Hz
Microphone Impedance	—	—	—	—	High	High	High	High
Microphone Sensitivity	—	—	—	—	-51dB	-51dB	-51dB	-51dB
Below 1 volt/microbar at 1kHz	—	—	—	—	±5dB	±5dB	±5dB	±5dB
Price:	\$9.95	\$11.65	\$28.30	\$37.90	\$42.80	\$56.90	\$68.30	\$54.50



Model C 610



Model C 1210



Model CM 1210



Model CM 1320S



Model C 610



Model CM 1210




Model C 1320

# TUFTS

Name \_\_\_\_\_ Call \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_  
Order: \_\_\_\_\_

Master Charge  
American Express

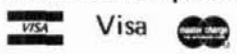

Radio Electronics  
209 Mystic Avenue  
Medford MA 02155  
(617) 395-8280

Check enclosed  Visa  Master Charge  American Express

**FREE Gift With Every Order!**

Credit card # \_\_\_\_\_  
Signature \_\_\_\_\_ Card expiration date \_\_\_\_\_

Prices FOB Medford MA. MA residents add 5% sales tax.

**Minimum \$3.00 for shipping & handling on ALL ORDERS.** Orders \$1200.00 & over deduct 5%.

HR

CALL TOLL FREE

# 1-800-228-4097

for Quality Ham Radio Products at Discount Prices

## YAESU SUPER DEALS - limited supply

### DEAL #1

Buy a Yaesu FT-301 (dial) for only \$769.00 and you get a FP-301 AC Power Supply and a CW Filter absolutely FREE. Total Value \$966.00  
SAVE \$197.00

### DEAL #2

Buy a Yaesu FT-301d (digital) for only \$935.00 and you get a FP-301 AC Power Supply and a CW Filter absolutely FREE. Total Value \$1132.00  
SAVE \$197.00

Kenwood  
Yaesu  
Drake  
Hy-Gain  
ICOM  
Ten-Tec  
Dentron  
Swan  
Tempo  
Wilson  
Midland  
Bearcat  
CDE Rotors  
ETO Alpha

Call for similar savings on all these excellent lines



## Communications Center

The Radio Store

443 N. 48th, Lincoln, Nebraska 68504

In Nebraska Call (402)466-8402



## VHF-FM RECEIVER

Compact — High Performance

## LOW COST KIT

Model 144-5

Sensitivity under .15  $\mu$ V SINAD

# \$59<sup>95</sup>



### ACCESSORIES

Handsome Compact Aluminum Case  
\$9.95

Speaker / Control Kit  
\$19.95

• 5 channels, remote switchable • 6 pole crystal filter provides better than 75dB adjacent channel rejection • Image rejection better than 75 dB; all other spurious better than 100 dB • Audio output 250 mW • Compact — 2.35 x 4" board, ideal for pocket receiver or can be built into existing equipment, home-brew transceiver • Operates from 8-20 VDC; 15 mA nominal drain, squelched



Electronic Signal Products, Inc.

2250 G Landmeier Rd., Elk Grove, IL 60007 (312) 364-0080

Also models for 29, 50, 220 and 440 Mhz

Commercial versions for other frequencies can also be supplied

Electronic Signal Products, Inc.  
2250 G Landmeier Rd., Elk Grove, IL 60007

Name \_\_\_\_\_ Call \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

BANK AMERICARD



Please ship \_\_\_\_\_

VISA

Please ship \_\_\_\_\_

Illinois residents add 5% sales tax

144-5 receiver kits at \$59.95 each

29  50  220 receiver kits at \$59.95 each

440 kit at \$69.95

Check or money order for \$ \_\_\_\_\_ enclosed

Charge my VISA/BankAmericard # \_\_\_\_\_

Card expires \_\_\_\_\_ Signature \_\_\_\_\_

## ENERGY CRISIS SOLVED!

Personal energy crisis? Get precious RF on DX target with World Record Breaking antenna that won W6TYP the QRP ARC 1,000,000 miles/watt award.

### THE JOYSTICK VFA

(Variable freq. anti gives low angle, omnidirectional, harmonic free radiation on all bands 160 thru 10) - MARS and receive on all BC & SW.

1000's of glowing reports in our files of the VFA in use, often in poor QTH and/or under ORP. contests, etc.

SYSTEM 'A' \$75.00

250W P.E.P. &/or Receiving Only

SYSTEM 'J' \$99.00

500W P.E.P. &/or Improved Q Factor Receive

Air Mail cost included. (Each system 3 sections easily assembled to make unit 7' 6" long. Matching ATU). Not only will you save space but you will save \$\$\$ at present low exch. rate and by buying direct UK manu. Rush your order - Mastercharge or check, or ask for brochure.

PARTRIDGE (HR)  
ELECTRONICS LTD.

Broadstairs, Kent, England  
Tel. Thanet 62535

G3CED

G3VFA

## RADIO WORLD

CENTRAL NEW YORK'S FASTEST GROWING HAM DEALER



FT-101E

ICOM IC-211

Featuring - Yaesu, ICOM, Drake, Atlas, Dentron, Ten-Tec, Swan, Regency, Standard, Tempo, KLM, Hy-Gain, Mosley, Larsen, Midland, Wilson, Southwest Tech Products. We service everything we sell! Write or call for quote. YOU WON'T BE DISAPPOINTED.

We are just a few minutes off the NYS Thruway (I-90) - Exit 32.

## RADIO WORLD

ONEIDA COUNTY AIRPORT

TERMINAL BUILDING

ORISKANY, NY 13424

315-337-2622

Warren  
K2IXN

Bob  
WA2MSH





# This symbol is important to amateur radio... present and future. Watch for it.

## ARMA STATEMENT OF PURPOSE

The Radio Amateur Manufacturers Association is an organization comprised of individuals and companies whose products are intended to be sold to amateur radio operators throughout the world.

As a representative group of importers exporters, manufacturers and dealers in amateur equipment, ARMA is the official spokesman for this highly specialized industry, and has a vested interest in the fostering of continued growth of the radio amateur service, worldwide.

To further these goals, ARMA disseminates information from its headquarters on various proposals and actions that may affect its members, represents the industry in meetings, and on various committees to develop a favorable public attitude toward amateur radio, directs and advises the industry as to its best interests, and interprets industry wide technical standards as required. ARMA supports amateur radio worldwide through club, government and industry liasons.

## MEMBERSHIP ROSTER


CLEGG COMMUNICATIONS CORP.  
COMMUNICATIONS POWER, INC.  
COWAN PUBLISHING CORP.  
DENTRON RADIO CO., INC.  
GENERAL LINEAR SYSTEMS  
HAL COMMUNICATIONS CORP.  
HAM RADIO PUBLICATIONS  
HY-GAIN ELECTRONICS CORP.  
HAM RADIO CENTER, INC.  
DIGITAL ELECTRONICS INC.  
SUPEREX ELECTRONICS CORP.  
RADIO WORLD, INC.  
RUSH ELECTRONICS, INC.  
THE RADIO PLACE  
SPECTRUM COMM.  
EHRHORN TECH. OPERATIONS  
PAL ELECTRONICS

ICOM EAST, INC.  
KLM ELECTRONICS, INC.  
LUNAR ELECTRONICS  
73 MAGAZINE  
SPECTRONICS, INC.  
SWAN ELECTRONICS  
TEN-TEC, INC.  
TRIO-KENWOOD COMMUNICATIONS, INC.  
VHF ENGINEERING  
WESTCOM ENGINEERING  
YAESU ELECTRONICS CORPORATION  
MIDLAND INTERNATIONAL CORP.  
THE BASE STATION, INC.  
AMERICAN RADIO RELAY LEAGUE  
ANIXTER-MARK  
ATLAS RADIO COMPANY  
CIR INDUSTRIES, INC.

Comments and suggestions are invited from companies and individuals concerned with the present and future status of amateur radio. Such correspondence and requests for mem-

bership information should be referred to: Bernard Tower, Sec. Yaesu Electronics Corporation, 15954 Downey Avenue, Suite #19, Paramount, CA 90723

 C&K'S DPDT PUSH BUTTON SWITCH. \$1.50	<b>50 ohm COAX</b> RG 174 U 50 FT. \$2.75	<b>.1 ohm FIVE WATT</b> RESISTOR 5/\$1.00	 50-239 65¢ PL-259 65¢ 10/\$6.00 MIX/MATCH	<b>CIGARETTE LIGHTER</b> PLUG  79¢	<b>1N914</b> NEW HOUSE MARKED 100 for \$2.95	<b>NYLON CABLE TIES</b>  4 INCH 100/\$1.00 6 INCH 100/\$1.75
<b>1N4007</b> 1000 PIV AT 1 AMP NEW 8¢ PRIME	<b>toggle switch</b> P-C OR PANNEL MOUNT MINI SWITCH SPDT \$1.00 10/\$8.	<b>HEAT SHrink</b> ASSORTED SIZES 10 FOOT BUNDLE 95¢	<b>MJE3055</b> 90 WATTS 60VCE 10 AMPS NPN 2/\$1.50	<b>MOLEX PINS</b>  200 EACH \$1.95 1000 EACH \$7.95	<b>MALLOY SIGNAL</b> ELECTRONIC Signal Model SCR2-N 6 TO 28 VOLTS \$5.50	<b>30 AWG wire wrap</b> LT. GREEN DK. GREEN RED 100 FT. \$2.50
 <b>CHONERICS PAD</b> HAS A COMMON TERMINAL AND A TERMINAL FOR 0-9 CANCEL AND SEND. A GREAT VALUE FOR \$4.50	 <b>ULTRASONIC TRANSDUCER</b> WITH RCA JACK 37 KHZ \$1.95 40 KHZ \$1.95	<b>KEYBOARDS</b> THESE KEYBOARDS ARE FACTORY NEW IN THE BOX. FORTY-SEVEN KEYS, MOS ENCODED, DUAL MODE AND EBCDIC. (EXTENDED BINARY CODED DECIMAL CODE.) THE BUTTON KEY TOPS ARE GRAY AND WHITE. COMPLETE DOCUMENTATION IS GIVEN WITH EACH KEYBOARD, EASY TO MOUNT. (BRACKET INCLUDED) THIS FINE QUALITY KEYBOARD, WITH ORIGINAL COST OF \$96.00, IS NOW OFFERED TO YOU FOR ONLY... <b>\$12.95</b>		TYPE WATT IC VCEO <b>MJ1000</b> NPN 90 8 60 \$1.25 <b>MJ900</b> PNP 90 8 60 \$1.65		
 <b>SOLDER TAIL IC SOCKETS</b> 8 PIN \$2.20 14 PIN \$1.16 16 PIN \$1.18 24 PIN \$1.35 40 PIN \$1.85	 <b>MDA 970-2 BRIDGE</b> 100 PIV 4 AMP. \$1.75	 THIS ASSORTMENT OF POTS ARE NEW. WE JUST HAVE NOT HAD TIME TO SORT THEM. ALL ARE PC TYPE. 10/\$1.00	 <b>NICADS</b> 4 'AA' SIZE CELL 500 MILL. AT 5 V \$3.95	 <b>THUMBWHEEL SWITCH</b> BCD SINGLE MOUNT 12 POSITION 0-11 \$1.25 5/\$6.00	 <b>CRYSTAL OSCILLATOR</b> 4 MHz OSC. DIP SQU.WAVE Vcc 5V \$3.50	
 <b>WIREWRAPE IC SOCKETS</b> 14 PIN \$3.35 16 PIN \$3.38 24 PIN \$3.75 40 PIN \$3.95	 <b>115 VOLT OUTLET WITH SWITCH TAKES A 1X2 7/16IN.HOLE</b> \$1.75 3/\$2.00	 <b>T-TONE PAD HOUSING</b> BLACK ONLY \$2.75	 BNC-F/BNC-F UG-914U \$2.00	 BNC-F/UHF-M UG-273U \$2.50	 BNC-M/UHF-F UG-255U \$3.00	
 <b>Variable Power Supply</b> *12-28V ADJUSTABLE POWER SUPPLY AT 28V 250MA THERMALLY PROTECTED. * 5-12V ADJUSTABLE POWER SUPPLY AT 12V 500MA ADJUSTABLE POT. ALL PARTS INCLUDED *TRANSFORMER *PC BOARD *POT & RESISTOR *HEAT SINK *OSC. SUPPRESSION CAP. *DIODES *1000UF CAP. *INSTRUCTIONS *REGULATOR 7805 OR 7812 *HARDWARE P51 5-12V \$5.95 P52 12-28V \$5.95	<b>MARLIN P JONES &amp; ASSOCIATES</b> PO BOX 9023 RIVIERA BEACH, FLORIDA 33404 (305) 848-8236		*FLA. RESIDENTS ADD. 4¢ *MASTER CHARGE AND VISA ACCEPTED *ADD \$1.00 FOR ORDERS UNDER \$10.00 *USA ORDERS ADD 5¢ FOR SHIPPING *FOREIGN PLEASE ALLOW SUFFICIENT POSTAGE			



# omni-j

## ANTENNAS

MODEL OJA-146

TWO METER AMATEUR BAND 146-148MHz

- NO GROUND PLANE REQUIRED
- USE FIXED, MOBILE, OR PORTABLE
- 5dB GAIN OVER ISOTROPIC IN MOST MOBILE APPLICATIONS
- OVERALL LENGTH: LESS THAN 64 INCHES
- COLLAPSIBLE TO 22 INCHES. MAY BE PACKED IN SUITCASE FOR THOSE OUT-OF-TOWN TRIPS
- STEEL WHIP AND ADAPTER INCLUDED FOR MOBILE AND FIXED APPLICATIONS
- VSWR: LESS THAN 1.2:1

**PRICE \$29.95** UPS Prepaid  
220 MHz — \$27.95    450 MHz — \$27.95

### MADISON

#### ELECTRONICS SUPPLY, INC.

1508 McKINNEY HOUSTON, TEXAS 77002  
713/658-0268    Nites 713/497-5683

# New!

Please don't squeeze the  
**Feather Touch.**



**only \$69.95**

### Kantronics Feather Touch keyer

Why keep wrestling with the mechanics in your electronic keyer?

The Kantronics Feather Touch keyer has moved the "state-of-the-art" in electronic keying years ahead! By engineering a truly electronic, electronic keyer, we've eliminated the most cumbersome part of sending Morse code: the adjusting and readjusting of mechanical connections.

The Feather Touch responds to your lightest touch, freeing you from slapping, sloshing or squeezing. Order your Feather Touch now, or write for information and a list of authorized dealers.

At Kantronics, we think sending Morse code should be an art, not an effort.

**Order now!**

## KANTRONICS

The Lightweight Champs.

1202 East 23rd St  
Lawrence, Kansas 66044    Telephone 913 842 7745

When the winter winds blow you need...

# TOWER POWER by TRISTAO

Superior Quality and Construction at a price you can afford.

Tristao is a pioneer. Years of designing and manufacturing show in structural performance and practical pricing. Certified welded construction; sand-blasted surfaces; hot-dipped galvanized; heavy duty for capacity, strength, safety. Send for FREE Catalog.

Dealer Inquires always invited.

## Self-supporting or Guyed TOWERS

### CZ SERIES

Self-supporting 38' to 84' for most tri-band beams in 60 mph winds. Equipped with heavy duty winch.

### CTL SERIES

Guyed crank-up 18' thru 105' for tri-band beams to 8 sq. ft. Takes CDR HAM II and similar rotors. Complete installation packages available.

## TRISTAO MAST MASTER

Self-supporting  
Rotating - Crank-up

### SUPER AND STANDARD MINI-MASTS

Supports 10 sq. ft. antenna in 50 mph winds. Self-supporting. With winch and cable. Models from 40' to 67'.

### FULL-LINE OF MINI-MAST ACCESSORIES

### NEW EXCLUSIVE ROTOR BASE

For standard CDE or others including HAM II. Entire mast is rotated from ground level.

### CUSTOM TOWERS BUILT TO YOUR SPECIFICATIONS

Masts priced from \$198.50

All specs available on request.

## TRISTAO TOWER

Division of Palmer Industries, Inc.

415 E. 5th St. - P.O. Box 115  
Hanford, CA 93230 / Ph. (209)582-9016

Send me your complete catalog.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_

More Details? CHECK - OFF Page 126



# Regency

the first name in solid state

## INTRODUCES THE VERSATILE NEW



# HR-312

- More Channels...at the flip of a switch  
Unlock the unique mode switch and 12 channels become 144
- More Sensitivity, Less Interference  
.25  $\mu$ V Sensitivity plus 75 db adjacent channel selectivity and 70 db image rejection
- More Power Out  
35 watts nominal with a minimum of 30 watts across the band

... for a lot less

## \$269<sup>00</sup>

Amateur Net



© 1976

REGENCY ELECTRONICS, INC. 7707 Records Street  
Indianapolis, Indiana 46226

## THE FM LEADER

2 METER

220 MHz

6 METER

440 MHz



## Ham Radio's guide to help you find your local

### Alabama

#### LONG'S ELECTRONICS

2808 7TH AVENUE SOUTH  
BIRMINGHAM, AL 35202  
800-633-3410

Call us Toll Free to place your order

### Alaska

#### RELIABLE ELECTRONICS

3306 COPE STREET  
ANCHORAGE, AK 99503  
907-279-5100

Kenwood, Yaesu, DenTron, Wilson,  
Atlas, ICOM, Rohn, Tri-Ex.

### Arizona

#### HAM SHACK

4506 A NORTH 16TH STREET  
PHOENIX, AZ 85016  
602-279-HAMS

Serving all amateurs from  
beginner to expert.

#### KRYDER ELECTRONICS

5520 NORTH 7TH AVENUE  
NORTH 7TH AVE. SHOPPING CTR.  
PHOENIX, AZ 85013  
602-249-3739

We service what we sell.

#### POWER COMMUNICATIONS

6012 NORTH 27th AVE.  
PHOENIX, AZ 85017  
602-242-6030

Arizona's #1 Ham Store.  
Kenwood, Drake, ICOM & more.

#### QSA 599 AMATEUR RADIO CENTER

11 SOUTH MORRIS STREET  
MESA, AZ 85202  
602-833-8051

Eimac Distributor. New & Used  
Equipment, Parts - Surplus tool!

### California

#### C & A ELECTRONIC ENTERPRISES

2529 EAST CARSON ST.  
P. O. BOX 5232  
CARSON, CA 90745  
213-834-5868

Not the Biggest, but the Best —  
since 1962.

#### COMMUNICATIONS CENTER

705 AMADOR STREET  
VALLEJO, CA 94590  
707-642-7223

Who else has a Spectrum  
Analyzer?

#### HAM RADIO OUTLET

999 HOWARD AVENUE  
BURLINGAME, CA 94010  
415-342-5757

Visit our stores in Van Nuys  
and Anaheim.

#### QUEMENT ELECTRONICS

1000 SO. BASCOM AVENUE  
SAN JOSE, CA 95128  
408-998-5900

Serving the world's Radio Amateurs  
since 1933.

#### TOWER ELECTRONICS CORP.

24001 ALICIA PARKWAY  
MISSION VIEJO, CA 92675  
714-768-8900

Authorized Yaesu Sales & Service.  
Mail orders welcome.

### Colorado

#### MILE-HI COMMUNICATIONS, INC.

1970 SOUTH NAVAJO  
DENVER, CO 80223  
303-936-7108

Rocky Mountain's newest  
ham store. Lee Tingle KØLT.

### Connecticut

#### ARCOMM ELECTRONICS

2865 MAIN STREET  
BRIDGEPORT, CT 06606  
203-335-9850

Featuring Ten-Tec and DenTron.

#### AUDIOTRONICS INC.

18 ISAAC STREET  
NORWALK, CT 06850  
203-838-4877

The Northeast's fastest growing  
Ham Dept. dedicated to service.

### Florida

#### AGL ELECTRONICS, INC.

1800-B DREW ST.  
CLEARWATER, FL 33515  
813-461-HAMS

West Coast's only full service  
Amateur Radio Store.

#### MARC'S

CENTRAL EQUIPMENT CO., INC.  
18451 W. DIXIE HIGHWAY  
NORTH MIAMI BEACH, FL 33160  
305-932-1818

See Marc, WD4AAS, for complete  
Amateur Sales & Service.

#### RAY'S AMATEUR RADIO

1590 US HIGHWAY 19 SO.  
CLEARWATER, FL 33516  
813-535-1416

West coast's only dealer:  
Drake, Icom, Cushcraft, Hustler.

### Illinois

#### ERICKSON COMMUNICATIONS, INC.

5935 NORTH MILWAUKEE AVE.  
CHICAGO, IL 60646  
312-631-5181

Hours: 9:30-9 Mon. & Th.; 9:30-5  
Tu, Wed, Fri.; 9-3 Sat.

#### KLAUS RADIO, INC.

8400 NORTH PIONEER PARKWAY  
PEORIA, IL 61614  
309-691-4840

Let us quote your Amateur needs.

#### SPECTRONICS, INC.

1009 GARFIELD STREET  
OAK PARK, IL 60304  
312-848-6777

Chicagoland's Amateur Radio  
leader.

### Indiana

#### HOOSIER ELECTRONICS, INC.

P. O. BOX 2001  
TERRE HAUTE, IN 47802  
812-238-1456

Ham Headquarters of the Midwest.  
Store in Meadows Shopping Center.

#### KRYDER ELECTRONICS

GEORGETOWN NORTH  
SHOPPING CENTER  
2810 MAPLECREST RD.  
FORT WAYNE, IN 46815  
219-484-4946

We service what we sell. 10-9 T,  
TH, F; 10-5 W, SAT.

### Iowa

#### BOB SMITH ELECTRONICS

RFD #3, HIGHWAY 169 and 7  
FT. DODGE, IA 50501  
515-576-3886

For an EZ deal.

### Kansas

#### ASSOCIATED RADIO

8012 CONSER P. O. B. 4327  
OVERLAND PARK, KS 66204  
913-381-5901

Amateur Radio's Top Dealer.  
Buy — Sell — Trade

*Dealers - You should be here too! Contact Ham Radio today for complete details.*

# Amateur Radio Dealer

## Kentucky

**COHOON AMATEUR SUPPLY**  
HIGHWAY 475  
TRENTON, KY 42286  
502-886-4535  
Yaesu, Ten-Tec, Tempo, DenTron.  
Our service is the BEST.

## Maryland

**COMM CENTER, INC.**  
9624 FT. MEADE ROAD  
LAUREL PLAZA RT. 198  
LAUREL, MD 20810  
301-792-0600  
New & Used Amateur Equipment.  
Wilson, Ten-Tec, R. L. Drake, Tempo

**PROFESSIONAL  
ELECTRONICS CO., INC.**  
1710 JOAN AVENUE  
BALTIMORE, MD 21234  
301-661-2123  
A professional place for amateurs.  
Service-sales-design.

## Massachusetts

**TUFTS RADIO ELECTRONICS**  
209 MYSTIC AVENUE  
MEDFORD, MA 02155  
617-395-8280  
New England's friendliest  
ham store.

## Michigan

**RADIO SUPPLY & ENGINEERING**  
1207 WEST 14 MILE ROAD  
CLAWSON, MI 48017  
313-435-5660  
10001 Chalmers, Detroit, MI  
48213, 313-371-9050.

## Minnesota

**ELECTRONIC CENTER, INC.**  
127 THIRD AVENUE NORTH  
MINNEAPOLIS, MN 55401  
612-371-5240  
ECI is still your best buy.

**PAL ELECTRONICS INC.**  
3452 FREMONT AVE. NORTH  
MINNEAPOLIS, MN 55412  
612-521-4662  
The Midwest's Fastest Growing  
Ham Dealer.

## Missouri

**HAM RADIO CENTER, INC.**  
8340-42 OLIVE BLVD.  
ST. LOUIS, MO 63132  
800-325-3636  
See Our Ads  
In This Issue.

**MIDCOM ELECTRONICS, INC.**  
2506 SO. BRENTWOOD BLVD.  
ST. LOUIS, MO 63144  
314-961-9990  
At Midcom you can try before you  
buy!

## Nebraska

**COMMUNICATIONS CENTER, INC.**  
443 NORTH 48 ST.  
LINCOLN, NE 68504  
800-228-4097  
Yaesu, Drake, Tempo, Swan,  
HyGain - call Toll Free

## New Hampshire

**EVANS RADIO, INC.**  
BOX 893, RT. 3A BOW JUNCTION  
CONCORD, NH 03301  
603-224-9961  
Icom, DenTron & Yaesu dealer.  
We service what we sell.

## New Jersey

**ATKINSON & SMITH, INC.**  
17 LEWIS ST.  
EATONTOWN, NJ 07724  
201-542-2447  
Ham supplies since "55".

**RADIOS UNLIMITED**  
1760 EASTON AVENUE  
SOMERSET, NJ 08873  
201-469-4599  
New Jersey's newest  
complete Amateur Radio center

## New Mexico

**ELECTRONIC MODULE**  
601 N. TURNER  
HOBBS, NM 88240  
505-397-3012  
Yaesu, Kenwood, Swan, DenTron,  
Tempo, Atlas, Wilson, Cushcraft

## New York

**ADIRONDACK RADIO SUPPLY, INC.**  
185 W. MAIN STREET  
AMSTERDAM, NY 12010  
518-842-8350  
Yaesu dealer for the Northeast.

**GRAND CENTRAL RADIO**  
124 EAST 44 STREET  
NEW YORK, NY 10017  
212-682-3869  
Drake, Atlas, Ten-Tec, Midland,  
Hy-Gain, Mosley in stock

**RADIO WORLD**  
ONEIDA COUNTY AIRPORT  
TERMINAL BLDG.  
ORISKANY, NY 13424  
315-337-2622  
New & Used ham equipment.  
See Warren K2IXN or Bob WA2MSH.

## Ohio

**AMATEUR RADIO  
SALES & SERVICE INC.**  
2187 E. LIVINGSTON AVE.  
COLUMBUS, OH 43209  
614-236-1625  
Antennas for all services.

**UNIVERSAL AMATEUR RADIO, INC.**  
1280 AIDA DRIVE  
REYNOLDSBURG, (COLUMBUS) OH  
43068  
614-866-HAMS  
Drake, Yaesu, Ten-Tec, KDK, Wilson,  
DenTron, Tempo, Sigma.

## Oklahoma

**RADIO STORE, INC.**  
2102 SOUTHWEST 59th ST.  
(AT 59th & S. PENNSYLVANIA)  
OKLAHOMA CITY, OK 73119  
405-682-2929  
New and used equipment —  
parts and supply.

## Oregon

**PORTLAND RADIO SUPPLY CO.**  
1234 S.W. STARK STREET  
PORTLAND, OREGON 97205  
503-228-8647  
Second location, 1133 S. Riverside  
Avenue, Medford, OR 97501.

## Pennsylvania

**ARTCO ELECTRONICS**  
302 WYOMING AVENUE  
KINGSTON, PA 18704  
717-288-8585  
The largest variety of semiconduc-  
tors in Northeastern Pennsylvania

**ELECTRONIC EXCHANGE**  
136 N. MAIN STREET  
SOUDERTON, PA 18964  
215-723-1200  
New & Used Amateur Radio  
sales and service.

**"HAM" BUERGER, INC.**  
68 N. YORK ROAD  
WILLOW GROVE, PA 19090  
215-659-5900  
Communications specialists.  
Sales and service.



# HAM MART

HAMTRONICS, DIV. OF  
TREVISE ELECT.  
4033 BROWNSVILLE ROAD  
TREVISE, PA 19047  
215-357-1400  
Same location for 25 years.

## Tennessee

GERMANTOWN AMATEUR SUPPLY  
3203 SUMMER AVE.  
MEMPHIS, TN 38112  
800-238-6168  
No monkey business. Call  
Toll Free.

## Texas

AGL ELECTRONICS  
3068 FOREST LANE, SUITE 309  
DALLAS, TX 75234  
214-241-6414 (within Texas)  
Out-of-State, Call our toll-free  
number 800-527-7418.

HARDIN ELECTRONICS  
5635 E. ROSEDALE  
FT. WORTH, TX 76112  
817-461-9761  
Your Full Line Authorized  
Yaesu Dealer.

## Wisconsin

AMATEUR  
ELECTRONIC SUPPLY, INC.  
4828 WEST FOND du LAC AVENUE  
MILWAUKEE, WI 53216  
414-444-4200  
Open Mon & Fri 9-9, Tues, Wed,  
Thurs, 9-5:30, Sat, 9-3.

## Washington

AMATEUR RADIO SUPPLY CO.  
6213 13TH AVENUE SOUTH  
SEATTLE, WA 98108  
206-767-3222  
First in Ham Radio in Washington  
Northwest Bird Distributor

## Wyoming

DENCO COMMUNICATIONS CENTER  
1728 EAST 2nd STREET  
CASPER, WY 82601  
307-234-9197  
Sales, Service to Wyoming  
and the Northern Rockies.

# ALL-MODE VHF amplifiers

FOR BASE STATION & REPEATER USE



MODEL	INPUT	OUTPUT	PRICE
V70	10-20W	60-70W	\$298
V71	1-5W	60-70W	\$329
V130	25-40W	110-130W	\$389
V131	1-5W	110-130W	\$419
V135	5-10W	110-130W	\$419
V180	10-15W	180-200W	\$525
Universal 19" Rack Mount			\$25


\* All units: Harmonics exceed  
-60 dB specification of FCC  
R&O 20777

- ☆ 143-149 MHz No Tuning
- ☆ AM - FM - CW - SSB
- ☆ Low Harmonics
- ☆ Heavy Duty
- ☆ No Power Supply Needed
- ☆ Illuminated Panel Meter
- ☆ +13.5V/3 Amp Socket
- ☆ 115 or 230V AC
- ☆ 60dB Spurious
- ☆ Fully Protected Output
- ☆ Internal T/R Switch
- ☆ U.S. Manufactured
- ☆ 19" Rack Panel Option
- ☆ Size 8-1/2 x 13 x 7" H

Only two things are needed to put this power house on the air with your handy-talky or mobile transceiver: a two foot piece of coaxial cable and a 115 or 230 volt AC outlet. That's all. You do not need anything else. The mobile transceiver can be powered directly from the accessory socket located in the rear panel of the RFPL amplifier. It puts out +13.5 volts at 3 amperes. This is sufficient for powering most 15 watt transceivers.



DEALER INQUIRIES INVITED

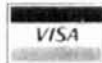

RF POWER LABS, INC.

11013-118th Place N.E. • Kirkland, Washington 98033 • Telephone: (206) 822-1251 • TELEX No. 32-1042

### DIPOLE ANTENNA CONNECTOR



HYE-QUE (HQ-1) dipole connector has coax SO-239 socket molded into glass fitted plastic body to accept coax PL-259 plug on feedline. Drip-cap keeps coax fittings dry. Instructions included. Guaranteed. At your dealers or \$4.95 postpaid. Companion insulators 2/\$.99.

BUDWIG MFG. Co. PO Box 97H, Ramona, CA 92065

### K-ENTERPRISES

Frequency Counters  
Prescalers  
Marker & Peaking  
Generators  
Power Supplies  
Amplifiers  
Frequency  
Standards

Write for Free Catalog  
Box 410 (Pump Sta. Rd.) Fairland, OK 74343  
Phone: 918-676-3752

## CFP ... FOR ALL YOUR AMATEUR NEEDS

ATLAS  
CUSHCRAFT  
DENTRON



DRAKE  
TEMPO  
TEN TEC

\*YAESU FT-101EX

REMEMBER, YOUR DEALER IS RESPONSIBLE FOR WARRANTY REPAIRS DURING WARRANTY PERIOD.

Mail Orders accepted. N. Y. residents add sales tax.

Transmitter sales to licensed amateurs only.



CFP COMMUNICATIONS

211 NORTH MAIN STREET  
HORSEHEADS, N. Y. 14845  
PHONE: 607-739-0187



Store Hours  
Tues. to Fri. 10-6 p.m.  
Sat. 10-4 p.m.  
Fri. & Sat. subject to  
Hamfest weekends  
Closed Sun. & Mon.



**There's  
nothing!  
like it**

**RADIO AMATEUR  
callbook**

*Respected worldwide as  
the only complete authority  
for radio amateur  
QSL and QTH information.*

The **U. S. Callbook** has over 300,000 W & K listings. It lists calls, license classes, names and addresses plus the many valuable back-up charts and references you come to expect from the **Callbook**.

Specialize in DX? Then you're looking for the **Foreign Callbook** with almost 300,000 calls, names and addresses of amateurs outside of the USA.

**U.S. Callbook \$14.95**

**Foreign Callbook \$13.95**

Order from your favorite electronics dealer or direct from the publisher. All direct orders add \$1.50 for shipping. Illinois residents add 5% Sales Tax.

**RADIO AMATEUR  
callbook INC.**  
Dept. E 925 Sherwood Drive  
Lake Bluff, Ill. 60044

**Our portable 2-meter radio  
goes anywhere you do!!!**

**Wilson ... WE-800**

**800 channel - synthesized  
1 and 12 Watt RF Output**

Anywhere you go . . . camping, boating, sporting events, ham-fests . . . or just "talking around town" in your car, the small and lightweight WE-800 portable is with you. Designed as an all-purpose 12 watt mobile or 1 watt portable unit, it's loaded with features to satisfy even the most discriminating amateur.

"800" is for channels, from 144-148 MHz in 5 KHz steps, up or down 500 KHz for your local repeater. There are also provisions for 5 pre-programmed frequencies of your choice.

Additional features: • Operates on rechargeable internal Nicad batteries (not included) • Built-in S-meter/output indicator • Hi-Lo power switch • Connectors for external antenna, speaker and power • Mounting bracket/handle, flex rubber antenna and 12 VDC power cord furnished.



**GENERAL SPECIFICATIONS:**

• Frequency Range: 144,000 - 147,995 MHz • No. of Channels: 799 @ 5 KHz or 399 @ 10 KHz • Operating Mode: Direct frequency modulation • Type of Communication: Simplex or transmitter offset  $\pm 600$  kHz • Operating Voltage: 13.6 VDC negative ground (10 to 15 VDC range) • Current Drain: Transmit: 290 mA @ 1 watt output, 2 amps @ 12 watts output. Receive: 45 mA squelched, 250 mA at full AF rated output • Antenna impedance: 50 ohms nominal • Size: 8-1/4 x 6-3/4 x 1-7/8 inches (209.6 x 171.5 x 47.6 mm) • Weight: 1 lb. 15 oz. (4.13 Kg): (3 lb. 11 oz. (8.16 Kg) with batteries • Frequency Determination Method: C-MOS phase locked loop • Offset Option: Two optional offset TX positions also available.

**PERFORMANCE SPECIFICATIONS:**

**TRANSMITTER:** • RF Output: Hi-12W, Lo-1W • Frequency Stability: 001% -10°C ~ +60°C • Local Oscillator: Simplex, 21.4 MHz; Offset +600 kHz, 22 MHz; -600 kHz, 20.8 MHz (Options for two more offsets other than 600 kHz) • Harmonics & Spurious: More than 60 dB below carrier • Deviation:  $\pm 5$  kHz • Audio Response: +1; -3 dB of 6 dB/Octave. Pre-emphasis characteristics from 300 to 3000 Hz.  
**RECEIVER:** • Receiving System: Double conversion Superheterodyne • First Local Oscillator: PLL output of (F-21.4 MHz) • First IF: 21.4 MHz (with 2 pole monolithic filter) • Second IF: 455 kHz (with a ceramic filter) • Stability: 001% -10°C ~ +60°C • Sensitivity: 3  $\mu$ V for 20 dB quieting • Squelch Sensitivity: 2  $\mu$ V • Spurious & Image Rejection: Better than 80 dB • Intermodulation: 60 dB • Selectivity:  $\pm 6$  kHz at 3 dB,  $\pm 15$  kHz at 80 dB • Channel Spacing: 15 kHz • Audio Output: 2 W (10% distortion to 4 ohm)

*For the "best" in amateur antennas, crank-up tower and  
2 meter radio equipment, depend on WILSON . . .  
demand it from your nearest amateur dealer.*



**Wilson Electronics Corp.**

P.O. BOX 19000 • LAS VEGAS • NEVADA • 89119 • (702) 739-1931 • TELEX 684-522

**NEW AMATEUR DEALERS NEEDED IN CERTAIN AREAS  
... WRITE FOR DETAILS!!!**

# HAMVENTION<sup>®</sup>

April 28, 29, 30.  
At Hara Arena,  
Dayton, Ohio

This year's Dayton Hamvention promises to be the biggest and best yet!

Start with more exhibit and flea market space than before. Then: • informative programs • new products • technical sessions • ARRL and FCC forums • special and group meetings • ladies' programs • transmitter hunts • total value of prizes exceeds \$15,000.

Top it all off with the Grand Banquet, Saturday evening April 29.

# '78

If you have registered within the last 3 years you will receive a program and information brochure in March.

Admission \$3 in advance, \$4 at the door. Saturday night banquet \$8 per person. Flea Market space \$5 to \$8 per space depending on number of spaces. At door only. Make check payable to: Dayton Hamvention, P.O. Box 44, Dayton, Ohio 45401.

For special hotel/motel rates and reservations information write to above address. Inquiries: call 513-854-4126.

See you at the world's largest Ham Convention!

## FREE! NEW '78 AMATEUR RADIO CATALOG

Choose from the top names in selected ham equipment. Plus—get the full details on Clegg's unique purchase plans for Drake/Yaesu/KLM/Dentron/Alpha/Microwave modules/Atlas and other quality products.

Phone toll-free today for your new Clegg catalog!

**1-800-233-0250**

In Pennsylvania call collect  
717-299-7221.

Clegg Communications Corp., 1911  
Old Homestead Lane, Greenfield  
Industrial Park East,  
Lancaster, PA 17601.



# Clegg

FOR FASTER SERVICE!

## D & V RADIO PARTS

VARIABLE & TRIMMER CAPACITORS-HF CHOKES-AIR WOUND COILS-TOROIDS-FEED THRU'S-TUBULAR TRIMMERS-KNOB-WIRE-COUPPLINGS-TRANSMATCH COMPONENTS.

No minimum order-low cost shipping.  
First class stamp for complete flyer.  
12805 W. SARLE, FREELAND, MICHIGAN 48623

## MILITARY SURPLUS WANTED

Space buys more and pays more. Highest prices ever on U.S. Military surplus, especially on Collins equipment or parts. We pay freight. Call collect now for our high offer. 201 440-8787.

**SPACE ELECTRONICS CO.**  
div. of Military Electronics Corp.  
35 Ruta Court, S. Hackensack, N.J. 07606

## NEW ELECTRONIC PARTS

IC'S - TRANSISTORS - PROTOBOARDS - RESISTORS  
CAPACITORS - DIODES - SWITCHES - CONNECTORS  
VOLTAGE REGULATORS - CABINETS - HEAT SINKS  
FUSES & MUCH MORE--STAMP BRINGS CATALOG

## SPECIALS

### KEYBOARD ENCLOSURES

TWO SIZES	W	D	H	PRICE
	14	8.3	3	\$13.50*
	14	11.3	3	\$14.50*

BLUE BASE SPECIFY  
WHITE OR BLACK TOP

### BREADBOARD KIT \$10.75\*



# New!

## Better than a pet rock!



**Kantronics Freedom VFO**

only  
**\$69.95**

With almost 350,000 licensed amateurs on the air, variable frequency operation isn't a luxury, it's a necessity.

If you've tried to operate a rock-bound transmitter on the HF bands today, you know there must be a better way. There is.

The **Kantronics Freedom VFO** will drive the high impedance oscillator tubes of transmitters like the HW-16, DX-60, DX-35 and other "oldie-but-goodies."

The **Freedom VFO** sets you free to roam from 3.650 to 3.750 MHz and 7.000 to 7.200 MHz.

**Give your pet rocks to a trusted friend and order a Freedom VFO today.** Or write us for information and a list of authorized **Kantronics** dealers.

Order now!

**KANTRONICS**

*The Lightweight Champs.*

1202 East 23rd St  
Lawrence, Kansas 66044

Telephone 913 842 7745

# Larsen... the coolest antenna in town gives you the hottest performance!

Since the first Larsen Antenna was introduced some 15 years ago, this basic fact has not changed: **Larsen Mobile Antennas are designed and built to outperform.**

With the introduction of the Larsen exclusive K lrod whip, this superior performance is a fact more than ever.

We're not going to confuse you with details on metallurgy, radiation resistance, plating systems and all that. Instead we suggest that you make this simple test:

Take any antenna other than a Larsen... one with a regular unplated 17-7 PH stainless steel (.100/.050) tapered whip. Apply a good husky signal to it... 100 watts, for, say, a full minute. Then, power off, feel the antenna. *Careful! Burn blisters aren't pleasant.*

Next... try a Larsen K lrod Antenna. Put it to the same test.

Amazing isn't it!

That's our story. Heat means power... power that isn't radiated... power you shouldn't throw away. With the Larsen K lrod, power goes into communicating instead of heating the antenna. That's why you can **HEAR the difference.**

Larsen Antennas are available to fit all styles of mounts and to cover Amateur frequencies from 6 meters through 450 MHz. Write for complete catalog and list of dealers nearest you.



## Larsen Antennas

11611 N.E. 50th Ave.  
P.O. Box 1686  
Vancouver, WA 98663  
Phone: 206/573-2722


*In Canada write to:*  
Canadian Larsen  
Electronics, Ltd.  
1340 Clark Drive  
Vancouver, B.C. V5L 3K9  
Phone: 604/254-4936

\* K lrod is a Registered  
Trademark of Larsen  
Electronics, Inc.


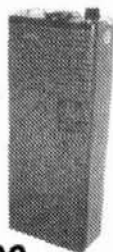
## 2 METER PORTABLE G.E. MASTER PR36 132-150 MHz — 5 Watts

**All Solid State  
with Ni-cad Battery  
\$228.00**



**Vehicular Charger 4EP63A**

(sold only with unit) ..... **\$25.00**

**A.C. Charger**

(subject to availability) ..... **\$25.00**

**Speaker/Mike Type EM36** ..... **\$15.00**




**GREGORY ELECTRONICS CORP.**

245 Rt. 46, Saddle Brook, N.J. 07662  
Phone: (201) 489-9000



# TOROID CORES

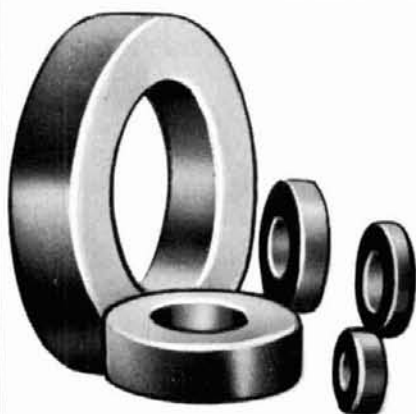

- ✓ All the popular sizes and mixes.
- ✓ Fast Service. Same day shipment via first class mail or air.
- ✓ No minimum order.

## IRON POWDER TOROIDS:

CORE SIZE	MIX 2 5-30 MHz u = 10	MIX 6 10-90 MHz u = 8.5	MIX 12 60-200 MHz u = 4	SIZE OD (in.)	PRICE USA \$
T-200	120			2.00	3.25
T-106	135			1.06	1.50
T-80	55	45		.80	.80
T-68	57	47	21	.68	.65
T-50	51	40	18	.50	.55
T-25	34	27	12	.25	.40

## RF FERRITE TOROIDS:

CORE SIZE	MIX Q1 u = 125 1-70 MHz	MIX Q2 u = 40 10-150 MHz	SIZE OD (in.)	PRICE USA \$
F-240	1300	400	2.40	6.00
F-125	900	300	1.25	3.00
F-87	600	190	.87	2.05
F-50	500	190	.50	1.25
F-37	400	140	.37	1.25
F-23	190	60	.23	1.10

Chart shows uH per 100 turns.

## FERRITE BEADS:



\$2.00 DOZEN

## WIDE BAND CHOKES



95¢ EACH

TO ORDER: Specify both core size and mix for toroids. Packing and shipping 50 cents per order USA and Canada. Californians add 6% sales tax.

Fast service. Free brochure and winding chart on request.

# PALOMAR ENGINEERS

BOX 455, ESCONDIDO, CA 92025  
Phone: (714) 747-3343

## 8K ECONORAM II™: kit \$135, 3 kits for \$375, assembled and tested \$155.

This is the board that thousands of owners swear on, not at. There are lots of reasons, such as unique addressing options, reliability, full buffering, fast access time, a full set of sockets... but probably the most popular feature is the price, which is all the more remarkable because of the high level of quality. One owner reviewed this board in the 1/77 issue of *Kilobaud*, closing with the words: "If you're not convinced by now that the Econoram II is one of the best memory buys on the market today, you really have to be one tough cookie—either that or you work for someone else who makes memory boards."

## 12K ECONORAM VI™: \$235

We proudly welcome our newest memory board family member, designed from the ground up for full compatibility with the Heath Company H8. Organized as two independent blocks, one 8K block and one 4K. Has the same basic features as our ECONORAM II™—all static design, switch selected protect and phantom, sockets for all ICs, full buffering—plus the required hardware and edge connector to mate mechanically with the H8. You can have our 12K board for the price of the Heath Company's 8K... with the performance you have come to expect from products carrying the ECONORAM trade mark.

## A Message:

Now you can have the quality of Godbout products and the convenience of local shopping many computer stores and other electronic outlets stock a number of our items. From individual components to complete board kits.

We always welcome new dealers; if you have a store and want to know more about adding these popular products to your line, write or phone and ask for our dealer package.

Finally, we'd like to add that even inveterate optimists such as ourselves have been amazed and delighted at the response to our computer kits. We thank you very much for your support (and your patience during our period of heaviest expansion). It will enable us to keep you excited with more new goodies in the months ahead.



## MORE COMPUTER ITEMS

"8K X 8 ECONORAM III™" Dynamic memories have a reputation for low power, economy — and difficulty of use. If you'd like to have the good without the bad, then this is the board for you. Not a kit; comes assembled, tested, and ready to run in any S-100 machine (Altair, IMSAI, etc.). Configuration as two separate 4K blocks. Zero wait states with 8080 CPU. 1 year warranty. **\$149.00**

"Vector #8803 Bare 10 Slot Motherboard" This is a version of our 10 slot motherboard, but contains no edge connectors, active termination circuitry, or other components — just the board. Great for experimenters or people with small systems who don't need the full kit. **\$29.50**

## 10 SLOT MOTHERBOARD ..... \$90

18 SLOT MOTHERBOARD ..... \$124  
These S-100 bus motherboards come with edge connectors and active termination circuitry.

We got our start in this business selling components to fanatical hobbyists who couldn't find the parts of their dreams anywhere else. What with all the attention being lavished on our computer kits, music kits, and hobby kits, we wanted to take this opportunity to remind you that we still sell parts... at the same outrageously low prices that got us going in the first place.

Need more resistors? Capacitors? Or maybe some ICs... CMOS... linear... memories... Vector products (like the Slit-N-Wrap or wire pencil)... or a really classy chassis to dress up your next project... we've got all that, and then some.



How about an American made, Switchcraft RCA phono jack? (Closed circuit too — that's a rare bird). Comes mounted on a little plastic carrier with screw holes for easy mounting. At 7 for \$1, here is a chance to stock up on some top quality connectors.

Send  
for  
our  
flyer

Terms: Cal res add tax. Allow 5% shipping, excess refunded. MasterCard® /VISA® orders (\$15 min) call (415) 562-0636, 24 hrs. COD OR with street address.

# GODBOUT

BILL GODBOUT ELECTRONICS  
BOX 2355, OAKLAND AIRPORT, CA 94614

# SEMICONDUCTOR SUPERMART

## FREQUENCY COUNTER CHIPS

7207A	\$5.75
7208	\$15.95
9368	\$2.60
74196	\$1.41
5,24288 MHz Xtal	\$6.95
95H90	\$9.25
11C90	\$15.25

## VOLTAGE REGULATOR

### SPECIAL

## POSITIVE OR NEGATIVE

### YOUR CHOICE

### ONLY .99 EA.

7805	7905
7806	7906
7808	7908
7812	7912
7815	7915
7818	7918
7824	7924

### ALSO

78H05 5V, 5 amp	\$8.50
78H12 12V, 5 amp	\$8.50

## ZENER DIODES (1-WATT)

### 3 FOR \$1.00

1N4733A 1W, 5.1V	1N4743A 1W, 13V
1N4734A 1W, 5.6V	1N4744A 1W, 15V
1N4735A 1W, 6.2V	1N4745A 1W, 16V
1N4736A 1W, 6.8V	1N4746A 1W, 18V
1N4737A 1W, 7.5V	1N4747A 1W, 20V
1N4738A 1W, 8.2V	1N4748A 1W, 22V
1N4739A 1W, 9.1V	1N4749A 1W, 24V
1N4740A 1W, 10V	1N4750A 1W, 27V
1N4741A 1W, 11V	1N4751A 1W, 30V
1N4742A 1W, 12V	1N4752A 1W, 33V

## TRANSISTORS — FETS

2N5179	\$ .70
40673	\$1.25
MPF102	\$ .50
2N6081	\$8.60
2N6082	\$11.50
2N6084	\$13.95
2N5589	\$4.95
2N5590	\$6.95
2N5591	\$10.95
MRF449A	\$12.00
MRF450A	\$15.55
MRF901	\$4.50
MRF902	\$13.80

## CIRCUIT SPECIALISTS CO.

BOX 3047  
SCOTTSDALE, AZ 85257



State  
of the art



by  
**K.V.G.**

### CRYSTAL FILTERS and DISCRIMINATORS

#### 9.0 MHz FILTERS

XF9-A	2.5 kHz	SSB TX	\$33.55
XF9-B	2.4 kHz	SSB RX/TX	\$47.75
XF9-C	3.75 kHz	AM	\$51.40
XF9-D	5.0 kHz	AM	\$51.40
XF9-E	12.0 kHz	NB FM	\$51.40
XF9-M	0.5 kHz	CW (4 pole)	\$35.95
XF9-NB	0.5 kHz	CW (8 pole)	\$63.95

Export  
Inquiries  
Invited

#### 9.0 MHz CRYSTALS (Hc25/u)

XF9001	9000.0 kHz	Carrier	\$4.15
XF901	8998.5 kHz	USB	\$4.15
XF902	9001.5 kHz	LSB	\$4.15
XF903	8999.0 kHz	BFO	\$4.15
F-05	Hc25/u	Socket Chassis	.50
F-06	Hc25/u	Socket P.C. Board	.50

Shipping  
\$1.25  
per filter

#### ALSO AVAILABLE FROM KVG

10.7 MHz CRYSTAL FILTERS AND XTAL DISCRIMINATORS  
OSCILLATOR CRYSTALS 50 kHz TO 150 MHz

Write for Details

### PRE-SELECTOR FILTERS



ELIMINATE IMD "BIRDIES"  
FROM YOUR RECEIVER.  
CLEAN UP YOUR TRANSMITTER OUTPUT.

432 MHz	PSf432	\$39.95
1206 MHz	PSf1296	\$39.95
1691 MHz	PSf1691	\$52.45
Shipping		\$3.50

### 432 MHz SSB TRANSVERTERS

Use your HF Transceiver on the 432 MHz band with the addition of the MMt432 linear Transverter. The MMt432 operates on all modes; SSB, CW, AM, FM. It contains BOTH the linear transmit up-converter and the receive down-converter. An internal PIN diode T/R connects to your Transceiver T/R line. The MMt432 is FT101 and similar HF rig compatible. Add the 70/MBM48 MULTIBEAM and operate direct into OSCAR 7 mode B. Write for application note.

#### Specifications:

Output Power	10 W PEP
Drive, 10 Meters	1/2 W max
Receiver N.F.	3.0 dB typ
Receiver gain	30 dB typ
Prime Power	12 V D.C.

Shipping: \$3.50

MMt432-28 MKA	\$249.95	MMt144-28	\$199.95
MMt432-50	\$249.95	Also Available:	
MMt432-ATV	\$259.95	FMT440-146	\$154.95
MMt432-144	\$319.95	QMt432-144	\$154.95



### ANTENNAS (FOB CONCORD, VIA UPS)

#### 144-148 MHz

8 OVER 8 J-SLOT	+12.3 dBd	DB/2M	\$41.95
8 BY 8 VERTICAL POL.		DB/2M-VERT.	\$49.95
8XY/2M	\$41.95		



#### 420-450 MHz MULTIBEAMS

48 EL.	GAIN +15.7 dBd	70/MBM48	\$47.95
88 EL.	GAIN +18.5 dBd	70/MBM88	\$73.50

#### UHF LOOP YAGIS

26 LOOPS	GAIN +20 dBi		
1250-1340 MHz	1296-LY		\$56.95
1650-1750 MHz	1691-LY		\$83.95

Send 26¢ (2 stamps) for full line catalogue of KVG crystal products and all your VHF & UHF equipment requirements.

Pre-Selector Filters	Amplifiers	SSB Transverters
Varactor Triplers	Crystal Filters	FM Transverters
Decade Pre-Scalers	Frequency Meters	VHF Converters
Antennas	Oscillator Crystals	UHF Converters

**si**

Spectrum  
International, Inc.  
Post Office Box 1084  
Concord, Mass. 01742, USA

# TPL 1/4 KILOWATT LINEAR AMPLIFIER

TPL proudly presents the first true power 1/4KW  
SSB/AM, FM or CW solid state  
2 meter linear amplifier



Model 2002

The 2002 utilizes the latest state of the art engineering including micro-strip circuitry and modular construction. The three final transistors combine to produce 250W when driven by 15W or more at 13.8VDC.

A remote control plug allows you to operate with the amplifier ON or OFF, or in SSB/AM, FM or CW from the dashboard. This broad band amplifier will cover the entire 2 meter band with no degradation and will also cover the adjacent MARS channels with only a slight degradation. No tuning is required.

A seven pole low pass filter attenuates all harmonics 60dB or greater as required by the FCC.

Model 2002 \* \$479.00

\* can be ordered for repeater application.  
19" rack and panel mounted with cooling fan

#### POWER INPUT:

5-20W Carrier FM or CW  
20W PEP maximum SSB or AM

#### POWER OUTPUT:

200-250W carrier FM or CW  
300W PEP SSB or AM

#### FREQUENCY RANGE:

144 to 148 MHz\*  
\* will operate with slight degradation at  
142 and 150 MHz.

#### HARMONIC ATTENUATION:

All Harmonics Attenuated 60 dB or Greater

#### CURRENT DRAIN:

FM-40 Amps @ 250W  
SSB-30 Amps @ 300W PEP

#### DUTY CYCLE:

FM 50% @ 150W 33% @ 250W  
SSB 60% @ 150W 50% @ 250W

**TPL** for additional information contact  
**COMMUNICATIONS INC.**

1324 W. 135TH ST., GARDENA, CA 90247 (213) 538-9814

Canada:

Lenbrook Industries, Ltd., 1145 Bellamy Rd., Scarborough, Ontario M1H1H5  
Export: EMEC Inc., 2350 South 30th Avenue, Hallandale, Florida 33009

## WARBLE ALARM CAR-VAN CLOCK WITH HEADLIGHT ALARM



- ELAPSED TIMER
- SECONDS DISPLAY SWITCH
- 9 MINUTE SNOOZE ALARM
- SIMPLE 4 WIRE HOOK UP
- JUMBO 1/2" LED DISPLAY
- 1 TO 59 MINUTE COUNTDOWN TIMER RUNS SIMULTANEOUSLY WITH CLOCK!
- RUGGED ABS CASE
- QUARTZ CRYSTAL ACCURACY

COMPLETE KIT \$35.95  
ASSEMBLED \$45.95

## DIGITAL AUTO INSTRUMENTS SEVEN MODELS!

- #1 TACHOMETER
- #2 WATER TEMP.
- #3 FUEL LEVEL
- #4 SPEEDOMETER\*
- #5 OIL PRESSURE
- #6 OIL TEMP.
- #7 BATTERY MONITOR



- KIT INCLUDES:
- CASE & ALL HARDWARE
  - PRESSURE & TEMP. SENSORS
  - ASSEMBLED MAIN PC BOARD
- FEATURES:
- 4" ORANGE LED'S
  - 4" x 4" x 2" ABS CASE

\*ADD \$10 FOR REQUIRED SPEED SENDER. \$15 FOR SPEED SENDER ALONE  
KIT: \$49.95 . . . . . ASSEMBLED: \$59.95

## ELECTRONIC 'PENDULUM' CLOCK



- SWING PENDULUM
- 7" HOURS AND MINUTES DISPLAY
- TIME SET PUSH BUTTONS
- ALARM FEATURE

KIT-UNFINISHED CASE . . . . . \$59.95  
ASSEMBLED-STAINED CASE . . . . . \$69.95

## QUARTZ DIGITAL AUTO CLOCK OR ELAPSED TIMER!

ELAPSED TIMER: HRS, MINS & SECS  
SIMPLE PUSHBUTTON RESET & HOLD TOGGLE SWITCH



KIT INCLUDES EVERYTHING. NOTHING ELSE TO BUY! 4" LED'S! INTERNAL BATTERY BACKUP! NON POLAR INPUT!

12 OR 24 HR MODE  
DIMENSIONS: 4" x 4" x 2"  
KIT: \$27.95 . . . . . ASSEMBLED: \$37.95

## NOW WITH ELAPSED TIME!



## 3 1/2" DIGITAL CLOCK

- 4 DIGIT KIT \$49.95 • 4 DIGIT ASSEMBLED \$59.95
- 6 DIGIT KIT \$69.95 • 6 DIGIT ASSEMBLED \$79.95

117 VAC 12 OR 24 HR MODE . . . . . KIT COMES COMPLETE!  
6 DIGIT VERSION: 27" x 5" x 1 1/2" • 4 DIGIT VERSION: 18" x 5" x 1 1/2"

## TV-WALL CLOCK

- 25" VIEWING DISTANCE
- 6" HOURS & MINUTES
- .3" SECONDS
- COMPLETE WITH WOOD CASE



KIT: \$34.95 . . . . . ASSEMBLED: \$39.95

## ECONOMY CAR CLOCK

- 1/2" LED MODULE!
- COMPLETE WITH CASE, BRACKET & TIME SET PUSHBUTTONS
- ALARM OPTION



KIT: \$19.95 . . . . . ASSEMBLED: \$26.95

## PENDULUM

GIVE YOUR DIGITAL CLOCK A PENDULUM SWING  
9 TO 12V DC 60 HZ INPUT  
SIMPLE HOOK UP TO ANY CLOCK



\$14.95 CASE WITH BRACKET \$3.75

## MARK FOSKETS' SOLID STATE TIME



P.O. BOX 2159  
DUBLIN, CALIF. 94566  
ORDERS (415) 828-1923



24 HR PHONE



CALIFORNIA RESIDENTS - ADD 6% SALES TAX

# This MFJ RF Noise Bridge . . .

lets you adjust your antenna quickly for maximum performance. Measure resonant frequency, radiation resistance and reactance. Exclusive range extender and expanded capacitance range gives you much extended measuring range.



# \$49<sup>95</sup>

This new MFJ-202 RF Noise Bridge lets you quickly adjust your single or multiband dipole, inverted Vee, beam, vertical, mobile whip or random system for maximum performance.

Tells resonant frequency and whether to shorten or lengthen your antenna for minimum SWR over any portion of a band.

MFJ's exclusive range extender (included) and expanded capacitance range ( $\pm 150$  pF) gives unparalleled impedance measurements from 1 to 100 MHz.

Works with any receiver or transceiver. SO-239 connectors. 2 x 3 x 4 inches. 9 volt battery.

Other uses: tune transmatch; adjust tuned circuits; measure inductance, RF impedance of amplifiers, baluns, transformers; electrical length, velocity factor, impedance of coax; synthesize RF impedances with transmatch and dummy load.

Order from MFJ and try it — no obligation. If not delighted, return it within 30 days for a refund (less shipping). This bridge is unconditionally guaranteed for one year.

To order, simply call us toll free 800-647-8660 and charge it on your VISA or Master Charge or mail us a check or money order for \$49.95 plus \$2.00 for shipping and handling.

Don't wait any longer to enjoy maximum antenna performance. Order today.

## MFJ ENTERPRISES

P. O. BOX 494  
MISSISSIPPI STATE, MS. 39762  
CALL TOLL FREE . . . . 800-647-8660  
For technical information, order and repair status, and in Mississippi, call 601-323-5869.

# "THE PROFESSIONALS"

## NEW

MODEL CTR-2A • 500 MHz & 1 GHz

## COUNTERS

NEW Period Measurement



NEW Built-in Pre-Amp

1 us to 1 sec.

10 mv @ 150 MHz

The New Model CTR-2A Series Counters are designed and built to the highest standards to fulfill the needs of commercial communications, engineering labs and serious experimenters. With an accuracy of + .00005% (oven option) the CTR-2A can handle the most critical measurements and is about half the cost of other commercial counters.

If you need a reliable counter at an affordable price, the CTR-2A is the answer.

- Built-in Pre-Amp 10 mv @ 150 MHz
- 8 Digit .3" LED Display
- High Stability TCXO Time Base
- Built-in VHF-UHF Prescaler
- Automatic Dp Placement
- TCXO Std.  $\pm 2$  ppm
- Period Measurement (Optional)
- Input Diode Protected
- 12V-DC Operation (Optional)
- Oven Controlled Crystal (Optional)  $\pm .5$  ppm
- Selectible Gate Times - .1 & 1 sec.

500 MHz Kit CTR-2A-500K . . . . .	\$249.95
500 MHz Assembled CTR-2A-500A . . . . .	349.95
1GHz Kit CTR-2A-1000K . . . . .	399.95
1GHz Assembled CTR-2A-1000A . . . . .	549.95

OPTIONS . . . . .

02) Oven Crystal . . . . .	\$49.95	05) 10 sec. Time Base . . . . .	\$ 5.00
03) .43" LED . . . . .	10.00	06) Period . . . . .	15.00
04) 12 V-DC . . . . .	10.00	07) Handle . . . . .	10.00



See You at the Dayton Show



PROBES  
Hi-Z \$15.00  
•  
Low Pass \$15.00

DAVIS ELECTRONICS 636 Sheridan Dr., Tona., N.Y. 14150 716/874-5848

# REPEATER USERS — Stay in Touch — with DSI

## UNIVERSAL

The Data Signal TTP Series of keyboard encoders is used to generate the standard 12 or 16 DTMF digits. The encoders provide fully automatic transmitter keying and feature a delayed Transmit Ready light, an interdigit timer, and a built-in audio monitor. Features also include all solid-state, crystal-controlled, digitally-synthesized tones and an optional internal mount Automatic Number Identifier (ANI).

TTP-1 (12-digit) \$59.00  
TTP-2 (16-digit) \$69.00

MODEL DTM — Completely self-contained miniature encoder for hand-held portables. Only 5/16" thick. Three wire connection. Automatic PTT keying optional. With your choice of keyboards. Price: DTM - \$49.50, DTM-PTT - \$59.50.

\*Touch-Tone is a registered trade name of AT&T.

## TOUCH-TONE®

## ENCODERS

TTP-1



DTM



TTP-2




## SUB-MINIATURE ENCODERS



MODEL SME — Smallest available Touch Tone Encoder. Thin, only .05" thick, keyboard mounts directly to front of hand-held portable, while sub-miniature tone module fits inside. This keyboard allows use of battery chargers. Price \$34.50, with your choice of keyboards.

## AUTOPATCH — Ready to go!

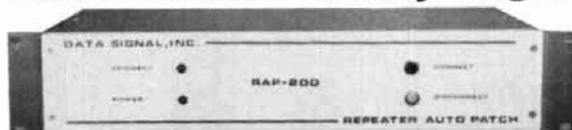

A Complete Autopatch facility that requires only a repeater and a telephone line. Features include single-digit access/disconnect, direct dialing from mobile or hand-held radios, adjustable amplifiers for transmitter and telephone audio, and tone-burst transponder for acknowledgement of patch disconnect.

RAP-200 P. C. Card \$199.50  
RAP-200R Rack Mount \$249.50



# DATA SIGNAL, INC.

2403 COMMERCE LANE  
ALBANY, GEORGIA 31707, 912-883-4703



## The Leader in the Northwest!

ATLAS ICOM KENWOOD YAESU

NEW from KENWOOD!



KENWOOD Transceiver  
TS-820S 160 thru 10M \$1098.



KENWOOD Transceiver  
TS-520S 160 thru 10M \$739. (less DG-5)



KENWOOD Linear Amplifier  
TL-922 Price to be announced.



ICOM Transceiver 2M FM  
SSB IC 211 \$749.

ICOM  
2M FM



IC 225  
\$299.



ICOM Transceiver 2M FM  
IC 245 \$499.



YAESU Transceiver  
FT-301, 160 thru 10M \$769.



YAESU FT-221R  
2 meter FM-SSB \$688.

Other locations:  
(Walk-in customers only)  
Bellevue - 12001 N. E. 12th  
Everett - 6920 Evergreen Way



17550 15th AVE. N.E.  
SEATTLE, WASH. 98155  
206-364-8300



TO PLACE ORDER  
CALL TOLL FREE  
IN STATE OF WASH.  
1-800-562-7625



# Advertisers check-off

... for literature, in a hurry — we'll rush your name to the companies whose names you "check-off"

Place your check mark in the space between name and number. Ex: Ham Radio  234

## INDEX

ABC 571	Icom 065
AGL 558	Integ. Circuits 518
ALDA 625	Int. Crystal 066
Aldelco 347	James Elect. 333
Aluma 589	Jan 067
Am. Elect. Supply 659	Jones 626
Am. Wholesale	K-Enterprises 071
Elect. 003	Kantronics 605
Antler 547	Kengore 538
Arma *	Kenwood *
Atlantic Surplus 644	Kester *
Atlas 198	Klaus 430
Bauman 017	Lafayette 598
Buckeye 672	Larsen 078
Budwig 233	Long's 468
Bullet 328	Lunar 577
Burbank 669	Lyle 373
CFP 022	MFJ 082
CW Elect. 533	Madison *
Circuit Spec. 026	NuData 455
Clegg 027	Oak Hill Am. Radio
Communications	Sess 213
Center 534	Optoelectronics 352
Comm. Spec. 330	Palomar 093
Cont. Spec. 348	Partridge 439
Crystal Banking 573	Pipo 481
Cushcraft 035	P. C. P. 648
D&V Radio *	RF Power Labs 602
DSI 656	Callbook 100
Dames Comm. 551	Radio Sys. Tech. 422
Dames, Ted 324	Radio World *
Data Signal 270	Ramsey 442
Davis Elect. 332	Regency 102
Dayton Hamvention *	Rochester Hamfest *
DenTron 259	Rockwell, Collins 258
Drake 039	SST 375
E. T. O. *	Securtron 461
Electrocom 663	Sherwood 435
Elect. Distr. 044	Slep 232
Elect. Equip. Bank 288	Solid State Time 636
Elect. Signal 670	Space 107
Eng. Specialties 658	Spectronics 191
Erickson 047	Spectrum Int. 108
FT Accessories 646	TPL 240
Fluke 049	TX RX 671
GLB 552	Ten-Tec *
Godbout 647	Tristao 118
Gray 055	Tufts 321
Gregory *	VHF Eng. 121
Gull 635	Vanguard *
Hal 057	Varian 043
Hal Tronix 254	Webster Assoc. 423
Ham Center 491	Weinschenker 122
H R C B 150	Western *
Hamtronics 246	Whitehouse 378
Heath 060	Wilson Elect. 123
Henry 062	Yaesu 127

\*Please contact this advertiser directly.

Limit 15 inquiries per request.

April 1978

Please use before May 31, 1978

Tear off and mail to

HAM RADIO MAGAZINE — "check off"  
Greenville, N. H. 03048

NAME .....

CALL .....

STREET .....

CITY .....

STATE ..... ZIP .....

# AGL would like you to CONSIDER KENWOOD

For example, the AT-200; a new and versatile accessory that belongs in every station. The AT-200 is an antenna tuner, but it's also much more — it's an antenna switch, an SWR bridge, and an in-line watt-meter. The AT-200 reduces the clutter and increases the operating efficiency of your station.

— or —

How about the SP-820, an external speaker designed for use with the Kenwood TS-520 and TS-820 transceivers, in place of the internal speakers. The SP-820 features built-in, selectable tone filters to attenuate high or low-frequency response inputs, and two-channel, selectable headphone outputs switchable through the tone filters.



SP-820



AT-200



AGL also takes great pride in stocking these other great lines of Amateur radio equipment.



Vhf engineering



We'll see you in Dayton  
April 28th, 29th and 30th!



CALL US TODAY  
TOLL FREE AT  
1-800-527-7418



CALL 214-241-6414 (in Texas)

ART K9TRG

GORDON N5AU

MIKE N5FL

MIKE N5MP

TOM K5TM

BOB W5XC

We service and repair all major lines of Amateur Radio equipment.



3068 FOREST LANE, SUITE 309  
DALLAS, TEXAS 75234

# Advertisers index

ABC Communications	125
AGL Electronics	126
ALDA Communications	37
Aldelco	104
Aluma Tower Co.	102
Amateur Electronic Supply	108
Amateur Wholesale Electronics	80, 81
Antler Antenna	88
Arma	113
Atlantic Surplus Sales	106
Atlas Radio	69
R. H. Bauman Sales Co.	94
Budwig Mfg. Co.	118
Bullet	100
Burbank Electronics	106
CFP Communications	118
CW Electronic Sales Company	98
Circuit Specialists	122
Clegg	120
Communications Center	112
Communications Specialists	58, 59
Continental Specialties	79
Crystal Banking Service	102
Cushcraft	70, 71
D&V Radio Parts	120
DSI Instruments	76, 77
Dames Communications Systems	94
Dames, Ted	110
Data Signal, Inc.	125
Davis Electronics	94, 124
Dayton Hamvention	7, 30
DenTron Radio Company	7, 30
Drake Co., R. L.	42, 43, 84
Ehrhorn Technological Operations	127
Electrocom Industries	98
Electronic Distributors	104
Electronic Equipment Bank	112
Electronic Signal Products	105
Engineering Specialties	104
Erickson Communications	92
FT Accessories	78
Fluke Manufacturing Co.	86
GLB	122
Godbout Electronics	106
Gray Electronics	121
Gregory Electronics	101
Gull Electronics	52, 53
Hal Communications Corp.	97
Ham Radio Center	96
Ham Radio's	78, 86, 89
Communications Bookstore	91
Hamtronics, Inc.	33
Heath Company	Cover II
Henry Radio Stores	5
Icom	107
Integrated Circuits Unlimited	85
International Crystal	103
James Electronics	88
Jan Crystals	114
Jones, Marlin P. & Assoc.	118
K-Enterprises	114, 121
Kantronics	108
Kengore Corp.	8, 9, 64, 65
Trio-Kenwood Communications, Inc.	86
Kester Solder	94
Klaus Radio, Inc.	84, 108
Lafayette Radio Electronics	121
Larsen Antennas	128
Long's Electronics	92
Lunar Electronics	96
Lyle Products	2, 124
MFJ Enterprises	98, 102, 114
Madison Electronic Supply	120
NuData Electronics	88
Oak Hill Academy Amateur Radio Session	49
Optoelectronics	83, 122
Palomar Engineers	112
Partridge (HR) Electronics	90
Pipo Communications	94
Printed Circuit Products	118
RF Power Labs	90, 119
Radio Amateur Callbook	96
Radio Systems Technology, Inc.	112
Radio World	105
Ramsey Electronics	115
Regency Electronics	110
Rochester Hamfest	1
Rockwell International	99
Collins Groups	32
SST Electronics	32
Securtron	32
Sherwood Engineering	106
Slep Electronics Co.	124
Solid State Time	120
Space Electronics	93
Spectronics	123
Spectrum International	123
TPL Communications	110
TX RX Systems, Inc.	87
Ten-Tec	115
Tristao Tower	95
Tufts Radio Electronics	110
VHF Engineering, Div. of Brownian	Cover IV
Vanguard Labs	108
Varian, Ermac Division	98
Webster Associates	108
Weinschenker	96
Western Electronics	119
Whitehouse, G. R. & Co.	Cover III
Wilson Electronics	
Yaesu Electronics Corp.	

# It won't hurt



# an ALPHA

ETO builds every ALPHA Linear Amplifier to run maximum legal power NTL\* with high efficiency on all bands and in all modes. \*(No Time Limit)


#### QST says it: ALPHA 374

- "(ALPHA 374 is) an amplifier fully capable of continuous operation at the legal power limit . . . hardly larger than the average ssb transceiver."
- ". . . no-tune-up . . . high power operation requires no more adjustment than that involved in operating the exciter."
- ". . . there is no need to worry about whether the tubes or the power supply can handle a full kilowatt."
- "At no time . . . including two contest weekends when it was subject to constant use . . . did the writer feel that the amplifier capabilities were even close to being taxed." (QST, April 1975, p. 42-45.)

#### QST says it: ALPHA 76

- "Typically excellent ETO construction techniques . . . in the (ALPHA) 76."
- "The transformer . . . is a 1.5 KVA continuous-service unit."
- "The unit runs cool and quiet."
- "The ALPHA 76 more than exceeds harmonic attenuation (requirements.) . . . Third-order products are approximately 40 dB down . . ."
- ". . . 1 kW cw input provides excellent efficiency . . ."
- "Output efficiency as measured in the ARRL laboratory was better than 60% for both 2000 watts PEP and 1000 watts cw input on all bands." (QST, January 1978, p. 35-36.)

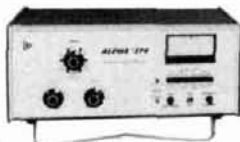**FIRST CLASS IS ALPHA: Sure you can buy a cheaper linear . . . but is that *really* what you want?**



#### ALPHA 374

- No Tune Up, 80-10 meters!
  - 2+ KW PEP, 1 KW avg., NTL
  - RF output typically 1200+ watts PEP into 1.5:1 SWR
  - Harmonics -50db; IMD -30 db
  - 0.9 cu. ft.; 52 pounds
- 18 MONTH WARRANTY**



#### ALPHA/VOMAX

- New split band speech processor can boost your "talk power" 10db or more when conditions get rough. Very low distortion, easy to install and use with any rig.
- 18 MONTH WARRANTY**



#### ALPHA 76

- 2+ KW PEP, 160-10 meters
  - 1000 watts average, NTL
  - Full pi-L; harmonics -52db
  - Nominal efficiency over 60%
  - Just 1 cu. ft.; 70 pounds. (Light-weight option, 50 lb.)
- 18 MONTH WARRANTY**

CALL OR WRITE YOUR DEALER—OR ETO DIRECT—FOR DETAILED LITERATURE AND FAST SERVICE ON THESE AND ALL ALPHA PRODUCTS

**ETO** Ehrhorn Technological Operations, Inc.

P.O. Box 708 · Cañon City, Colorado 81212 · (303) 275-1613



# KENWOOD SUPER BUYS

CALL TOLL FREE! 1-800-633-3410



## KENWOOD TS-820S transceiver

The NEW Kenwood TS-820S features a factory installed digital frequency readout. • 160 thru 10 meter coverage • Integral IF shift • RF speech processor • VOX • Noise blander • PLL • Built-in 25 KHz calibrator • CW side tone & semi-break-in • IF OUT, RTTY, & XVTR • Phone patch IN and OUT terminals.

**1098.00** is list price. Call Toll-Free for quote.

## KENWOOD TR-7500 2m FM transceiver

The NEW TR-7500 has the features you need! Check these: • PLL synthesized • 100 channels (88 pre-programmed, 12 extra diode programmable) • Single knob channel selection • 2-DIGIT LED frequency display • Powered tone pad connection • Helical resonators • 10 watts HI output, 1 watt LOW output. Available very soon! Call us for quote.

**299.00** list price. Call for quote.



## KENWOOD TS-520S SSB transceiver

TS-520S features: • 160 thru 10 meter coverage • Optional DG-5 frequency display (on top of unit) • New speech processor with audio compression amplifier • Built-in AC power supply (DC-DC converter, optional) • RF attenuator • Provision for separate receive antenna & phone-patch.

**739.00** list price. Call for quote.



## KENWOOD TR-7400A 2m FM transceiver

Features: • CTCSS provisions, encode and decode • 25 watt output RF • Solid-state final stage • LED readout • PLL gives 800 discrete channels • Repeater offset circuit • PLL unlock protection circuit • MOS FET.

**399.00** list price. Call for quote.



## KENWOOD SP-820 speaker

Now you can have an external speaker in your shack that's designed just for your TS-820S transceiver. Matching appearance, plus built-in selectable tone filters, 2 channel selectable headphone output switchable through the tone filters.

**49.00** Call for yours today.

Remember, you can call TOLL-FREE: 1-800-633-3410 in U.S.A. or call 1-800-292-8668 in Alabama for our low price quote. Store hours: 9:00 AM til 5:30 PM, Monday thru Friday




# Long's Electronics



## BOARDS INSIDE CABINET

- 1 CARR OSC unit
- 2 VOX unit
- 3 AF unit
- 4 IF unit
- 5 Filter unit
- 6 Noise Blanker/RF Processor
- 7 Rectifier unit
- 8 Rectifier unit
- 9 Power XFMR
- 10 Final Amplifier unit
- 11 VCO unit
- 12 TUNE control
- 13 PLL unit
- 14 RF unit
- 15 Counter Display unit
- 16 FM unit

# FT-901DM

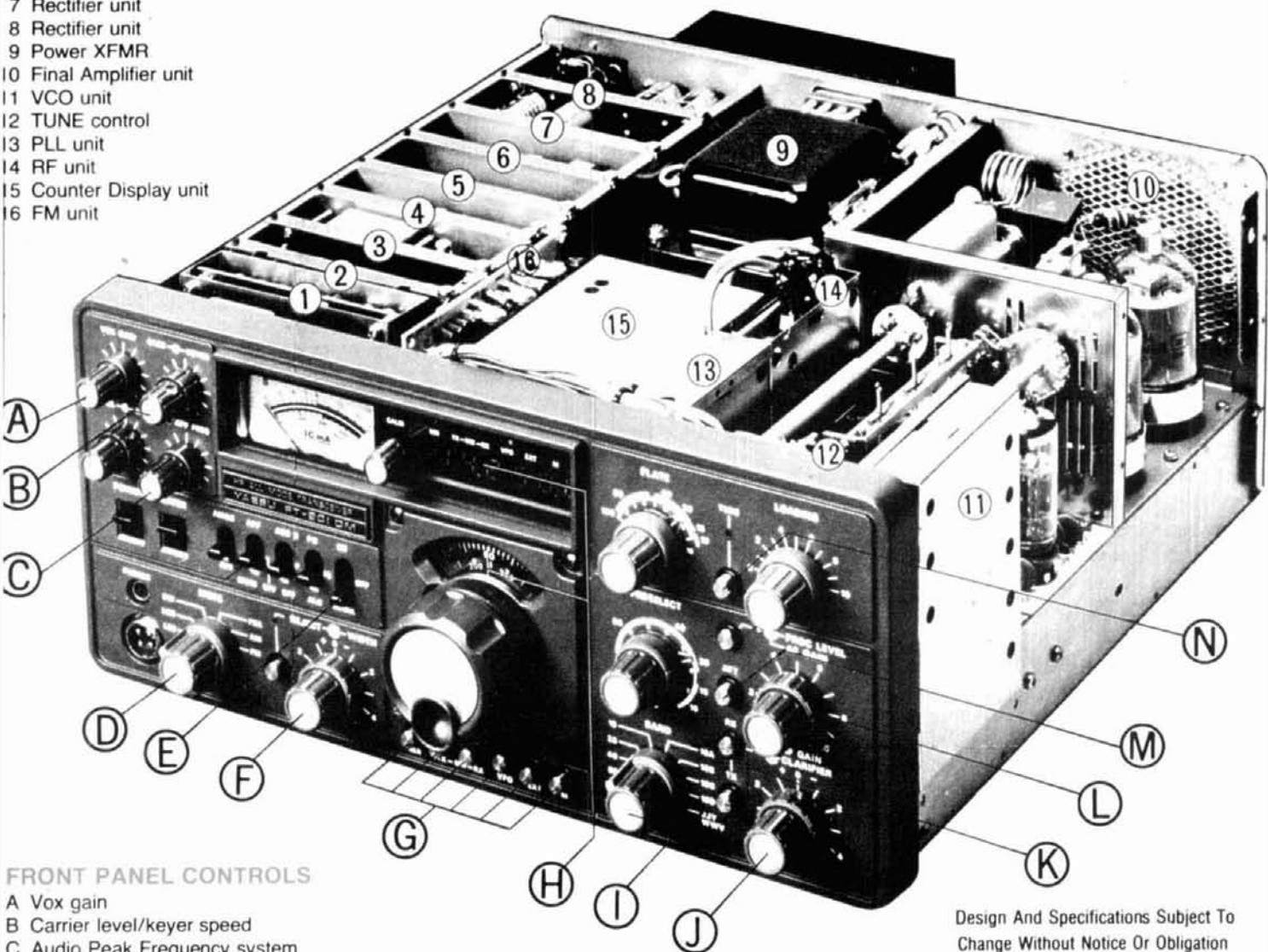

## FRONT PANEL CONTROLS

- A Vox gain
- B Carrier level/keyer speed
- C Audio Peak Frequency system
- D MODE switch (SSB, CW, FSK, AM, FM)
- E Crystal calibrator/Noise blanker
- F Rejection tuning/variable IF passband tuning
- G Frequency memory system
- H Digital plus analog frequency readout
- I Band switch (160-10 meters + WWV/JJY receive)
- J Clarifier control
- K RX/TX Clarifier selector
- L RF Processor level
- M RF attenuator
- N TUNE control (Places transmitter in "TUNE" condition for ten seconds, then returns to "receive" condition to protect final tubes from excessive key-down time)

Design And Specifications Subject To  
Change Without Notice Or Obligation



## THE SYMBOL OF TECHNICAL EXCELLENCE

# YAESU

# **The smart radio**

1C78



YAESU ELECTRONICS CORP., 15954 Downey Ave., Paramount, CA 90723 (213) 633-4007  
YAESU ELECTRONICS CORP., Eastern Service Ctr., 613 Redna Ter., Cincinnati, OH 45215

The first three of a new family of power tubes are available today from EIMAC. These ceramic-metal triodes provide the high power, gain and efficiency of tetrodes, along with long life and reliability up into the UHF spectrum.

EIMAC can supply cavity or cavity design guidance for these tubes in CW as well as pulse service. Because of the circuit simplicity of triodes, this EIMAC family allows the circuit designer to take full ad-

Look at the numbers:

EIMAC Type	Typical CW Performance Data			Maximum Ratings	
	Gain	Power Output	Frequency	Plate Dissipation	Maximum Frequency
3CX400U7	13.5dB	225W	900MHz	400W	1000MHz
3CX600U7	14.0dB	445W	775MHz	600W	1000MHz
8938	12.8dB	1570W	400MHz	1500W	500MHz

vantage of simple cavity design. No tricky screen bypass capacitors or critical isolation circuits are required.

For full information, contact Varian, EIMAC Division, 301 Industrial Way, San Carlos, California 94070. Telephone (415) 592-1221. Or call any of the more than 30 Varian Electron Device Group Sales Offices throughout the world.

# EIMAC delivers triode simplicity with tetrode performance at UHF.



# FREE



**THE NEW  
HEATHKIT  
CATALOG**

Send for your copy of the world's largest selection of quality electronic products in easy-to-build, money-saving kit form! Nearly 400 kits in all — all with Heath's world-famous assembly manuals that take you step-by-step from unpacking to final plug-in.

**fill in card and mail today**

**Please rush me my personal copy of the new Heathkit catalog.**

I am not on your mailing list.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

PC-126 \_\_\_\_\_ Zip \_\_\_\_\_

HAM RADIO \_\_\_\_\_ Dept. 122-400





**HEATH COMPANY**  
**Benton Harbor MI 49022**

**FREE**  
**HEATHKIT**  
**CATALOG**

**PLACE  
STAMP  
HERE**  
The Post Office  
will not deliver  
mail without postage

Send for your  
**FREE**  
**HEATHKIT CATALOG**



Complete descriptions and  
specifications of nearly 400  
electronic kits

including:

stereo compo-  
nents; auto,  
marine and  
aircraft acces-  
sories; digital  
clocks and  
weather  
instruments;  
Amateur  
Radio;  
color TV;  
personal  
computers  
and lots more!

